

PROBLEM SET #4

Issued: Thursday, Feb.14, 2013

Due (at 8 a.m.): Friday, Feb. 22, 2013, in the EE 140/240A HW box near 125 Cory.

1. Fig. PS4.1 shows different active loads being used in analog circuits.
 - (a) Calculate the DC operating points including the current flowing through each branch and DC voltage at each node and transistor small-signal parameters (i.e. g_m , r_o , C_{gs} , C_{gd})
 - (b) Provide expressions and calculate the numerical values for the output resistance, R_{out} ; and gain, v_{out}/v_{in} .
 - (c) Estimate the high-frequency cut-off f_H of the amplifiers.

MOS parameters:

$$V_{GS1}=1\text{V}, |V_{th}|=0.5\text{V}, k_n'=200\mu\text{A}/\text{V}^2, k_p'=100\mu\text{A}/\text{V}^2, \lambda=0.05\text{V}^{-1}, V_{DD}=3\text{V}, V_{B1}=2.7\text{V}, V_{B2}=V_{B3}=1.5\text{V}, C_{ox}=4\text{fF}/\mu\text{m}^2, C_{ol}=3\text{fF}, C_{sb}=C_{db}=5\text{fF};$$

$$(W/L)_1=10\mu\text{m}/0.25\mu\text{m}, (W/L)_{2,3}=2.5\mu\text{m}/0.25\mu\text{m}, (W/L)_4=10\mu\text{m}/0.25\mu\text{m};$$

$$(W/L)_{5,6}=5\mu\text{m}/0.25\mu\text{m}, (W/L)_7=4.5\mu\text{m}/0.25\mu\text{m}, (W/L)_8=0.5\mu\text{m}/0.25\mu\text{m}.$$

Note that the active load in circuit (iii) is depletion-mode NMOS and hence its threshold voltage is negative (i.e. $V_{th4}=-0.5\text{V}$).

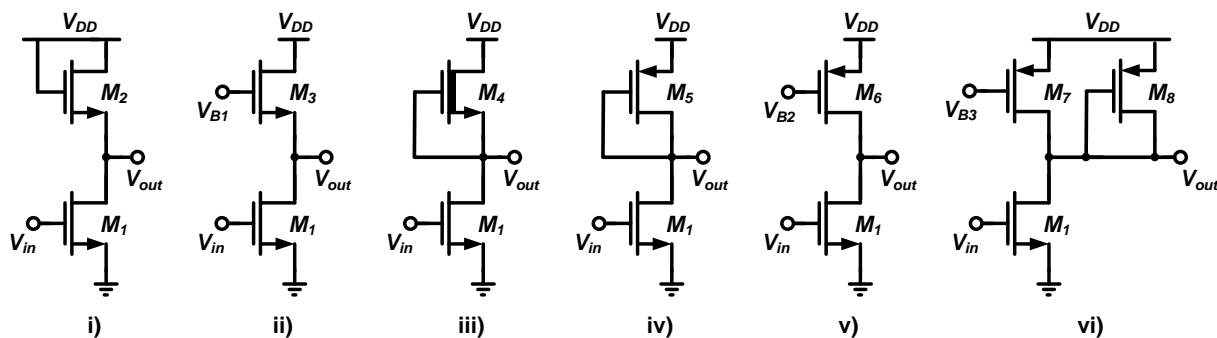


Fig. PS4.1

2. Due to a manufacturing error, resistor R_P has appeared in series with the base of Q_{REF} in Fig. PS4.2. If I_1 is 10% greater than its nominal value, express the value of R_P in terms of other circuit parameters. Assume Q_{REF} and Q_1 are identical.

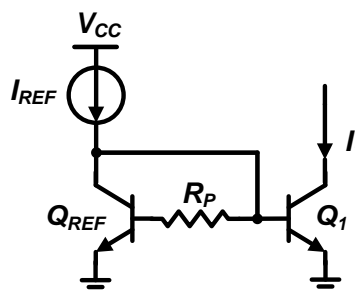


Fig. PS4.2

3. Determine the value of R_P in the circuit of Fig. PS4.3 such that $I_1 = I_{REF}/2$. With this choice of R_P , does I_1 change if the threshold voltage of both transistors increases by ΔV ?

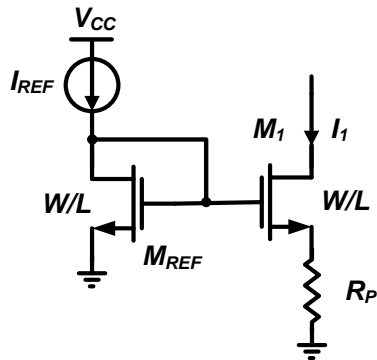


Fig. PS4.3

4. Fig. PS4.4 depicts a simple amplifier circuit using active load. Assume that the output voltage is set at 1V.
- Calculate the DC operating points including the current flowing through each branch and DC voltage at each node.
 - Calculate transistor small-signal parameters (i.e. g_m , g_{mb} , r_o , C_{gs} , C_{gd}).
 - Provide expressions and calculate the numerical values for the output resistance, R_{out} ; and gain, v_{out}/v_{in} .
 - Estimate the high-frequency cut-off f_H of the amplifier.

MOS parameters: (for both NMOS and PMOS, unless otherwise stated)

$$|V_{th}|=0.5\text{V}, k_n'=200\mu\text{A}/\text{V}^2, k_p'=100\mu\text{A}/\text{V}^2, V_{DD}=2.5\text{V},$$

$$\lambda=0.05\text{V}^{-1}, \chi=0.1, C_{ox}=5\text{fF}/\mu\text{m}^2, C_{ol}=3\text{fF}, C_{sb}=C_{db}=5\text{fF}$$

$$(W/L)_1=2.25\mu\text{m}/0.25\mu\text{m}, (W/L)_2=4.5\mu\text{m}/0.25\mu\text{m}, (W/L)_{3,4}=3.75\mu\text{m}/0.25\mu\text{m},$$

$$(W/L)_{5,6}=11.25\mu\text{m}/0.25\mu\text{m}, (W/L)_7=37.5\mu\text{m}/0.25\mu\text{m}, (W/L)_8=7.5\mu\text{m}/0.25\mu\text{m},$$

$$(W/L)_9=6.25\mu\text{m}/0.25\mu\text{m}, (W/L)_{10}=12.5\mu\text{m}/0.25\mu\text{m}, (W/L)_{11}=11.25\mu\text{m}/0.25\mu\text{m}.$$

Hint: Since the current into the transistor M_1 is fixed by the ideal current source, there is no change at its gate voltage, i.e. it is *ac* ground. You can assume the same is true for M_3 and M_4 , too.

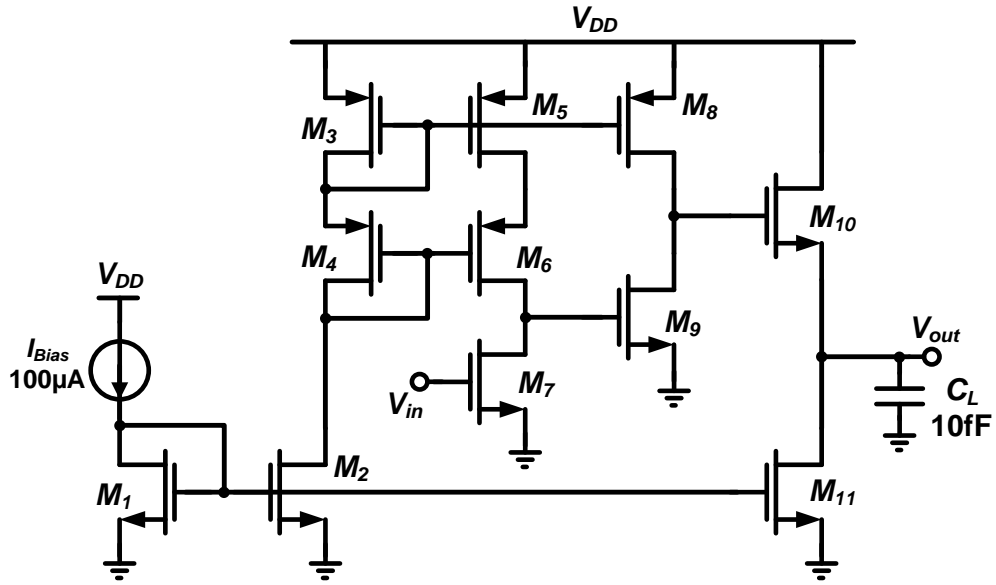


Fig. PS4.4