

**PROBLEM SET #5**

Issued: Thursday, Feb.21, 2013

Due (at 8 a.m.): Friday, Mar. 1, 2013, in the EE 140/240A HW box near 125 Cory.

1. In the circuit shown in Fig. PS5.1, a source follower using a wide transistor  $M_4$  and a small bias current is inserted in series with the gate of  $M_3$  so as to bias  $M_2$  at the edge of saturation. Assuming  $M_0 - M_3$  are identical and  $\lambda \neq 0$ , estimate the mismatch between  $I_{out}$  and  $I_{REF}$  if:

- (a)  $\gamma = 0$
- (b)  $\gamma \neq 0$


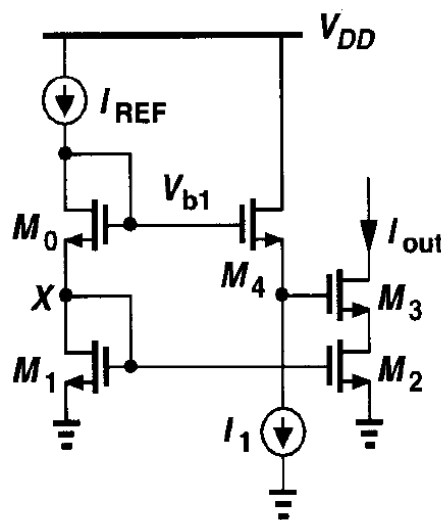


Fig. PS5.1

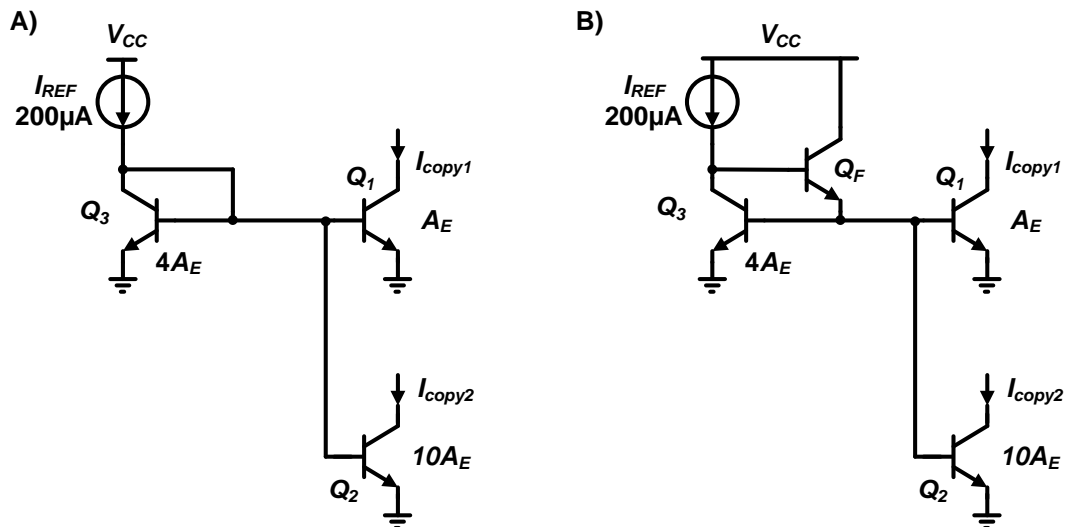2. Compute the error, defined as  $(I_{REF} - I_{copy})/I_{REF}$ , in  $I_{copy1}$  and  $I_{copy2}$  for both circuits in Fig. PS5.2. Assume  $\beta = 20$ .





4. Fig. PS5.4 depicts a self-biasing  $V_t$  reference circuit which is capable of providing a current reference independent of biasing voltage.

(a) Provide expressions for the DC output current  $I_{OUT}$  and biasing currents  $I_{BIAS1}$  and  $I_{BIAS2}$  in terms of circuit elements and transistor parameters and calculate numerical values. Ignore body effect and channel length modulation.

(b) Calculate the ratio of small-signal variations in  $I_{OUT}$  to small-signal variations in  $V_{DD}$  at low frequencies. Ignore the body effect but include finite transistor  $r_o$  in this calculation.

MOS parameters:

$|V_{th}|=0.5\text{V}$ ,  $k_n'=200\mu\text{A}/\text{V}^2$ ,  $k_p'=100\mu\text{A}/\text{V}^2$ ,  $\lambda=0.05\text{V}^{-1}$ ,  $V_{DD}=3\text{V}$ ,  $R=1.75\text{k}\Omega$ ,

$(W/L)_1=12.5\mu\text{m}/0.25\mu\text{m}$ ,  $(W/L)_2=6.25\mu\text{m}/0.25\mu\text{m}$ ,  $(W/L)_3=31.25\mu\text{m}/0.25\mu\text{m}$ ,

$(W/L)_4=6.25\mu\text{m}/0.25\mu\text{m}$ ,  $(W/L)_5=12.5\mu\text{m}/0.25\mu\text{m}$ ,  $(W/L)_6=15.5\mu\text{m}/0.25\mu\text{m}$ .

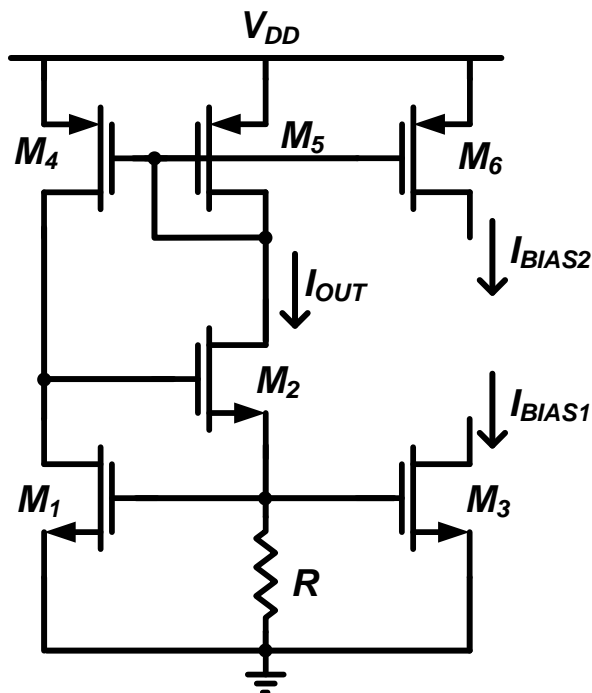


Fig. PS5.4