

PROBLEM SET #8

Issued: Thursday, Mar. 14, 2013

Due (at 8 a.m.): Tuesday, Mar. 19, 2013, in the EE 140/240A HW box near 125 Cory.

1. In the circuit of Fig. PS8.1, assume $(W/L)_{1-4} = 100\mu\text{m}/0.5\mu\text{m}$, $I_{SS} = 1\text{mA}$, $V_b = 1.4\text{V}$, $V_{TH} = 0.7\text{V}$, $\lambda = 0.2\text{V}^{-1}$, $K_n' = 60\mu\text{A}/\text{V}^2$, $K_p' = 30\mu\text{A}/\text{V}^2$, and $\gamma = 0$.
 - (a) If $M_5 - M_8$ are identical and have a length of $0.5\mu\text{m}$, calculate their minimum width such that M_3 operates in saturation.
 - (b) Calculate the maximum output voltage swing.
 - (c) What is the open-loop voltage gain?

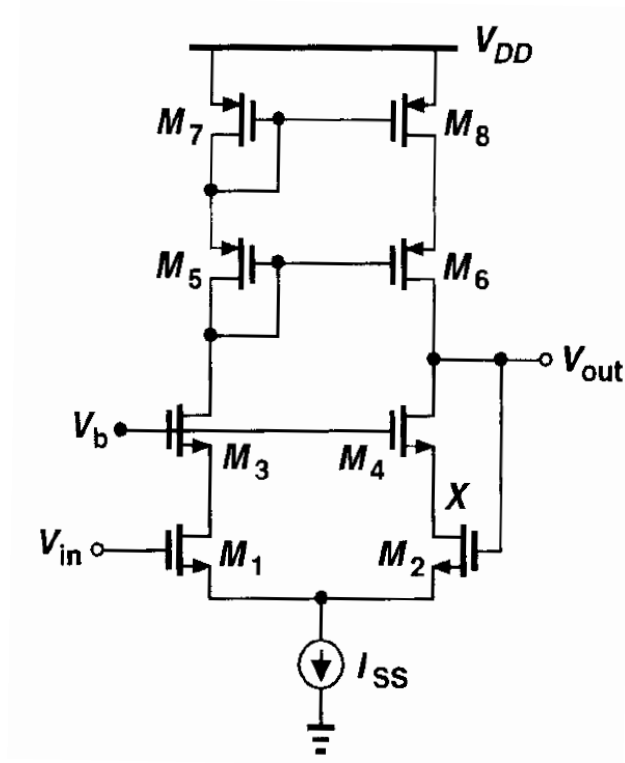


Fig. PS8.1

2. Consider the circuit in Fig. PS8.2. Assume the tail current source is ideal, and the transistors have parameters $\lambda = 0.1\text{V}^{-1}$ and $\gamma = 0$. The transistors are nominally biased so that:

$$I_{D-nom} = 2\text{mA}, g_{m1,2} = 10\text{mS}, g_{m3,4,5,6} = 5\text{mS}, g_{m7,8} = 10\text{mS}.$$
 Find the open-loop voltage gain $A = V_{out}/V_{in}$ for A_{dm} , A_{cm} , A_{dm-cm} , and A_{cm-dm} when:
 - (a) The amplifier is perfectly matched.
 - (b) The amplifier is mismatched such that $(I_{D-M1,3,5,7} - I_{D-M2,4,6,8})/I_{D-nom} = 2\%$, and $(g_{m1,3,5,7} - g_{m2,4,6,8})/g_{m,nom} = 5\%$.

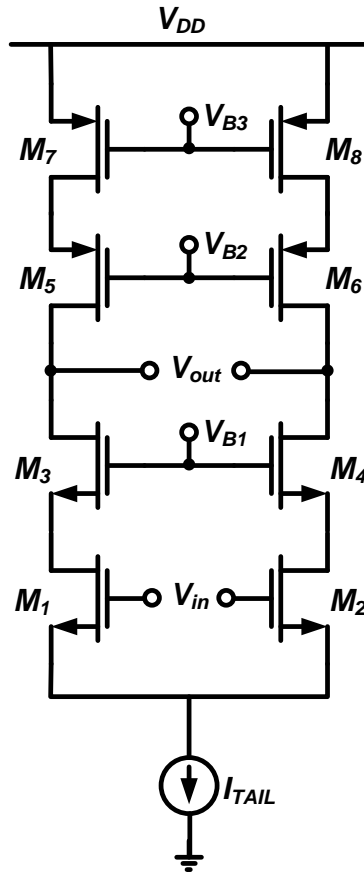


Fig. PS8.2