

## Homework 11

Due: Monday, April 28, 2014 at 1pm

**This is an individual assignment!****PROBLEM 1 (10pts):**

Using feedback techniques, determine the type of feedback, the input and output impedance and current gain ( $i_{out}/i_{in}$ ) of the circuit in Figure 1 using the two-port feedback analysis technique. Leave your answer in terms of variables ( $g_{m1}$ ,  $R_D$ ,  $r_{o1}$ , etc.) and assume  $\gamma = 0$ .

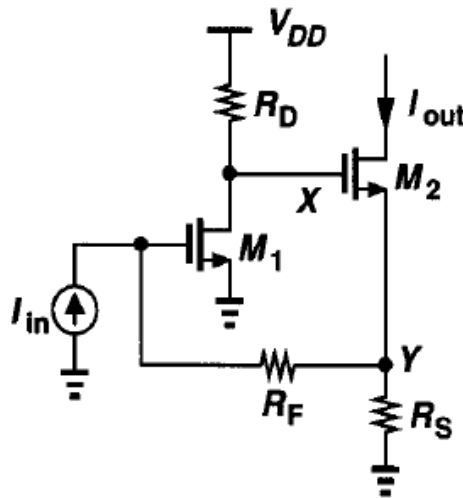


Figure 1

**PROBLEM 2 (10pts):**

Consider the circuit in Figure 2, where  $(W/L)_{1-4} = 50/0.5$ ,  $|I_{D1-4}| = 0.5$  mA,  $V_{tn} = 0.7$  V,  $V_{tp} = -0.8$  V,  $k_n' = 134$   $\mu\text{A}/\text{V}^2$ ,  $k_p' = 38$   $\mu\text{A}/\text{V}^2$ ,  $\lambda_n = 0.1$   $\text{V}^{-1}$ ,  $\lambda_p = 0.2$   $\text{V}^{-1}$ ,  $R_1 = 805$   $\Omega$  and  $R_2 = 3$  k $\Omega$ .

Calculate the loop-gain  $T=af$  and compare to the value of the Return Ratio.

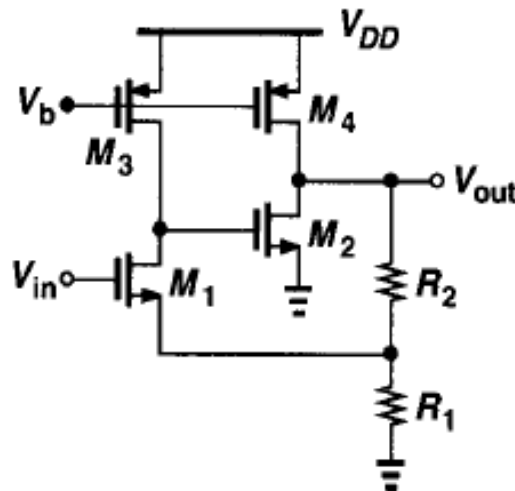


Figure 2

**PROBLEM 3 (15pts):**

A voltage-follower feedback circuit is shown in Figure 3. For the MOS transistor,  $I_D = 0.5 \text{ mA}$ ,  $k' = 180 \mu\text{A}/\text{V}^2$ ,  $r_o = \infty$ ,  $W/L = 100$ , and  $\gamma = 0$ . For the op-amp, assume that  $R_i = 1 \text{ M}\Omega$ ,  $R_o = 10 \text{ k}\Omega$ , and  $a_v = 1,000$ . Calculate input resistance, output resistance, loop transmission, and closed-loop gain:

- (a) Using the formulas from two-port analysis.  
 (b) Using the formulas from return-ratio analysis.

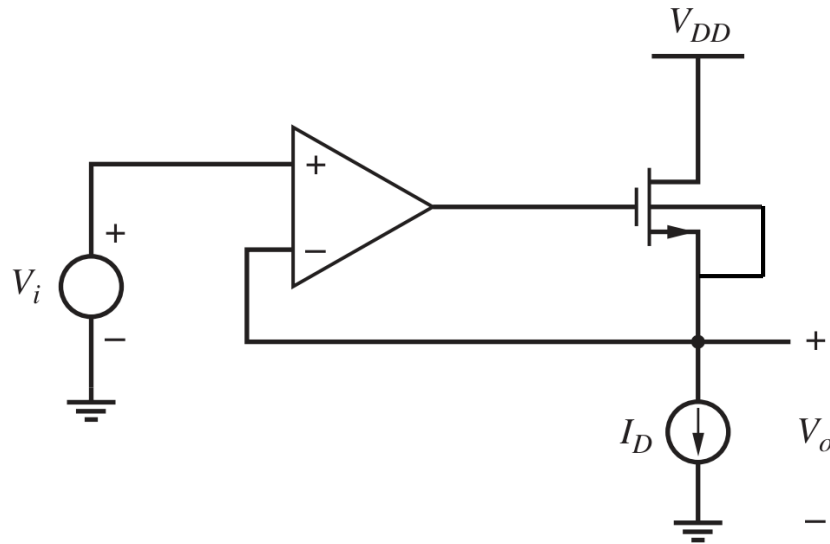


Figure 3

**EXTRA PROBLEM FOR EE 240A STUDENTS:**  
**PROBLEM 4 (15pts):**

In the circuit of Figure 4, suppose all resistors are equal to  $2 \text{ k}\Omega$  and  $gm_1 = gm_2 = 5 \text{ mS}$ . Assuming  $\lambda = \gamma = 0$ , calculate the closed-loop gain and output impedance.

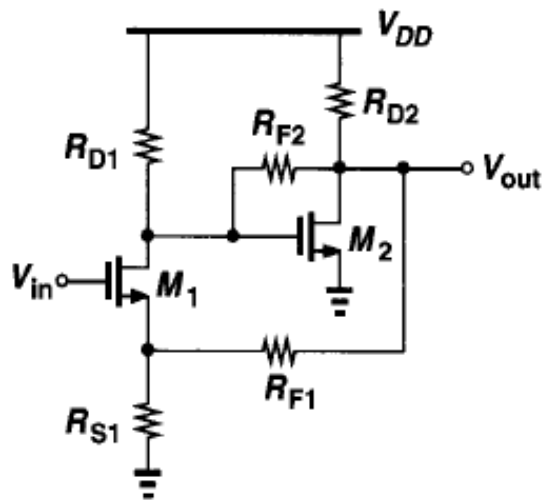


Figure 4