

Homework 2

Due: Friday, 7 February 2014 at 1pm

This is an individual assignment!

PROBLEM 1 (10pts):

Derive the expressions for input resistance R_{in} , output resistance R_{out} , voltage gain $A_v = v_{out}/v_{in}$ as a function of small-signal parameters (i.e. gm, rpi, ro, etc.) and given circuit elements for circuits in Figure 1a,b. Assume that all capacitors have infinite values.

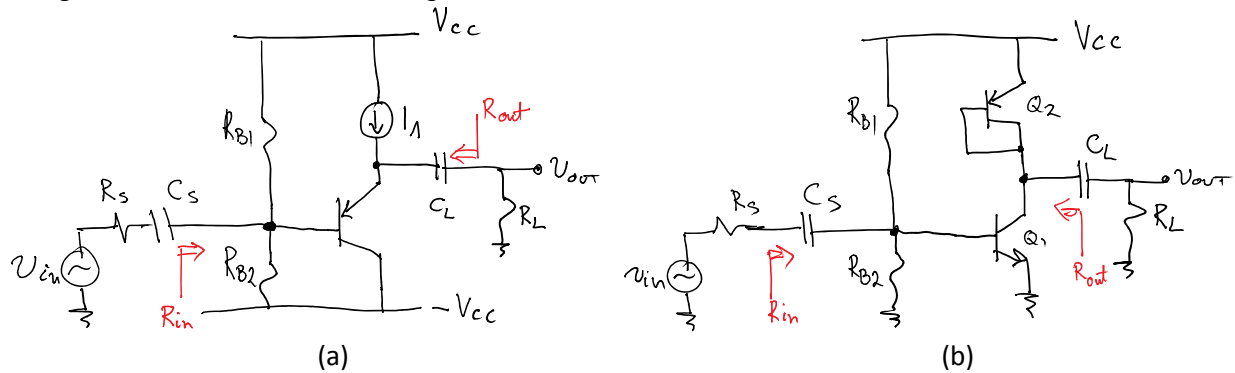


Figure 1

PROBLEM 2 (10pts):

An NMOS transistor has parameters $W=10\mu\text{m}$, $L=1\mu\text{m}$, $k'=190\mu\text{A}/\text{V}^2$, $\lambda = 0.02\text{V}^{-1}$, $t_{ox}=80\text{\AA}$, $\phi_f=0.3\text{V}$, $V_{i0}=0.6\text{V}$ and $N_A=5 \times 10^{15}\text{cm}^{-3}$. Ignore velocity saturation effects.

(a) Sketch the $I_{DS}-V_{DS}$ characteristics for V_{DS} from 0 to 2V and $V_{GS} = 1\text{V}$.

(b) Sketch the $I_{DS} - V_{GS}$ characteristics for $V_{DS} = 2\text{V}$ as V_G varies from 0 to 2V with $V_{SB} = 0$ and 1V.

(c) Derive and sketch the *complete* small-signal equivalent circuit for the device with $V_{GS}=1\text{V}$, $V_{DS}=2\text{V}$, and $V_{SB}=1\text{V}$. Use $\psi_0=0.7\text{V}$, $C_{sb0}=C_{db0}=20\text{fF}$, and $C_{gb}=5\text{fF}$. Overlap capacitance from gate to source and gate to drain is 2fF.

PROBLEM 3 (10pts):

For circuit in Figure 2 sketch the $V_O(V_I)$ output characteristic as V_I goes from 0V to $V_{DD}=2\text{V}$. Mark the regions and type of operation for both M1 and M2. Assume $V_{I1} = V_{I2} = 0.5\text{V}$ and $k_1 = 10k_2$. Find V_I for which the small-signal gain is the largest.

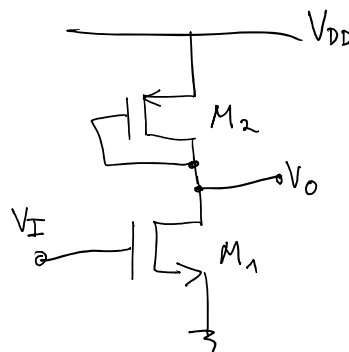


Figure 2

PROBLEM 4 (10pts):

Derive the expressions for input resistance R_{in} , output resistance R_{out} , voltage gain $A_v = v_{out}/v_{in}$ as a function of small-signal parameters and given circuit elements for MOS circuit in Figure 3. Assume that all capacitors have infinite values.

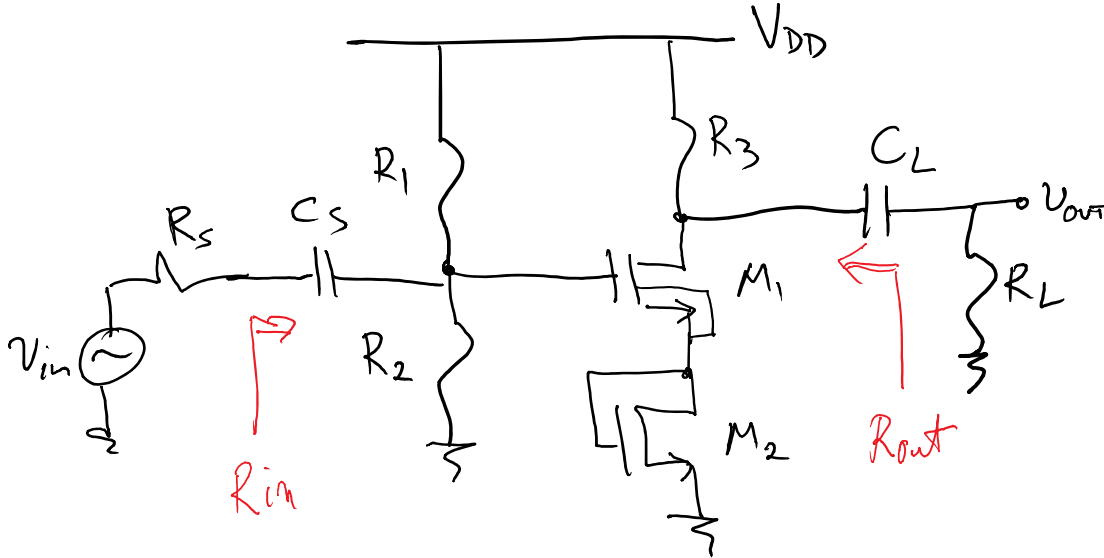


Figure 3

PROBLEM 5 (10pts):

Derive the expressions for input resistances $R_{in1,2}$, output resistances $R_{out1,2}$, voltage gains $A_{v1} = v_{out1}/v_{in}$, $A_{v2} = v_{out2}/v_{in}$ as a function of small-signal parameters and given circuit elements for BiCMOS circuit in Figure 4. Assume that all capacitors have infinite values.

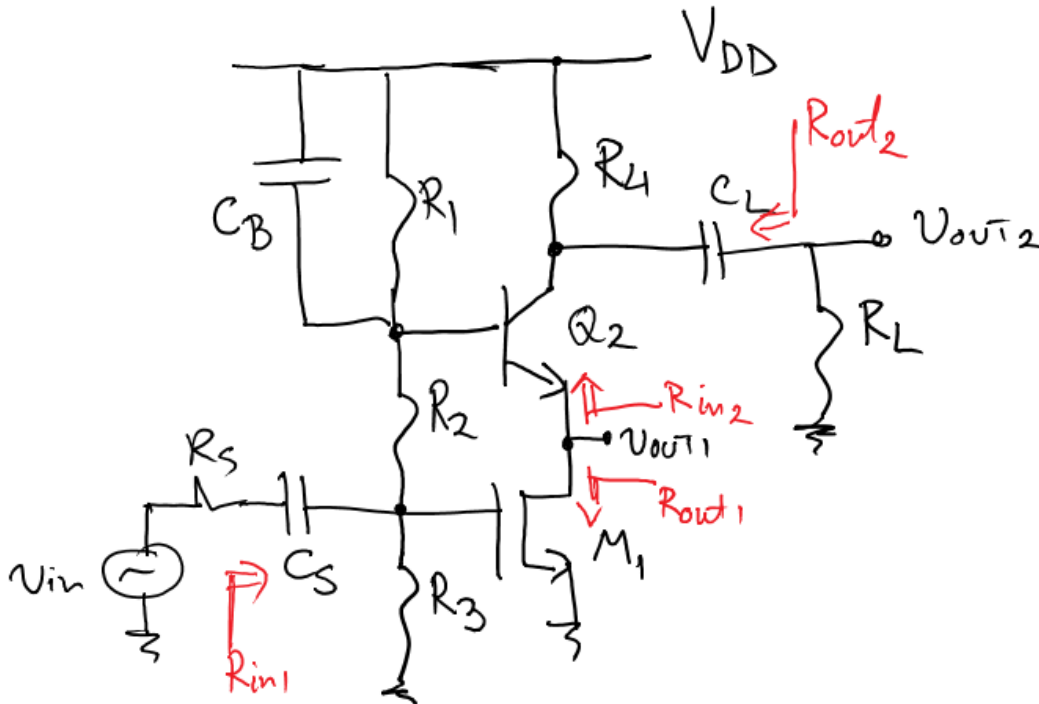


Figure 4

EXTRA PROBLEMS FOR EE 240A STUDENTS:**PROBLEM 5 (10pts):**

Derive the expressions for input resistance R_{in} , output resistance R_{out} , voltage gain $A_v = v_{out}/v_{in}$ as a function of small-signal parameters and given circuit elements for circuit in Figure 5. Assume that all capacitors have infinite values. Determine the biasing resistor values R_E , R_B , R_C to maximize the output swing and voltage gain. Assume $\beta_F=100$, $I_C=1\text{mA}$, $V_A=\infty$ and $R_S=10\Omega$.

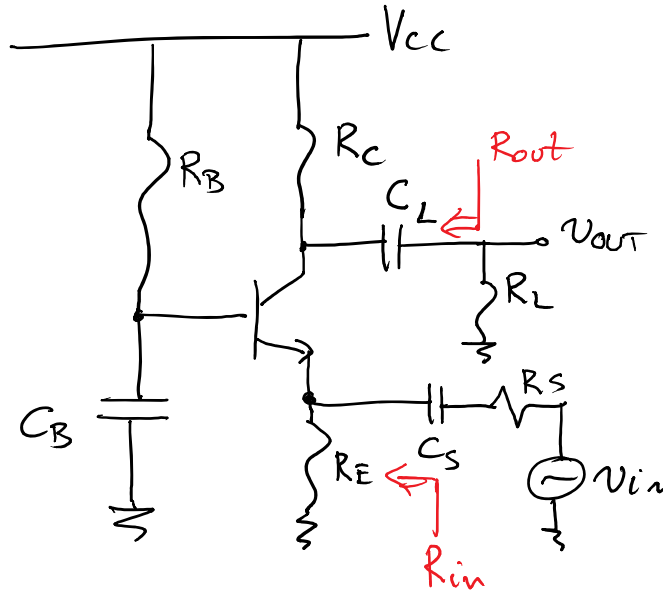


Figure 5

PROBLEM 6 (10pts):

Derive the expressions for input resistances $R_{in1,2}$, output resistances $R_{out1,2}$, voltage gains $A_{v1} = v_{out1}/v_{in}$, $A_{v2} = v_{out2}/v_{in}$ as a function of small-signal parameters and given circuit elements for circuit in Figure 6. Assume that all capacitors have infinite values.


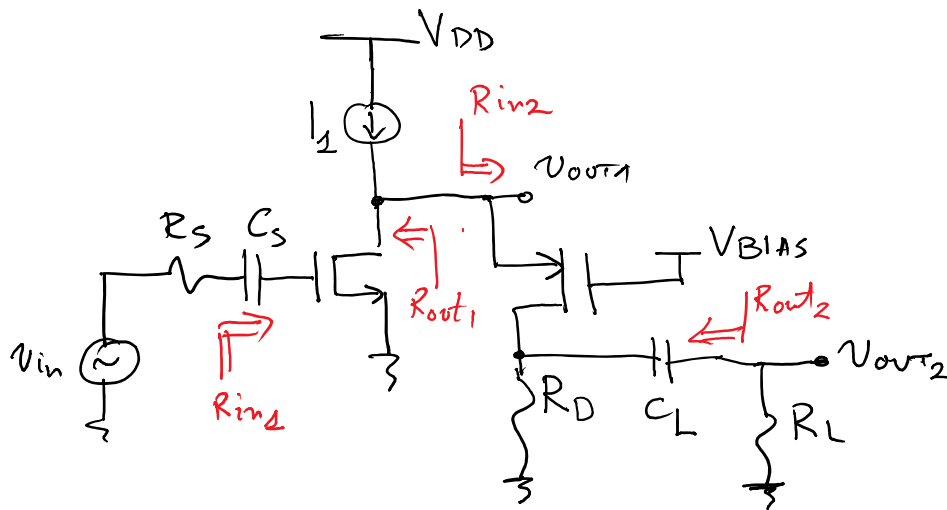



Figure 6

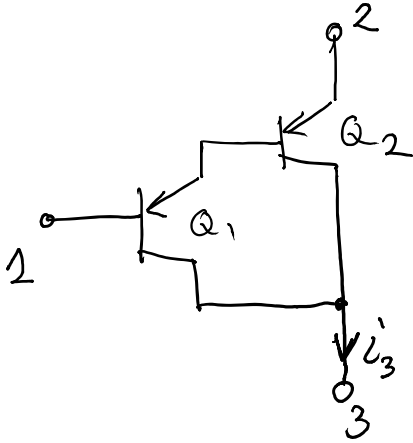PROBLEM 7 (10pts):

Determine the small-signal transconductance $i_3/(v_2-v_1)$ for circuits in Figure 7a,b, as a function of small-signal transistor parameters.



(a)

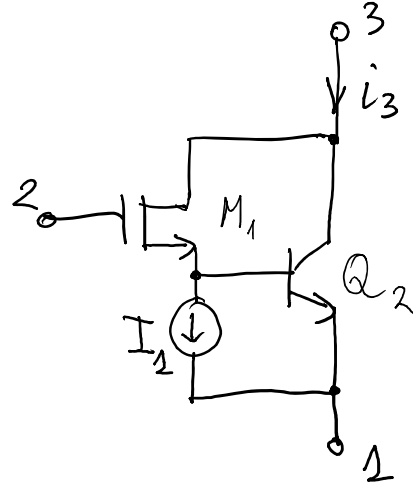

(b)

Figure 7