

Homework 3

Due: Friday, 14 February 2014 at 1pm

This is an individual assignment!**PROBLEM 1 (10pts):**

For both circuits depicted in Fig. 1, calculate the input impedance, output impedance, and voltage gain, v_{out}/v_{in} . Assume $\beta = 100$ and $V_A = \infty$. Repeat assuming $V_A = 100V$.

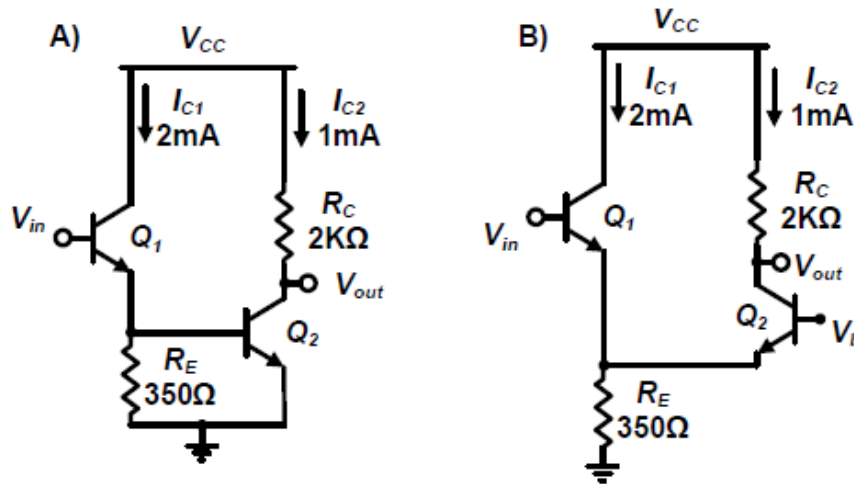


Figure 1

PROBLEM 2 (10pts):

For the small-signal circuits shown in Fig. 2, assume all transistors are identical and have the following parameters: $I_D = 2 \text{ mA}$, $W = 10 \text{ } \mu\text{m}$, $L_{drwn} = 130 \text{ nm}$, $L_d = 15 \text{ nm}$, $X_d = 0$, $k_p' = 200 \text{ } \mu\text{A/V}^2$, $\gamma = 0$, $\lambda = 0$, $C_{ox} = 15 \text{ fF/}\mu\text{m}^2$, $C_{sb} = C_{db} = 0$.

Given $R_S = 500 \text{ } \Omega$, $R_L = 1 \text{ k}\Omega$, and $C_L = 100 \text{ fF}$:

(a) Calculate the DC small-signal voltage gain v_o/v_i for circuit in Fig. 2A.

(b) Calculate the low -3dB cutoff frequency and mid-band voltage gain v_o/v_i for circuit in Fig. 2B.

(c) Calculate and compare the high 3-dB cutoff frequencies of the two circuits.

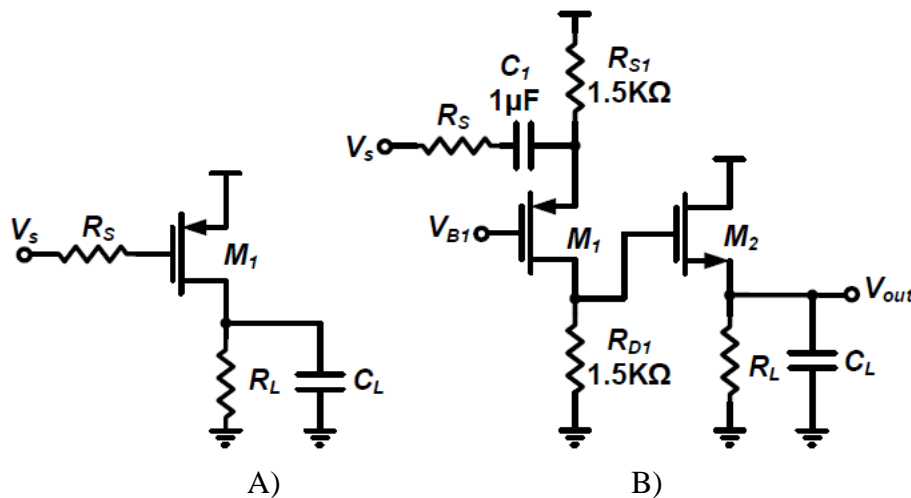


Figure 2

PROBLEM 3 (10pts):

The ac schematic of a wideband MOS current amplifier is shown in Fig. 3. The W/L of M_2 is four times that of M_1 and corresponding bias currents are $I_{D1} = 1\text{mA}$ and $I_{D2} = 4\text{mA}$. Calculate the low-frequency, small-signal current gain i_o/i_i and use the open-circuit time constant method to estimate the -3dB cutoff frequency. M_1 : $C_{gd} = 5\text{ fF}$, $C_{gs} = 20\text{ fF}$, $C_{sb} = C_{db} = 9\text{ fF}$, $V_{ov} = 0.3\text{V}$, and $r_o = \infty$. M_2 : $C_{gd} = 20\text{ fF}$, $C_{gs} = 80\text{ fF}$, $C_{sb} = C_{db} = 36\text{ fF}$, $V_{ov} = 0.3\text{V}$, and $r_o = \infty$.

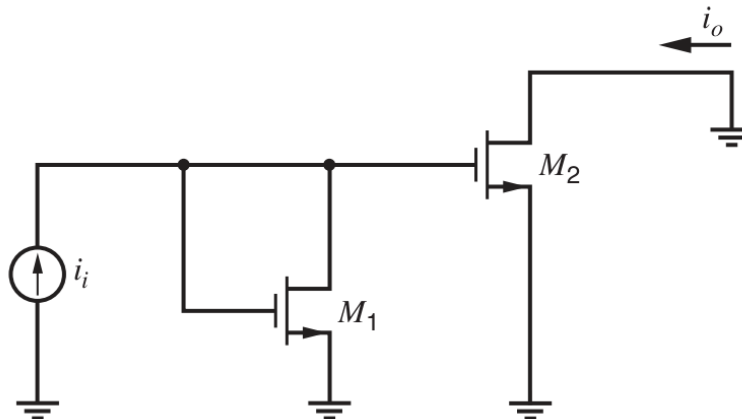


Figure 3

EXTRA PROBLEM FOR EE 240A STUDENTS:**PROBLEM 4 (20pts):**

A multistage BiCMOS amplifier circuit is shown in Fig. 1:

- Calculate the DC current flowing through each branch and DC voltage at each node.
- Calculate transistor small-signal parameters (i.e. g_m , r_π , r_o , C_π , C_μ , C_{gs} , C_{gd})
- Provide expressions and calculate numeric values for the input resistance, R_{in} ; output resistance, R_{out} ; first stage gain, v_{o1}/v_s ; second stage gain, v_{o2}/v_{o1} ; third stage gain, v_{out}/v_{o2} and total gain, v_{out}/v_s .
- Estimate the low frequency cut-off f_L and high frequency cut-off f_H of the amplifier using open and short-circuit time-constant methods.

BJT parameters: $\beta = 100$, $V_A = 100\text{V}$, $V_{BE(on)} = 0.7\text{V}$, $V_{CE(SAT)} = 0.2\text{V}$, $\tau_F = 150\text{ps}$, $C_{je} = 50\text{fF}$, $C_\mu = 1\text{pF}$, $V_T = 25\text{mV}$.

MOS parameters: $V_{th0} = 0.5\text{V}$, $k' = 160\mu\text{A}/\text{V}^2$, $W/L = 10\mu\text{m}/1\mu\text{m}$, $\lambda = 0.05\text{V}^{-1}$, $C_{ox} = 30\mu\text{F}/\text{cm}^2$, $C_{ol} = 1\text{pF}$, $\gamma = 0$.

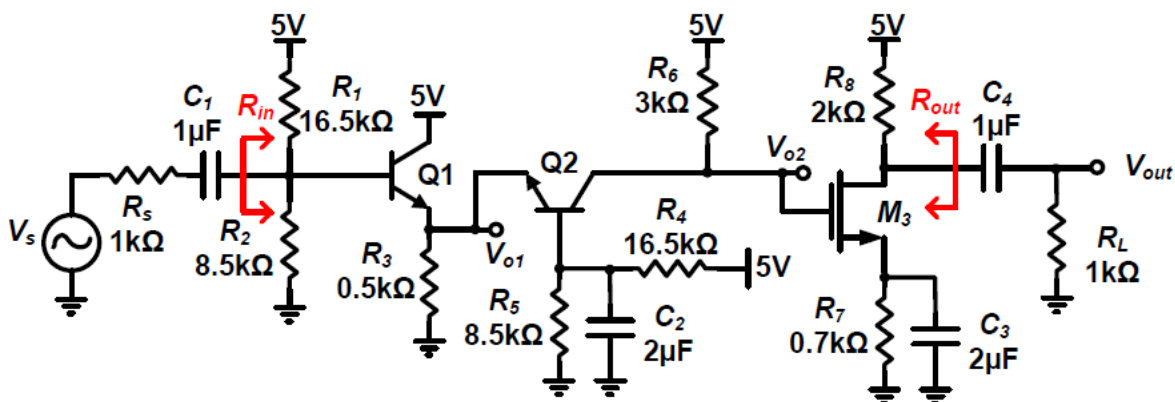


Figure 4