


**Homework Assignment #6**

Due by online submission **Wednesday 3/7/2018** (Thursday 9am)


1. Check out the datasheet for the [K2-W](#) tube op-amp. This op-amp, released in 1952, was the first production op-amp. It runs from a  $\pm 300\text{V}$  supply, and has a bandwidth of 300kHz (or k-cycles/s, as they said back then – the unit Hertz not having been established yet). There's a schematic on page 2. Pins 1, 2, and 6 on the bottom of the figure are  $V+$ ,  $V-$ , and  $V_{out}$ . VR1 and VR2 are neon bulbs that provide a low impedance level shift of roughly 100V to center the output between the rails. Redraw, print out, or cut and paste that schematic, and identify (circle and label)
  - a. input differential pair
  - b. diff-pair load resistor
  - c. tail current resistor.
  - d. Estimate the common mode gain and write it near the tail resistor.
  - e. Common-cathode gain stage (like CS or CE)
  - f. Cathode-follower output stage (like source-follower or emitter follower, CD, CC)
  - g. Miller-multiplied compensation capacitor from the output back to the input of the gain stage.
  - h. Bonus points if you can identify positive feedback in this amplifier, designed to increase the low-frequency gain (which ended up at about 20,000).
2. You have an opamp with a low-frequency gain of 1,000 and a single pole at 100Mrad/s. Plot the location of the pole as a function of the feedback factor  $f$  from  $f=0$  to 1. Now with  $f=0.1$ 
  - a. Sketch the Bode plot of the closed-loop amplifier
  - b. What is the fractional gain error?
  - c. What is the time constant of the step response? How does it compare to the open-loop time constant?
  - d. What is the unity gain frequency? How does it compare to the open-loop unity gain frequency?
3. You have an opamp with a low-frequency gain of 1,000 and three poles at 100Mrad/s. Plot the location of the three poles as a function of the feedback factor  $f$ . At the point where the poles cross the  $j\omega$  axis, annotate the plot with the value of  $f$  that gives this pole location.
4. Estimate the output resistance of a CMOS differential amplifier with current mirror load. You may assume that  $g_m r_o \gg 1$  for all combinations of  $g_m$  and  $r_o$ . The following steps may help.
  - a. Estimate the impedance seen looking into the source of M1A
  - b. Estimate the impedance seen looking down from the source of M1B
  - c. Estimate the impedance seen looking into the drain of M1B
  - d. For the  $R_o$  calculation, estimate  $i_{d1B}$  as a function of  $v_o$ .
  - e. The current in  $i_{d2B}$  is due to both the output resistance and the mirrored current. Estimate both parts.
  - f. Estimate the total output current  $i_o = i_{d1B} + i_{d2B}$
  - g. Show that  $R_o$  is equal to  $(r_{o1B} \parallel r_{o2B})$ . Magic!
5. A single-stage op-amp has a low frequency gain of 200 and a dominant pole at 10Mrad/sec.
  - a. Draw the s-plane with the real axis from  $-10^7$  to 0, and the imaginary axis from 0 to  $10^7$ . Mark the pole location with an x, and draw a dot at  $10^7 j$ .
  - b. Draw the vector from the pole to  $10^7 j$ . Calculate the magnitude and phase of this vector.
  - c. Draw a dot at  $10^6 j$ . Draw the vector from the pole to  $10^6 j$ . Calculate the magnitude and phase of this vector.
  - d. Repeat parts a. and b., but with the imaginary axis from 0 to  $10^8$  and the dot at  $10^8 j$ .
  - e. Draw a Bode plot of the gain of your amplifier, with frequency running from  $10^5$  to  $10^9$  rad/s. Use the straight-line approximations for the Bode plot, and then add dots showing the results of parts b, c, and d.
6. A two-stage CMOS op-amp running at a particular bias point has the following parameters:  
 $G_{m1}=1\text{mS}$ ,  $R_{o1}=1\text{M}\Omega$ ,  $C_1=0.1\text{pF}$ ,  $C_c=0\text{pF}$ ,  $G_{m2}=1\text{mS}$ ,  $R_{o1}=100\text{k}\Omega$ ,  $C_2=10\text{pF}$ .

- a. Plot the magnitude and phase of the overall gain of this uncompensated amplifier.
  - b. Where are the poles of the uncompensated amplifier? Is it unity-gain stable?
7. For the same amplifier as above, we now add  $C_c=1\text{pF}$ . For this problem, you may ignore the RHP zero that this introduces. On the figures provided below,
  - a. Plot the magnitude of the second stage gain vs. frequency
  - b. Plot the magnitude of the input *capacitance* of the second stage (including  $C_c$ ) vs. frequency
  - c. Plot the magnitude of the input *impedance* of the second stage vs. frequency. Add a line for the output impedance of the first stage.
  - d. Now plot the magnitude of the gain of the first stage on the top plot, and the magnitude of the overall gain of the amplifier
  - e. What are the compensated poles of the amplifier? If  $C_c$  were 0, where would the poles of the amplifier be?
8. [ee240a] For a standard 5 transistor CMOS differential amplifier show that the gain from a differential input to the (so called virtual ground!) tail voltage is  $1/4$ . You can assume that  $g_m r_o \gg 1$  for all combinations of  $g_m$  and  $r_o$ . You can win bets with experienced IC designers with this knowledge!

Second stage gain –  $|A_{v2,0}|$ , and first stage and overall gains

 

 magnitude of second stage input (Miller) capacitance



second stage input impedance, and  $R_{o1}$

