 


Homework Assignment #5

Due by online submission **Wednesday 3/4/2018** (Thursday 9am)

1. We usually approximate the closed loop gain $A_0/(1+A_0f)$ by $1/f$. How good or bad an estimate is that? Show that the fractional gain error ($\text{gain_error}/\text{gain}$) is $-1/(A_0f)$.
2. In a single pole op-amp with $A_0=100,000$, $\omega_p=1\text{k rad/s}$, a feedback factor of $f=0.01$ is used. Find:
 - a. the exact low-frequency closed loop gain $A_0/(1+A_0f)$ (use a calculator if needed)
 - b. the approximate low-frequency closed-loop gain, $1/f$
 - c. the fractional gain error, using the result from the previous problem. Does it agree with your results above?
 - d. Above the pole frequency, amplifier gain decreases, and gain error increases. What is the fractional gain error at $10\omega_p$? $100\omega_p$?
3. Check out the datasheet for the LM324 quad op-amp. <http://www.ti.com/lit/ds/symlink/lm324.pdf>
There's a schematic on page 2. Redraw (or cut and paste) that schematic, and identify (circle and label)
 - a. input differential pair (Darlington)
 - b. current mirror active load
 - c. emitter-follower level shifter(s)
 - d. compensation capacitor
 - e. common emitter amplifier (Darlington)
 - f. output stage
4. Assuming the same process parameters (e.g. V_A , β), how will the performance of the LM324 design compare to the amplifier that you built in Lab3 in the following areas
 - a. Input impedance. How does bias current and Darlington affect this?
 - b. Impedance at the output of the first stage? How does the emitter-follower affect this?
 - c. Output impedance of the amplifier. How does output stage affect this?
5. Given a diode-connected NPN transistor Q1 which has a $6\mu\text{A}$ reference current flowing through it, design a bipolar circuit to generate all four of the current supplies shown in the LM324 schematic. The $50\mu\text{A}$ and $100\mu\text{A}$ currents don't need to be exactly right, but should be close. Label your transistors as multiples of each other as appropriate, e.g. $Q_2=5Q_1$. You may assume infinite beta.
6. For the differential amplifier in the figure below you may assume that the transistors have $\lambda=0$. Estimate the change in V_{tail} , I_{tail} , I_{d1a} , I_{d1b} , and V_o due to
 - a. An increase of ΔV in both V_+ and V_-
 - b. An increase of $\Delta V/2$ in V_+ , and $-\Delta V/2$ in V_-
 - c. An increase of ΔV in just V_+
 - d. What is the common mode rejection ratio of this amplifier?
 - e. What is the common mode input range in terms of V_{tn} and V_{ov} ?
 - f. Sketch V_{ov} vs. V_{cm} over that input range.
 - g. Sketch the bounds of the output swing over that input range.



7. Now answer questions a, e, f, and g above for an NMOS-input 5 transistor CMOS differential amplifier, with non-zero λ .
8. Design a 2-stage NMOS input CMOS op-amp with the following specs:
 - a. 80uA tail current
 - b. able to sink 200uA from the load
 - c. output swing to within 200mV of the rails
 - d. input common mode range to within 200mV of the top rail

Process specs $\mu_n C_{ox} = 200 \mu A/V^2$, $\mu_p C_{ox} = 100 \mu A/V^2$, $\lambda = 1/(5V)$, $-V_{tp} = V_{tn} = 0.5V$, $V_{DD} = 2V$, $L_{min} = 0.5 \mu m$, $C_{ox} = 5fF/\mu m^2$, $C'_{ol} = 0.5fF/\mu m$. You may use 1 resistor in your design. Draw the schematic, and label the device sizes.

9. For the amplifier in the previous problem,
 - a. calculate and tabulate I_d , V_{ov} , g_m , r_o , C_{gs} , and C_{gd} for all devices
 - b. calculate the 1st and 2nd stage gain, and the overall gain for both differential and common mode signals.
 - c. calculate the common mode input range, and the variation in tail current over that range.
 - d. calculate the gain across C_{gd1a} .
 - e. calculate the output pole frequency with a 100fF load capacitance.
 - f. calculate the input capacitance of the second stage for frequencies below the output pole frequency
 - g. calculate the first stage output pole frequency, assuming that it is lower than the output pole
 - h. calculate the input capacitance of the second stage above the second stage unity gain frequency
10. [ee240A] For the current supplies that you designed for the LM324 above, estimate the actual current assuming a transistor beta of 100. Use a beta helper (Figure 4.6 GHLM, or google “beta helper current mirror”) to alleviate this problem. How much did the accuracy improve?
11. [ee240A] If the same amplifier were run at $V_{ov} = 0$, how will that affect the gains and pole frequency?