


PROBLEM SET #1

Issued: Thursday, Jan. 28, 2010

Due: Thursday, Feb. 4, 2010, 7:00 p.m. in the EE 143 homework box in 240 Cory

I. MOSFET Characteristics

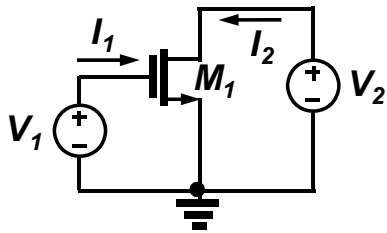
1. Consider the following circuit. Assume transistor M_1 is in saturation and that its bias voltages, V_1 and V_2 , process parameter $K (= \mu_n C_{OX})$, and threshold voltage V_{TH} can be changed independently. Indicate in the table how an *increase* in each of these parameters changes the gate current I_1 , the drain current I_2 , the small-signal transconductance g_m , and the small-signal output resistance r_d of M_1 . Use symbols: \uparrow for increase, \downarrow for decrease, -- for no change.



	I_1	I_2	g_m	r_d
$V_1 \uparrow$				
$V_2 \uparrow$				
$K \uparrow$				
$V_{TH} \uparrow$				

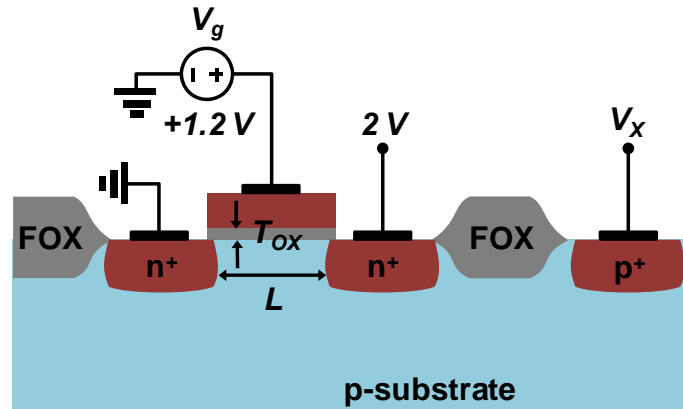2. Consider the cross-section shown below for an NMOS device under dc biasing where the supply voltage $V_{DD} = 2V$, and the gate bias $V_G = 1.2V$.

Assume $L = 0.5 \mu m$, $W = 50 \mu m$, $T_{OX} = 9 nm$, $2\Phi_F = 0.8 V$, $V_{TH0} = 0.7V$, substrate doping = $9 \times 10^{14} cm^{-3}$, relative permittivity of Si = 11.8, and of $SiO_2 = 3.9$, channel mobility = $350 cm^2/V/S$.




- Calculate the threshold voltage if $V_X = V_{DD} = 2V$.
- (Continued) Compared to V_{TH0} , does the threshold voltage increase or decrease? Is this desirable? Why or why not?
- Plot drain current versus V_X if V_X varies from $-\infty$ to 0.

II. MOSFET Amplifier

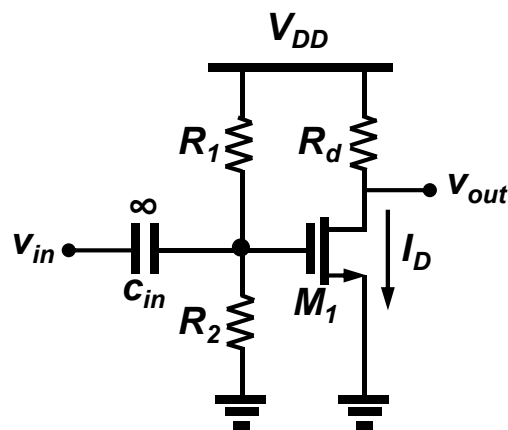3. Consider the MOSFET amplifier given below, where

$$I_{DS} = \frac{K}{2}(V_{GS} - V_T)^2, V_{DD} = 5V, R_d = 2k\Omega, K = 1 \text{ mA/V}^2, \text{ and } V_{TH} = 1V.$$



- Derive an expression for the transistor dc bias point (i.e., dc bias voltage) at the gate terminal as a function of V_{DD} , R_1 and R_2 .
- Determine the required ratio of R_1/R_2 such that the MOSFET transconductance $g_m = 1 \text{ mA/V}$.
- What is the dc bias voltage at the output V_{out} ?
- Draw the small-signal model for the amplifier. Write an expression for its gain v_{out}/v_{in} and calculate its numerical value. Clearly label the components and input/output.

III. Fabrication Yield/Cost

- The cost of processing a wafer in a particular process is \$1,000. Assume that 35% of the fabricated dice are good. For this problem, use Fig. 1.1(c) in the textbook to determine the number of dice.
 - Determine the cost per good die for a 150 mm wafer.
 - Repeat for a 200 mm wafer.