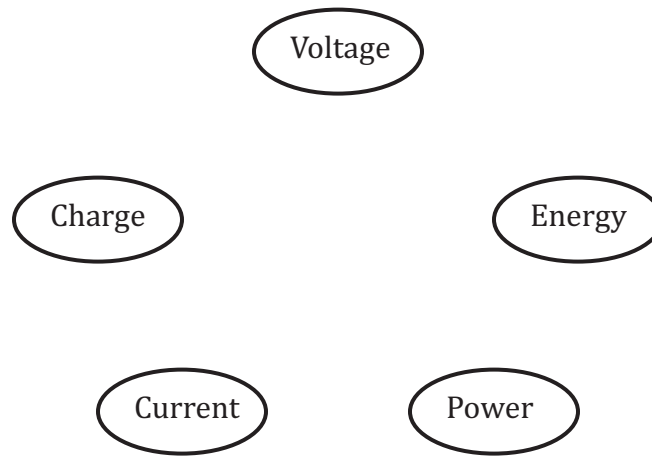


### 1. Breadboards and Schematics

Please draw the schematics associated with the two breadboards shown in discussion.

### 2. Fundamental Quantities in Electronics



- Write down three things that you associate with each bubble.
- Draw lines between intrinsically connected quantities.
- For each line that you drew, write an equation describing the relationship.

### 3. A tiny spark!

Your friend Beatrix has made the mistake of rubbing her feet on a shaggy rug before touching a doorknob. When her hand gets close, a tiny spark shoots from her fingertip!

- Suppose that you know that the electric field required for this event to occur is  $3 \times 10^6$  V/m. How much voltage does Beatrix's body have if the length of the spark is 1mm?
- Now let's say that you use a very precisely calibrated charge measuring device to determine that Beatrix had accumulated a total of 600pC of charge before the spark. Quantify the amount of energy in the spark.
- A spark like this typically lasts around  $1 \mu\text{s}$ . Quantify the current in the air between Beatrix and the doorknob as well as the power in the spark.
- Now let's talk about a bigger spark. A bolt of lightning also takes around  $1 \mu\text{s}$ . But it happens over a distance of 1km. And a storm cloud has approximately  $1 \mu\text{C}$  of charge. How much power is in a lightning strike?

#### 4. Jump starting a car

Your discussion TA left their lights on and their car won't start. Lucky for them, a friendly former Governor happened to be driving by and he has a few minutes to help.

- (a) Given two cables (one red and one black), connect your TA's battery to the governor's.
- (b) A fully charged car battery has a voltage across its terminals of 12V. Your TA's battery is measuring a measly 10V. What will happen when you connect the two?
- (c) Your TA's car draws 100A when you turn the ignition. Describe what happens if:
  - i. Immediately after connecting the two batteries, you attempt to start the car.
  - ii. You wait a long time between connecting the two batteries and then attempt to start the car.