
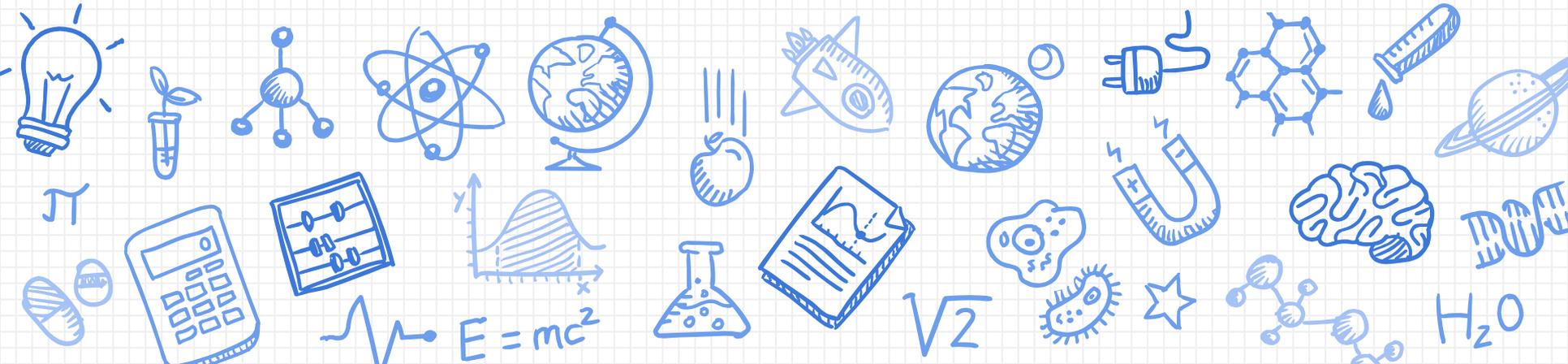


EE16A Lab: Touchscreen 3b

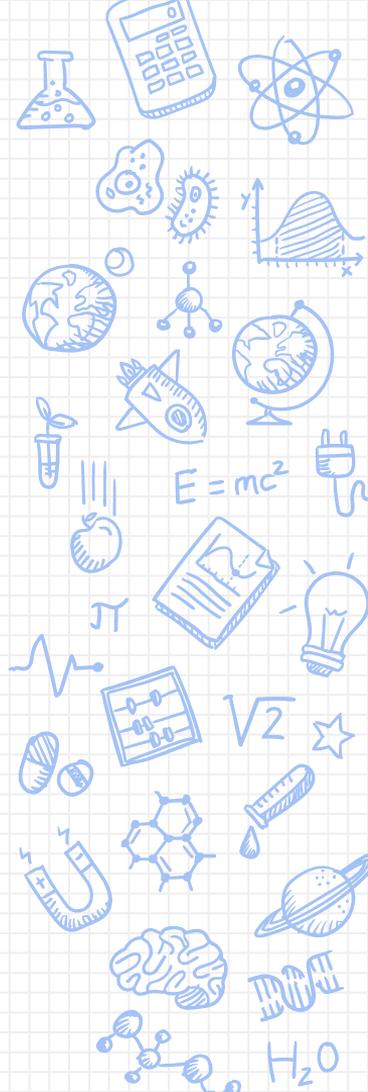




Announcements

- Wrapping up circuits with Touch 3B
 - If you can't finish today, make it up in APS Buffer Week
- Can use your own computer for this lab




Last Week: Touch 3A

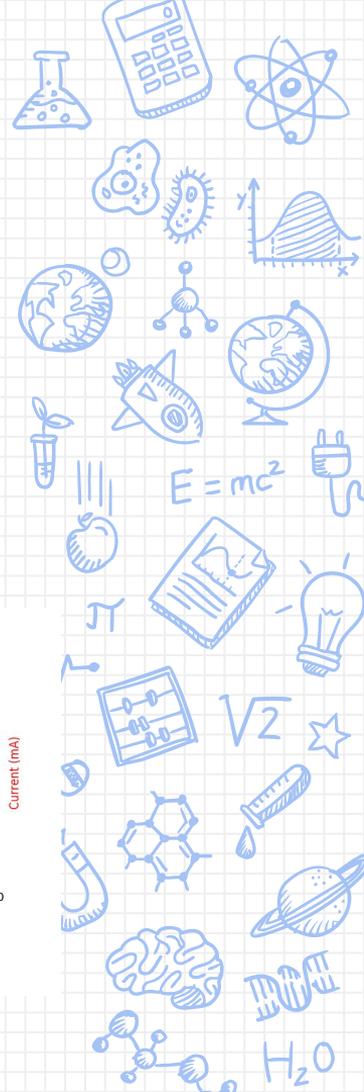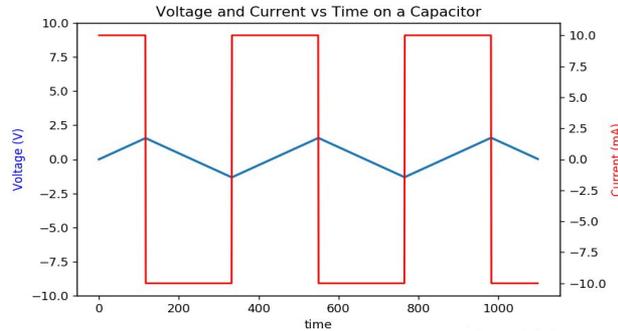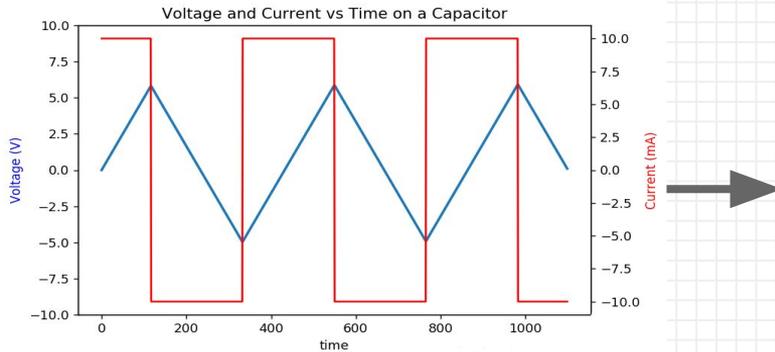- Simulated a touch-sensing circuit
 - Current source onto cap gave $V(t) = \frac{I}{C}t + V_0$
 - Periodically charging and discharging gives a triangular shaped waveform
- **What changed between touch and no touch?**
 - Can tell apart this change with a comparator!





Last Week: Touch 3A

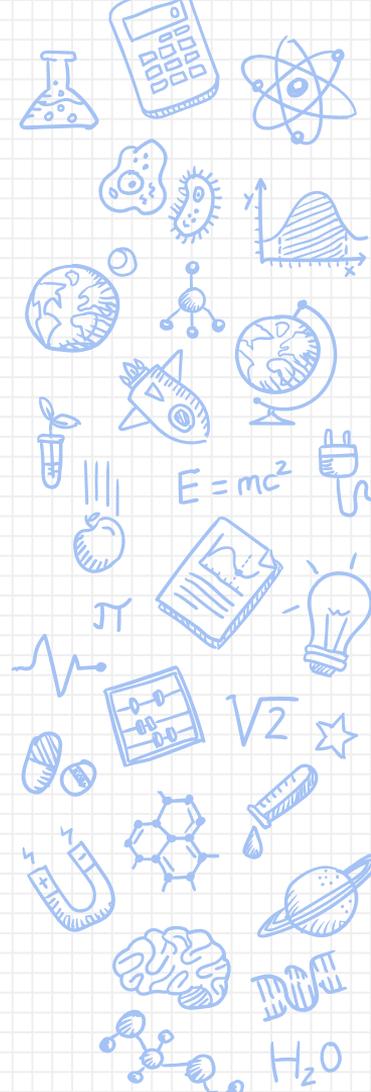- Problem: we don't have ideal square current sources
 - Need another way to implement last lab's waveforms (the triangle wave output)
 - How do we go about creating a similar system that still fits our model?




First Attempt at a Current Source

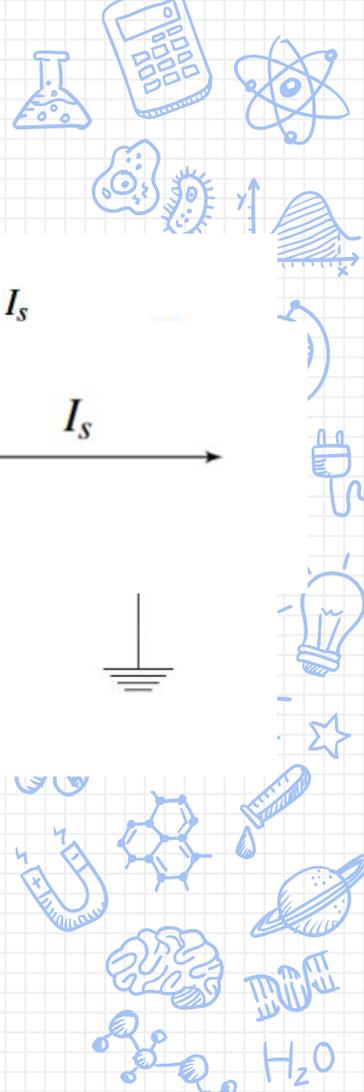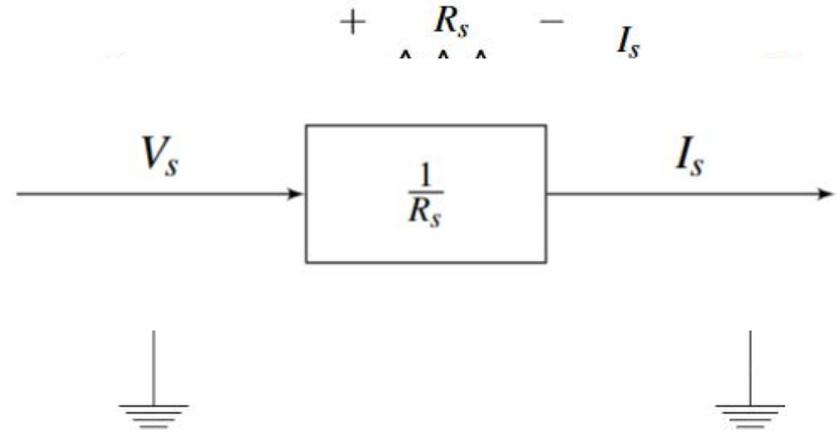- If we have a voltage source and a resistor then we can create a “current source”
- The current is just $(V_s - 0)/R_s$ since the other side is $0V$



First Attempt Evaluation

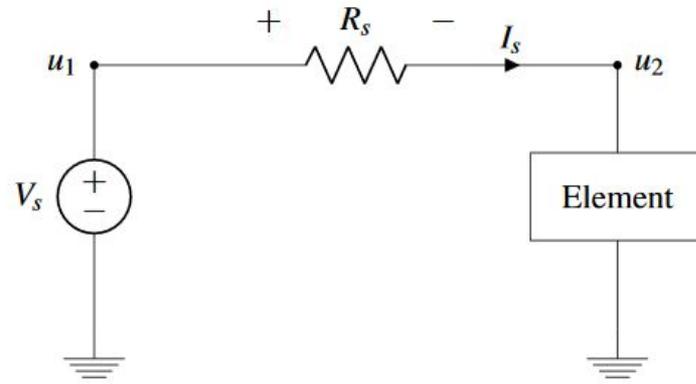- Ok, now let's attach our load
- Assume that the element is a resistor of value R_L
- **Does this work?**




NOPE, it changes the current

$$I_s = \frac{V_s}{R_s + R_L}$$



Note 20: An “almost” current source

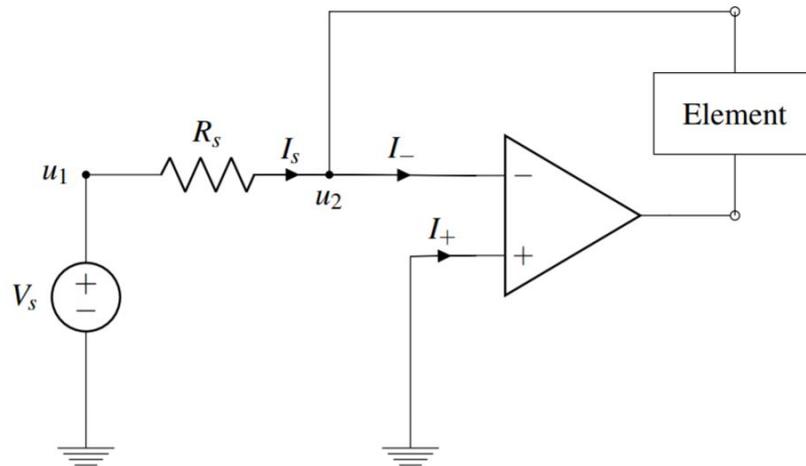- Since we are in negative feedback, $u_2 = 0V$
 - $I_s = \frac{V_s - 0}{R_S}$
- All current will go to the element, since $I_- = 0$



Sensing a Completion


- Hook up our capacitive touch screen
- We get a constant current through the capacitor
- **What's the output of this circuit?**

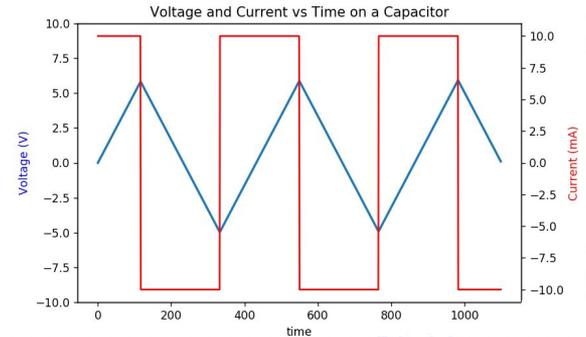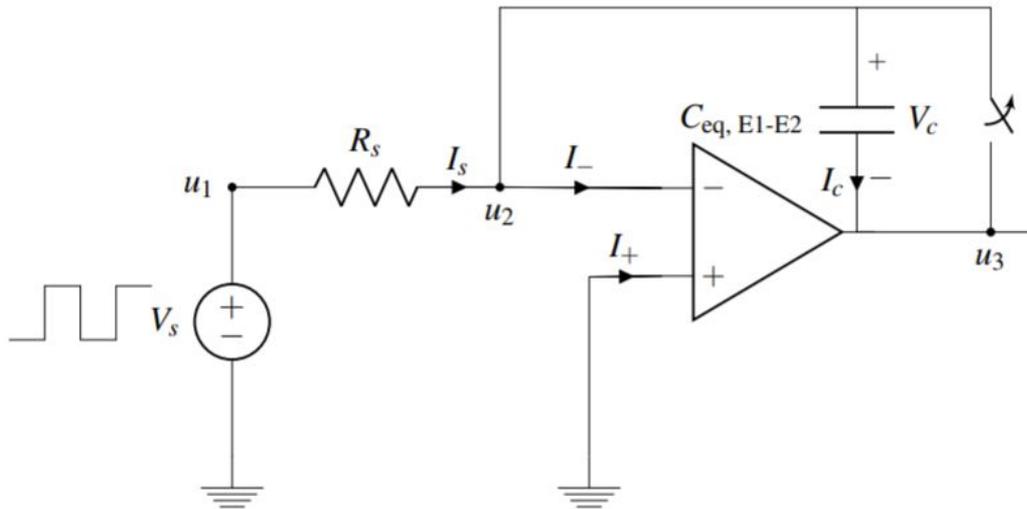

Note 20: An “almost” current source

- Constant current is cool, but we want periodic current to discharge the cap.
- What if we periodically switch voltage?
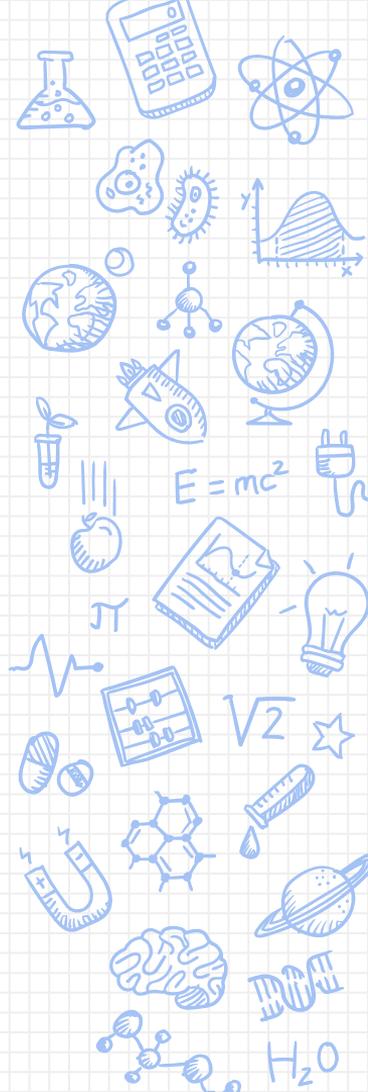
$$I_S = \frac{V_s}{R} \longrightarrow I_S = \frac{-V_s}{R}$$





An Alternate Viewpoint

- Note that the output of this circuit is $V_{out} = -\frac{1}{R_s C} \int_0^t V_s dt$
- It's also an integral, just like last week. You can think of our new circuit as an “almost current source” or just trading current for voltage.
- We're now integrating a constant voltage instead of a current, but the net result is the same as last week
- *We traded one type of input for another!*
- *Variable voltage sources do exist, so this is good! What are they like though?*


What's our new input?

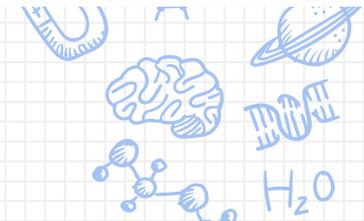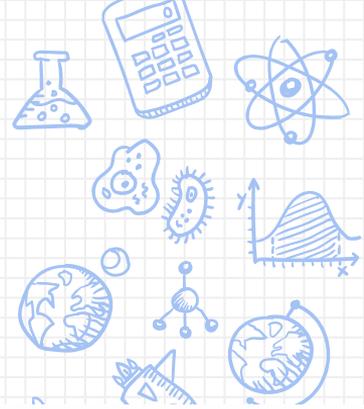- Function generator
- Can create different waves
- Treat it as a non-constant voltage source
- Now we can make the current source of our dreams!





Processing the rest of our system


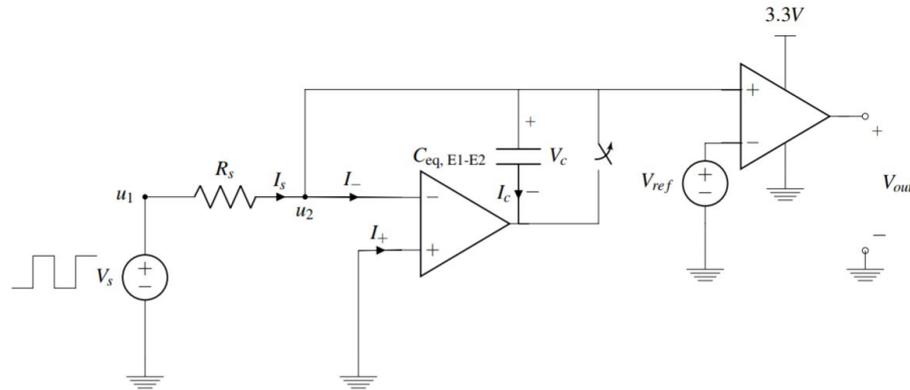
- Our circuit behaves just like we saw last week, great!
- Plus, no need to change how we do the processing: just feed the signal into a comparator



Our real world circuit

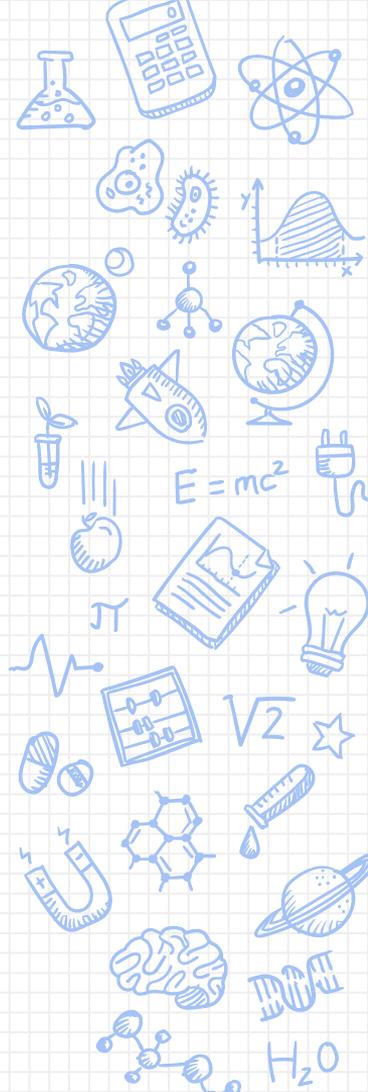
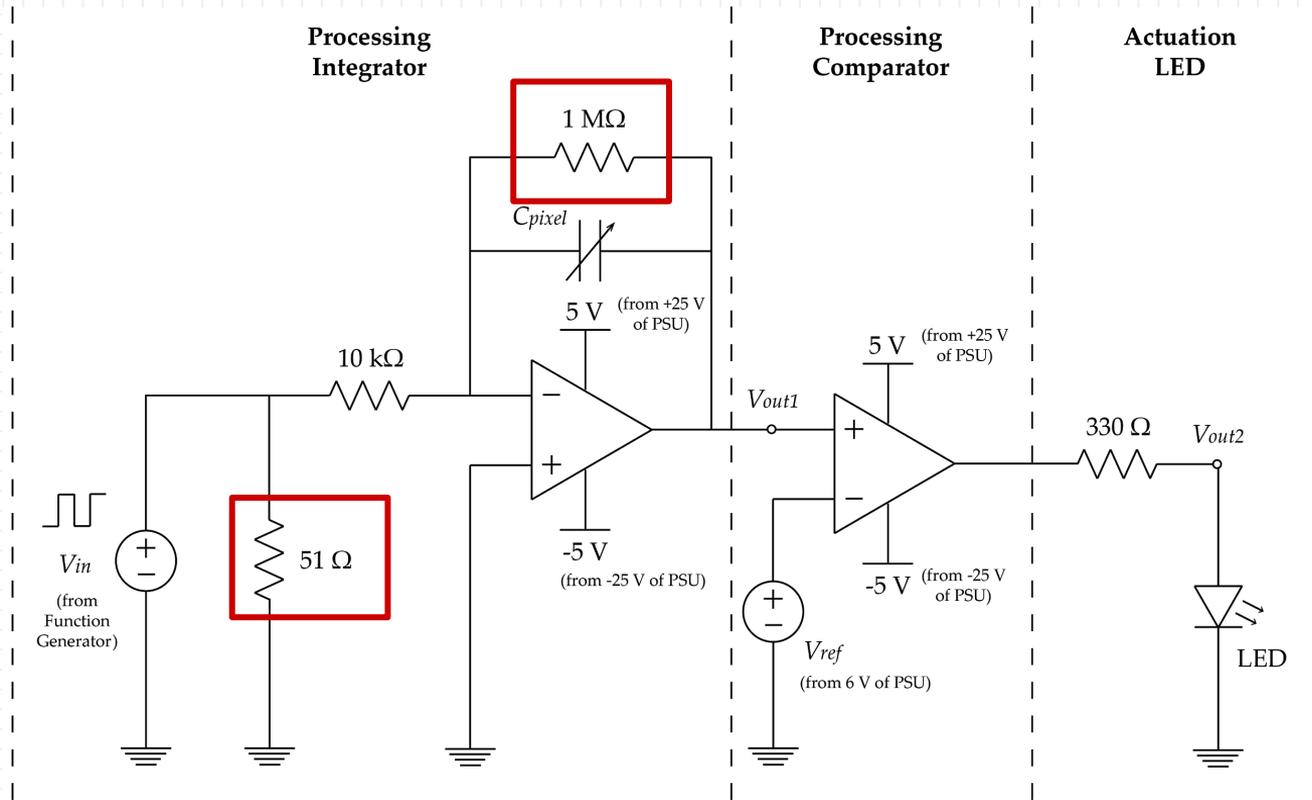


Our real world circuit

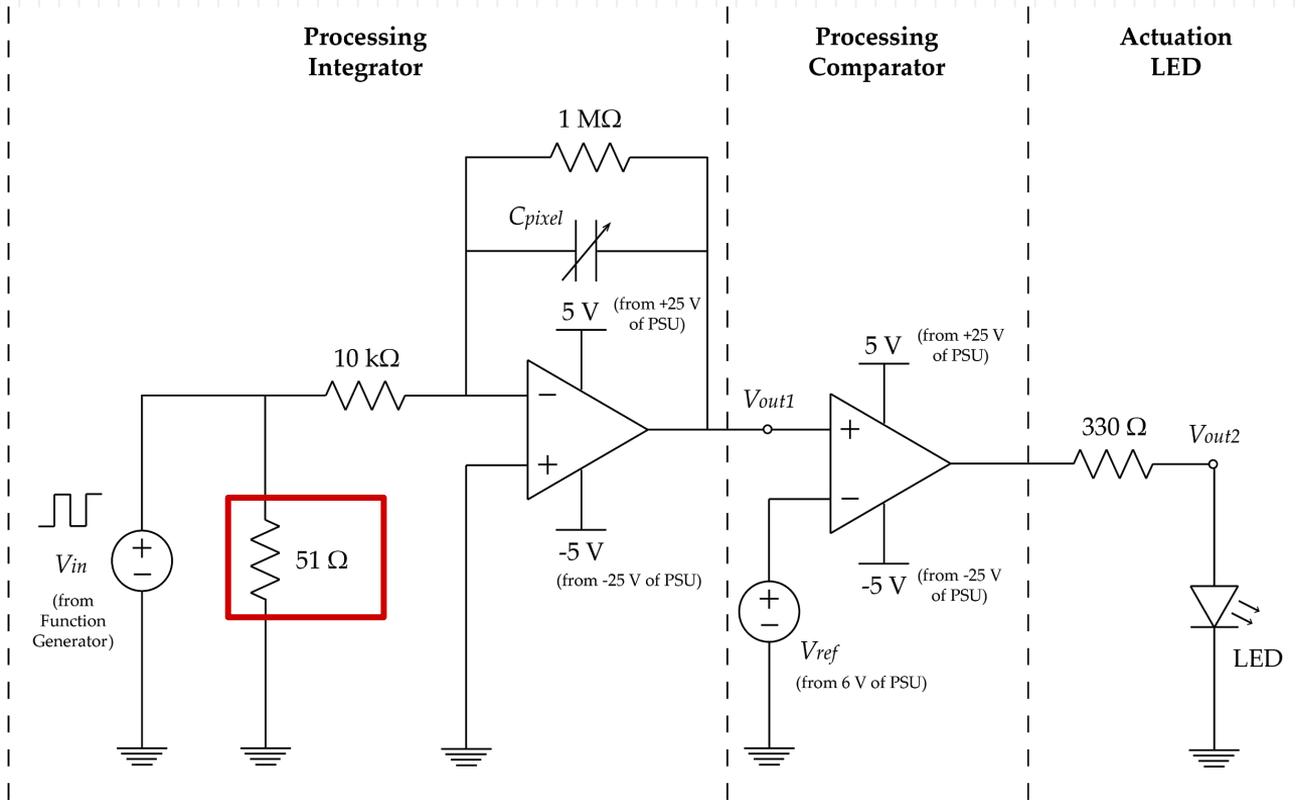
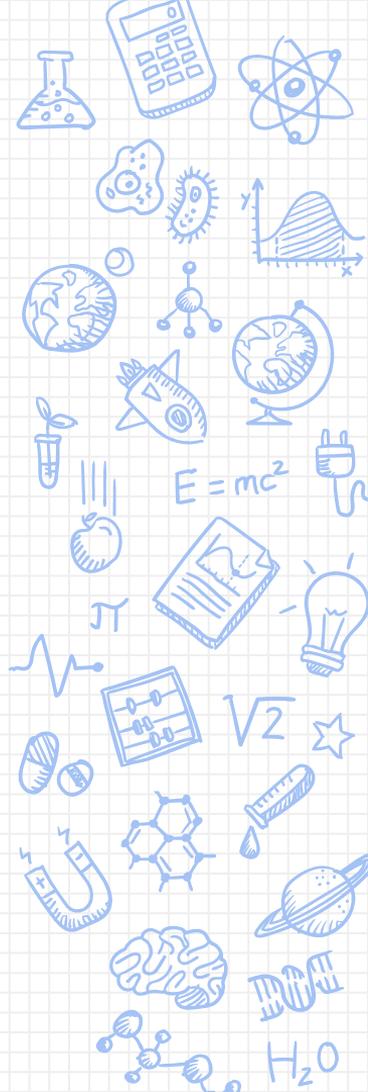


How does it help?

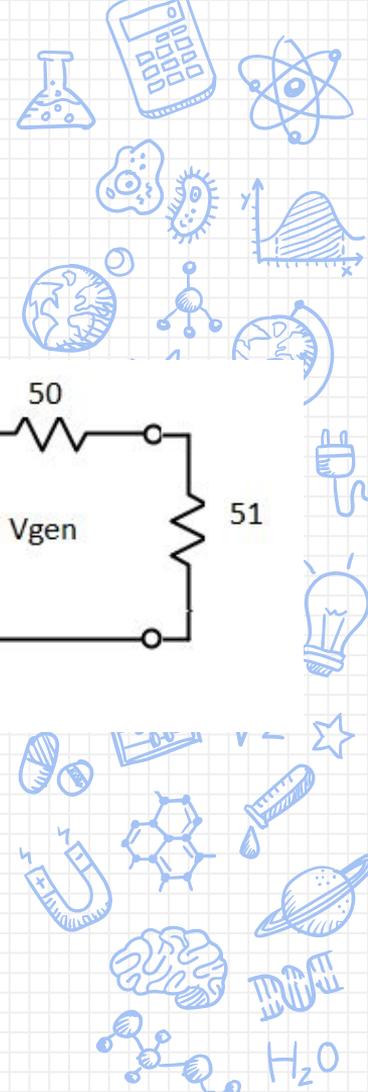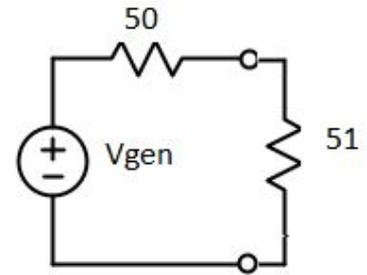- Compute the thevenin resistance of our circuit from the input port
 - It's about 51 Ohms
- Our circuit looks like a 51 ohm load with respect to the input, so the function generator is happy!
- (Note 50 Ohm resistors basically don't exist so we use 51 because it's the next closest value)




Our real world circuit

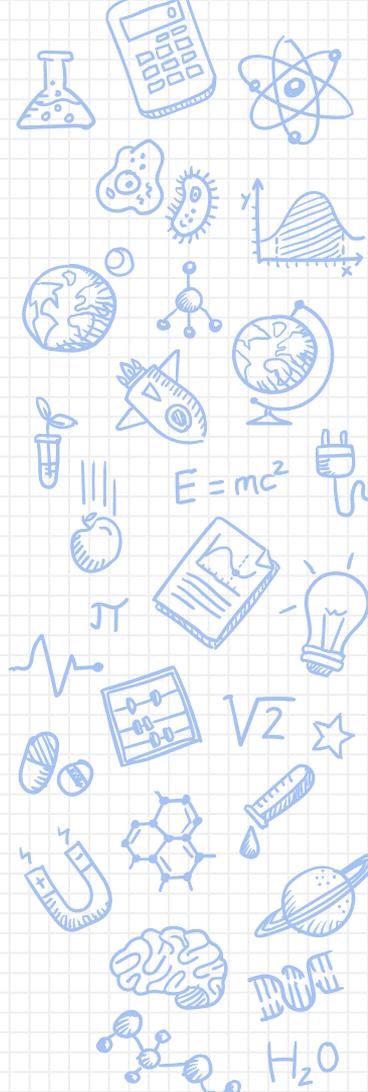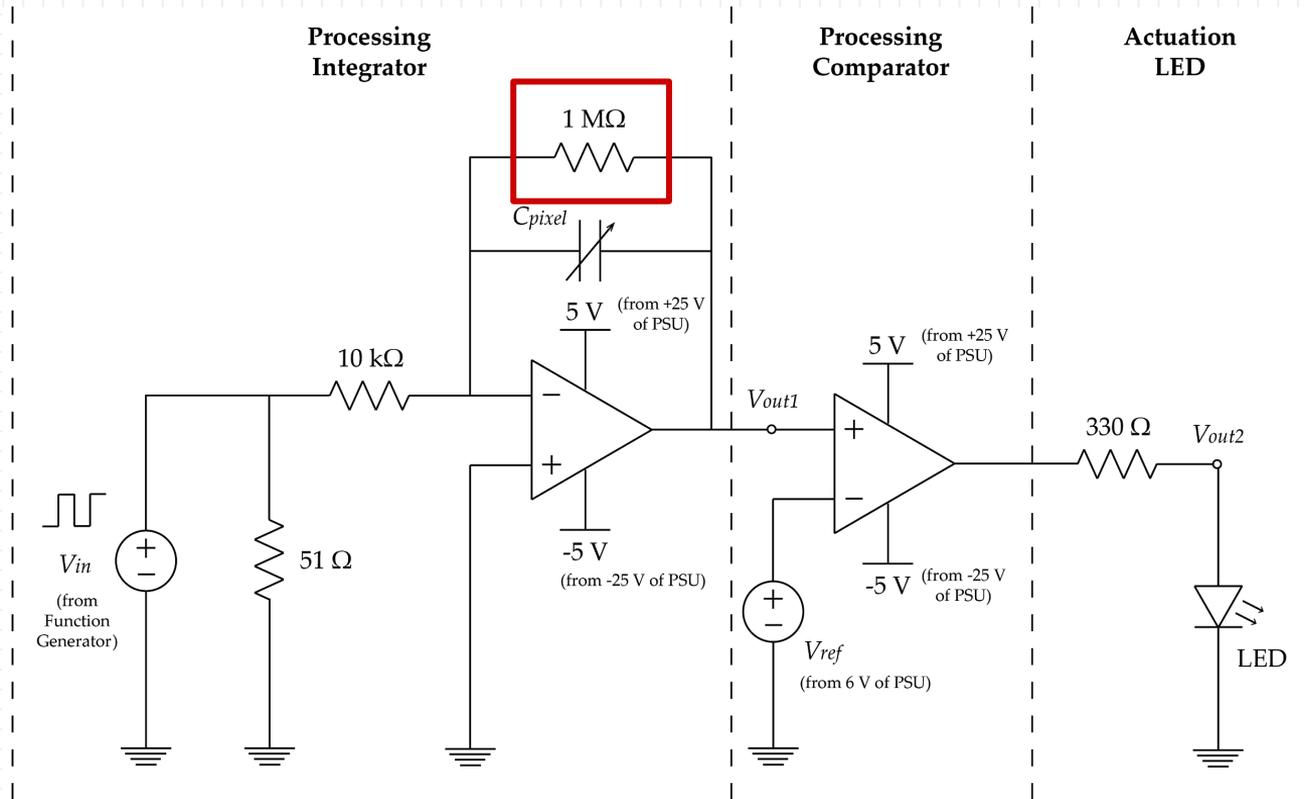


Another difference:

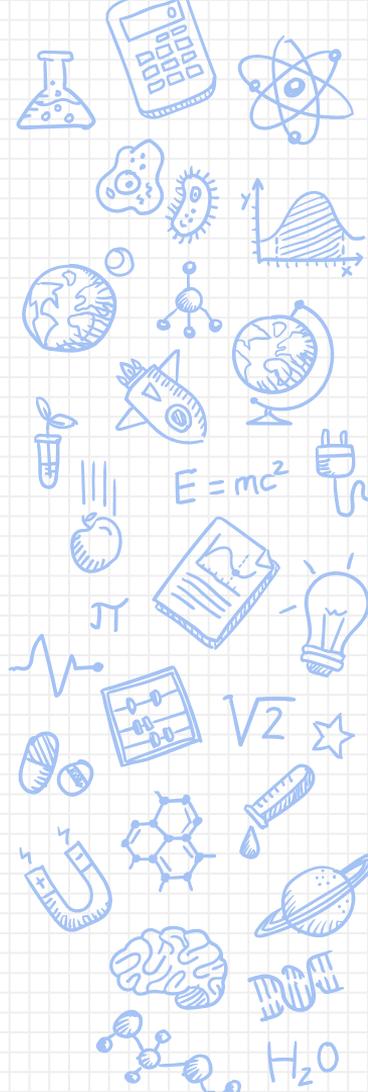
- It's a little out of scope
- It ensures that the circuit is always in negative feedback
 - Since it's 1 million Ohms it draws almost 0 current, and thus doesn't really affect our analysis
- If it was not there, the Capacitor acts as an open during constant voltage, so there is no feedback




Taking the Limit

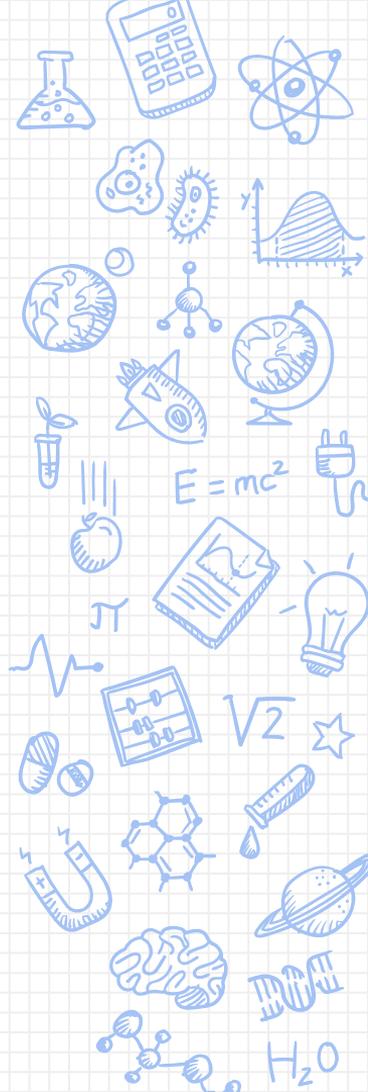- Make the caps really small, put them in the size of a screen
- Thousands of these sensing circuits can be made incredibly small
 - (less than 4mm x 4mm)
- Put a thousand of these and you can recognize 1000 different touch points
- No moving parts, much better (and more accurate) than the resistive touchscreen



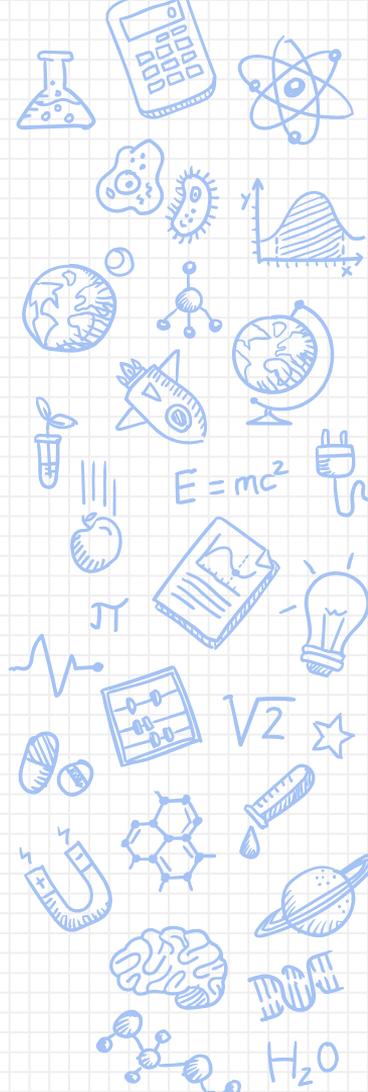


And that's it!

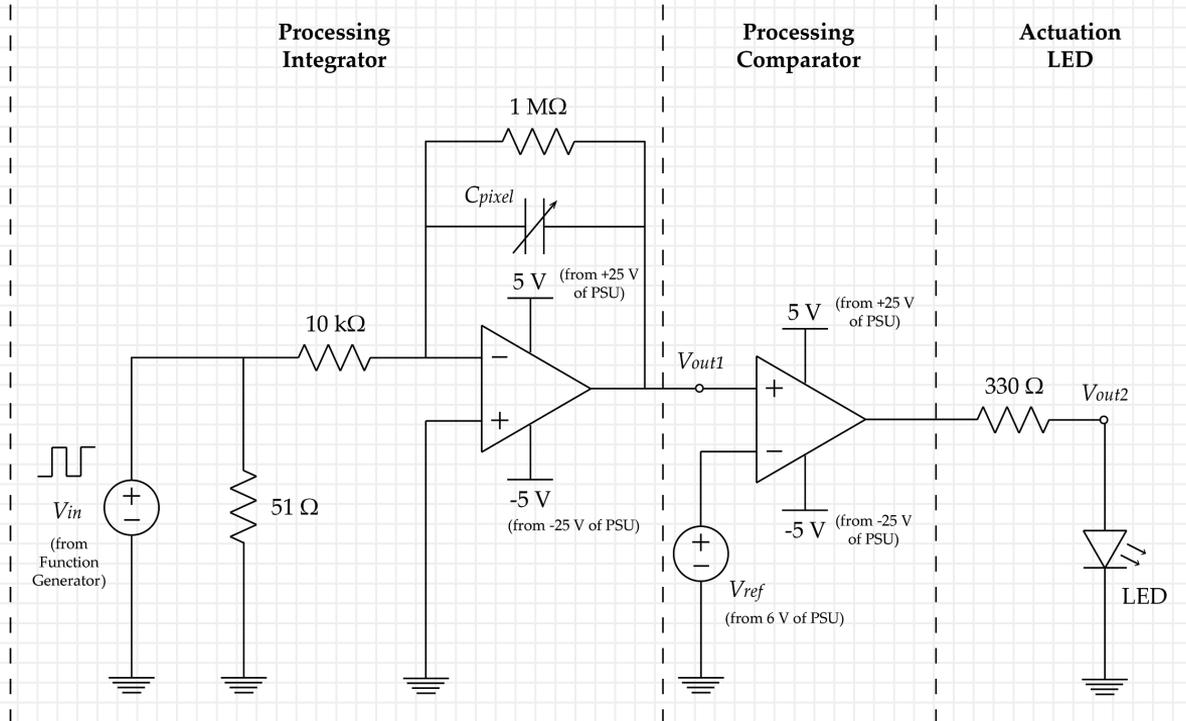


A Quick note

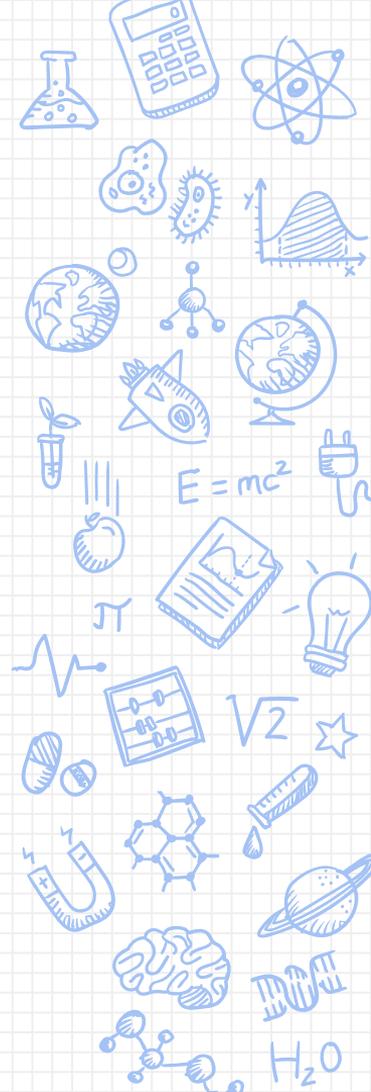- Planar wiring **required**
- We can and will refuse to help you fix your circuit if it's too messy
 - Use the copper wires at the TA desk and the wire strippers at your stations
 - Cut wires and resistors to be as short as you can and have them still work.




Why do u gotta be so strict tho :(

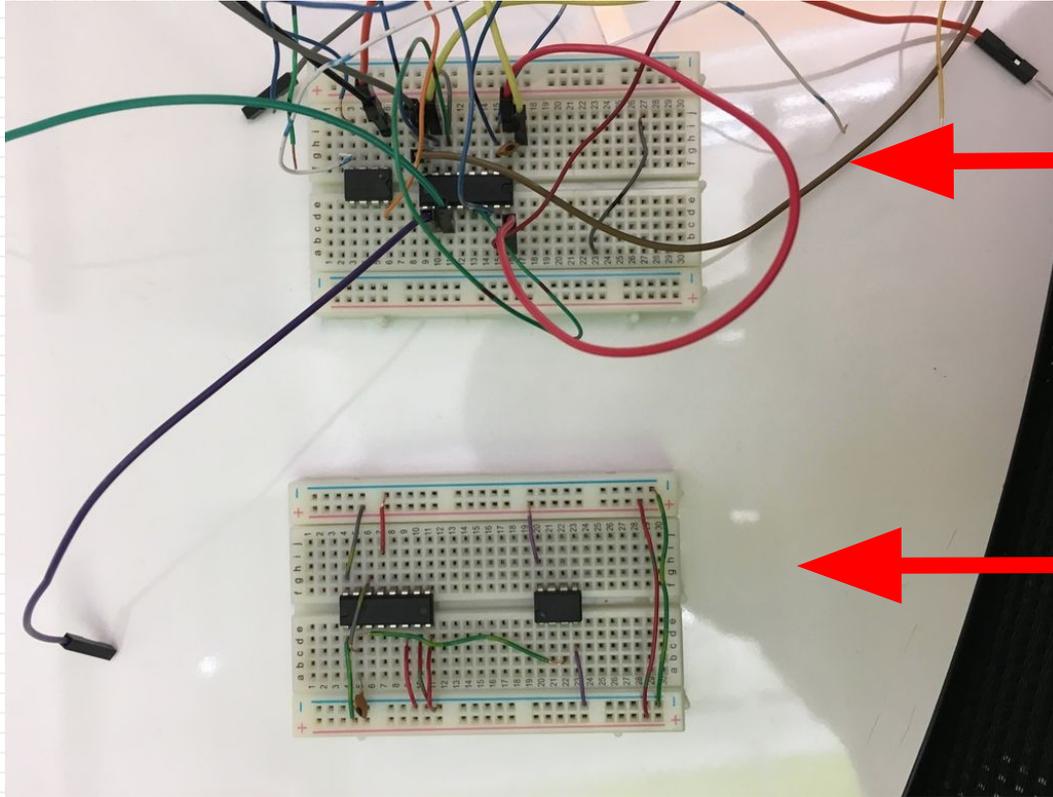

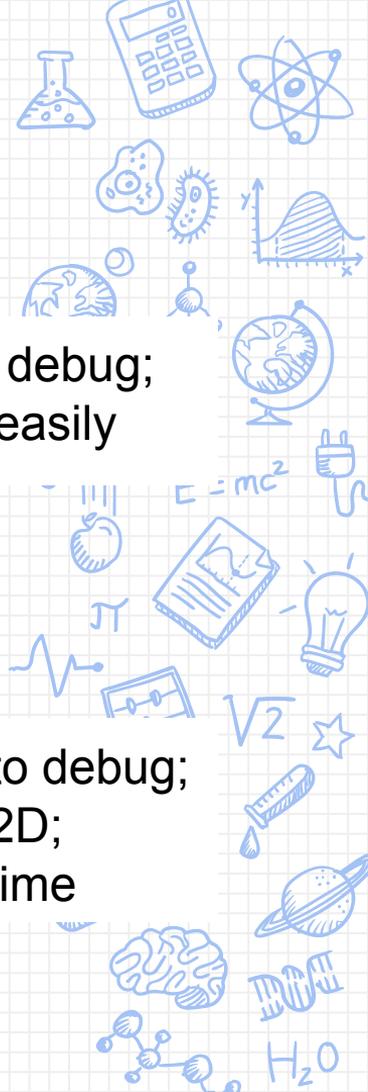1.5 Hour to debug;
Falls apart easily

5 seconds to debug;
Practically 2D;
Lasts a lifetime



Keep your circuits neat!

- **Cut wires to correct lengths.**
- Place op amp across the middle of your breadboard.
- If circuit is not neat, will not debug until it is.

