

(21)

# Lecture 8 - Module 2


EE16A

Today:

Note 18

- \* 2D Touchscreen wrap-up
- \* Audio system (DAC example)
- \* Intro to negative feedback
  - \* Golden rules
  - \* NFB examples
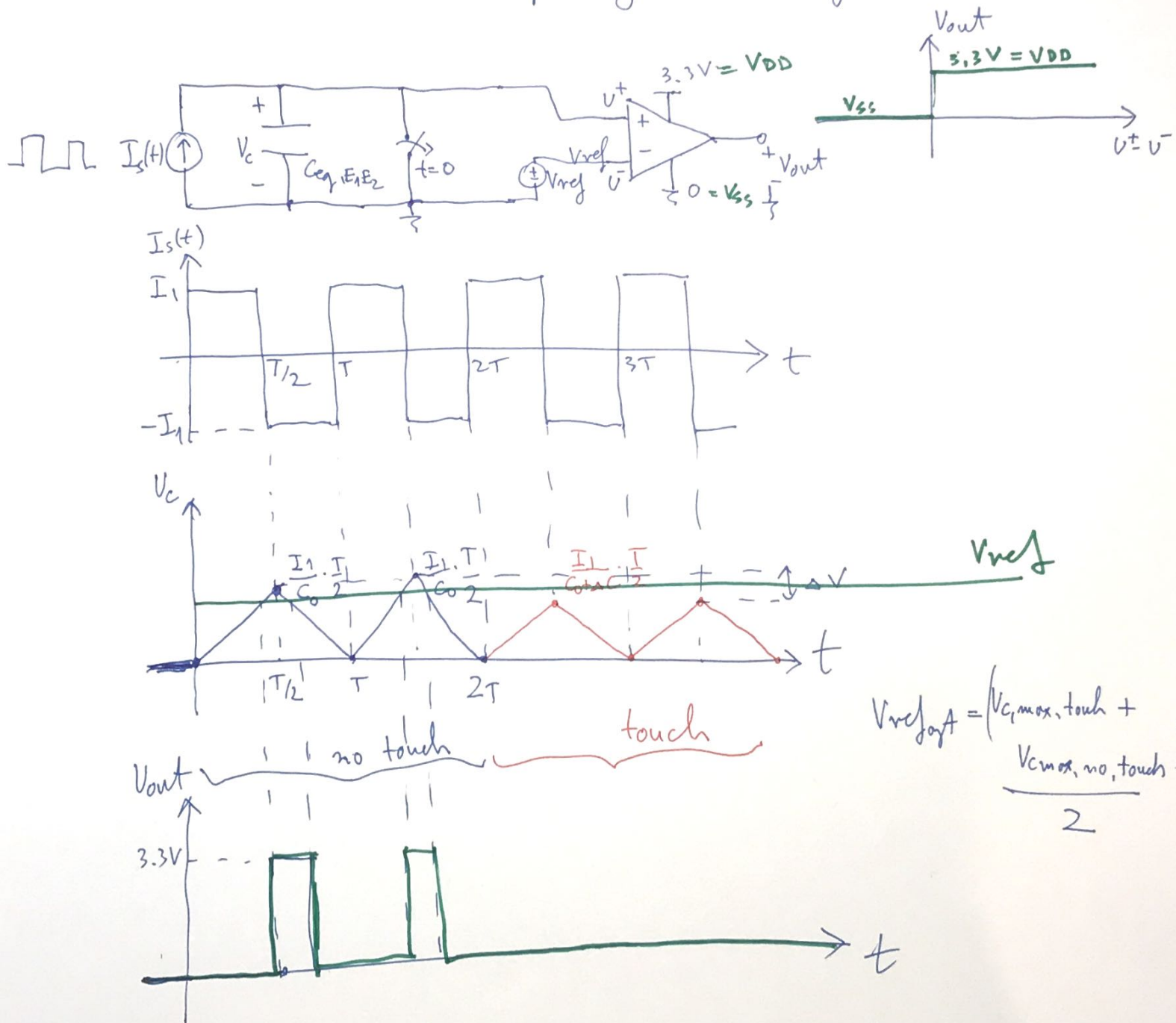
## 2D Touchscreen - putting it all together




l2

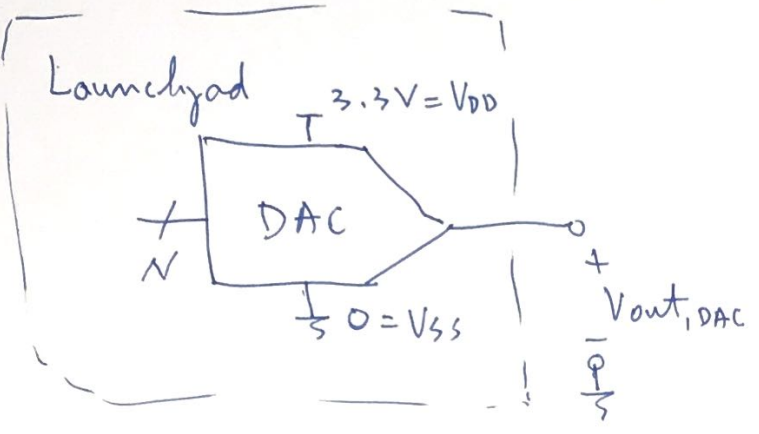
# "16A Boombox"

DAC: Digital-to-analog converter

(turns a digital-binary value into analog voltage)




Model

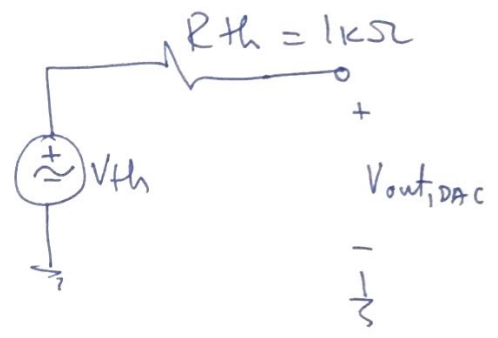


$$V_{th} \in [0, 3.3V]$$

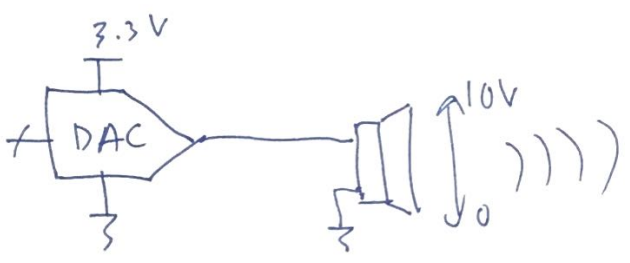$\parallel$   $V_{SS}$        $\parallel$   $V_{DD}$




Model

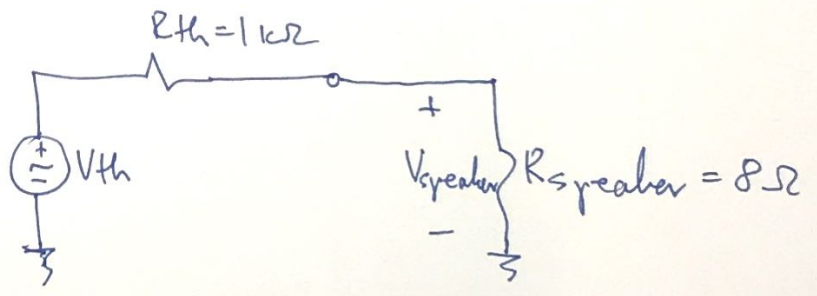

$$V_{speaker} = \frac{R_{speaker}}{R_{th} + R_{speaker}} \cdot V_{th} = \frac{8\Omega}{1k\Omega + 8\Omega} \cdot V_{th} = \frac{V_{th}}{126}$$

voltage divider

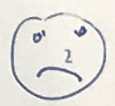


Loading effect !  
0

l3

Need to isolate the DAC from speaker

(use op-amp)


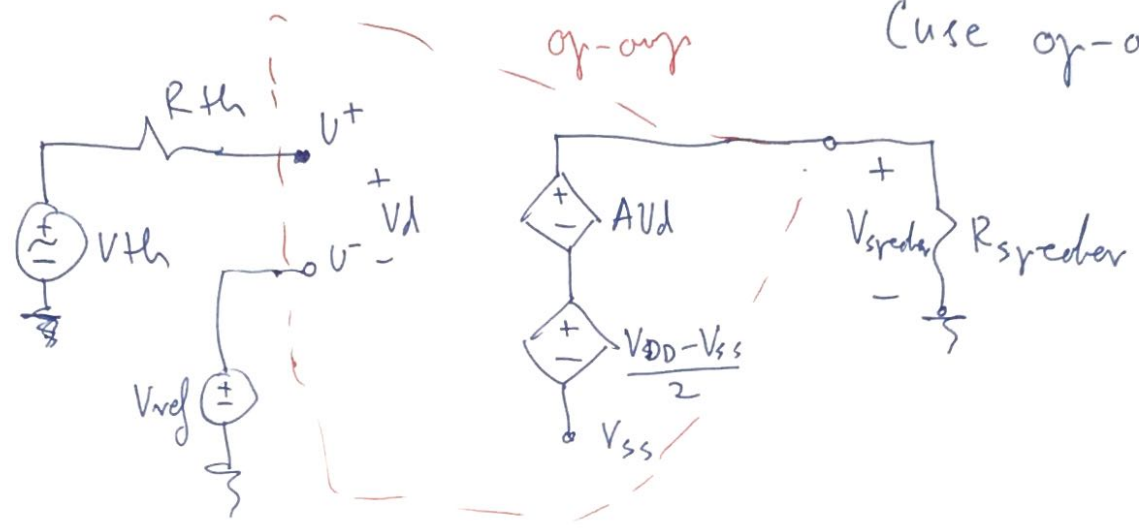


$$V_{DD} = -V_{SS} = 5V$$

(KVL)  $V_{speaker} = V_{SS} + \frac{V_{DD} - V_{SS}}{2} + AV_d = AV_d$  when  $V_{SS} < A \cdot V_d < V_{DD}$

~~$\frac{V_{DD} + V_{SS}}{2} \rightarrow 0$~~

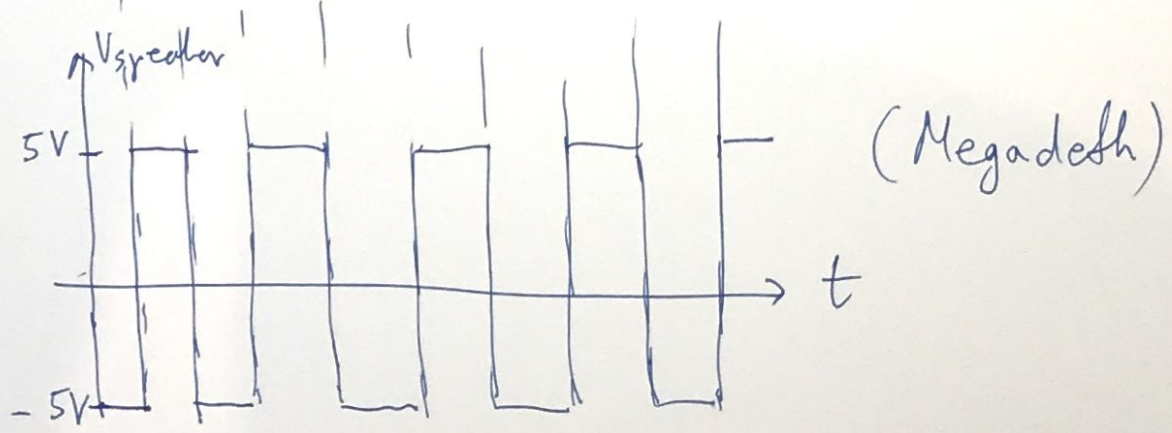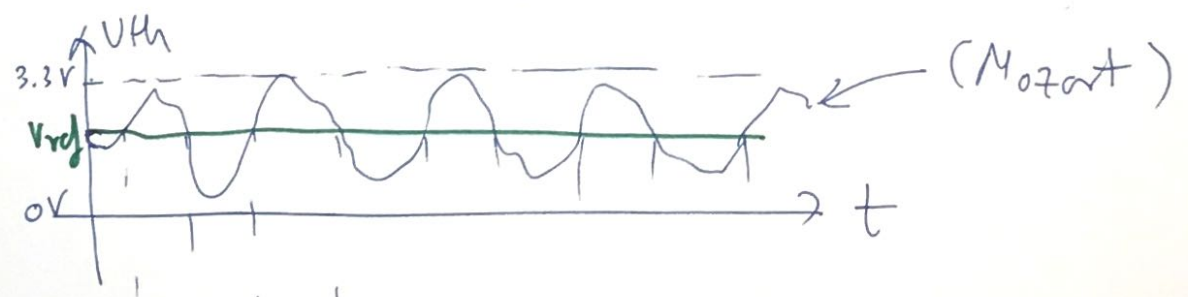(input)  $V_d = U^+ - U^- = V_{th} - V_{ref}$




Want isolation with controllable gain (e.g. 3x). Need a way to "tame" the op-amp.

(24)

# Negative feedback

Concept:

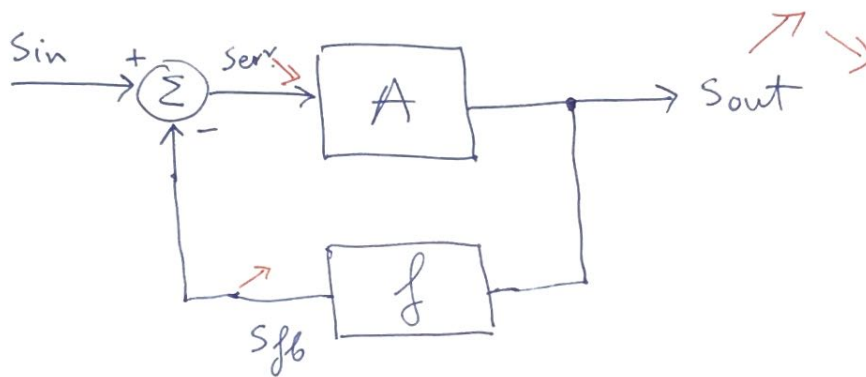

$$S_{err} = S_{in} - S_{fb}$$

$$S_{out} = A \cdot S_{err}$$

$$S_{fb} = f \cdot S_{out}$$

$$\Rightarrow \frac{S_{out}}{A} = S_{in} - f S_{out}$$

$$S_{out} \left( \frac{1}{A} + f \right) = S_{in}$$

$$\frac{S_{out}}{S_{in}} = \frac{1}{\frac{1}{A} + f} = \frac{A}{1 + Af}$$


$\frac{S_{out}}{S_{in}}$	$\xrightarrow{A \rightarrow \infty}$	$\frac{1}{f}$
--------------------------	--------------------------------------	---------------



25

of - any example NFB

(non-inverting amplifier)



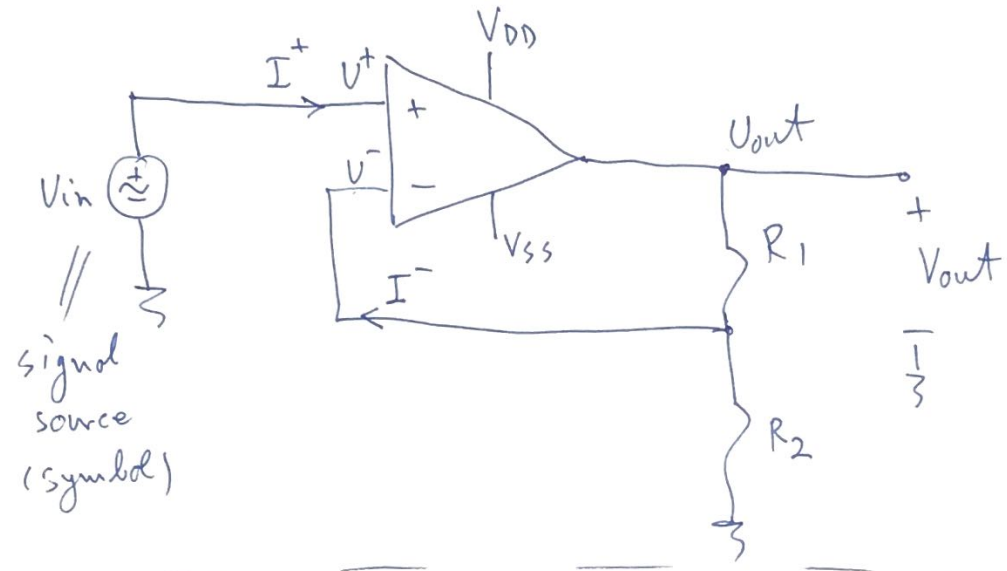


$U^+ \equiv \text{Sine}$   
 $V_{out} = S_{out}$

$U^- = \text{Sfb}$


$U^+ - U^- \equiv \text{sew}$

In NFB:

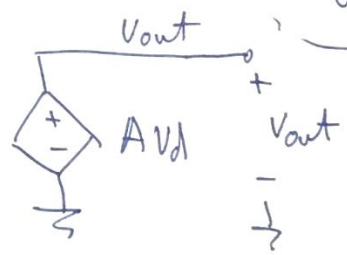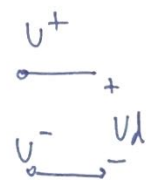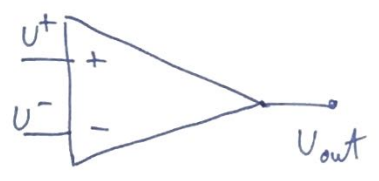

only for

$V_{SS} < V_{out} < V_{DD}$

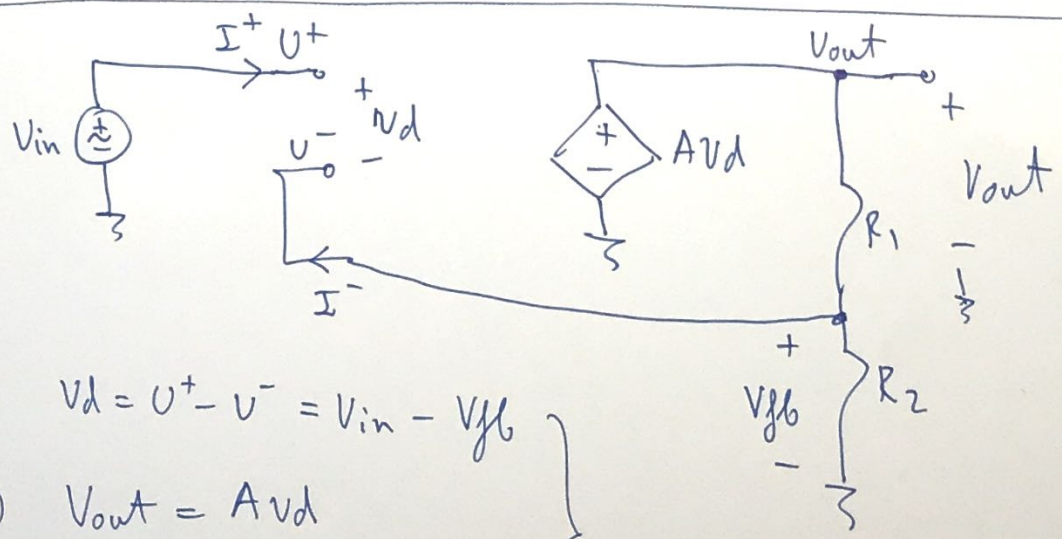

(1)  $V_d = U^+ - U^- = V_{in} - V_{fb}$

(2)  $V_{out} = A V_d$

(3)  $V_{fb} = \frac{R_2}{R_1 + R_2} V_{out} = f V_{out}$

$\Rightarrow V_{out} = A (V_{in} - f \cdot V_{out})$

26

$$V_{out} = A (V_{in} - \beta V_{out})$$

$$V_{out} (1 + A\beta) = A V_{in}$$

$$A_v = \text{Gain} = \frac{V_{out}}{V_{in}} = \frac{A}{1 + A\beta}$$

$$A_v \underset{A \rightarrow \infty}{=} \frac{1}{\beta} = \frac{R_1 + R_2}{R_2} = \boxed{1 + \frac{R_1}{R_2}}$$

$$A_v = 3 \Rightarrow R_1 = 2R_2$$

$$v_d = \frac{V_{out}}{A} \underset{A \rightarrow \infty}{=} \frac{1}{A} \cdot \frac{A}{1 + A\beta} V_{in} = \frac{V_{in}}{1 + A\beta} = 0$$

$$\boxed{\text{In NFB: } V^+ = V^- \text{ and } A \rightarrow \infty}$$

Golden rules:

(1)  $I^+ = I^- = 0$  (always true)

(2)  $V^+ = V^-$  (only in NFB &  $A \rightarrow \infty$ )