

Lecture 9 - Module 2


Today:
Note 19

- * NFB inspection
- * Summing op-amp / Neuron
- * Cascading det blocks (building large functions)

Determining the polarity of NFB:


- ① Turn-off independent sources
- ② Apply a disturbance at the output & follow the feedback to see if it's suppressed at the output

example:

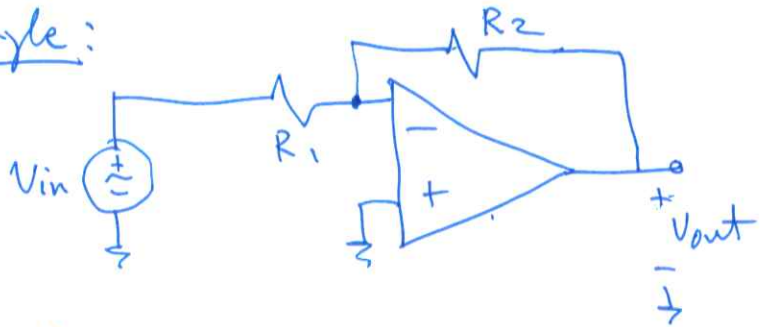


check for NFB:

step 1:
Null the source

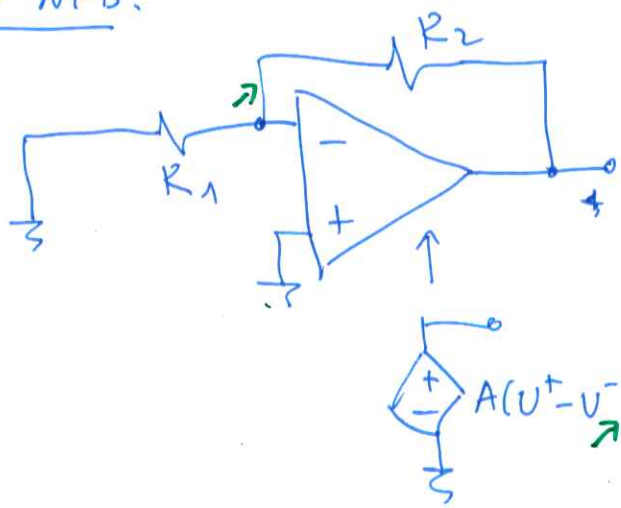

step 2: Apply disturbance

(NFB) 😊

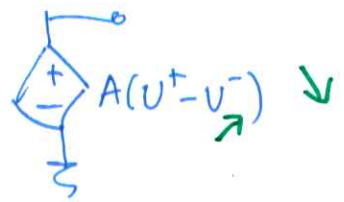


(2)

Solve:

NFB \Rightarrow

GR #2 applies $U^+ = U^-$

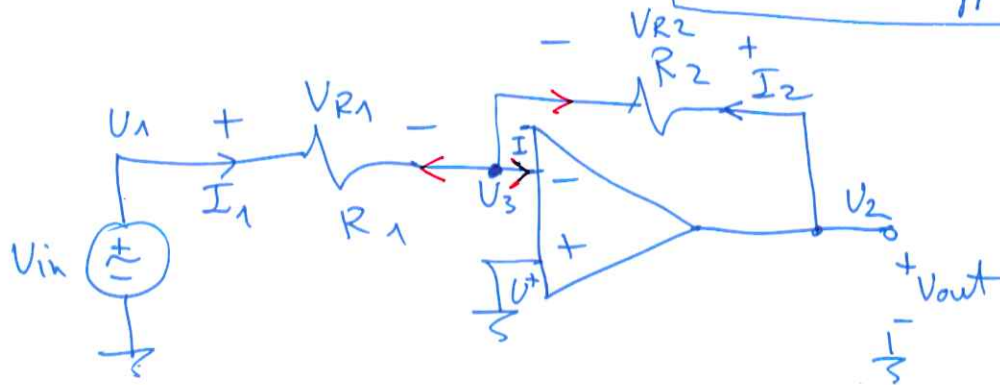

$$U_1 = V_{in}$$

$$U_2 = V_{out}$$

$U_3 = 0$ (clat in NFB \Rightarrow GR2 applies $U^+ = U^-$)
 also know $U^+ = 0 \Rightarrow U^- = 0$
 GR2

$$V_{R1} = I_1 R_1$$

$$V_{R2} = I_2 R_2$$

} elem. def.

$$U^- = U_3 = 0 \Rightarrow U_3 = 0$$

$$V_{R1} = U_1 - U_3 \overset{0}{=} = U_1 = V_{in}$$

$$V_{R2} = U_2 - U_3 \overset{0}{=} = U_2 = V_{out}$$

(KCL) $I_1 + I_2 = I \overset{0}{=} 0$ (GR #1)

$$V_{in} = I_1 R_1, \quad V_{out} = I_2 R_2$$

$$\underbrace{\frac{V_{in}}{R_1}}_{I_1} + \underbrace{\frac{V_{out}}{R_2}}_{I_2} = 0 \Rightarrow V_{out} = -\frac{R_2}{R_1} \cdot V_{in}$$

$$A_V = \frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1}$$

inverting amplifier

l3

A faster way:

GR2: $V^+ = V^-$, $V_3 = V^-$ \Rightarrow $V_3 = 0$

$V^+ = 0$


GR1 & KCL:

$$\frac{V_3 - V_1}{R_1} + \frac{V_3 - V_2}{R_2} + I = 0$$


$$-\frac{V_{in}}{R_1} - \frac{V_{out}}{R_2} = 0$$

$$V_{out} = -\frac{R_2}{R_1} V_{in}$$

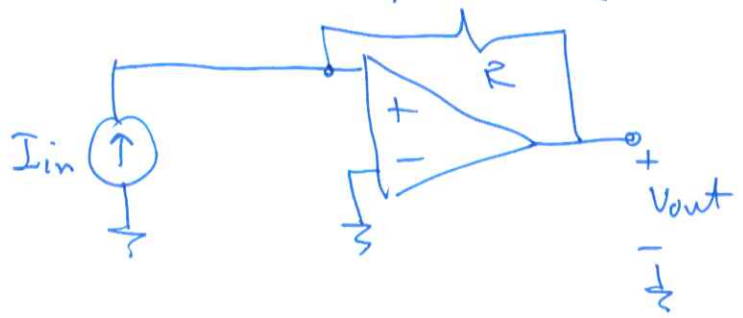Another example: (trans-resistance amplifier)





check NFB:

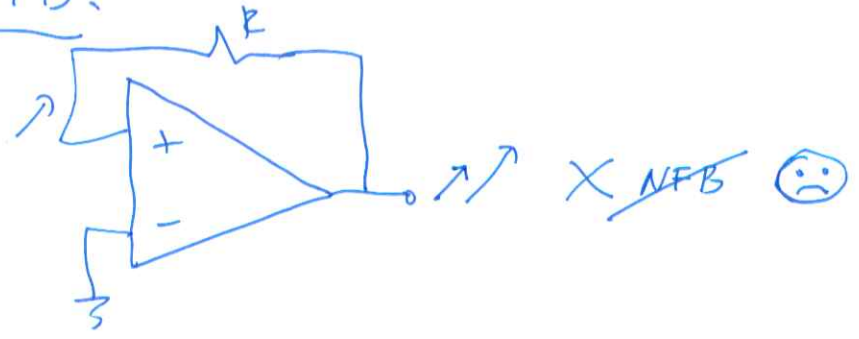

(2h)

Flip - He polarity :

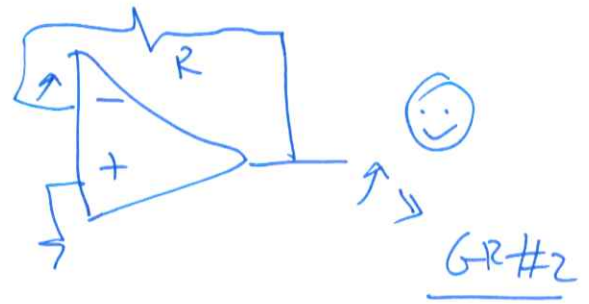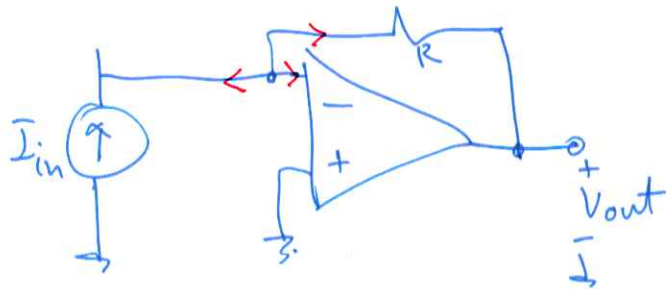

✓ NFB: $U^+ = U^-$ $U^+ = 0$
 $\rightarrow U^- = 0$


$$\overset{\text{GR\#2}}{\circ} \left(\frac{V^+ - V_{out}}{R} + (-I_{in}) + \overset{\text{GR\#1}}{\circ} I \right) = 0$$

$$V_{out} = -I_{in} \cdot R$$


$$\boxed{\frac{V_{out}}{I_{in}} = -R}$$

25


Another example:

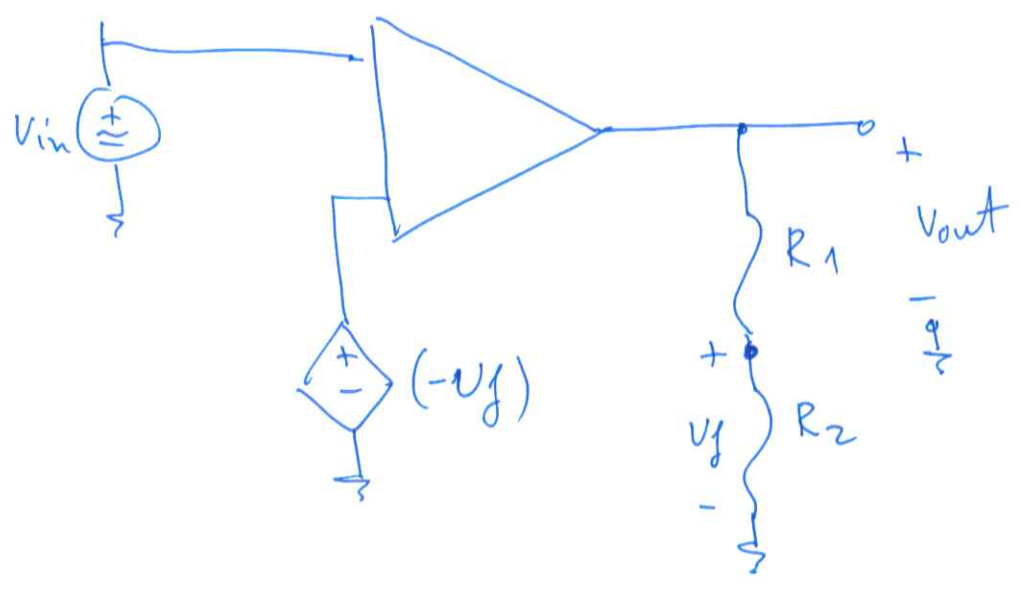

Check NFB:

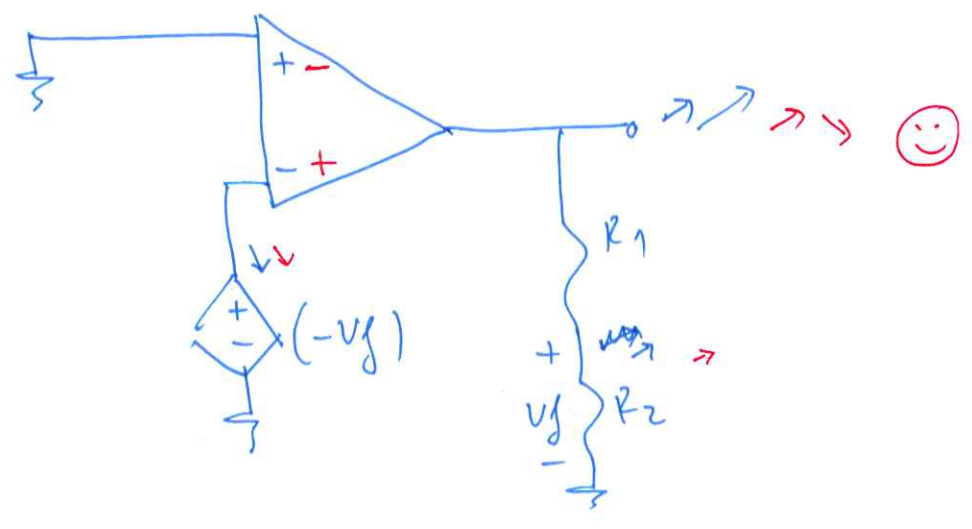

solve:

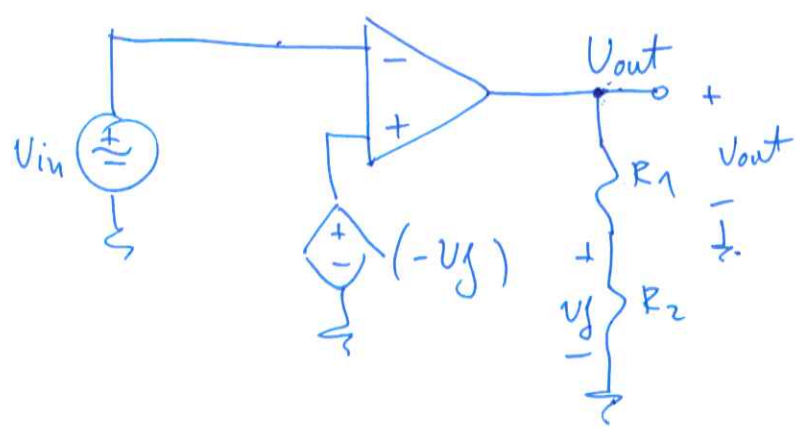

voltage divider:

$$V_f = \frac{V_{out} \cdot R_2}{R_1 + R_2}$$


NFB (GR #2)

$$V_{in} = -V_f$$

$$V_{in} = -\frac{R_2}{R_1 + R_2} V_{out} \Rightarrow \left\{ A_v = \frac{V_{out}}{V_{in}} = -\left(1 + \frac{R_1}{R_2}\right) \right\}$$

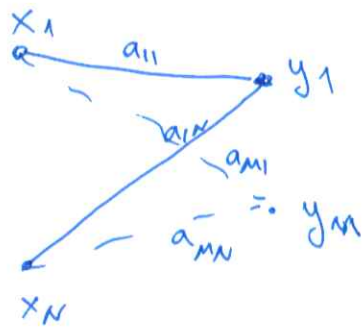Q6

Building energy-efficient deep neural networks





$$\vec{y} = A \vec{x}$$

$$\begin{bmatrix} y_1 \\ \vdots \\ y_m \end{bmatrix} = \begin{bmatrix} a_{11} & \dots & a_{1N} \\ \vdots & \ddots & \vdots \\ a_{m1} & \dots & a_{mN} \end{bmatrix} \begin{bmatrix} x_1 \\ \vdots \\ x_N \end{bmatrix}$$

(inverting summer)

check for NFB:

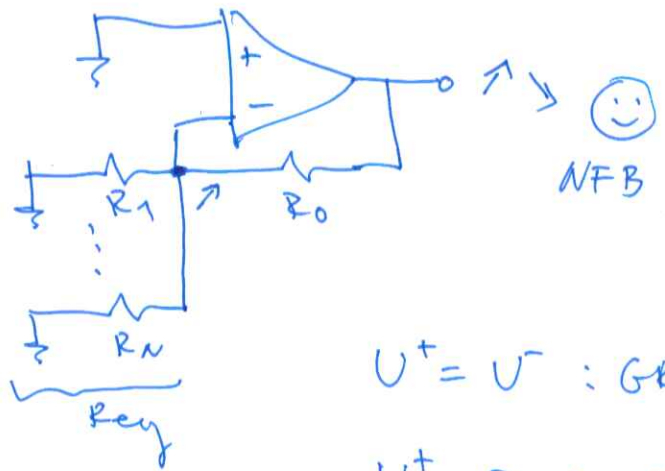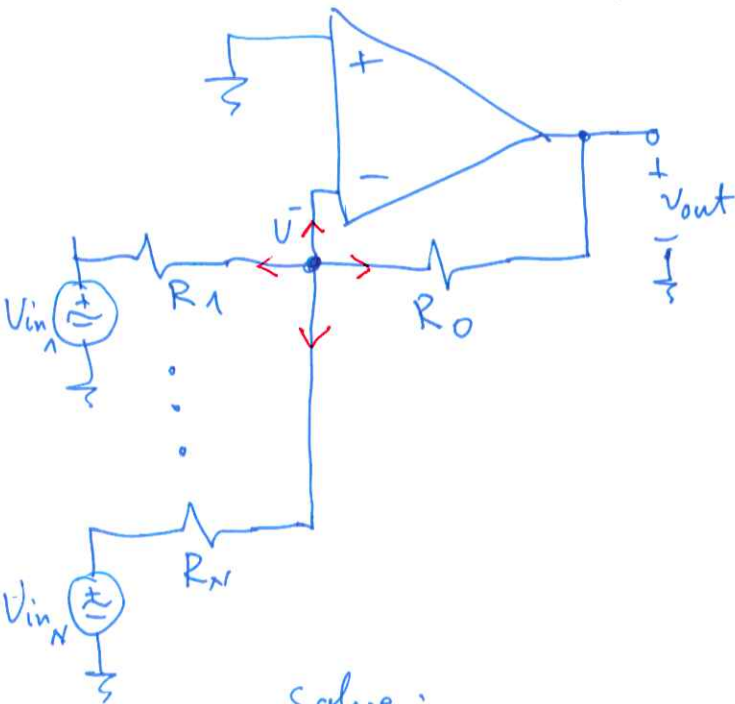

Solve:

$$U^+ = U^- : \text{GRZ}$$

$$U^+ = 0 \Rightarrow U^- = 0$$

KCL:


$$\frac{0 - V_{in1}}{R_1} + \dots + \frac{0 - V_{inN}}{R_N} + \frac{0 - V_{out}}{R_0} + I = 0$$

$$y_1 = \underbrace{-\frac{R_0}{R_1}}_{a_{11}} V_{in1} + \dots + \underbrace{\left(-\frac{R_0}{R_N}\right)}_{a_{1N}} V_{inN}$$


(7)

Think in block diagrams:


Concept:

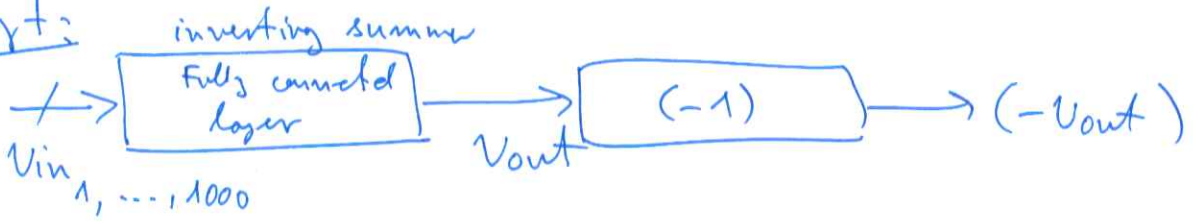

Implementation:

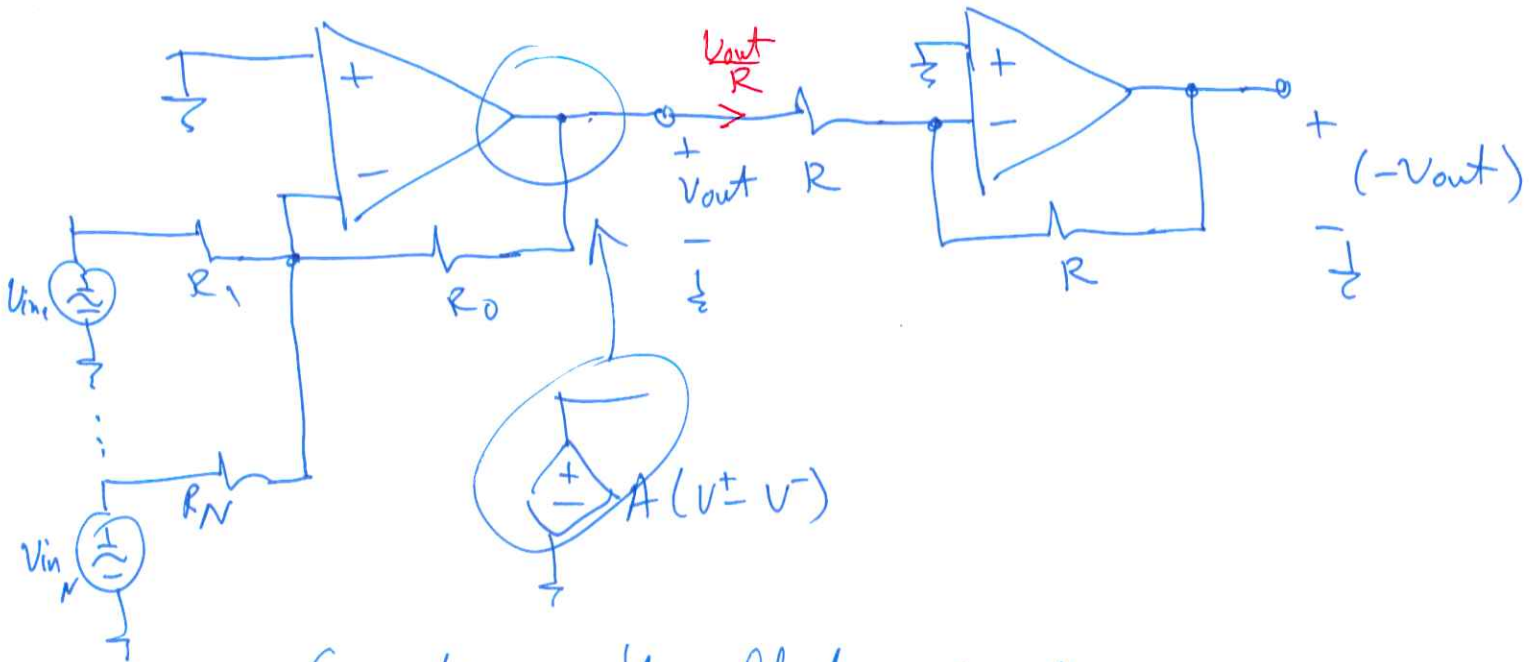

Cascading the blocks (safe way):

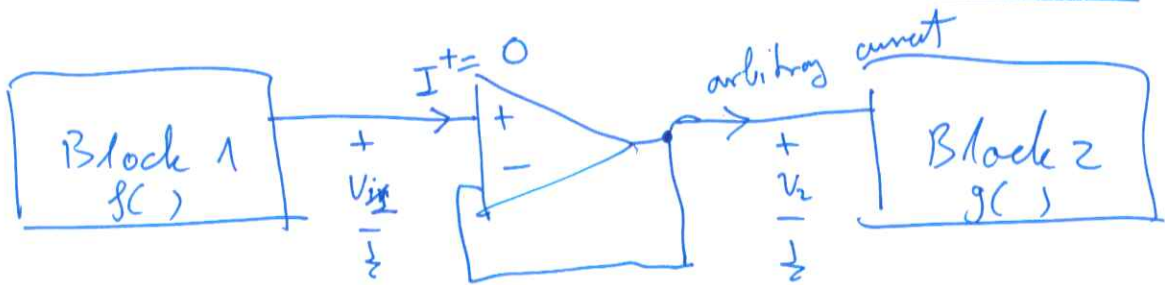

$$V_1 = V_2$$

NFB:

$$V^+ = V^-$$

$$V_{in} = V_{out}$$

(Unity gain buffer)