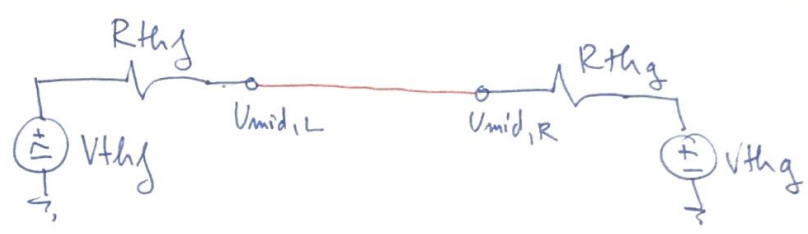




# Lecture 10 - Module 2

Today:  
Note 20

- \* Composing blocks (continued)
- \* Design procedure
- \* Design examples



$V_{mid,L,oc} = V_{thf} \neq V_{mid,L} = \frac{R_{thg}}{R_{thf} + R_{thg}} \cdot V_{thf} + \frac{R_{thf}}{R_{thf} + R_{thg}} V_{thg}$   
 in general

Ideal isolation:


except when:  $R_{thf} = 0$

or  $R_{thg} \rightarrow \infty$  is o.c.

From perspective of block f  $\Rightarrow$  see an open-circuit


From perspective of block g  $\Rightarrow$  see a voltage source

i.e.  $R_{thf} = 0$

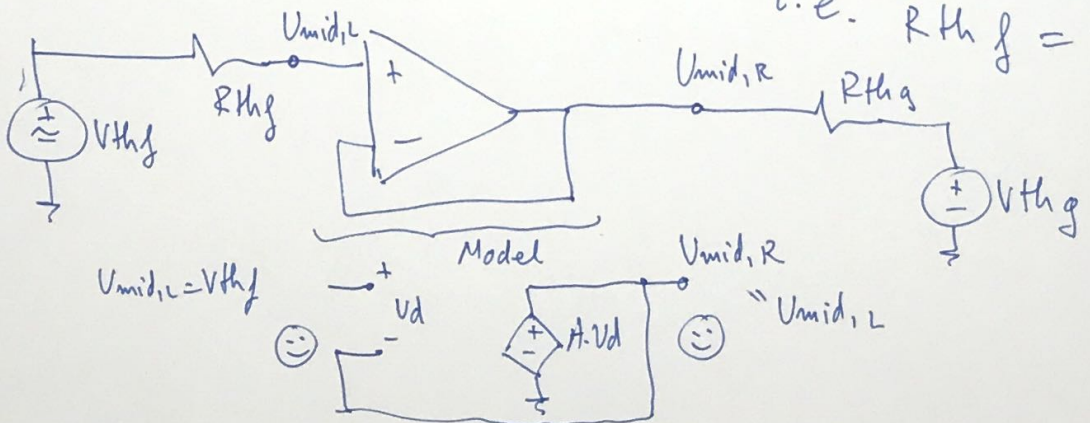


Q2

Example 1: Want this:

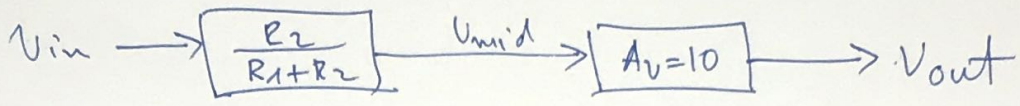

Implement:

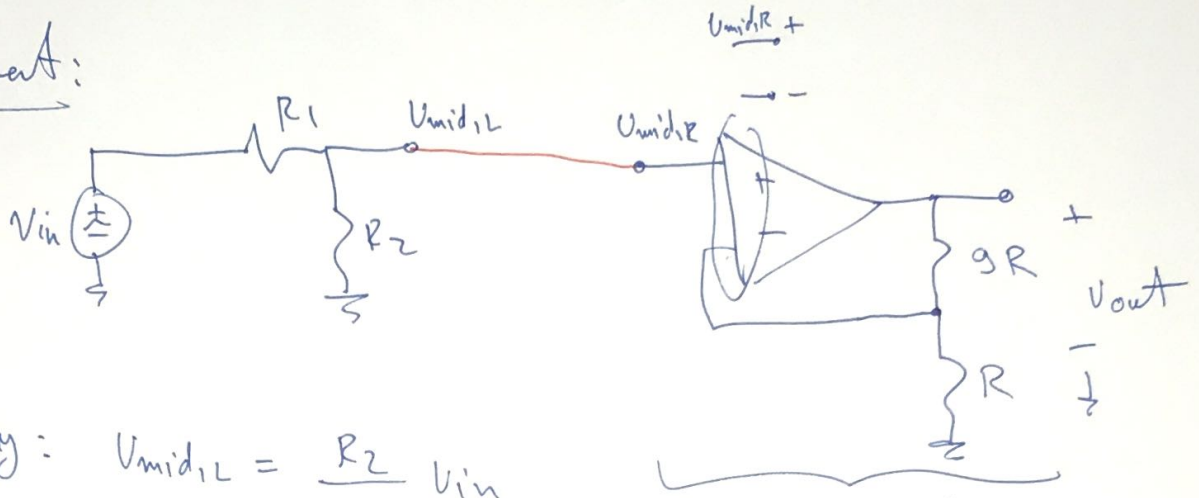


Verify:  $U_{mid,L} = \frac{R_2}{R_1 + R_2} V_{in}$   
 $U_{mid,L} = U_{mid,R}$



$A_v = \frac{V_{out}}{U_{mid,R}} = 10$

Example 2:

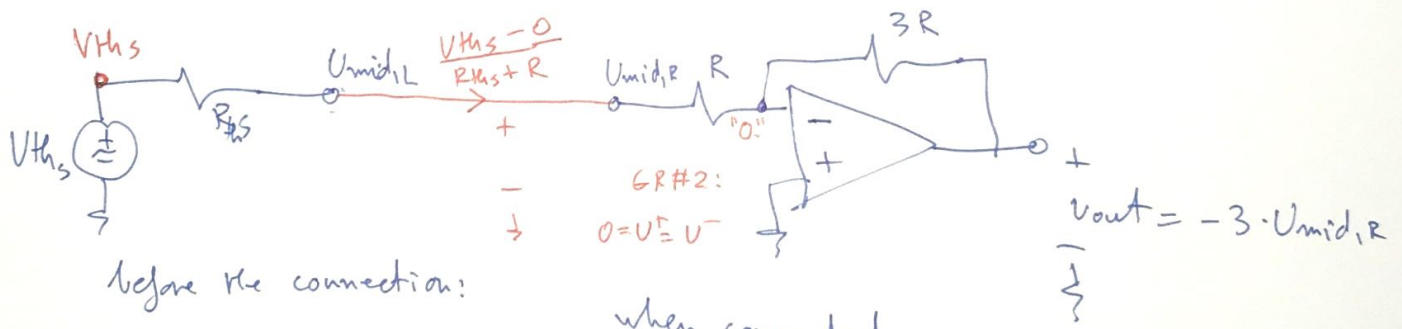


before the connection:  
 $U_{mid,L} = V_{th,s}$

when connected:

$U_{mid,L} = \frac{R}{R + R_{th,s}} \cdot V_{th,s} \neq V_{th,s}$

salm:

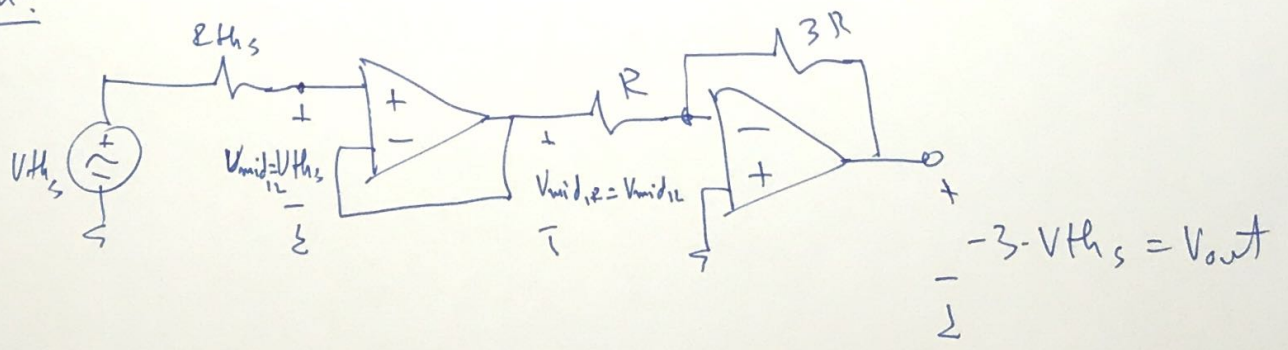

l3

## Design procedure

step 1:  
(specification)

Concretely (re)state your goal for the design. (most often from a word spec)

step 2:  
(strategy)

Describe (often as a block diagram) the strategy to achieve the goal.

↳ often review what you can measure vs. what you wanted to know

↳ what is the relationship between the two (e.g. touch / no-touch)

touch / no-touch → change in cap → change in voltage

step 3:  
(Implementation)

Implement the components within the strategy

↳ Remind yourself of blocks you know that can provide the desired block function

↳ Think about how to extend / modify the blocks you know (at least #1000)


step 4:  
(Verification/analysis)

Does the implementation in step 3 do what is specified in step 1?




↳ check for block-to-block connections

Q4

# Example design #1: ("Countdown timer")

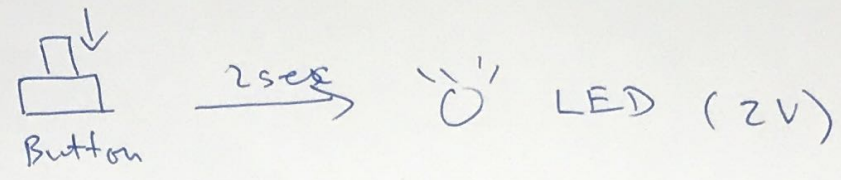

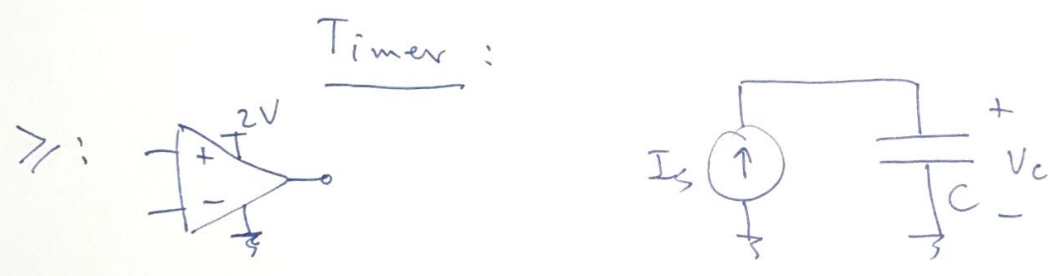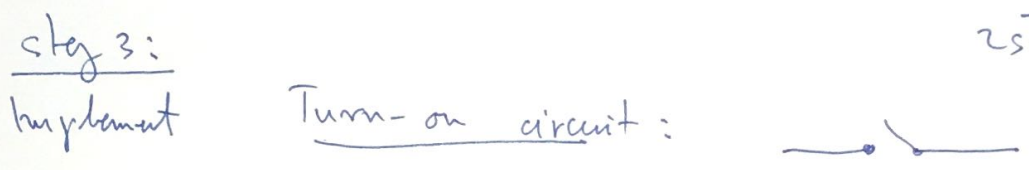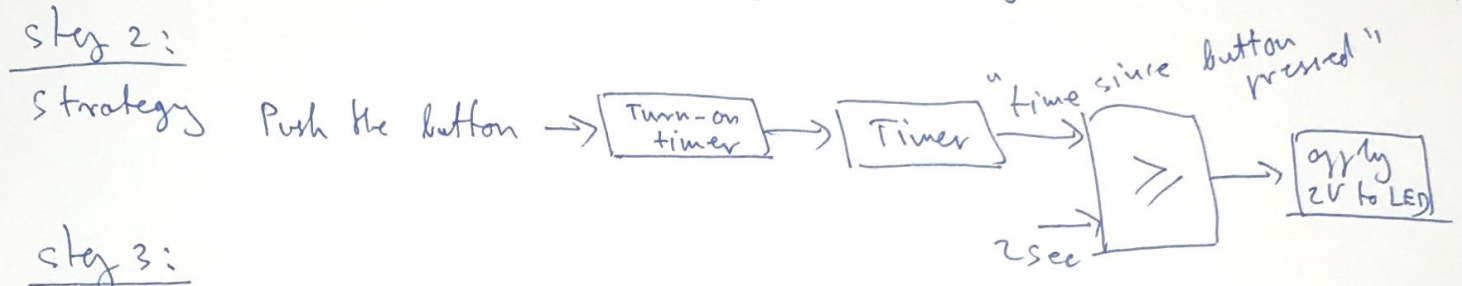step 1: Build a circuit that after a button is pressed (spec) measures 2s and will then apply 2V across the LED. (I assume you can only push the button once)




$$I_c = C \frac{dV_c}{dt}$$


$$V_c(t) = \frac{I_s}{C} \cdot t + V_c(0)$$

$V_{time}$

Together:

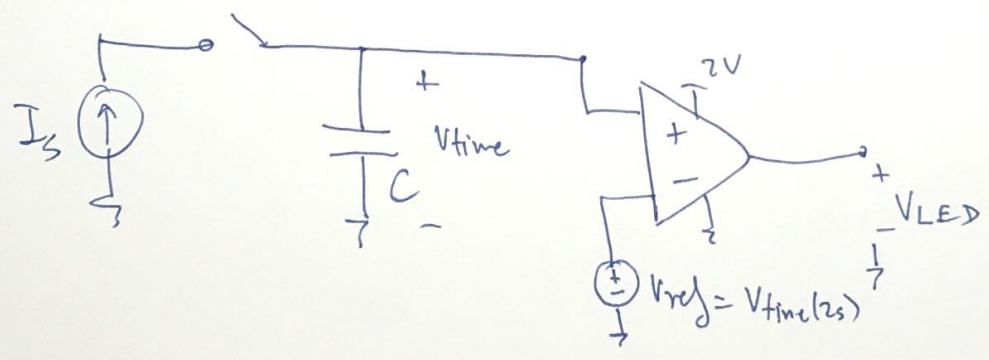


Q5 step 4: Verify

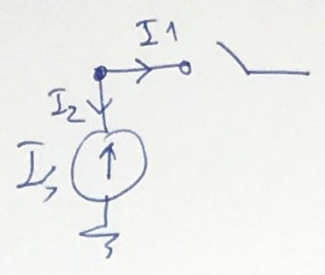


$I_1 = 0$  (o.c. def)  
 $I_2 = -I_s$  (curr. source elem. def)  
 $I_1 + I_2 = 0$  (KCL)  
 $0 + (-I_s) = 0$  ✗ violation

revise:

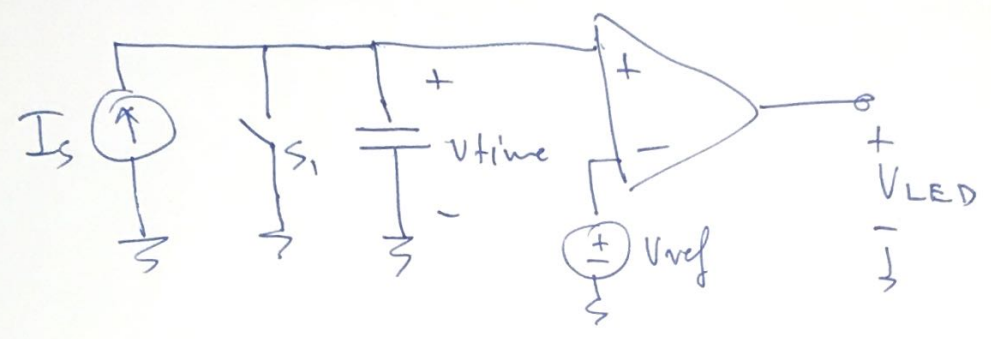


Before the button is pushed: S1 is on

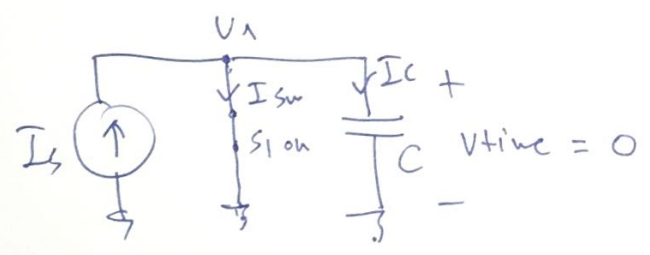

$V_1 = 0$  (wire def)  
 $V_{time} = V_1 = 0$   
 $I_c = C \frac{dV_{time}}{dt} = 0$   
 by KCL  $I_s = I_{sw} + I_c$   
 $I_s = I_{sw}$

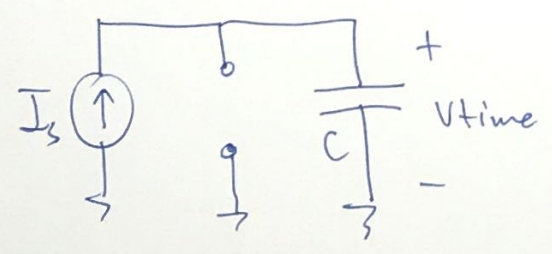when you push the button: S1 is off @  $t = t_0$



$V_{time}(t_0) = 0$   
 $V_{time}(t) = \frac{I_s}{C} \cdot (t - t_0) + 0$   
 $V_{time}(t_0 + 2s) = V_{ref}$