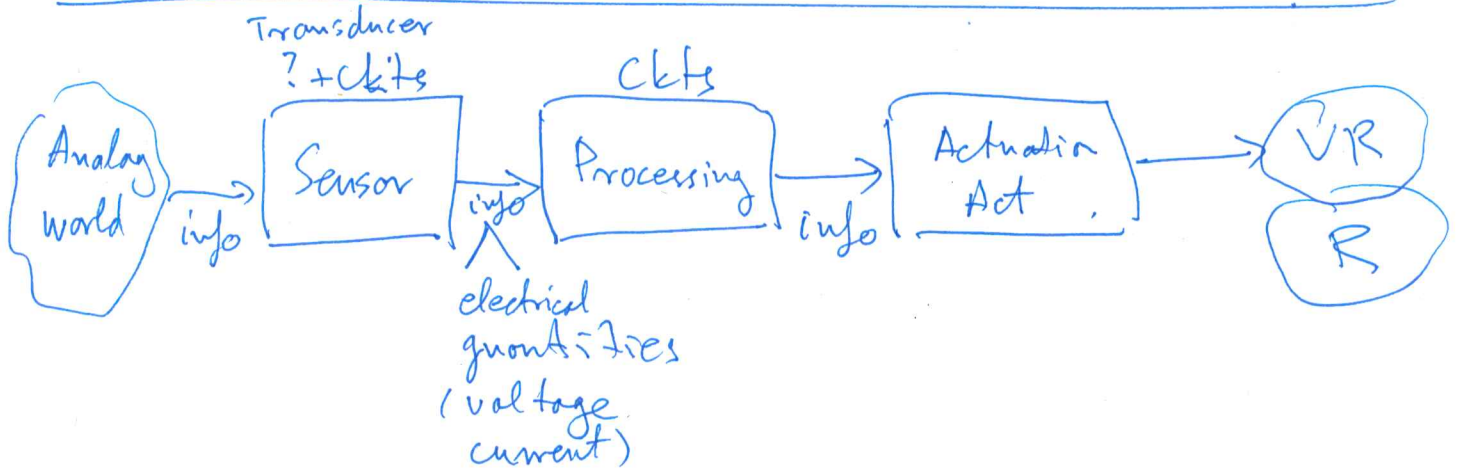


# Lecture 1 - Module 2

Today:

\* Sensing, Processing & Actuation Systems

\* Circuit Analysis Algorithm (Note 11)




## Electrical Circuit Analysis Algorithm (tool)

SPICE

<u>Quantities:</u>	<u>Analytical Symbol</u>	<u>Units</u>
Voltage	V	Volts [V]
Current	I	Amps [A]
Resistance	R	Ohms [ $\Omega$ ]

Circuit diagram

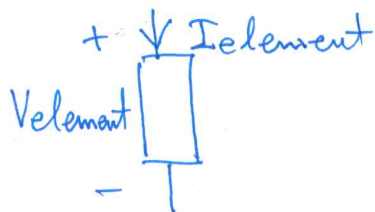


(collection of elements, where each element has some voltage across it and some current through it)


(2)

# Key circuit elements:


① Wire

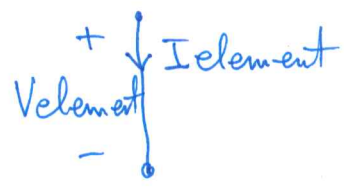

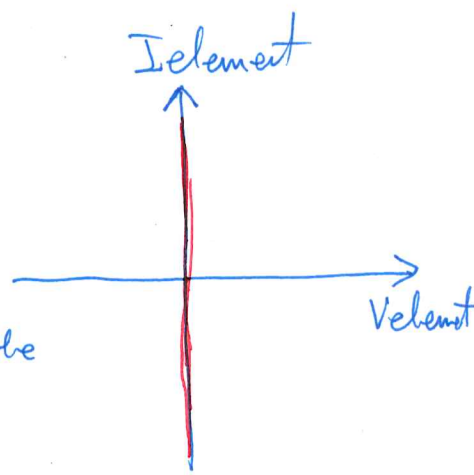
$V_{element} = 0$   
 $I_{element} = ?$   
 (set by the ext. circuit)




② Resistor

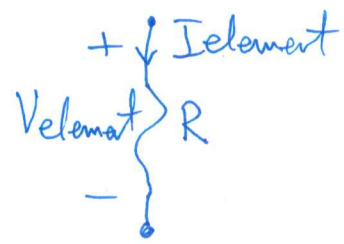

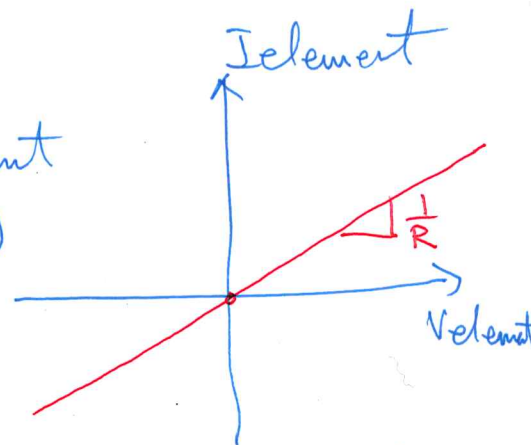
$V_{element} = R \cdot I_{element}$   
 $\Leftrightarrow$  (Ohm's law)




③ "Open" circuit

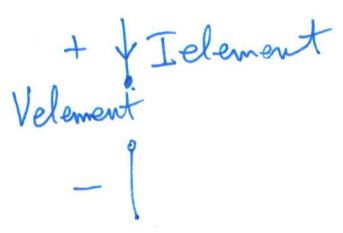

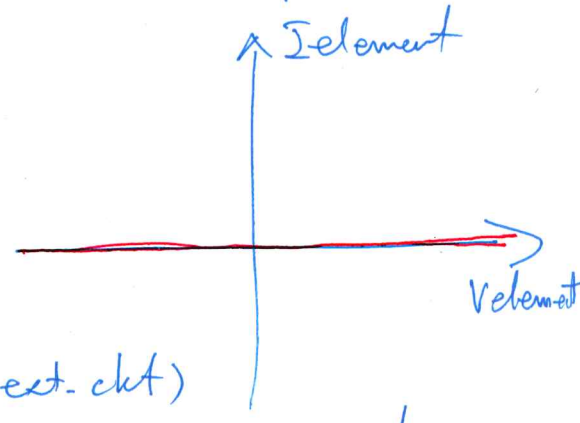
$I_{element} = 0$   
 $V_{element} = ?$   
 (set by ext. ckt)




④ Voltage source

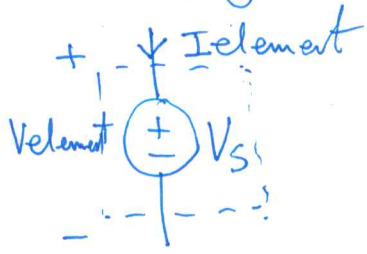

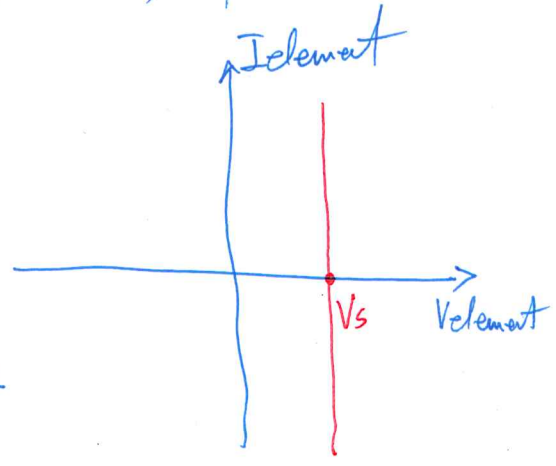
$V_{element} = V_s$   
 $I_{element} = ?$   
 (set by ext. ckt)



Q3 5 Current source

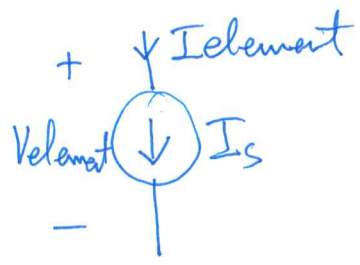

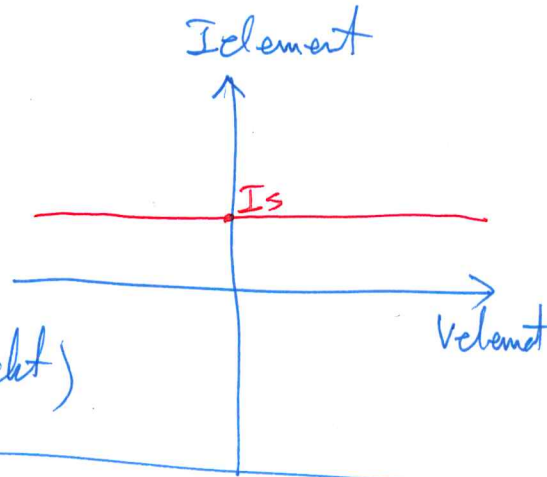$I_{element} = I_s$   
 $V_{element} = ?$   
 (set by ext. ckt)




$V_{element}$  and  $I_{element}$  can be positive or negative.

Rules for circuit analysis:

① KVL : sum of voltages across the elements in a loop = 0

example:

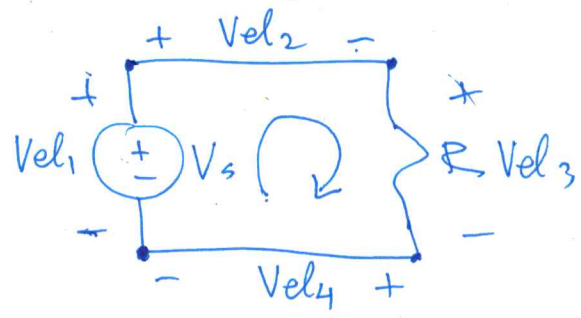

$$V_1 - V_2 - V_3 - V_4 = 0$$

$$+ V_1$$

$$- V_2$$



$$+ V_3$$

$$- V_4$$

② KCL : The current flowing into any junction must equal the current flowing out

example:

$$I_{el1} + I_{el2} = 0$$

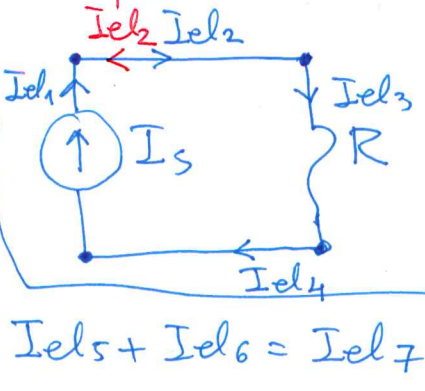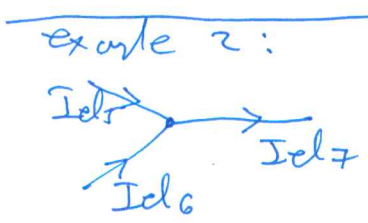


$$I_{el5} + I_{el6} = I_{el7}$$

$$I_{el1} = I_{el2} \quad I_{el2} - I_{el1} = 0$$


$$I_{el2} = I_{el3}$$

$$I_{el3} = I_{el4}$$
~~$$I_{el4} = I_{el1}$$~~

(24) KCL within the element

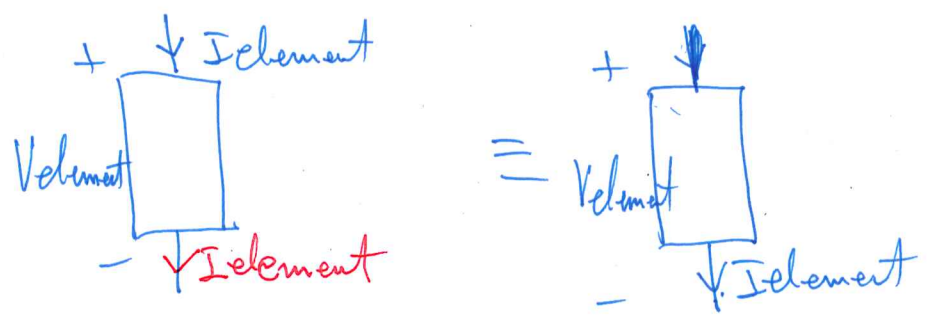


Passive sign convention

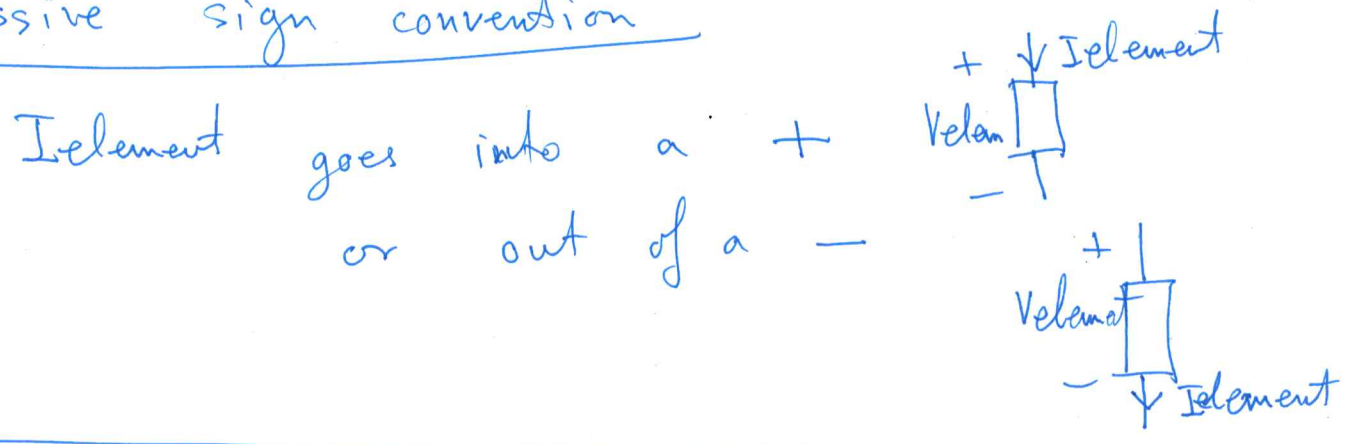


Circuit analysis algorithm:

voltage = difference of two potentials

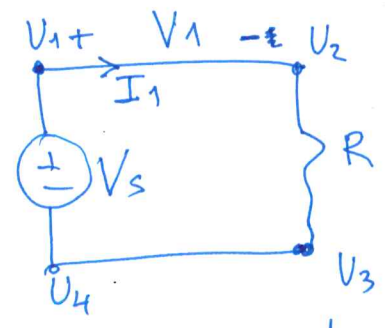Find : currents through elements and potentials of inputs / outputs of each element (junctions)



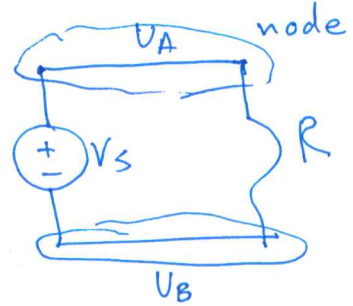$U_1, U_2$  potentials  
 $\rightarrow V_1 = U_1 - U_2$  (voltage)  
 $I_1$  (current)




$V_1 = 0$  |  $= U_1 - U_2 \Rightarrow U_1 = U_2$   
 wire element def.  
 collapse junctions with same potential into a node.




25

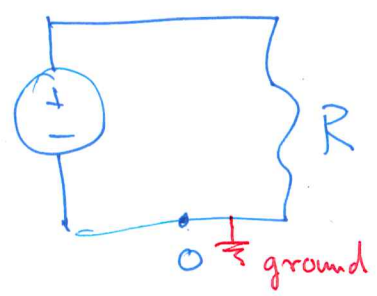Step 1: Pick a "reference" node and label it as a "0" potential. All voltages measured relative to this node.




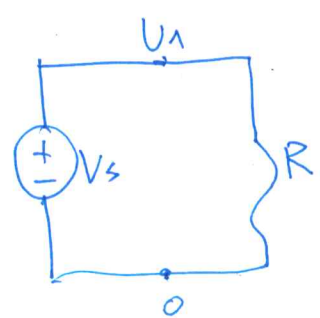Step 2: Label all remaining nodes as potentials  $V_i$  [ $V_1 \dots V_{n-1}$ ]




$V_1 - 0 = V_1$  (voltage between node 1 and node "0")

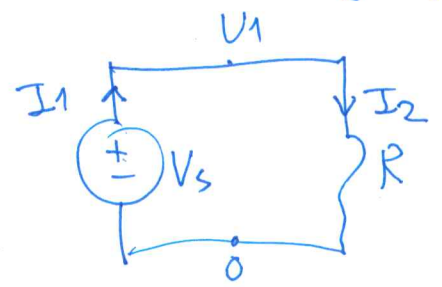Step 3: Label all branch currents with  $I_m$ . Arbitrarily pick directions of  $I_m$ . [ $I_1 \dots I_k$ ]



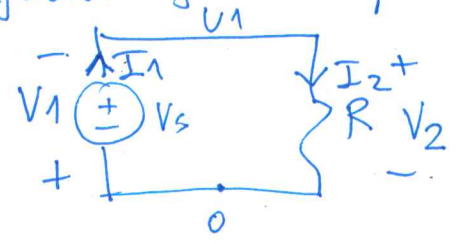Step 4: Add  $\pm$  element voltages to each element following the passive sign convention (independent of what is in the element)




46

step 5:  $A\vec{x} = \vec{b}$

$$\vec{x} = \begin{bmatrix} I_1 \\ \vdots \\ I_k \\ U_1 \\ \vdots \\ U_{N-1} \end{bmatrix}$$

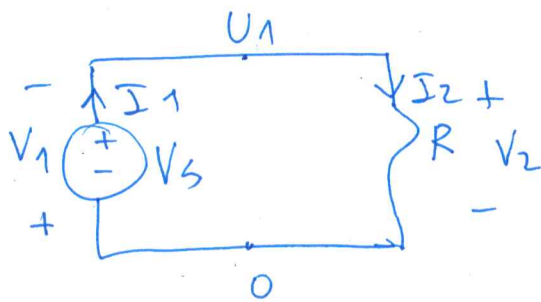
step 6: Use KCL to fill as many rows of  $A$  as possible (lin. indep) #Nodes - 1 =  $N - 1$



$$I_1 = I_2 \Rightarrow I_1 - I_2 = 0$$

$$\begin{bmatrix} 1 & -1 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ U_1 \end{bmatrix} = \begin{bmatrix} 0 \end{bmatrix}$$

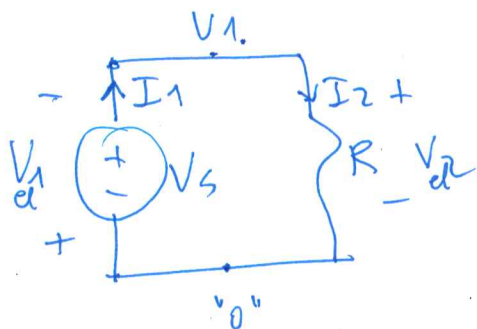step 7: Use current-voltage relationships for each element to fill the rest of the  $A$  matrix



Voltage source:  $V_{d1} = -V_s$

$$V_{d1} = 0 - U_1 = -U_1$$

$$\underline{U_1 = V_s} \quad \checkmark$$

Resistor:  $V_{d2} = I_2 \cdot R$

$$V_{d2} = U_1 - 0 = U_1$$

$$\Rightarrow U_1 = I_2 R \Rightarrow I_2 R - U_1 = 0$$

$$\begin{bmatrix} 1 & -1 & 0 \\ 0 & 0 & 1 \\ 0 & R & -1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ U_1 \end{bmatrix} = \begin{bmatrix} 0 \\ V_s \\ 0 \end{bmatrix} \Rightarrow \begin{bmatrix} U_1 = V_s \\ I_1 = \frac{V_s}{R} \\ I_2 = \frac{V_s}{R} \end{bmatrix}$$