
EE16A: Touch Screen Technology


Note Packet 2

Vivek Subramanian, Elad Alon, Babak Ayazifar,
Gireeja Ranade, Claire Tomlin


1

How does this relate to touch screens?

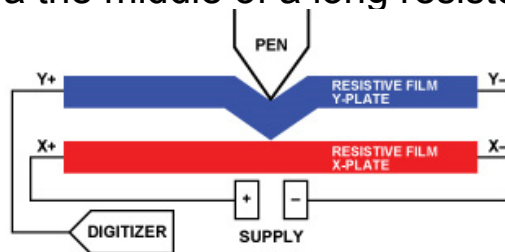- When we press at some point on the screen, we “tap” into a the middle of a long resistor



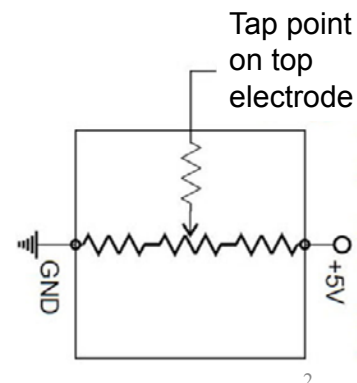- We can model this as a tap on a series connection of lots of resistors.
- We need to determine the voltage on the tap point and use this for position determination




2


1st design tool: Kirchhoff's Current Law (KCL)

Sum of currents entering a node is zero
Also holds for closed boundary
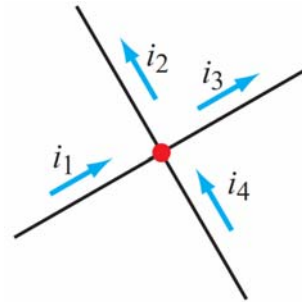
$$\sum_{n=1}^N i_n = 0 \quad (\text{KCL}),$$


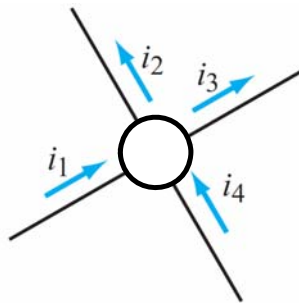
$$i_1 - i_2 - i_3 + i_4 = 0$$
$$i_1 + i_4 = i_2 + i_3$$



3


2nd Design tool: Kirchhoff's Voltage Law (KVL)

Sum of voltages around a closed path is zero
Sum of voltage drops = sum of voltage rises

$$\sum_{n=1}^N v_n = 0 \quad (\text{KVL}),$$

Sign Convention

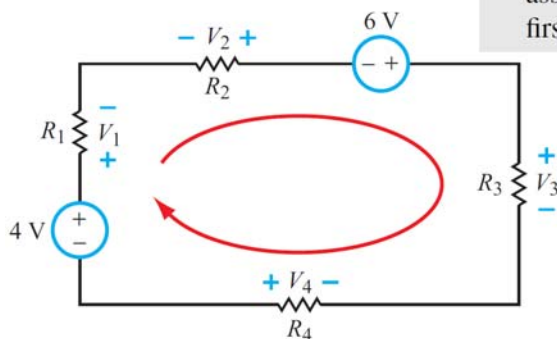- Add up the voltages in a systematic clockwise movement around the loop.
- Assign a positive sign to the voltage across an element if the (+) side of that voltage is encountered first, and assign a negative sign if the (−) side is encountered first.



$$-4 + V_1 - V_2 - 6 + V_3 - V_4 = 0$$


4

Combining Resistors – Series


For equivalence, currents and voltages must be the same

- Do a KVL:

Top Circuit

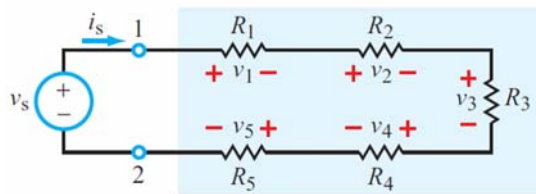

Bottom Circuit

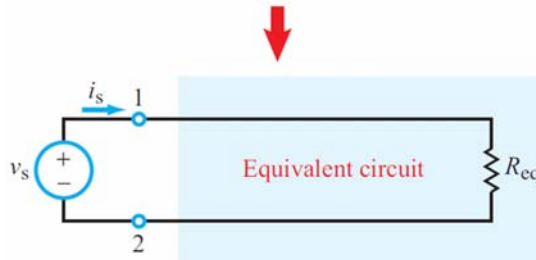


Equating:


5

Combining Resistors - Parallel

- Do a KCL

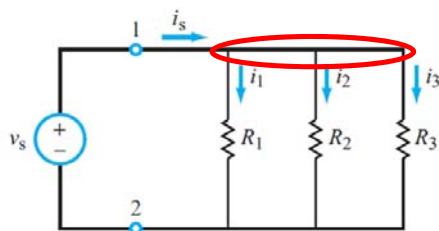

- In other words:

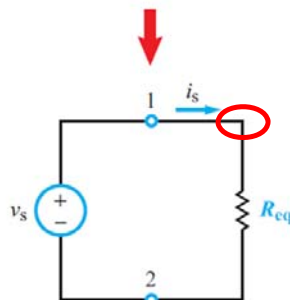

- More generally:



6

Useful Videos

- KVL and KCL: <http://youtu.be/MIwYUBe16C0>

7


Going back to that touch screen...

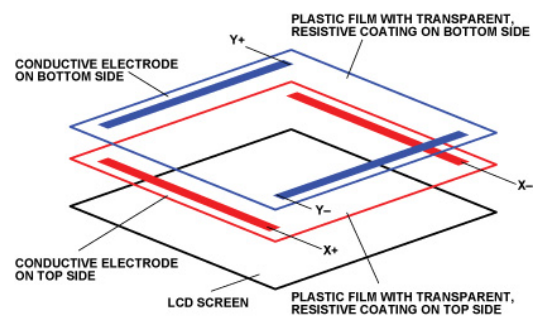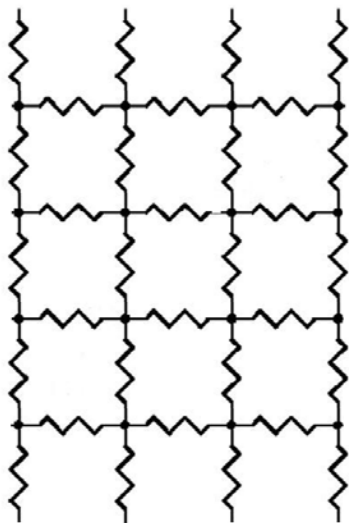

If the stripes are very conductive,
does the voltage vary laterally?


8

Exercise: Find I

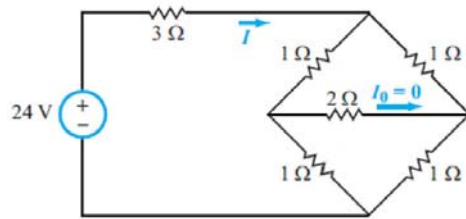

9


Exercise: Find I_0

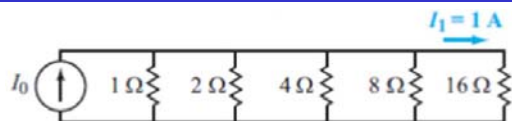


10

Going back to that touch screen...

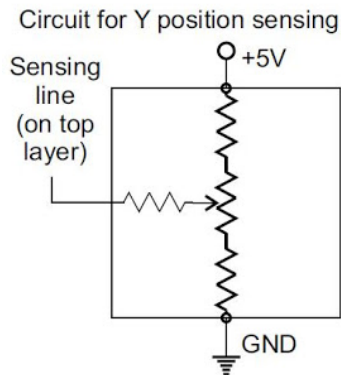- The “tapped” electrode line is called a voltage divider



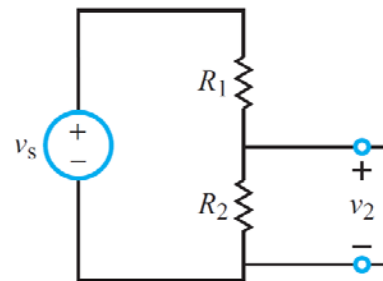For now, let's ignore the resistor on the tap and simplify / generalize to:




- Let's try a KVL:

So we've found the voltage.
Now to relate this to position....


11

What about that assumption?

- We just assumed

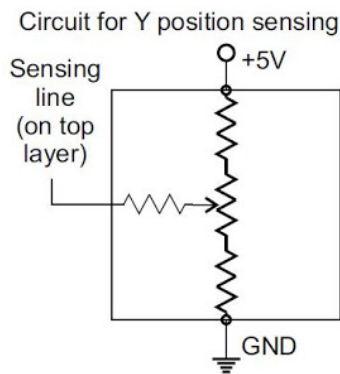

=

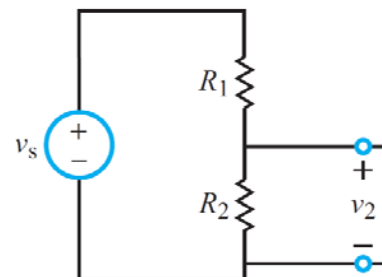


- What does this say about the voltage sensing circuitry?

12

Position determination

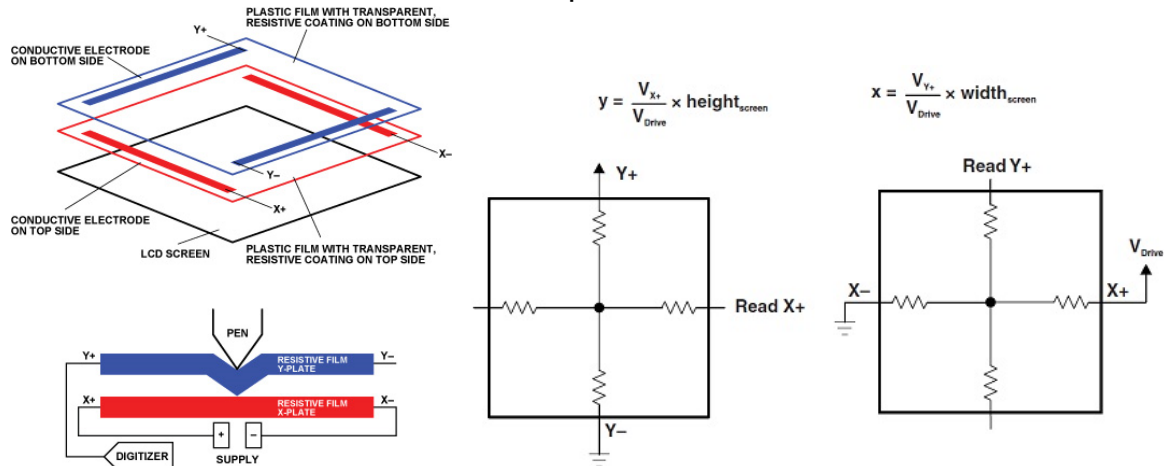
- A touch screen system drives the top and detects on the bottom, and vice versa to find X and Y positions



- Problems:
 - Requires “hard” contact
 - Cannot do multi-touch, since only one voltage is measured on the sensing plate

13

Exercise: Calculate voltages sensed


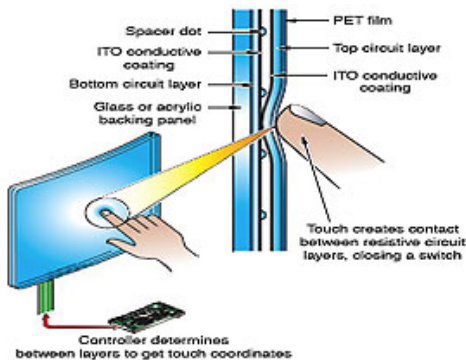


- Assume
 - Resistance is 1kΩ/cm of electrode line
 - Screen is 40cm × 30cm
 - $V_{applied} = 5V$
- What is V_x, V_y for touch at:
 - Center of screen
 - Center of top-left quadrant

14

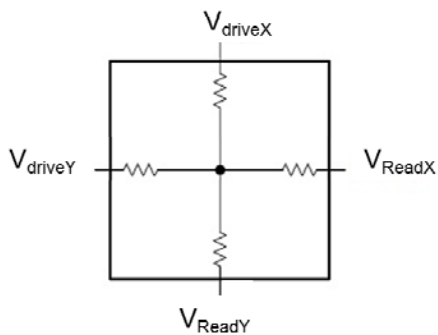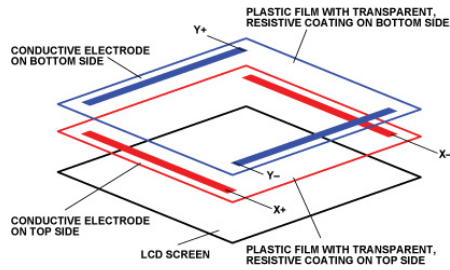
Exercise: Simultaneous X, Y determination

- Suppose I were to try to apply voltages on both layers to try to determine X and Y in one measurement, would this work?



15


Exercise: Find I_1 , I_2 , I_3 , I_4

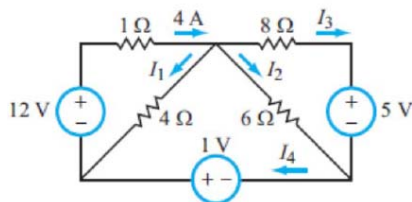

16

Independent Sources

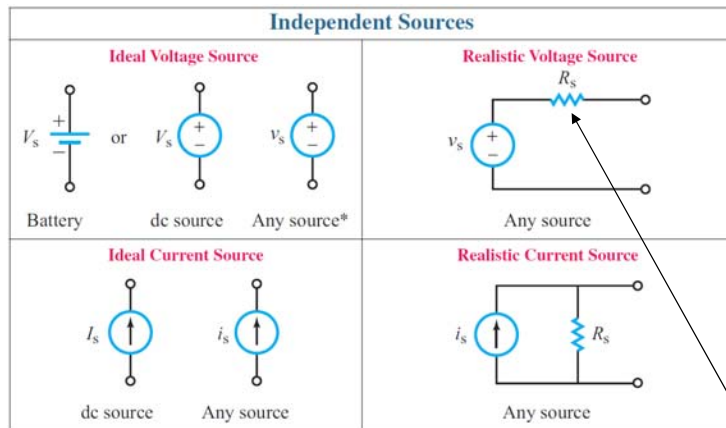- We can achieve multi-touch if we drive with a current rather than a voltage.
- In general, we can define independent sources as:




The resistance represents the fact that realistic sources “droop” when the load is increased (for example, car headlights often dim as you crank the engine to start)

17

Exercise: Realistic voltage source

- When I turn on my car headlights, my effective voltage of the 12V battery drops to 11.5V. What is the internal resistance of the battery?
 - Assume the bulb wattage is 50W per bulb

Exercise: Convert from V_s to I_s

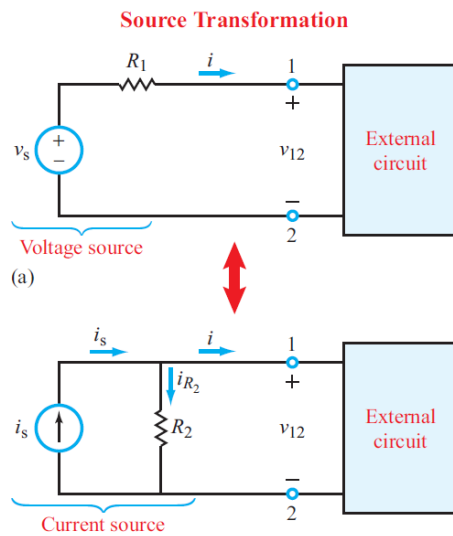

19

Useful Videos

- Transformations: <http://youtu.be/6Ujq1SeLhU8>
- Nodal: <http://youtu.be/RgR232M16bE>
- Mesh: <http://youtu.be/yzJI-KufYNq>
- Inspection: <http://youtu.be/Dfrn7Al-AuY>
- Linearity and Superposition: <http://youtu.be/ky0cfK-HQEA>
- Equivalence: <http://youtu.be/hNsZJKowd34>
- Equivalence Examples: <http://youtu.be/Ne-KPt4IFp4>

20