

(2)



EE16A - Module 2 - Lecture # 6

* Cap. Equivalence example

* Capacitor physics

* 2D-touch







* Cap measurements (sensor)

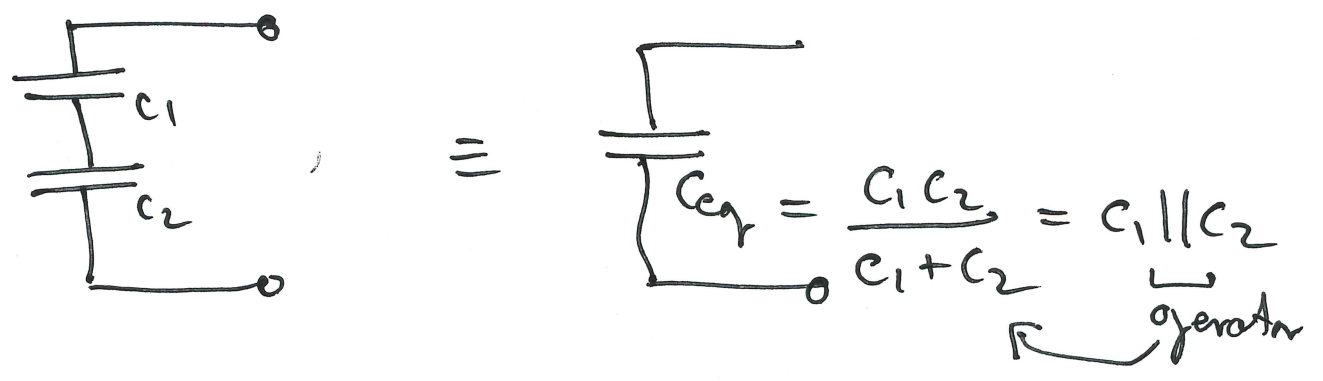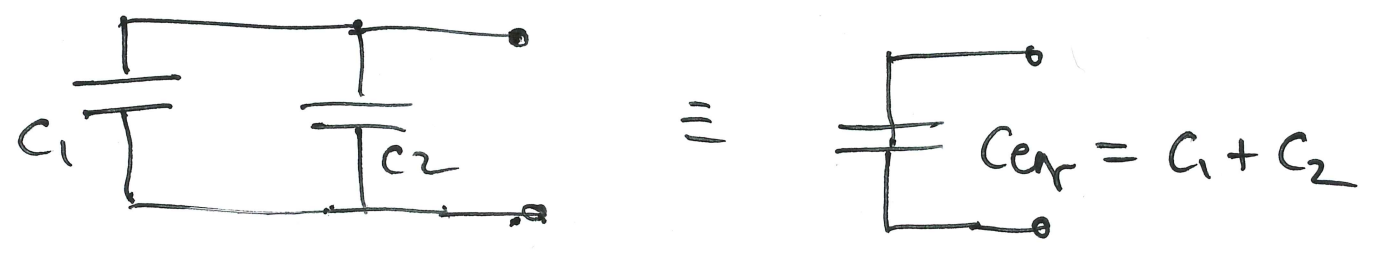


$$C_{eq} = \frac{I_{test}}{\frac{dV_{test}}{dt}}$$

(12)

example #3 :

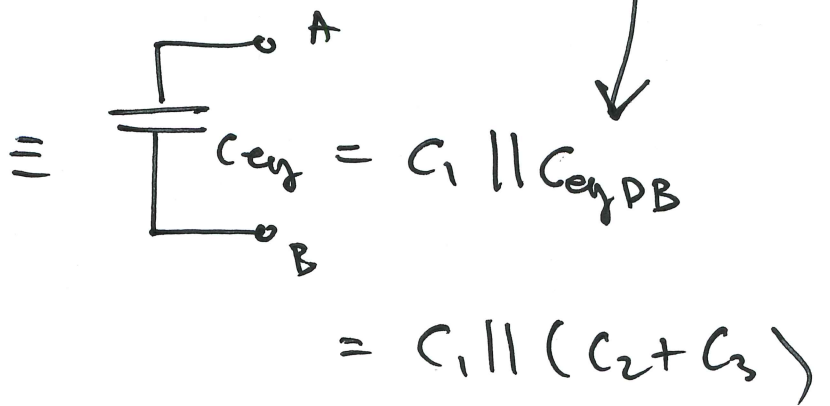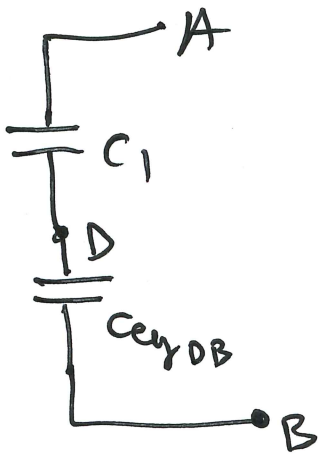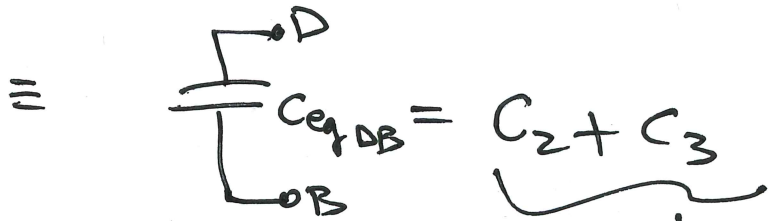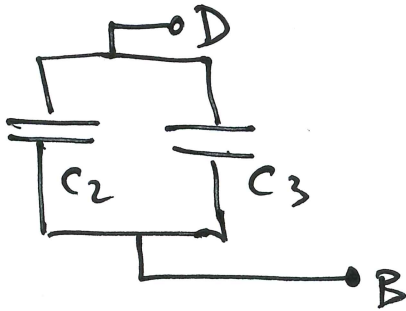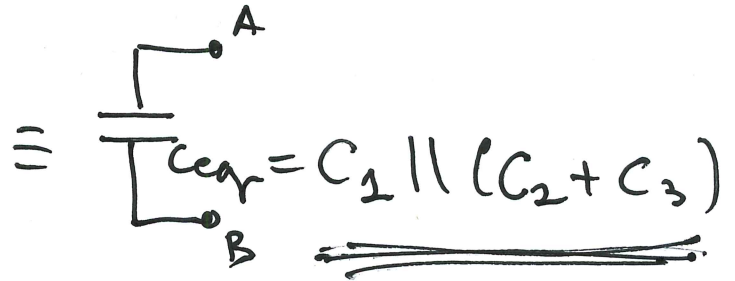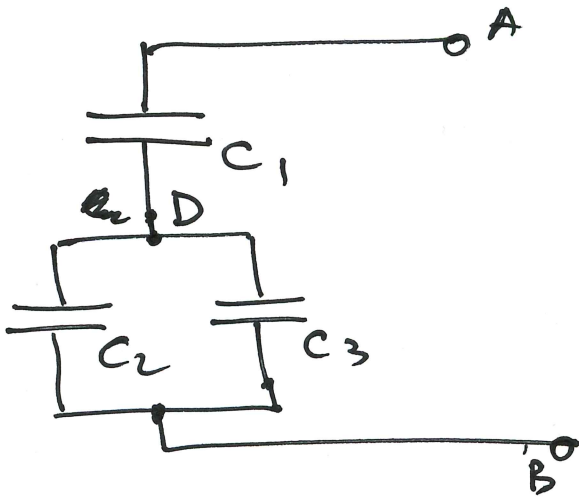

Q3

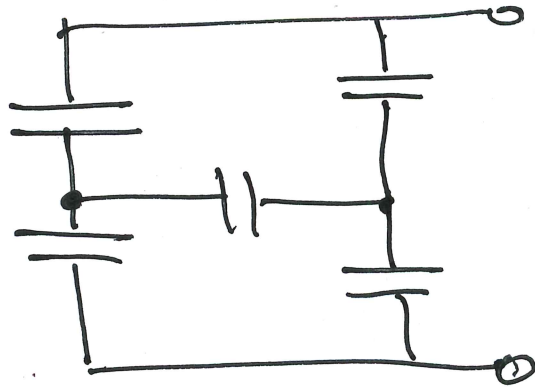


do for practice.

(14)

16A Capacitor physics

* Any two conductors separated by an insulator \Rightarrow capacitor
cannot carry current


$$Q = C \cdot V$$

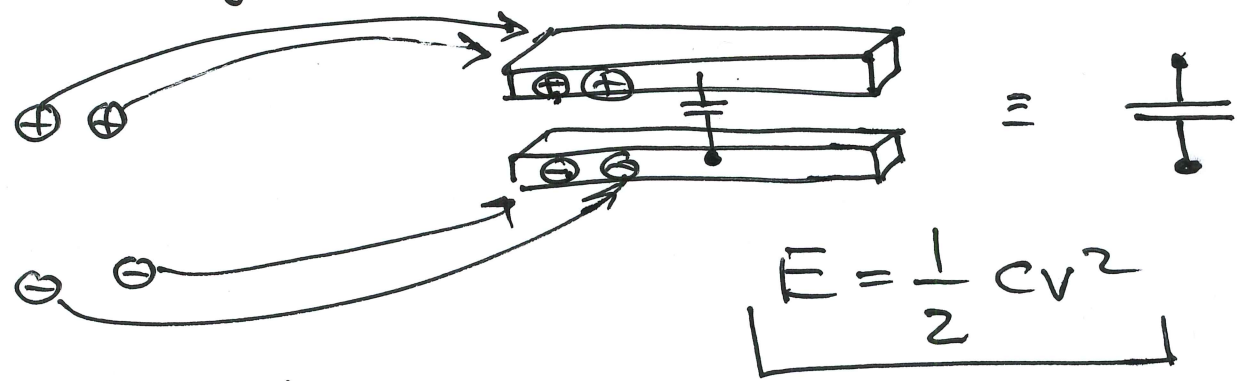


* capacitor is a "bucket" for charge

Capacitance depends on: 1) geometry of the conductors

side view:

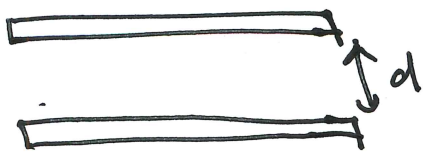

top view:

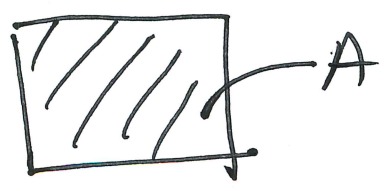

2) material properties of the insulator

- ϵ - permittivity [$\frac{F}{m}$]

$$\epsilon_0 = 8.85 \frac{\mu F}{m}$$


$$C = \epsilon \frac{A}{d} =$$

\uparrow \uparrow
 [F] [$\frac{F}{m}$] [$\frac{m^2}{m}$]


(15)

Touchscreen:

Side view:

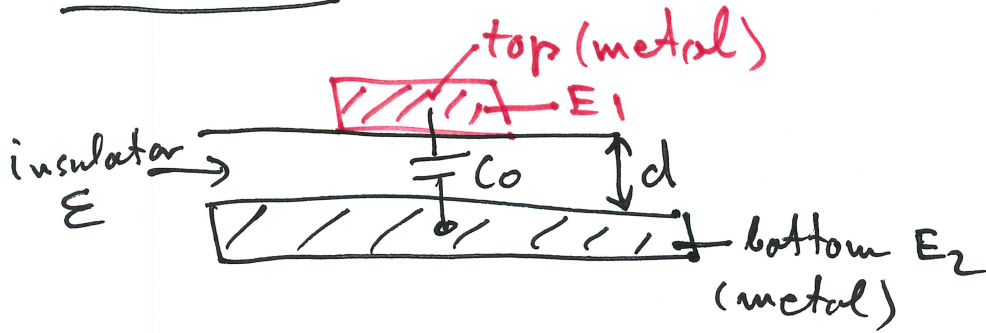


Top view:

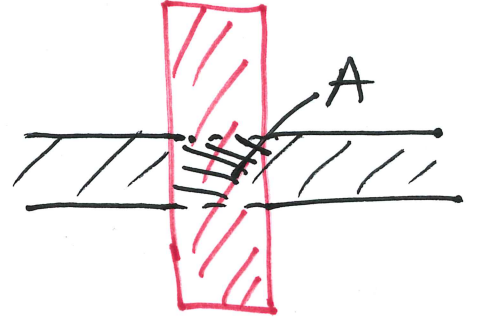


Model:

w/o touch

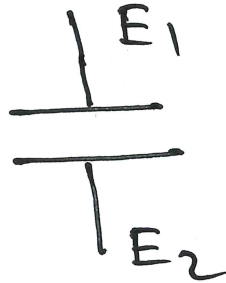


$$C_0 = \epsilon \cdot \frac{A}{d}$$

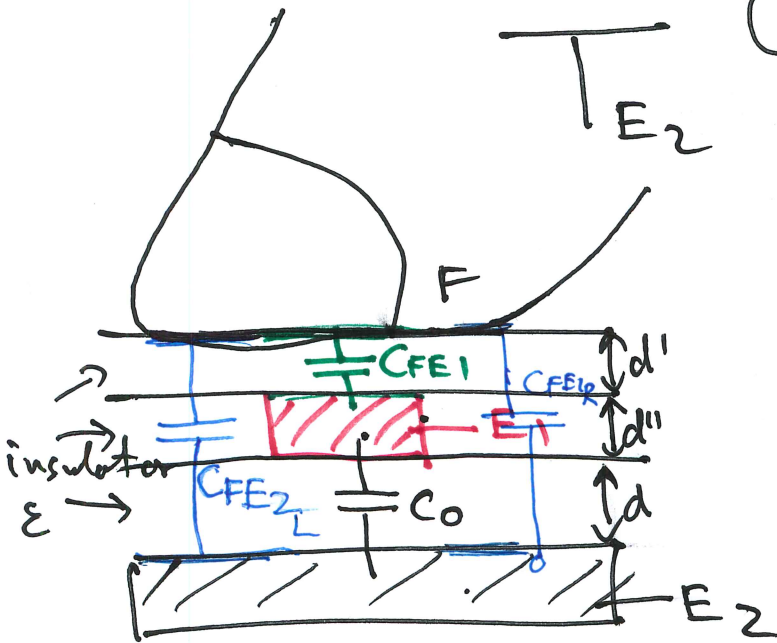




Model:
with touch

$$C_{FE2L} + C_{FE2R} = C_{FE2}$$

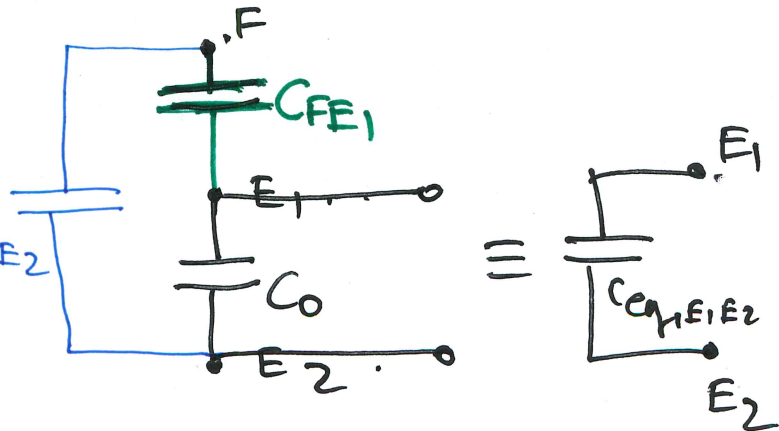


$$C_{eq, E1E2} = C_0 + \underbrace{C_{FE1} \parallel C_{FE2}}_{\Delta C > 0}$$

16

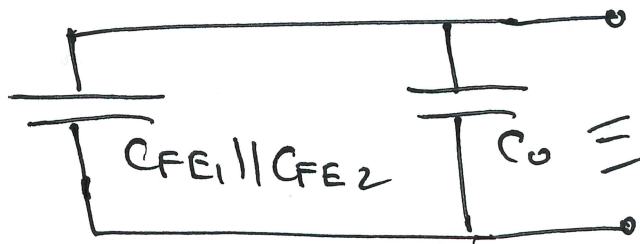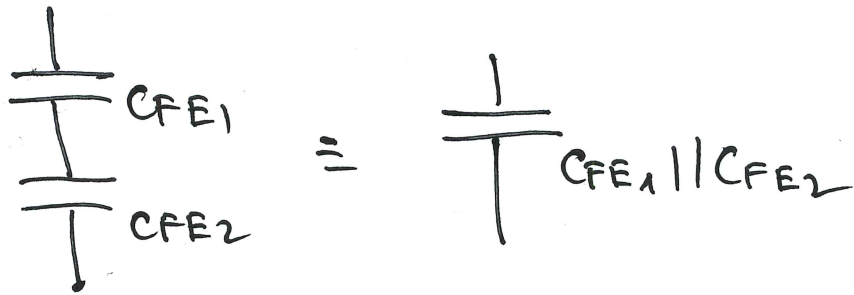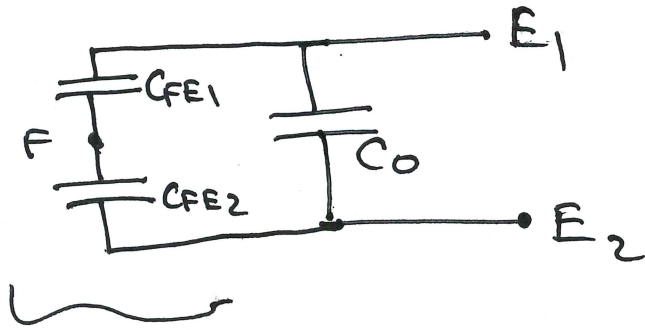

(27)

Expanding to 2D:

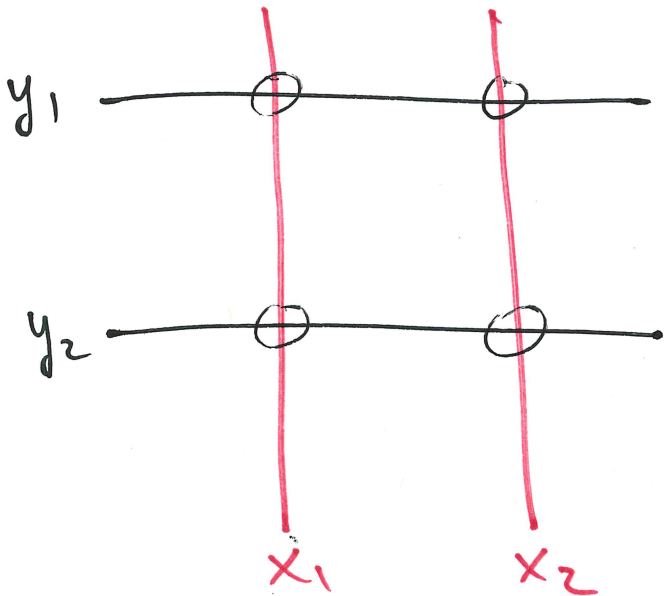


upper left = x_1, y_1

⋮


How do we measure capacitance?

$$Q = C \cdot V \Rightarrow V = \frac{Q}{C}$$

Attempt #1:

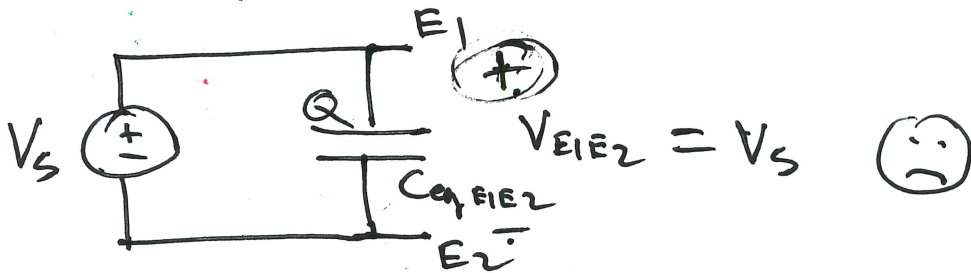

Attempt #2:

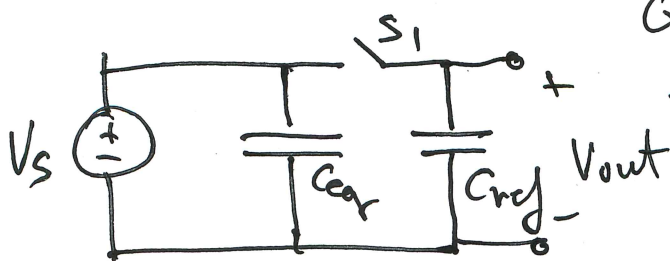

$$Q_{E1E2} = C_{eq, E1E2} \cdot V_s$$

\swarrow Q_0 \downarrow $Q_{ots} Q$ \swarrow C_0 \searrow $C_0 + \Delta C$


define a switch:

S_1 : on: wire


off: open circuit

Attempt #2 cont:


S_1 off:

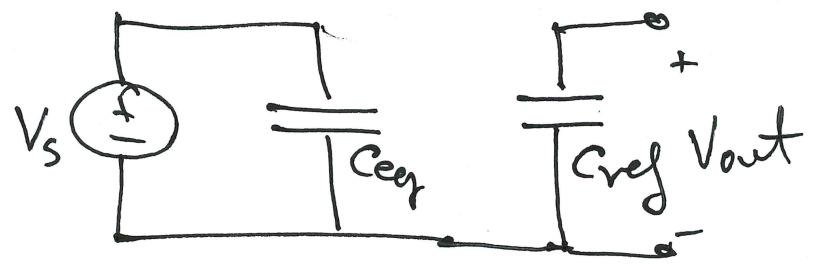


S_1 on:

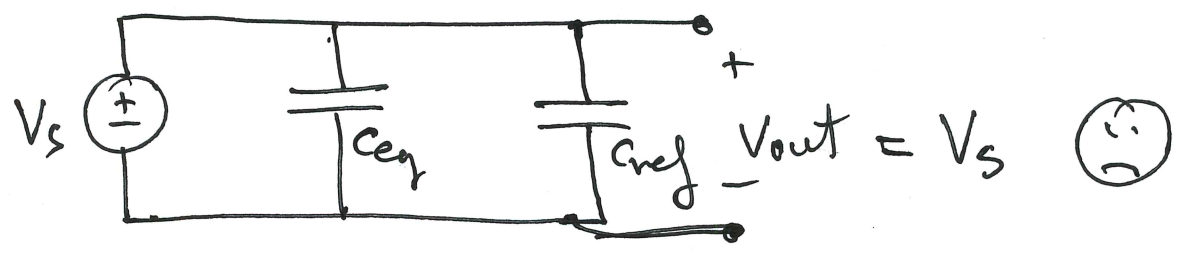


Attempt #3:

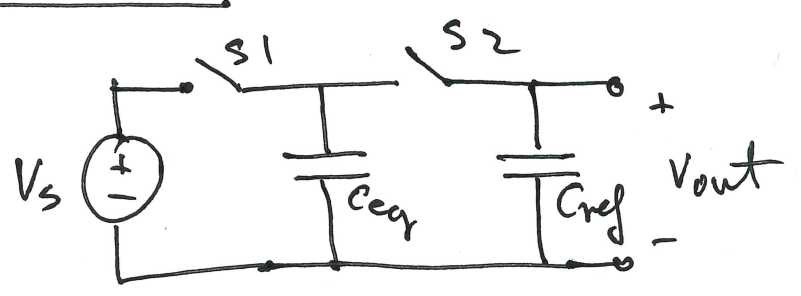

S_1 on, S_2 off:

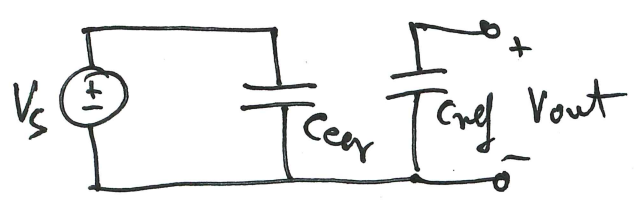


S_1 off, S_2 on:

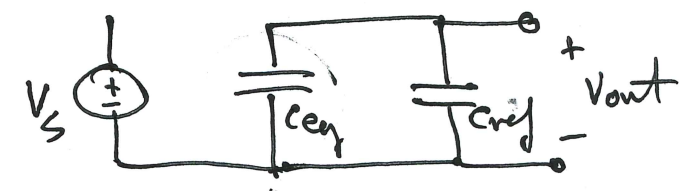



almost here. 😞

Q9 Attempt #4:

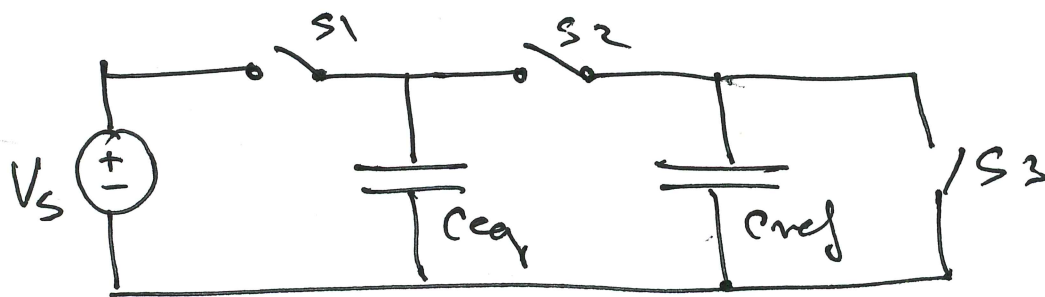

phase 1
S1 on, S2 off, S3 on

phase 2:
S1 off, S2 on, S3 off

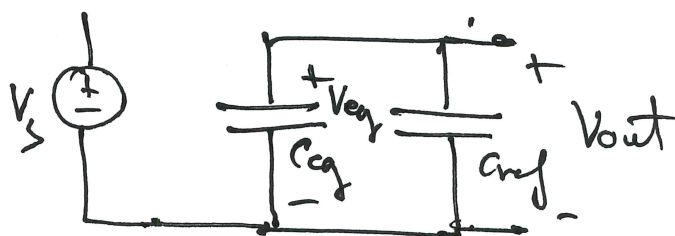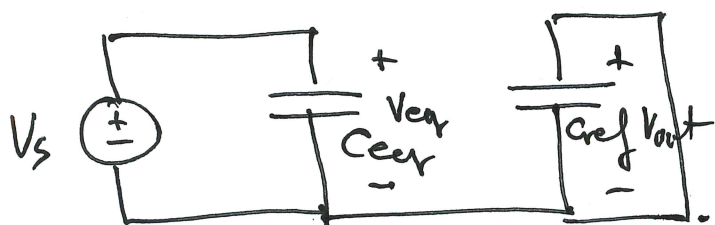

Charge needs to be conserved:

$$Q_{total, phase 1} = Q_{total, phase 2}$$

$$Q_{Ceq,1} + Q_{Cref,1} = Q_{Ceq,2} + Q_{Cref,2}$$

$$C_{eq} \cdot \frac{V_{eq,1}}{V_s} + C_{ref} \cdot \frac{V_{out,1}}{0} = C_{eq} \cdot \frac{V_{eq,2}}{V_{out,2}} + C_{ref} \cdot V_{out,2}$$

$$C_{eq} V_s = C_{eq} V_{out,2} + C_{ref} V_{out,2}$$

$$C_{eq} V_s = (C_{eq} + C_{ref}) V_{out,2}$$

$$V_{out,2} = \frac{C_{eq} V_s}{C_{eq} + C_{ref}}$$

