


(1)

EE16A - Module 2 - Lecture 8



- * Audio system (DAC example)
- * Intro to negative feedback
- * Golden rules
- * Op-amp NFB examples

"16A Boom box"

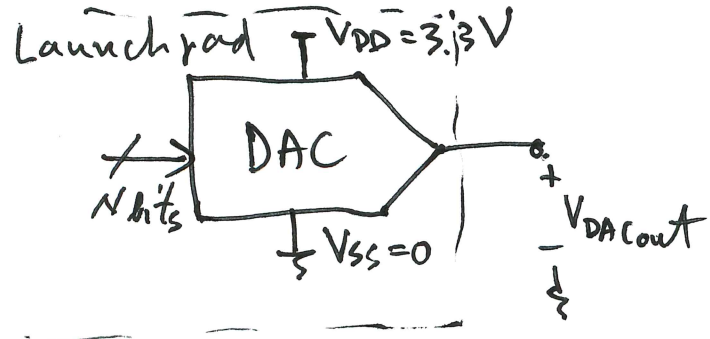
DAC: Digital-to-analog converter
(turns digital - binary values into analog voltage)



Model \equiv

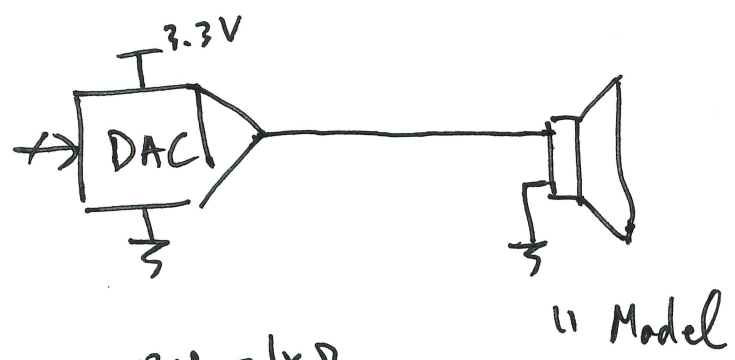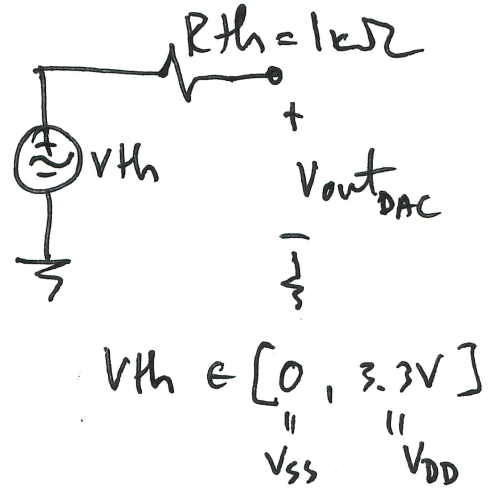

" Model


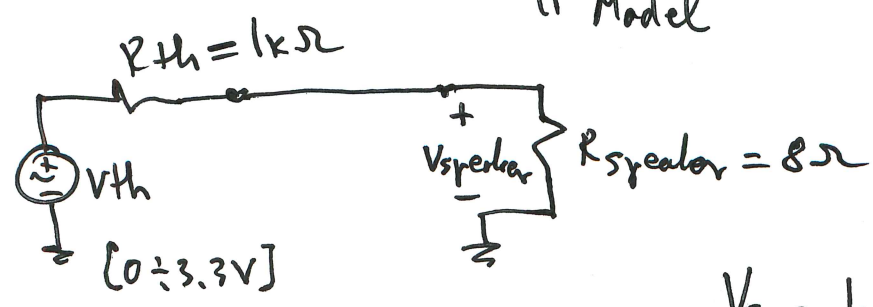


$$V_{\text{speaker}} = \frac{R_{\text{speaker}}}{R_{\text{speaker}} + R_{\text{Th}}} \cdot V_{\text{Th}}$$

12

$$V_{\text{speaker}} = \frac{1}{1 + \frac{R_{\text{th}}}{R_{\text{speaker}}}} \cdot V_{\text{th}} = \frac{1}{1 + \frac{1\text{k}\Omega}{8\Omega}} V_{\text{th}}$$

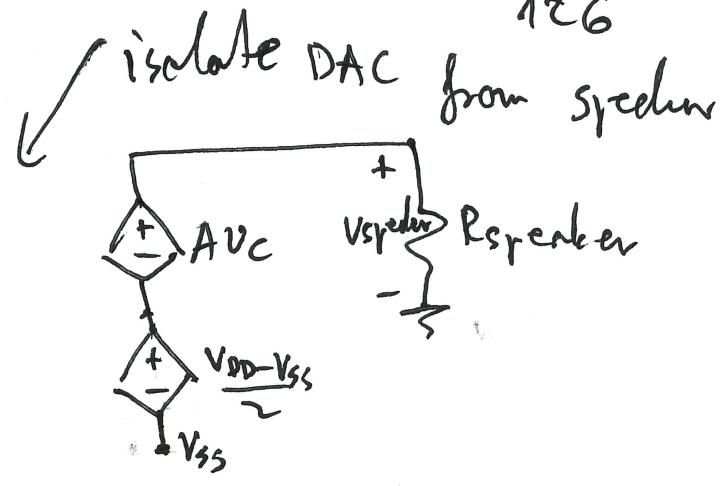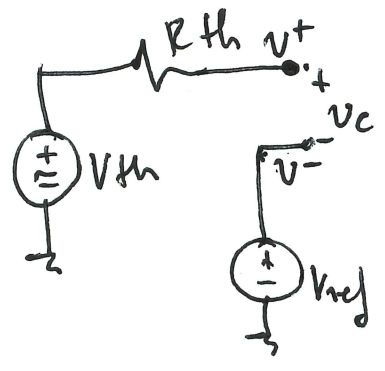
Loading effect $\approx 0 = \frac{V_{\text{th}}}{126}$




$$V_{\text{DD}} = V_{\text{+}} - V_{\text{SS}} = 5\text{V}$$

$$V_{\text{speaker}} = A \cdot v_{\text{c}}$$

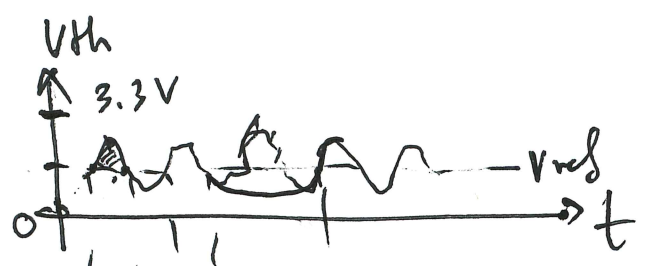
$$v_{\text{c}} = v^{+} - v^{-} = V_{\text{th}} - V_{\text{ref}}$$



(Mozart)

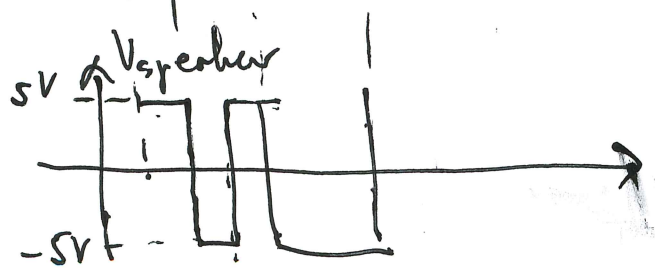

(Meadeth)

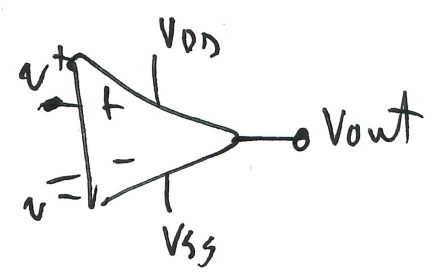


(23)

Want isolation with a controllable gain ξ (e.g. 3x).

Need a way to "tame" the op-amp.

Negative feedback

Concept:

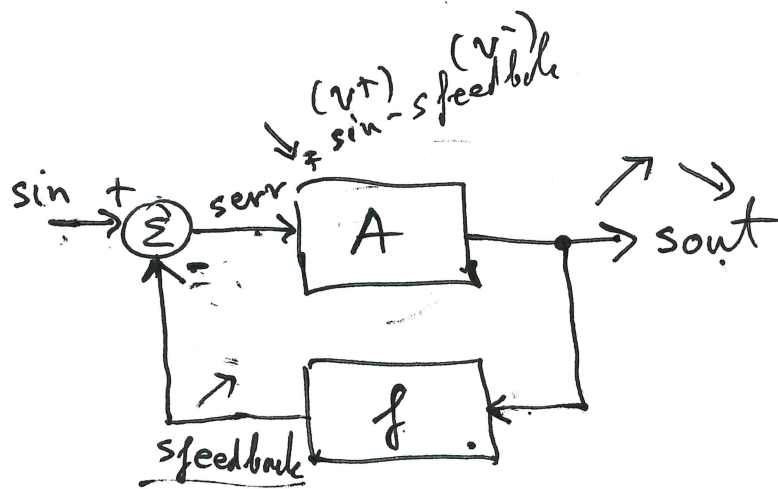



$$\left. \begin{aligned} serr &= sin - feedback \\ sout &= A \cdot serr \\ feedback &= f \cdot sout \end{aligned} \right\} \begin{aligned} \frac{sout}{A} &= sin - f \cdot sout \\ sout \left(\frac{1}{A} + f \right) &= sin \end{aligned}$$

$$\frac{sout}{sin} = \frac{1}{\frac{1}{A} + f} = \frac{A}{1 + Af}$$


$$\frac{sout}{sin} \approx \frac{1}{f} \quad \text{as } A \rightarrow \infty$$

24

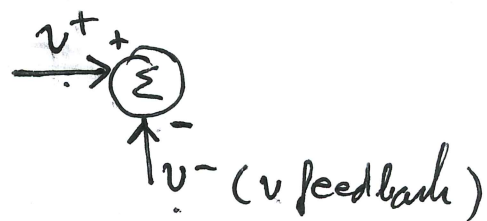
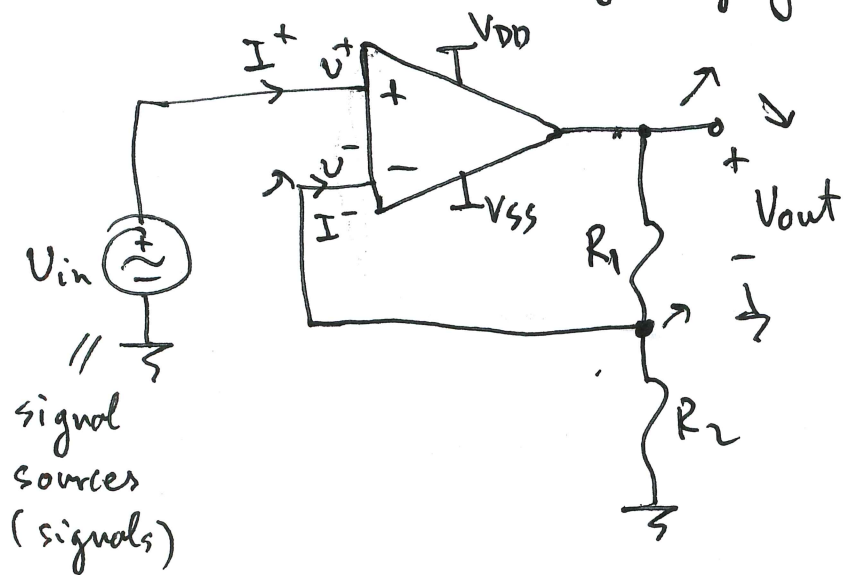
Op-amp NFB example:
(non-inverting amplifier)



In NFB:

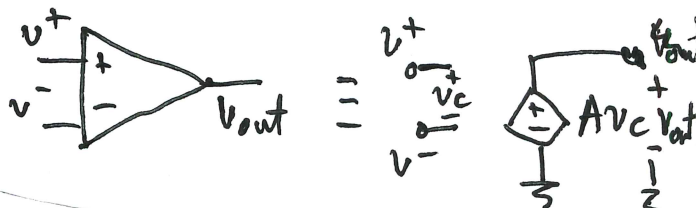

$v_c \equiv v_{in} - v_{out}$

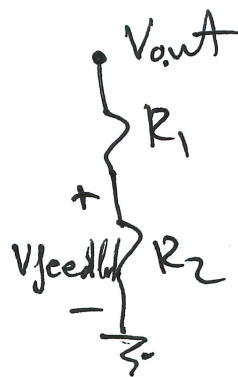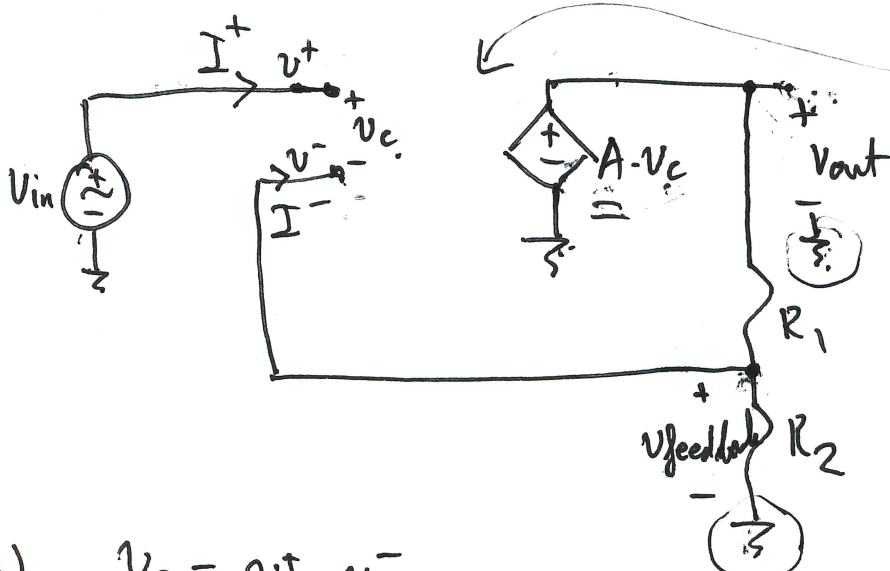

(1) $v_c = v^+ - v^- = v_{in} - v_{feedback}$

(2) $v_{out} = A \cdot v_c$

(3) feedback $v_{feedback} = \frac{R_2}{R_1 + R_2} \cdot v_{out}$

$v_{out} = A \cdot (v_{in} - \frac{R_2}{R_1 + R_2} \cdot v_{out})$

(25)

$$v_{out} = A \cdot (v_{in} - f \cdot v_{out})$$


$$v_{out} (1 + Af) = A \cdot v_{in}$$

$$\leftarrow v_{out} + Af v_{out} = A v_{in}$$

$$A_v = \frac{v_{out}}{v_{in}} = \frac{A}{1 + Af} = \frac{1}{\frac{1}{A} + f} = \left(1 + \frac{R_1}{R_2} \right)$$

$$v_c = \frac{v_{out}}{A} = \frac{1}{A} \cdot \frac{A}{1 + Af} \cdot v_{in} = \frac{v_{in}}{1 + Af} \xrightarrow{A \rightarrow \infty} 0$$

$$v_c = v^+ - v^- = 0 \Rightarrow$$

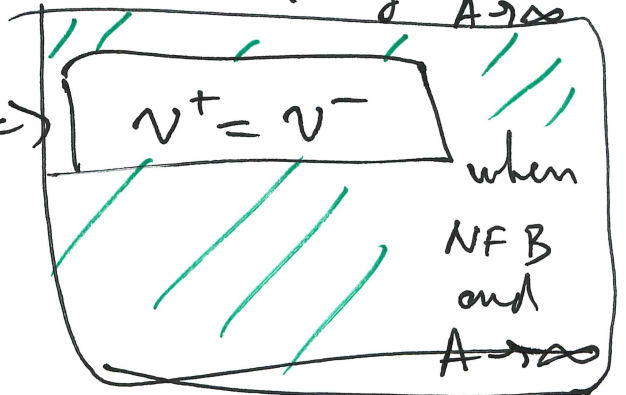

Golden rules



(1) $I^+ = I^- = 0$ (always true)

(2) $v^+ = v^-$ when NFB (and $A \rightarrow \infty$)

$$A_v = 3 = \frac{v_{out}}{v_{in}} \Rightarrow R_1 = 2 R_2$$


$$A_v = \left(1 + \frac{R_1}{R_2} \right) = 3$$

15

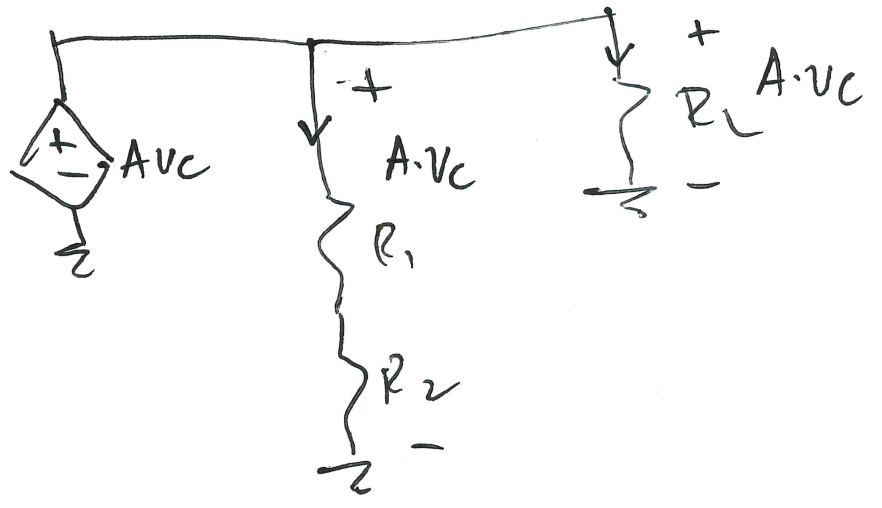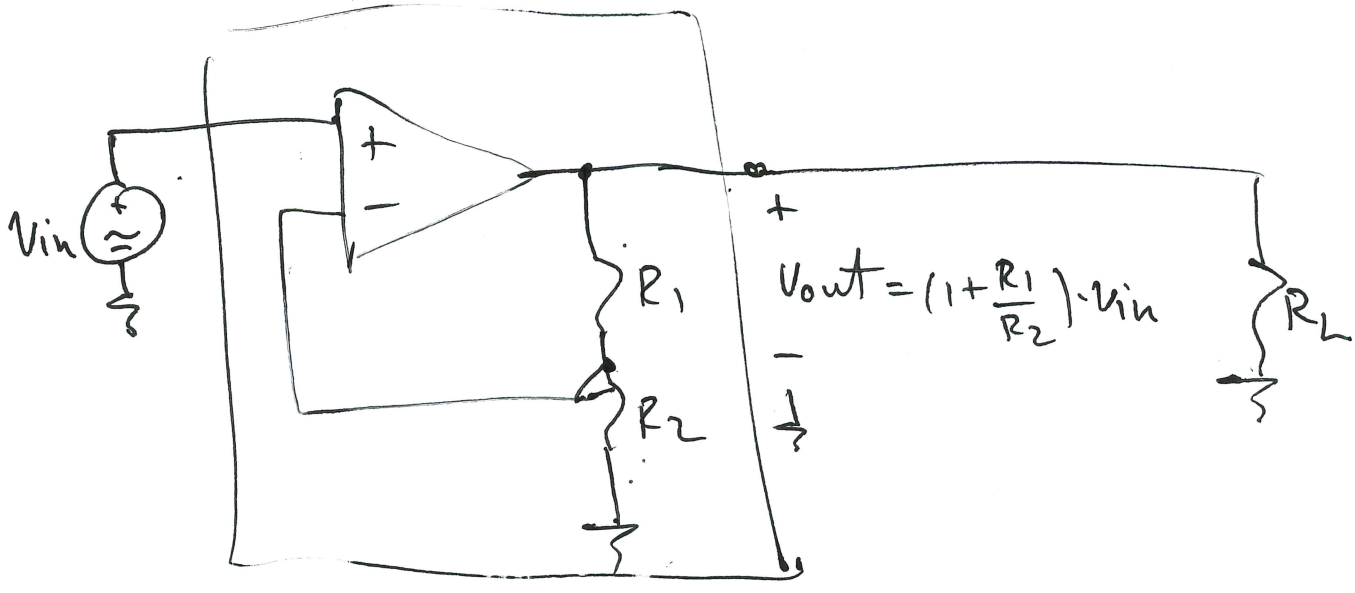


(17)

Another example :

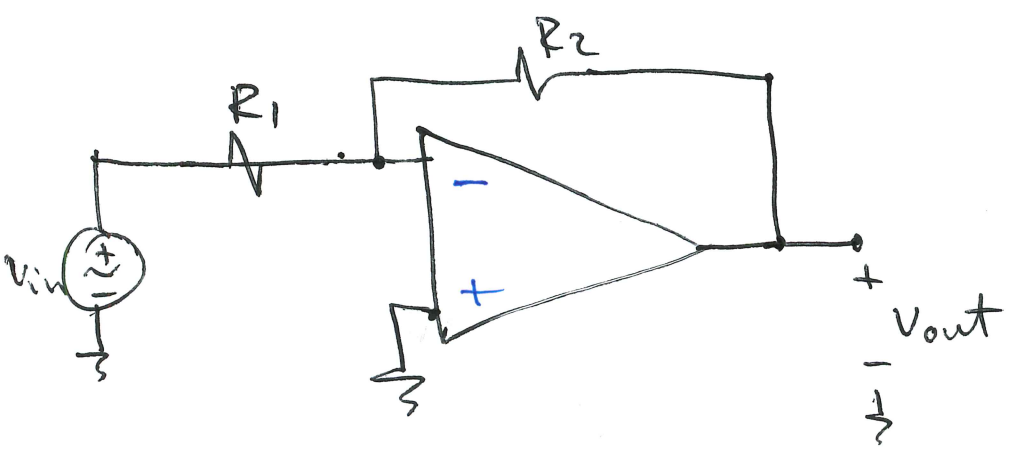

Determining the polarity for NFB :

① Turn-off indep. sources

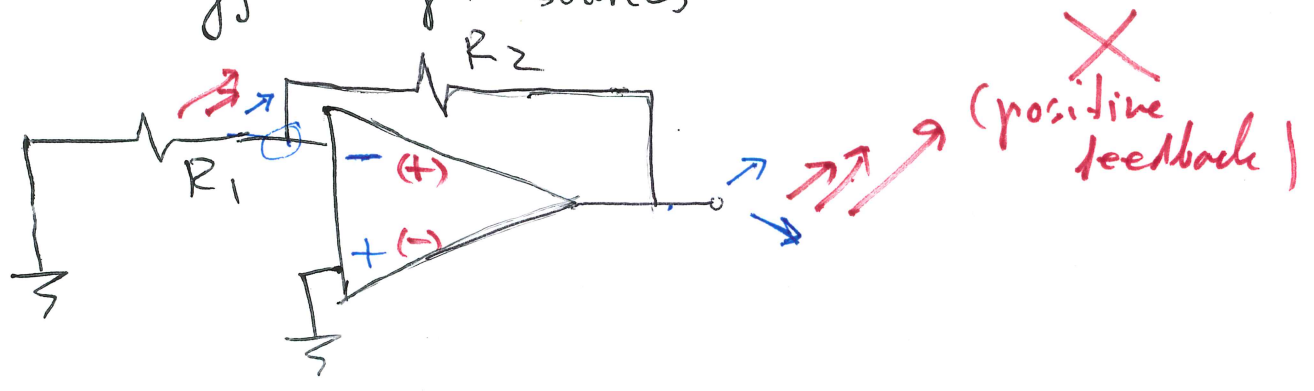

② Apply disturbance to the output (and follow the feedback)