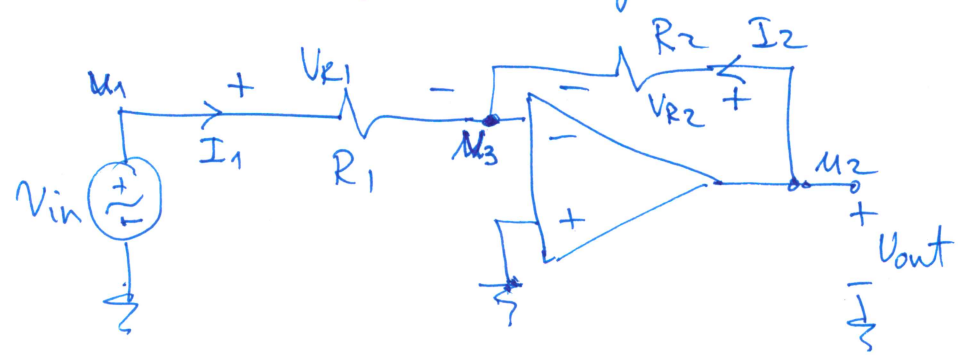


21

# EE16A - Module 2 - Lecture 9


- \* NFB inspection examples
- \* Summing amp / Neuron
- \* Cascading ckt blocks
- \* Design procedure

## Inverting amplifier example:



check for NFB!

step 1: Null indep sources

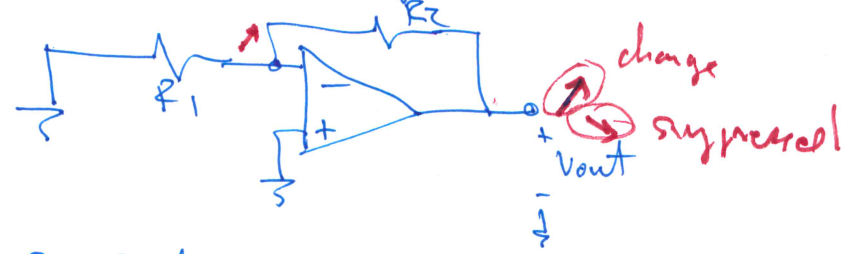

step 2: Dink the output & follow the change in feedback

$\Rightarrow$  NFB  $\Rightarrow$  GR#2 applies ( $v^+ = v^-$ )

$$\begin{aligned}
 u_1 &= v_{in} \\
 u_2 &= v_{out} \\
 u_3 &= 0 \text{ (b/c NFB } \Rightarrow \text{GR2)} \\
 0 &= v^+ = v^- = 0 \\
 \text{(KVL)} \quad v_{R1} &= u_1 - u_3 = v_{in} \\
 \text{(KVL)} \quad v_{R2} &= u_2 - u_3 = v_{out} \\
 v_{R1} &= I_1 R_1 \\
 v_{R2} &= I_2 R_2 \\
 \text{(KCL)} \quad I_1 + I_2 &= 0
 \end{aligned}$$

(2)

$$I_1 R_1 = V_{in} \Rightarrow I_1 = \frac{V_{in}}{R_1} = \frac{u_1 - u_3}{R_1}$$

$$I_2 R_2 = V_{out}$$

$$I_2 = \frac{V_{out}}{R_2} = \frac{u_2 - u_3}{R_2}$$


$$I_1 + I_2 = 0$$

$$\frac{V_{in}}{R_1} + \frac{V_{out}}{R_2} = 0 \Rightarrow \frac{V_{out}}{R_2} = -\frac{V_{in}}{R_1}$$


$$V_{out} = -\frac{R_2}{R_1} \cdot V_{in}$$

$$A_v = \frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1}$$


NFB example #3:

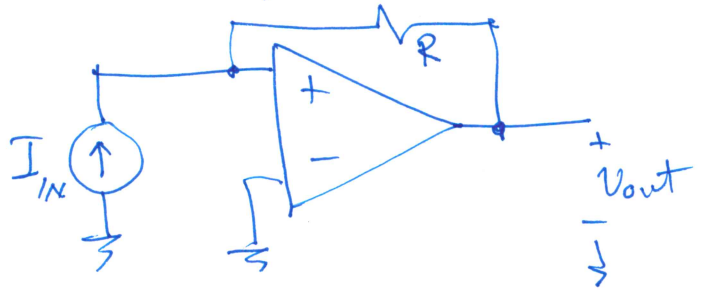


step 1:

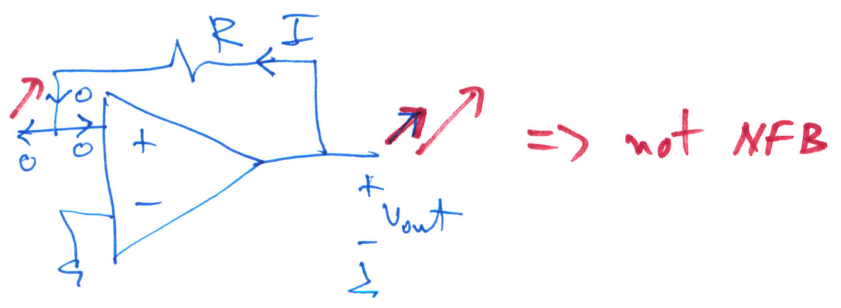

l3

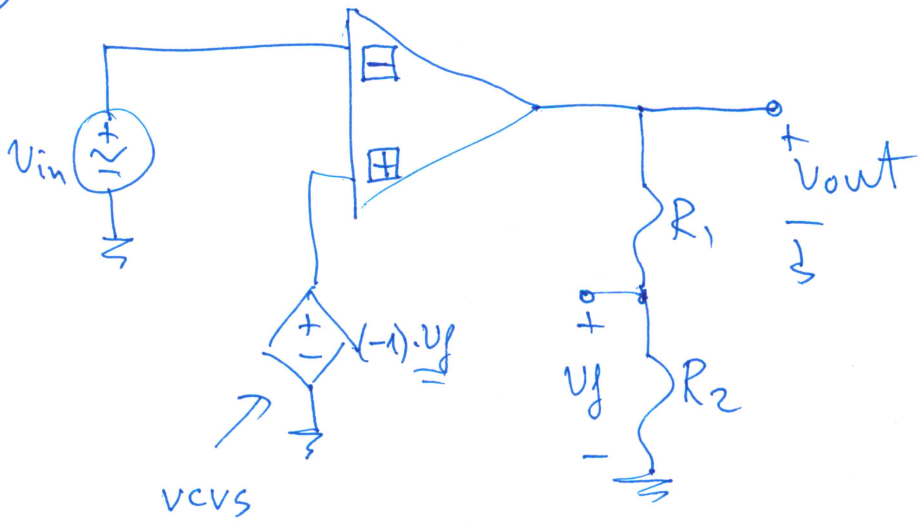

step 1:

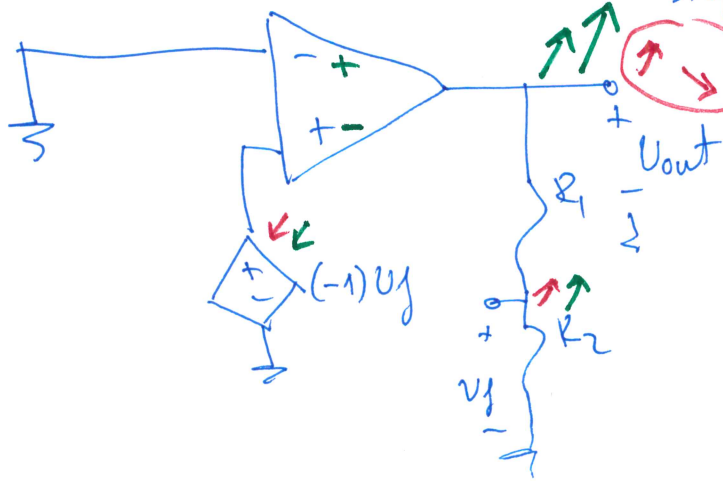


step 2:





$\Rightarrow$  NFB change is suppressed

(24)


# FC layer on a DNN

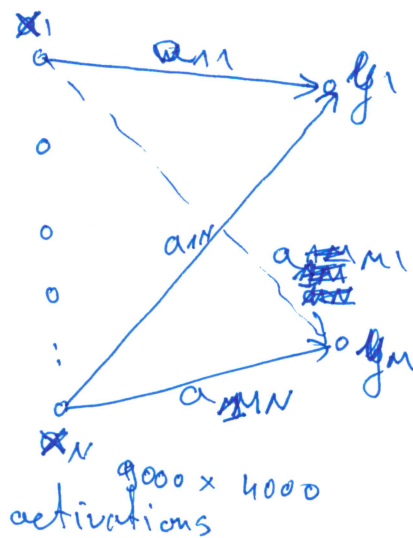
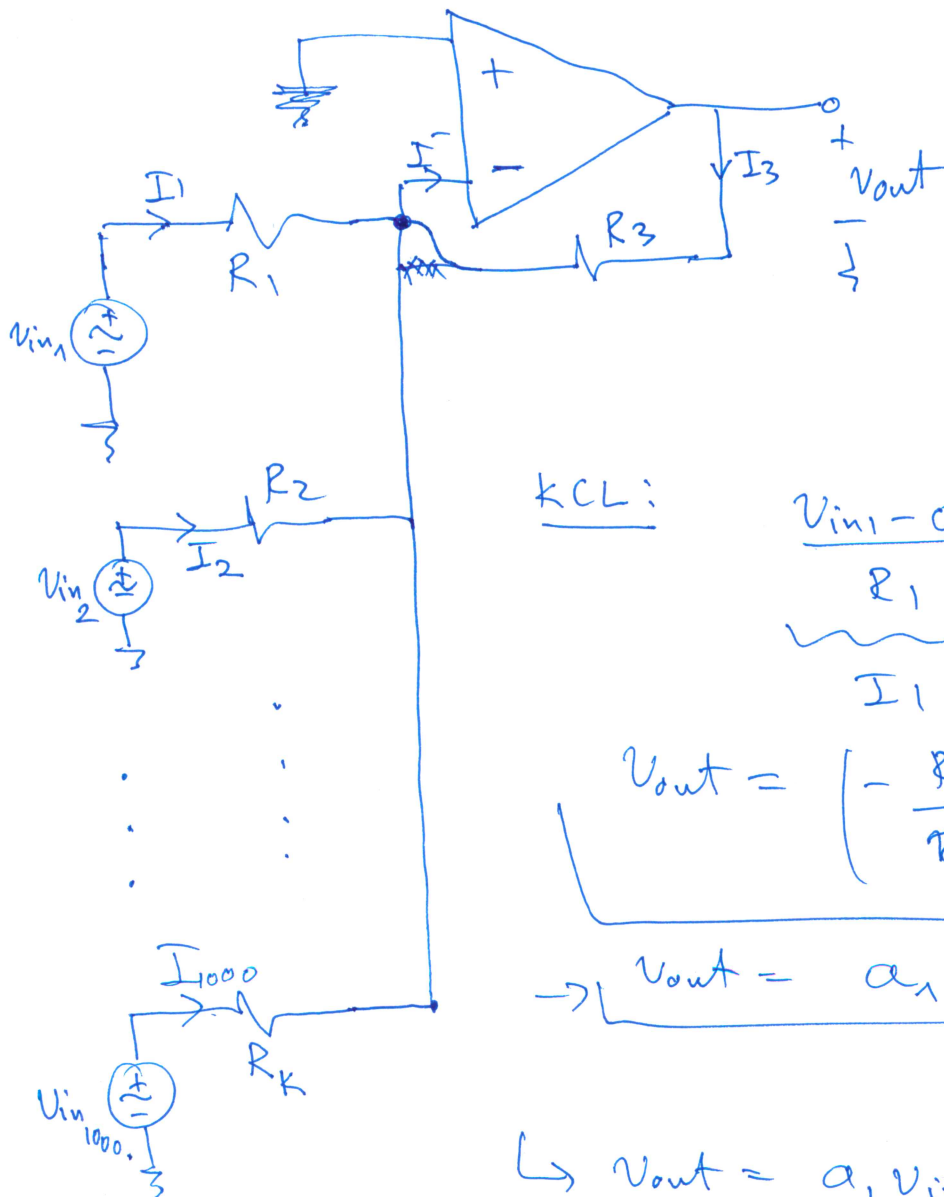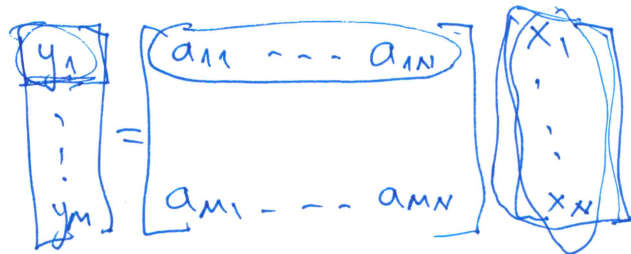
$$\underline{y} = A \cdot \underline{x}$$



① check NFB

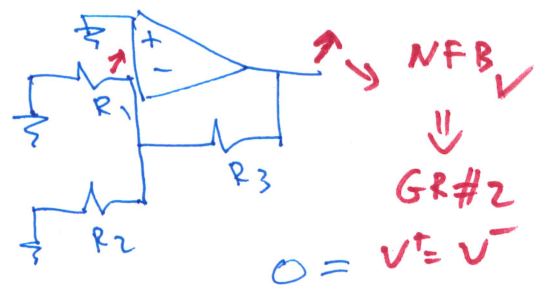

KCL:

$$\frac{V_{in1} - 0}{R_1} + \frac{V_{in2} - 0}{R_2} + \frac{V_{out} - 0}{R_3} = I^- = 0$$

$I_1 \qquad I_2 \qquad I_3$

$$V_{out} = \left(-\frac{R_3}{R_1}\right)V_{in1} + \left(-\frac{R_3}{R_2}\right)V_{in2}$$

$$\rightarrow V_{out} = a_1 \cdot V_{in1} + a_2 \cdot V_{in2}$$


$$\hookrightarrow V_{out} = a_1 V_{in1} + a_2 V_{in2} + \dots + a_k V_{in_{1000}}$$

$\left(-\frac{R_3}{R_k}\right)$

Q5

Superposition

step 1

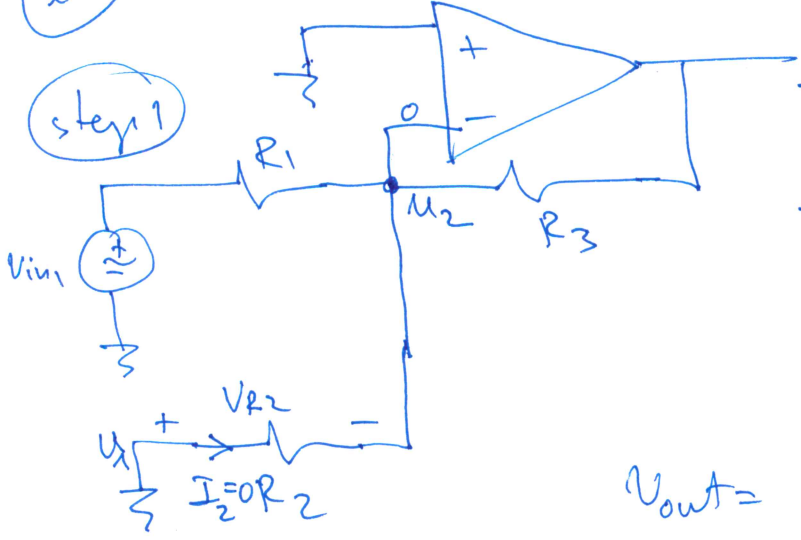

$$V_{out,1} = -\frac{R_3}{R_1} V_{in,1}$$

$$V_{out,2} = -\frac{R_3}{R_2} V_{in,2}$$

$$V_{out} = V_{out,1} + V_{out,2} = \left(-\frac{R_3}{R_1}\right) V_{in,1} +$$

$$\left(-\frac{R_3}{R_2}\right) V_{in,2}$$


$$I_2 = \frac{V_{R2}}{R_2} \text{ (ohm's law)}$$

$$V_{R2} = u_1 - u_2 = 0$$

$$\parallel$$

$$I_2 = 0$$




step 2:

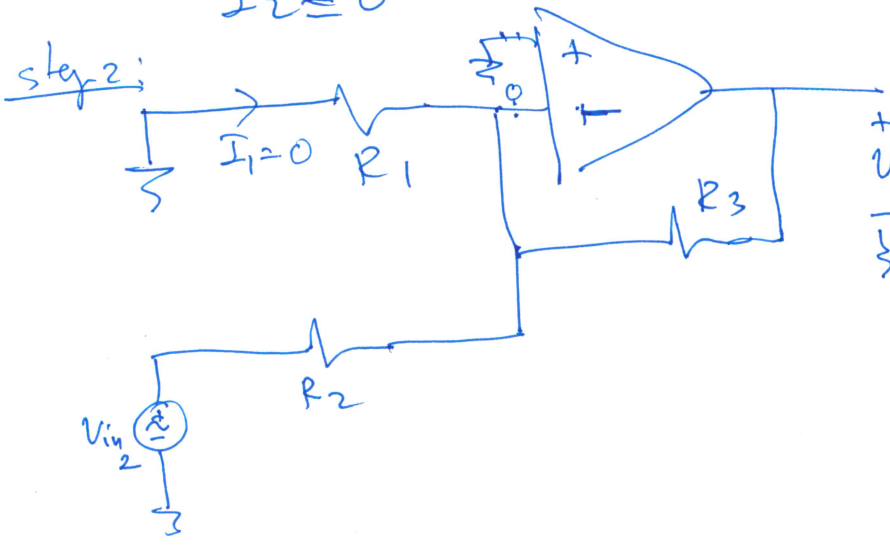

$$V_{out,2} = \left(-\frac{R_3}{R_2}\right) V_{in,2}$$


26

# Thinking in block diagrams:

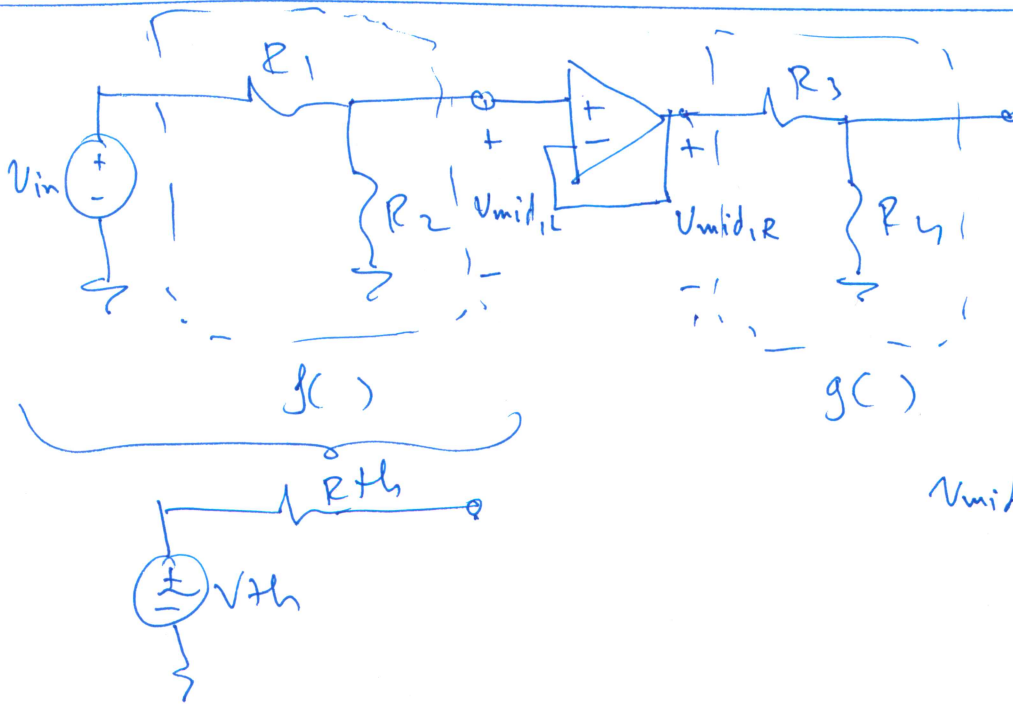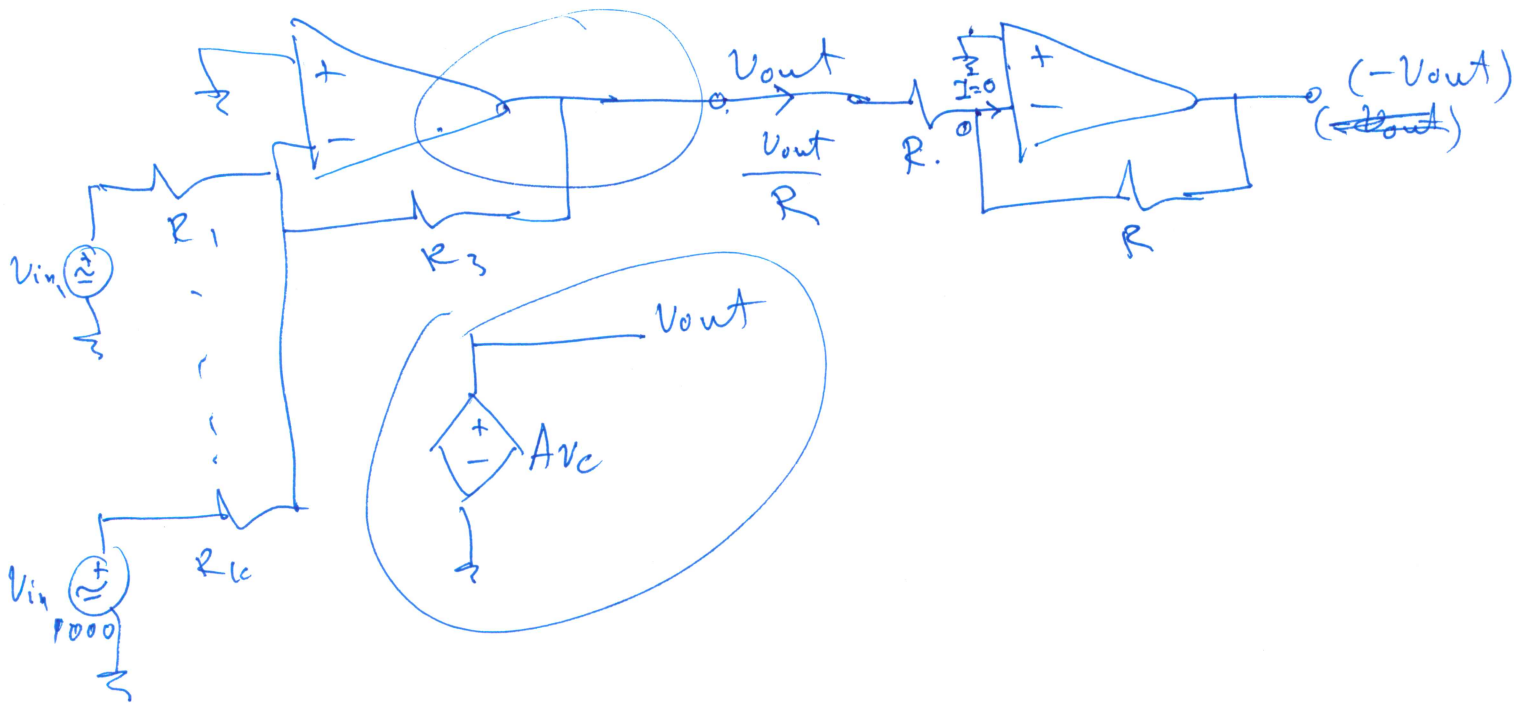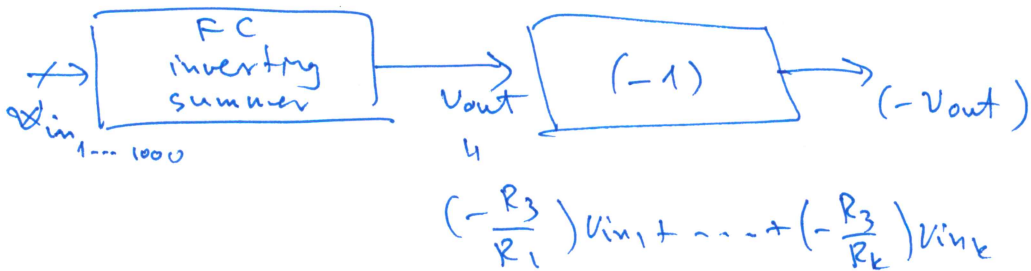

$$V_{mid,L} = V_{mid,R}$$

67

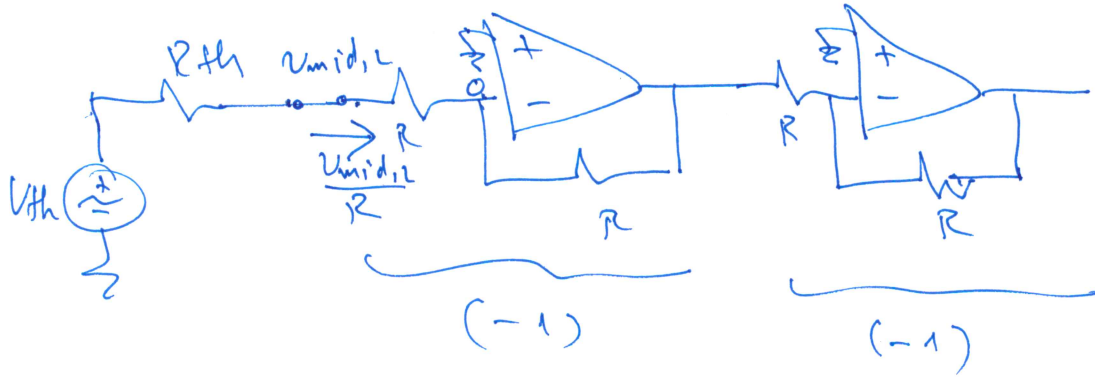

"Unity gain buffer"

