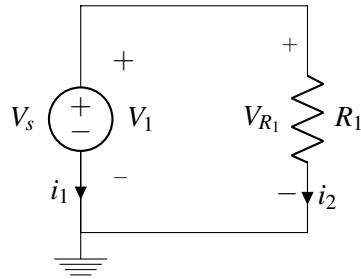



# EECS 16A Designing Information Devices and Systems I Discussion 7A

## 1. Passive Sign Convention and Power

- (a) Suppose we have the following circuit and label the currents as shown below. Calculate the power dissipated or supplied by every element in the circuit. Let  $V_s = 5\text{ V}$  and let  $R_1 = 5\ \Omega$ .




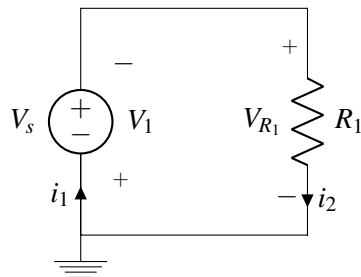- (b) Suppose we change the label of the currents in the circuit to be as shown below. Calculate the power dissipated or supplied by every element in the circuit. Let  $V_s = 5\text{ V}$  and let  $R_1 = 5\ \Omega$ .


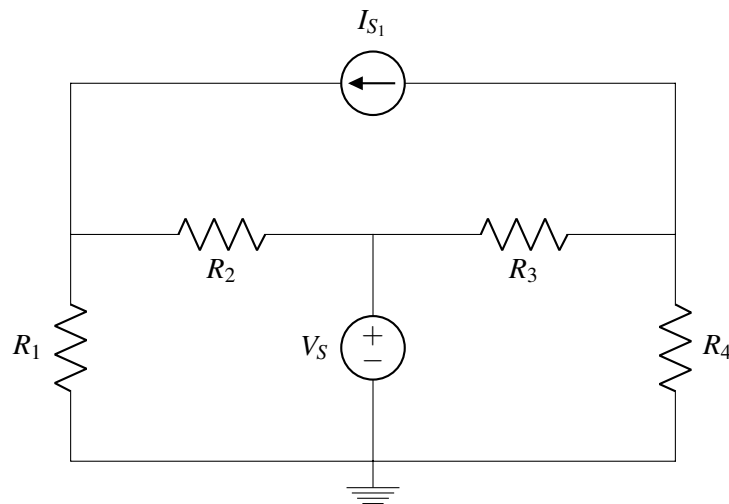
## 2. Circuit Analysis

Setup the matrix to solve for the voltages across and the currents flowing through each component.



### 3. Resist the Touch

In this question, we will be re-examining the 2-dimensional resistive touchscreen previously discussed in both lecture and lab. The general touch screen is shown in Figure 1 (a). The touchscreen has length  $L$  and width  $W$  and is composed of a rigid bottom layer and a flexible upper layer. The strips of a single layer are all connected by an ideal conducting plate on each side. The upper left corner is position  $(1, 1)$ .

The top layer has  $N$  vertical strips denoted by  $x_1, x_2, \dots, x_N$ . These vertical strips all have cross sectional area  $A$ , and resistivity  $\rho_x$ .

The bottom layer has  $N$  horizontal strips denoted by  $y_1, y_2, \dots, y_N$ . These horizontal strips all have cross sectional area  $A$  as well, and resistivity  $\rho_y$ .

Assume that all top layer resistive strips and bottom layer resistive strips are spaced apart equally. Also assume that all resistive strips are rectangular as shown by Figure 1 (b).

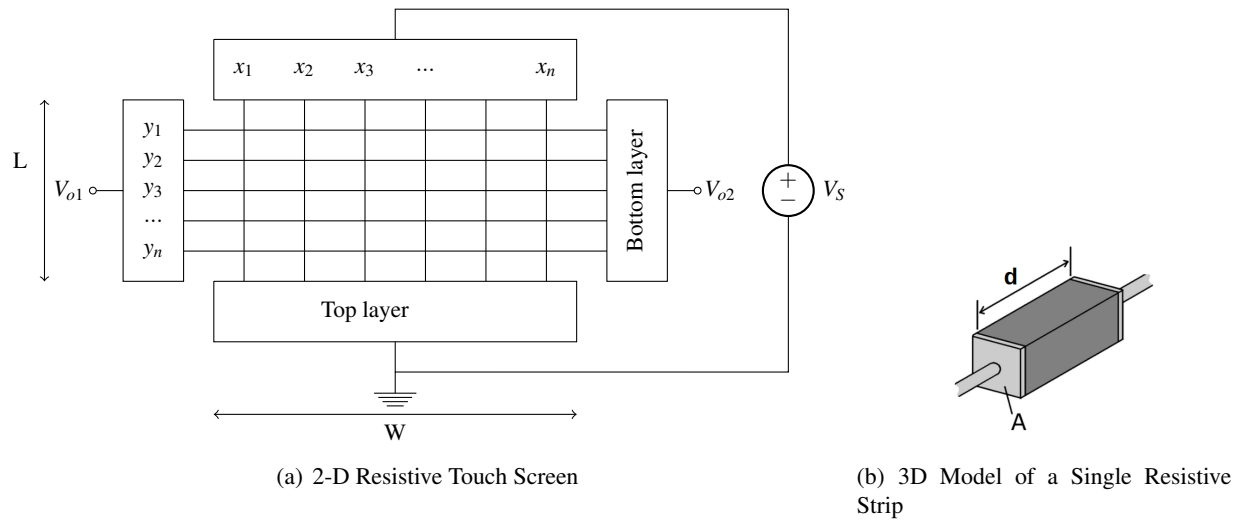
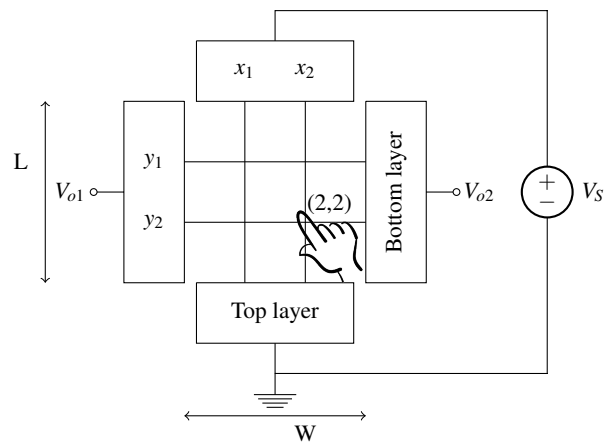


Figure 1:

(a) (3 points) Figure 1(b) shows a model for a single resistive strip. Find the equivalent resistance  $R_x$  for the vertical strips and  $R_y$  for the horizontal strips, as a function of the screen dimensions  $W$  and  $L$ , the respective resistivities, and the cross-sectional area  $A$ .

(b) (5 points) Consider a  $2 \times 2$  example for the touchscreen circuit.

Given that  $V_s = 3\text{V}$ ,  $R_x = 2000\Omega$ , and  $R_y = 2000\Omega$ , draw the equivalent circuit for when the point  $(2, 2)$  is pressed and solve for the voltage at terminal  $V_{O2}$  with respect to ground.

Figure 2:  $2 \times 2$  Case of the Resistive Touchscreen

- (c) (8 points) Suppose a touch occurs at coordinates  $(i, j)$  in Figure 1(a). Find an expression for  $V_{O2}$  as a function of  $V_s$ ,  $N$ ,  $i$ , and  $j$ . The upper left corner is the coordinate  $(1, 1)$  and the upper right coordinate is  $(N, 1)$ .