

Lecture 2 - Module 2

Touchscreen intro - modeling with circuit elements

Today:

- Complete circuit analysis
- Voltage divider example
- Touchscreen construction

Note 12
(reading)


- * Modeling
- * Analysis + Modeling to design a touchscreen

l2 step 5: summarize the unknowns

$$A \vec{x} = \vec{b}$$

$$\vec{x} = \begin{bmatrix} I_{el1} \\ \vdots \\ I_{elk} \\ U_1 \\ \vdots \\ U_{n-1} \end{bmatrix}$$

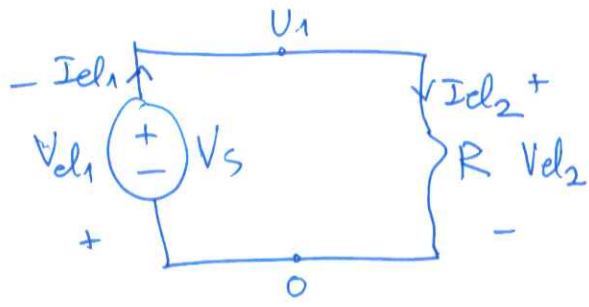
step 6: Use KCL to fill in as many rows of A as possible (lin. index) #Nodes - 1



$$I_{el1} = I_{el2} \Rightarrow I_{el1} - I_{el2} = 0 \quad (1)$$

$$\begin{bmatrix} 1 & -1 & 0 \end{bmatrix} \begin{bmatrix} I_{el1} \\ I_{el2} \\ U_1 \end{bmatrix} = \begin{bmatrix} 0 \end{bmatrix}$$

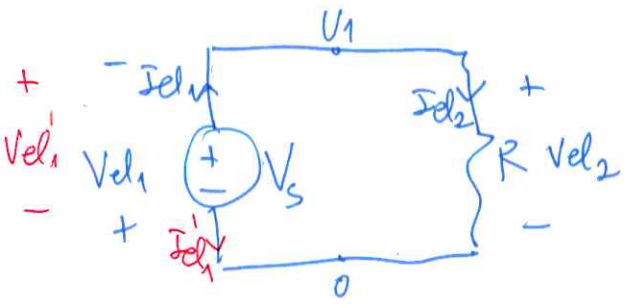step 7: Use I-V relationships for each element to fill the rest of the A matrix.



Voltage source: $Vel_1' = V_s$
 $Vel_1 = -V_s$

voltage def: $Vel_1 = 0 - U_1 = -U_1$
 subs. $-V_s = -U_1 \Rightarrow \boxed{U_1 = V_s} \quad (2)$


Resistor: $Vel_2 = I_{el2} \cdot R$

voltage def: $Vel_2 = U_1 - 0 = U_1 \rightarrow U_1 = I_{el2} \cdot R$
 $\boxed{R \cdot I_{el2} - U_1 = 0} \quad (3)$


$$\begin{bmatrix} 1 & -1 & 0 \\ 0 & 0 & 1 \\ 0 & R & -1 \end{bmatrix} \begin{bmatrix} I_{el1} \\ I_{el2} \\ U_1 \end{bmatrix} = \begin{bmatrix} 0 \\ V_s \\ 0 \end{bmatrix} \Rightarrow \begin{bmatrix} U_1 = V_s \\ I_{el1} = \frac{V_s}{R} \\ I_{el2} = \frac{V_s}{R} \end{bmatrix}$$

(3)

Voltage divider example:


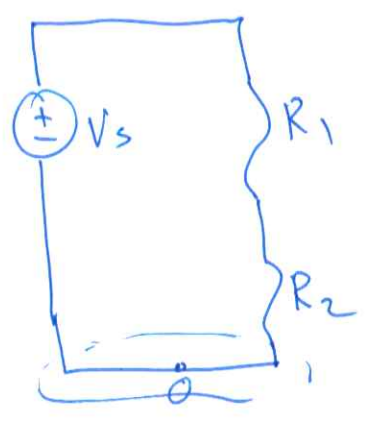


step 1
label
ref.
node

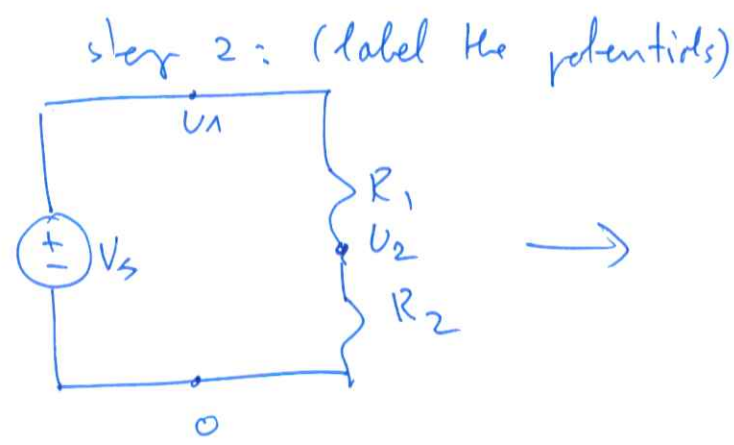

step 3: label the currents arbitrarily

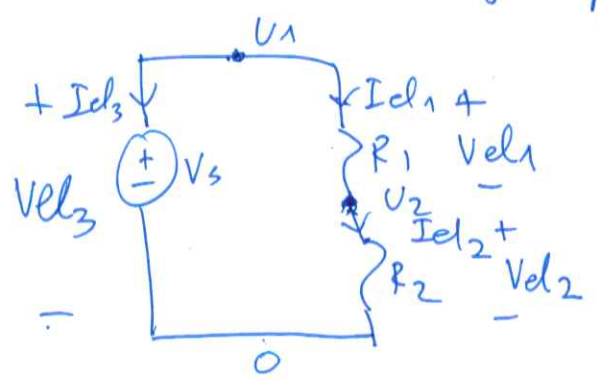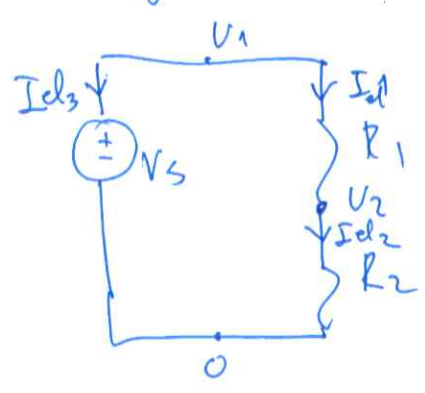step 4: "tricky" label the element voltages (possible sign conv.).



step 5: identify unknowns:

step 6: KCL

$$\vec{x} = \begin{bmatrix} I_{el1} \\ I_{el2} \\ I_{el3} \\ U_1 \\ U_2 \end{bmatrix}$$

(1)

$$I_{el1} + I_{el3} = 0$$

(2)

$$I_{el1} - I_{el2} = 0$$



step 7: I-V & voltage defs for elements:

~~Vel1~~ = Voltage-defs | element I-V

el. 1:

$$Vel_1 = U_1 - U_2 \quad \left. \begin{array}{l} \\ \end{array} \right\} Vel_1 = R_1 \cdot I_{el1} \Rightarrow U_1 - U_2 = R_1 I_{el1} \quad (3)$$

$$Vel_2 = U_2 - 0 = U_2 \quad Vel_2 = R_2 \cdot I_{el2} \Rightarrow U_2 = R_2 I_{el2} \quad (4)$$

$$Vel_3 = U_1 - 0 = U_1 \quad Vel_3 = V_s \Rightarrow U_1 = V_s \quad (5)$$

(3) $R_1 I_{el1} - U_1 + U_2 = 0$

(4) $R_2 I_{el2} - U_2 = 0$

(5) $U_1 = V_s$

(24)

$$\begin{bmatrix} 1 & 0 & 1 & 0 & 0 \\ 1 & -1 & 0 & 0 & 0 \\ R_1 & 0 & 0 & -1 & 1 \\ 0 & R_2 & 0 & 0 & -1 \\ 0 & 0 & 0 & 1 & 0 \end{bmatrix} \begin{bmatrix} I_{el1} \\ I_{el2} \\ I_{el3} \\ V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ V_s \end{bmatrix}$$



$$I_{el1} = \frac{V_s}{R_1 + R_2}, \quad I_{el2} = \frac{V_s}{R_1 + R_2}, \quad I_{el3} = -\frac{V_s}{R_1 + R_2}$$

$$V_1 = V_s, \quad \boxed{V_2 = \frac{R_2}{R_1 + R_2} \cdot V_s}$$

voltage divider

Q5

Resistive touchscreen

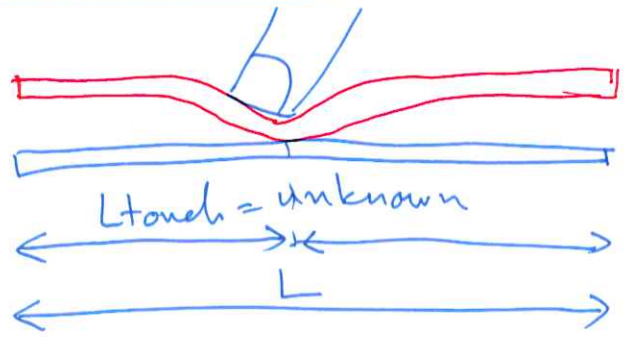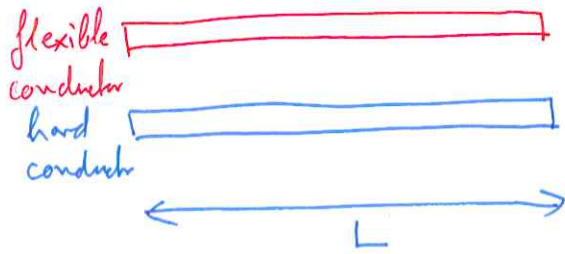

Want to measure $\frac{L_{touch}}{L}$.
 Need to convert electrical quantity.

16A Physics

* Charge - can be either positive or negative
 basic element of electrical flow (e.g. electron)


Unit: Coulomb [C]

* Current - Net amount of charge that passes through some cross-section area over some period of time:

$$[A] \rightarrow I = \frac{dQ \leftarrow [C]}{dt \leftarrow [s]}$$

Always do unit checks

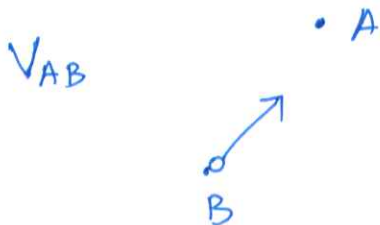
* Voltage: Represents the energy to move a positive unit of charge from one point to another:



$$[V] = \frac{[J] \leftarrow \text{energy unit}}{[C]}$$

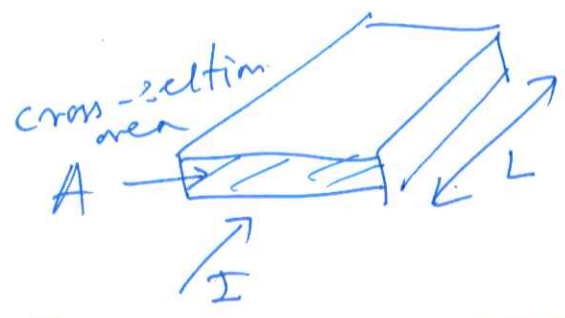
16) * Resistance - real pieces of metal always require a certain amount of energy to flow charge to flow through

$$V_{el} = I_{el} R \quad [V] = [A] \cdot [\Omega]$$



$$R = \rho \cdot \frac{L}{A}$$

Physical:

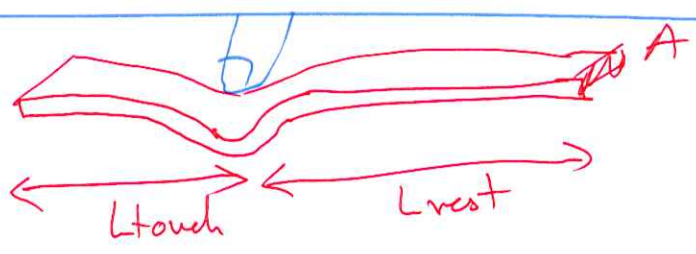


Model:



$$R_1 = \rho \cdot \frac{L_{rest}}{A}$$

$$R_2 = \rho \cdot \frac{L_{touch}}{A}$$

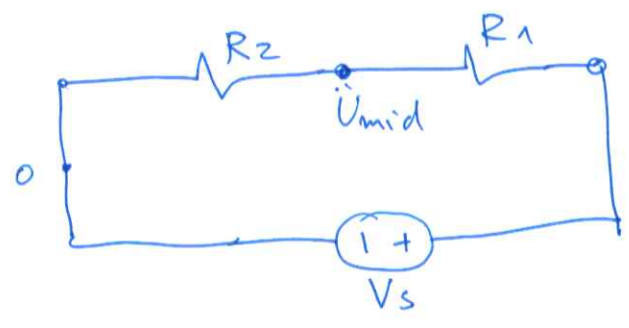Design task: Build a circuit using this model to measure $\frac{L_{touch}}{L}$ as an electric quantity.



$$V_{mid} = \frac{R_2}{R_1 + R_2} \cdot V_s$$

$$= \frac{\rho \cdot \frac{L_{touch}}{A}}{\rho \cdot \frac{L_{rest}}{A} + \rho \cdot \frac{L_{touch}}{A}} \cdot V_s$$

$$V_{mid} = \frac{L_{touch}}{L} \cdot V_s$$

$$V_{mid} = \frac{L_{touch}}{L_{rest} + L_{touch}} \cdot V_s$$

Q7

A more realistic model:

