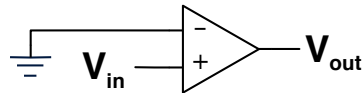


Solutions: Courtesy of John Noonan.

For each problem, assume the op-amp has a nominal gain of $G = 100$.

1. Op-Amps Without Feedback



- (a) For the circuit above, write $H(\omega) = V_{out}/V_{in}$.

Solutions:

$$V_{out} = G(V^+ - V^-)$$

$$V^- = 0 \quad V^+ = V_{in}$$


$$\text{Thus, } V_{out} = G(V_{in} - 0) = GV_{in}$$

$$H(\omega) = \frac{V_{out}}{V_{in}} = G$$

- (b) If G is 20% lower than its nominal value, what is the percent error in $H(\omega)$ relative to nominal?

Solutions: Since $H(\omega) = G$, the percent error will be 20%.

2. Op-Amps With Feedback

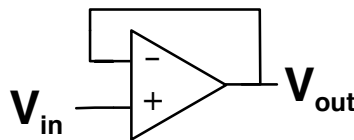

- (a) For the circuit above, approximate V_{out}/V_{in} using the op-amp golden rules.

Solutions:

Using the Golden Rules, we know that $V^+ = V^-$. And since V^- is connected to V_{out} in negative feedback, $V_{in} = V_{out}$. Thus, $\frac{V_{out}}{V_{in}} = 1$.

- (b) Now write V_{out}/V_{in} **without** the second op-amp golden rule (you can still assume no current flows into the amplifier inputs). How close is the result to the approximation from (a)? (Give a percentage.)

Solutions:

$$V_{out} = G(V_{in} - V_{out})$$

$$V_{out} + GV_{out} = GV_{in}$$

$$(1 + G)V_{out} = GV_{in}$$

$$\frac{V_{out}}{V_{in}} = \frac{G}{1 + G}$$

Thus, as G approaches ∞ , $\frac{V_{out}}{V_{in}}$ approaches 1, in which case $V_{out} = V_{in}$.


Percent error in $\frac{V_{out}}{V_{in}}$ relative to the approximation from (a): $(1 - \frac{G}{1+G}) * 100\% = (1 - \frac{100}{101}) * 100\% = 1.0\%$.

- (c) Now assume G is 20% lower than its nominal value. What is the percent error in V_{out}/V_{in} relative to the approximation from (a)?

Solutions:

Percent error in $\frac{V_{out}}{V_{in}}$ relative to the approximation from (a): $(1 - \frac{0.8G}{1+0.8G}) * 100\% = (1 - \frac{80}{81}) * 100\% = 1.23\%$.

3. Inverting Amplifier

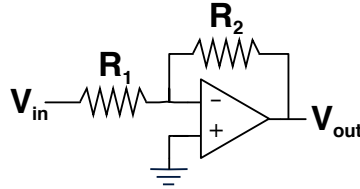

- (a) For the circuit above, approximate V_{out}/V_{in} using the op-amp golden rules.

Solutions: Using the golden rules, we get that $\frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1}$.

- (b) Now write V_{out}/V_{in} without the second op-amp golden rule (you can still assume no current flows into the amplifier inputs).

Solutions:

$$\frac{V_{in} - V_A}{R_1} = \frac{V_A - V_{out}}{R_2}$$

$$\text{Also, } V_{out} = G(0 - V_A)$$

$$V_{out} = -GV_A$$

$$V_A = -\frac{V_{out}}{G}$$

$$\frac{1}{R_1} V_{in} - \frac{1}{R_1} * -\frac{V_{out}}{G} = -\frac{1}{R_2} \frac{V_{out}}{G} - \frac{V_{out}}{R_2}$$

$$\frac{1}{R_1} V_{in} = -\left(\frac{1}{R_1} \frac{1}{G} + \frac{1}{R_2} \frac{1}{G} + \frac{1}{R_2}\right) V_{out}$$

$$\frac{V_{out}}{V_{in}} = \frac{1}{R_1} \frac{-1}{\frac{1}{R_1} \frac{1}{G} + \frac{1}{R_2} \frac{1}{G} + \frac{1}{R_2}}$$

$$= \frac{-1}{\frac{1}{G} + \frac{R_1}{R_2} \frac{1}{G} + \frac{R_1}{R_2}}$$

- (c) If $R_1 = 100\Omega$ and $R_2 = 500\Omega$, find the gain of the circuit using the models from both (a) and (b). What is the percent error?

Solutions:

$$\text{a: } -\frac{R_2}{R_1} = -\frac{500}{100} = -5$$

$$\text{b: } \frac{-1}{\frac{1}{100} + \frac{1}{5} \frac{1}{100} + \frac{1}{500}} = -4.72$$

About 5.6% error.

- (d) Now assume G is 20% lower than its nominal value and recalculate the gain. What is the new percent error compared to (a)?

Solutions:

$$\text{a: } -5$$

$$\text{b: } \frac{-1}{\frac{1}{80} + \frac{1}{5} \frac{1}{80} + \frac{1}{500}} = -4.65$$

About 7.0% error.