
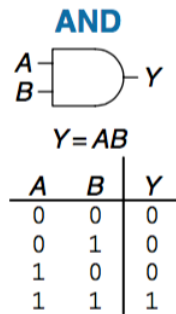


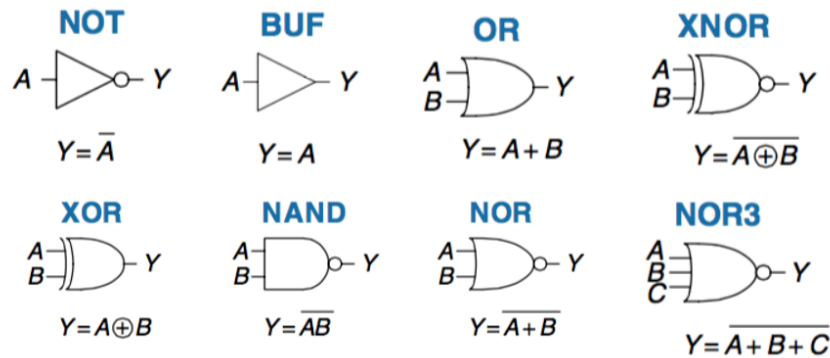1. **Common Logic Gates** A *truth table* is a list of all possible inputs of a Boolean function and the associated outputs. For example, the truth table of the AND function ($Y = AB$) is:




Write the truth tables for these common logic gates.



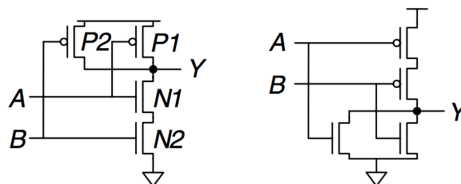2. Building Gates with Transistors

For each transistor schematic below:

- Write down the truth table and identify the logic function.
- Show which switches are ON and which are OFF when $A = 1$ and $B = 0$.
- Are the switches ever configured such that current flows directly from V_{DD} to ground? Show which combination of inputs can make this occur, or explain why it cannot.




3. More Gates

- Write the symbol, Boolean logic equation, truth table, and transistor schematic for a 3-input NAND gate.
- Can you build an AND gate out of transistors? Draw a schematic, or explain why you cannot.

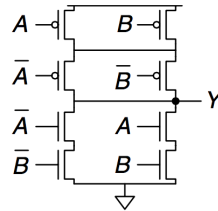
4. Transistors to Logic Functions

Write the truth table and a Boolean logic function for the schematic.



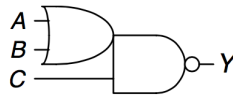5. Logic Functions to Transistors

Write the truth table and a Boolean logic function for the gate shown. Then implement the gate with transistors, using as few transistors as possible.



6. Simplifying Boolean Algebra

Write a truth table for each Boolean function.

- $Y = AC + \overline{A}BC$
- $Y = \overline{A}B + \overline{A}B\overline{C} + \overline{\overline{A} + \overline{C}}$
- $Y = \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C\overline{D} + \overline{A}BD + \overline{A}\overline{B}C\overline{D} + \overline{B}\overline{C}D + \overline{A}$

7. De Morgan's Theorem

De Morgan's Theorem is a property of Boolean logic. It states:

$$\overline{B_0 \cdot B_1 \cdot B_2 \cdot \dots} = \overline{B_0} + \overline{B_1} + \overline{B_2} + \dots$$

Prove De Morgan's Theorem for three variables B_0 , B_1 , and B_2 .

Note: In Boolean algebra, the fact that each variable can be either zero or one gives us a powerful tool for proving general properties. The technique of *perfect induction*, also known as "proof by exhaustion", simply shows that the theorem holds for all possible values of the variables. You might find this technique helpful here. (Start by writing a truth table...)