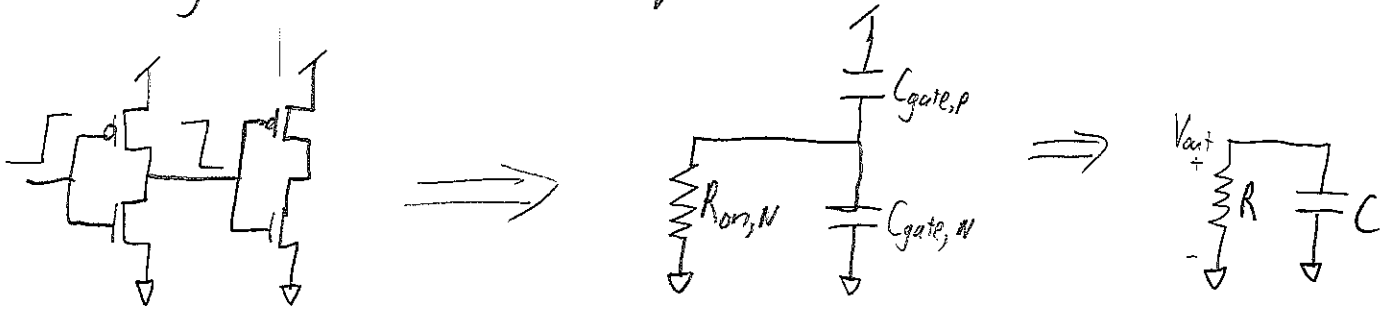


Solving our RC circuit equation:



$$V_{out}(0) = V_{DD}$$

$$V_{out} = -RC \frac{dV_{out}}{dt}$$

$$dt = -RC \frac{1}{V_{out}} dV_{out}$$

$$\int dt = -RC \int \frac{1}{V_{out}} dV_{out}$$

$$t + K_1 = -RC \ln V_{out}$$

$$\frac{-t}{RC} + \frac{-K_1}{RC} = \ln V_{out}$$

$$V_{out} = e^{-\frac{t}{RC} - \frac{K_1}{RC}}$$

$$= e^{-\frac{t}{RC}} e^{-\frac{K_1}{RC}}$$

$$= K e^{-\frac{t}{RC}}$$

Use our initial condition:

$$V_{out}(0) = V_{DD} = K e^{-\frac{0}{RC}} = K$$

$$\boxed{K = V_{DD}}$$

So:

$$V_{out}(t) = V_{DD} e^{-t/RC}$$

When does $V_{out} = V_{DD}/2$?

$$V_{DD}/2 = V_{DD} e^{-t/RC}$$


$$\frac{1}{2} = e^{-t/RC}$$

$$2 = e^{t/RC}$$

$$\ln 2 = t/RC$$

$$t = RC \ln 2 = 0.69 RC$$

Warmup:

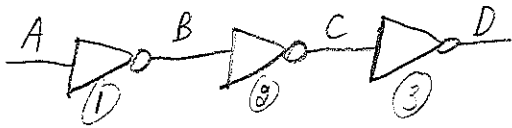


Find the delay from A to C when A transitions from low to high:

$R_{on} = 12.8k\Omega$ for all devices

$C_{gate} = 1fF$ for all devices

Answer:

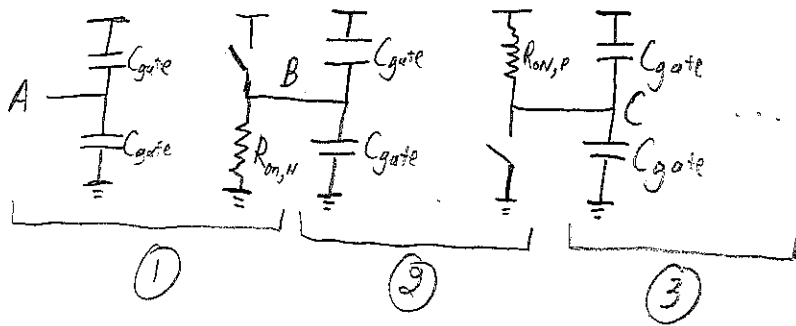

$t_{A-B} = \ln 2 R_{on,N} \cdot 2C_{gate} = 17.7ps$

$t_{B-C} = t_{A-B}$

$t_{A-C} = 35.5ps$

Questions from lecture?