 



1. Non-Uniform Delays



Find the delay from point *A* to point *D* in the circuit shown above for both rising and falling transitions at point *A*. Assume the following *R* and *C* values:

Inverter	$R_{ON,N}$	$R_{ON,P}$	$C_{gate,N}$	$C_{gate,P}$
1	8.5k Ω	10k Ω	0.2fF	0.4fF
2	2.5k Ω	3k Ω	0.6fF	1.2fF
3,4	1k Ω	1.2k Ω	2.5fF	5fF

2. Ring Oscillators

 

(a) Describe the behavior of each circuit drawn above. Assume node *A* is initially 0.

- (b) Circuit 2 is called a *ring oscillator* or RO. If each inverter in this circuit has $R_{ON,N} = R_{ON,P} = 5\text{k}\Omega$ and $C_{\text{gate},N} = C_{\text{gate},P} = 0.5\text{fF}$, at what frequency will node A oscillate?

3. Ring Oscillators, Really

In reality, it would be difficult to design transistors with the parameters given above because pMOS devices tend to be 1.5-3x weaker than nMOS devices of the same size. (This is because electrons, the charge carriers for nMOS devices, have a higher *mobility* than holes, the charge carriers for pMOS devices.) Let's investigate options for a more realistic ring oscillator.

- (a) First, we'll try leaving the nMOS and pMOS the same size. Using the same nMOS characteristics as Question 2, use $R_{ON,P} = 10\text{k}\Omega$ and $C_{\text{gate},P} = 0.5\text{fF}$ to find the new oscillation frequency of the RO.
- (b) Next, we'll increase the size of the pMOS to match the nMOS drive strength. Using the same nMOS characteristics as Question 2, use $R_{ON,P} = 5\text{k}\Omega$ and $C_{\text{gate},P} = 1\text{fF}$ to find the new oscillation frequency of the RO.
- (c) If we wanted to use the RO design from part (b) to generate a 1GHz clock, approximately how many inverter stages would be required?