
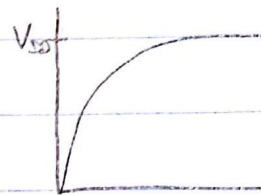
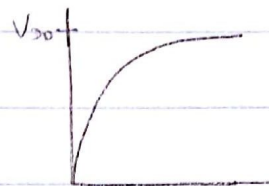
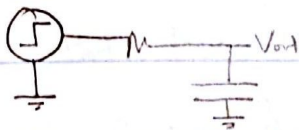
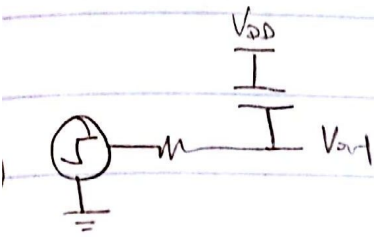
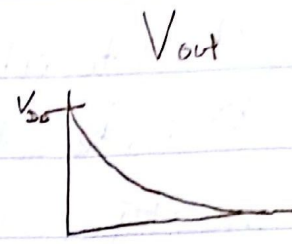
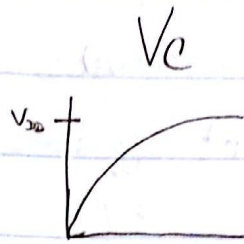


Discussion 6

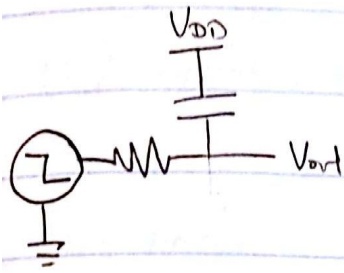

c) $V_R = V_{in} - V_{out}$

$I = \frac{V_{in} - V_{out}}{R} = C \frac{dV_{out}}{dt}$

$V_C = V_{out}$

$V_{out} + CR \frac{dV_{out}}{dt} = V_{in} = V_{DD}$ after $t=0$

First solve homogeneous,

$$V_{out} + RC \frac{dV_{out}}{dt} = 0$$

$$\frac{1}{RC} e^{st} + s e^{st} = 0$$

$$s = -\frac{1}{RC}$$

$$\Rightarrow V_{out}' = k e^{-\frac{t}{RC}}$$

Solve for the other side

$$A + RC \frac{dA}{dt} = V_{in}$$

$$A = V_{in}$$

$$V_{out}^A + V_{out}' = V_{out}$$

$$V_{out} = k e^{-t/RC} + V_{in}$$


Plug in init cond for const:

$$0 = k e^{-0/RC} + V_{in}$$

$$k = -V_{in} = -V_{DD}$$

$$\Rightarrow V_{out} = -V_{in} e^{-t/RC} + V_{DD}$$

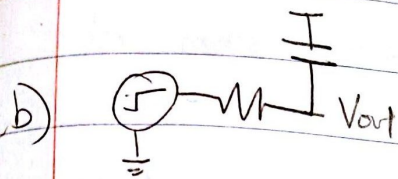- ① Find initial conditions
- ② Write out device voltages
- ③ Write out current equations
- ④ Plug in to get a Diff Eq
- ⑤ Solve the homogenous
- ⑥ Solve the Diff Eq
- ⑦ Plug in Initial Cond.



$$V_c = V_{dd} - 0$$

$$V_R = V_{in} - V_{out}$$

$$V_c = V_{DD} - V_{out}$$

$$I = \frac{V_R}{R} = C \frac{dV_c}{dt}$$

$$\frac{V_{in} - V_{out}}{R} = C \frac{d(V_{dd} - V_{out})}{dt}$$

$$V_{in} - V_{out} = RC \left(\frac{dV_{dd}}{dt} - \frac{dV_{out}}{dt} \right)$$

$$V_{in} - V_{out} = RC \frac{dV_{out}}{dt}$$

$$V_{out} + RC \frac{dV_{out}}{dt} = V_{in}$$

Solve homogenous

$$V_{out} + RC \frac{dV_{out}}{dt} = 0$$

$$V_{out} = K e^{-t/RC}$$

Solve constant

$$A + RC \frac{dA}{dt} = V_{in}$$

$$A = V_{in}$$

Plug in init. cond.


$$V_{out} = K e^{-t/RC} + V_{in}$$

$$0 = K e^{-0/RC} + V_{in}$$

$$K = -V_{in}$$

$$V_{out} = -V_{in} e^{-t/RC} + V_{in}$$

$$V_{out} = -V_{dd} e^{-t/RC} + V_{dd}$$

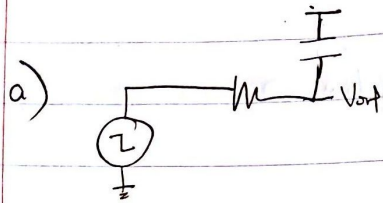

All the same things from last time apply,
but the initial cond, $\neq V_{in}$ are diff

$$\text{init cond} \Rightarrow V_{out}^0 = V_{DD}$$

$$V_{in}^0 = 0$$

$$V_{out} = Ke^{-t/RC} + V_{in}$$


$$V_{DD} = Ke^{-0/RC} + V_{in}$$

$$K = V_{DD} - V_{in}$$


$$V_{out} = (V_{DD} - V_{in})e^{-t/RC} + V_{in}$$

$$V_{out} = V_{DD}e^{-t/RC} + V_{in}$$



Go over setting up a second order:

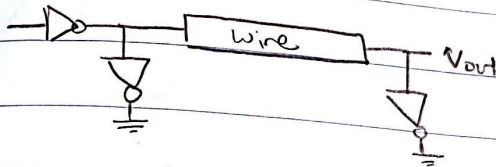

Where wire =

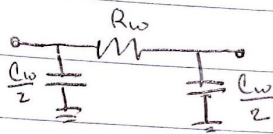

So we can rewrite:

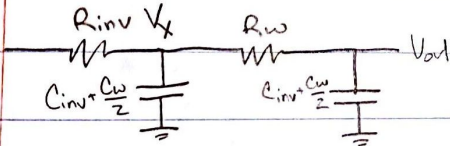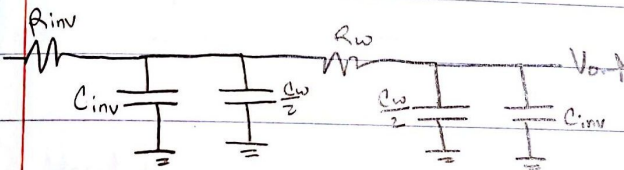

$$V_{R_{in}} = V_{in} - V_x \quad V_{R_w} = V_x - V_{out} \Rightarrow V_x = V_{out} + V_{R_w}$$

$$\frac{V_{R_{in}}}{R_{in}} - C \frac{dV_x}{dt} - \frac{V_{R_w}}{R_w} = 0 \quad \frac{V_{R_w}}{R_w} - C \frac{dV_{out}}{dt} = 0$$

$$V_{in} - V_x - R_{in} R_w C \frac{d(V_{out} - V_{out})}{dt} - \frac{V_{R_w}}{R_w} = 0$$

, where $V_{R_w} = R_w C \frac{dV_{out}}{dt}$

$$V_{in} - R_w C \frac{dV_{out}}{dt} - R_{in} R_w C \frac{d(R_w C \frac{dV_{out}}{dt})}{dt} - R_{in} R_w C \frac{dV_{out}}{dt} - C \frac{dV_{out}}{dt} = 0$$

arrange prettily, but don't solve!