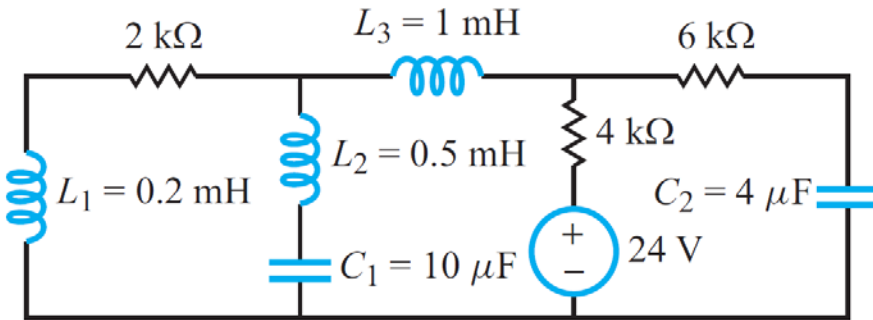

RL Circuits

Michel M. Maharbiz

Vivek Subramanian

RL Circuits at dc


At DC no voltage across inductors: **short circuit**





$$I_1 = \frac{24}{(2 + 4)\text{k}} = 4 \text{ mA},$$

and node voltage V is

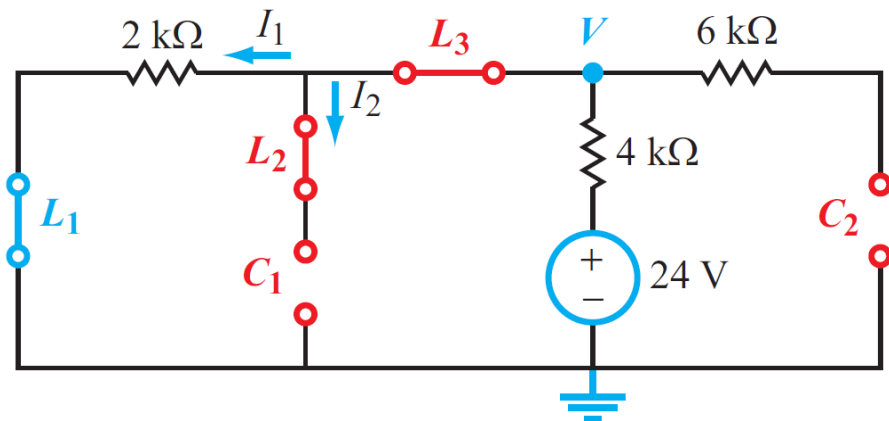
$$V = 24 - (4 \times 10^{-3} \times 4 \times 10^3) = 8 \text{ V}.$$



Natural Response of the RL Circuit

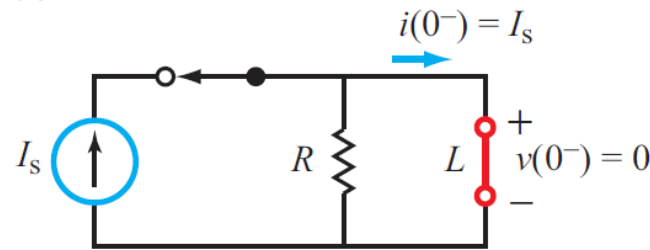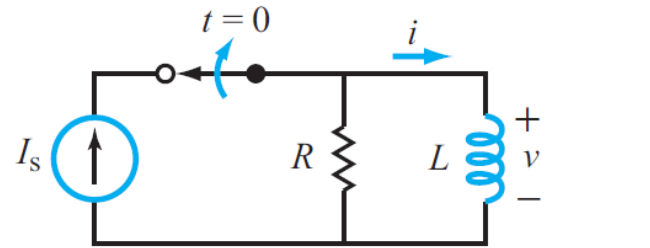

At $t = 0^-$

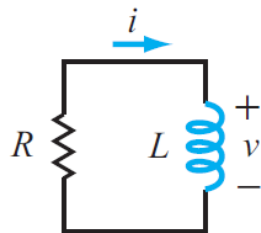

At $t \geq 0$

$$i(0) = i(0^-) = I_s$$

$$Ri + L \frac{di}{dt} = 0,$$

which can be cast in the form

$$\frac{di}{dt} + ai = 0,$$

where a is a temporary constant given by

$$a = \frac{R}{L}.$$




$$i(t) = i(0) e^{-t/\tau} \quad (\text{for } t \geq 0)$$

(natural response),

where for the RL circuit, the *time constant* is given by

$$\tau = \frac{1}{a} = \frac{L}{R}.$$

General Response of the RL Circuit

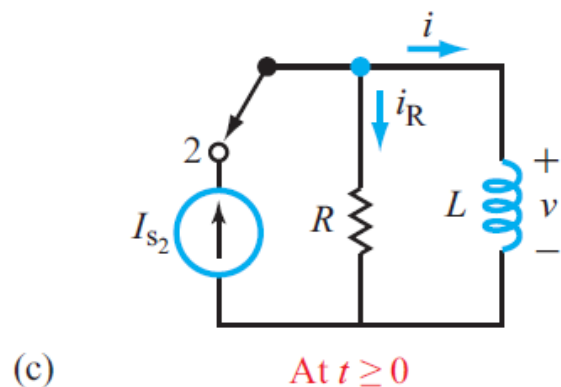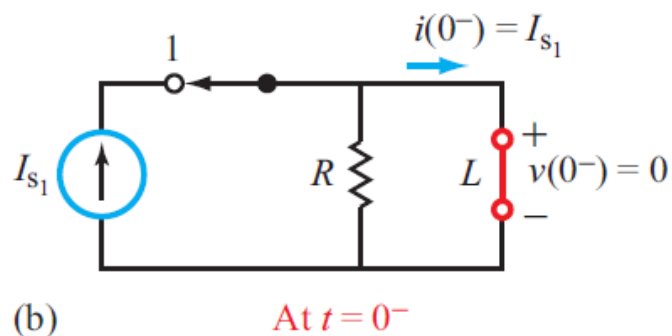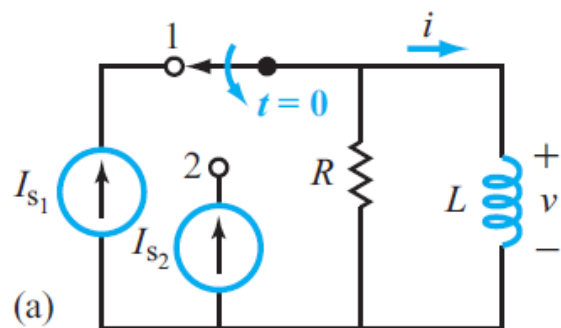

$$-I_{s2} + i_R + i = 0.$$

Since v is common to R and L , $i_R = v/R$, and by applying $v = L di/dt$, the KCL equation becomes

$$\frac{di}{dt} + ai = b, \quad (5.105)$$

where a is as given previously by Eq. (5.102) and

$$b = aI_{s2} = \frac{R}{L} I_{s2}. \quad (5.106)$$

$$i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau} \quad (\text{for } t \geq 0)$$

(switch action at $t = 0$),

If the sudden change in the circuit configuration happens at $t = T_0$ instead of at $t = 0$, the general expression for $i(t)$ becomes

$$i(t) = i(\infty) + [i(T_0) - i(\infty)]e^{-(t-T_0)/\tau} \quad (\text{for } t \geq T_0)$$

(switch action at $t = T_0$),