
Bode Plot Examples

Michel M. Maharbiz

Vivek Subramanian

Bandpass RLC Filter revisited

$$\mathbf{I} = \frac{\mathbf{V}_s}{R + j(\omega L - \frac{1}{\omega C})}$$

$$= \frac{j\omega C \mathbf{V}_s}{(1 - \omega^2 LC) + j\omega RC}$$

$$\mathbf{H}_{BP}(\omega) = \frac{\mathbf{V}_R}{\mathbf{V}_s} = \frac{R\mathbf{I}}{\mathbf{V}_s} = \frac{j\omega RC}{(1 - \omega^2 LC) + j\omega RC}$$

$$M_{BP}(\omega) = |\mathbf{H}_{BP}(\omega)| = \frac{\omega RC}{\sqrt{(1 - \omega^2 LC)^2 + \omega^2 R^2 C^2}}$$



$$\phi_R(\omega) = 90^\circ - \tan^{-1} \left[\frac{\omega RC}{1 - \omega^2 LC} \right]$$

$$\omega_{c1} = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\omega_{c2} = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

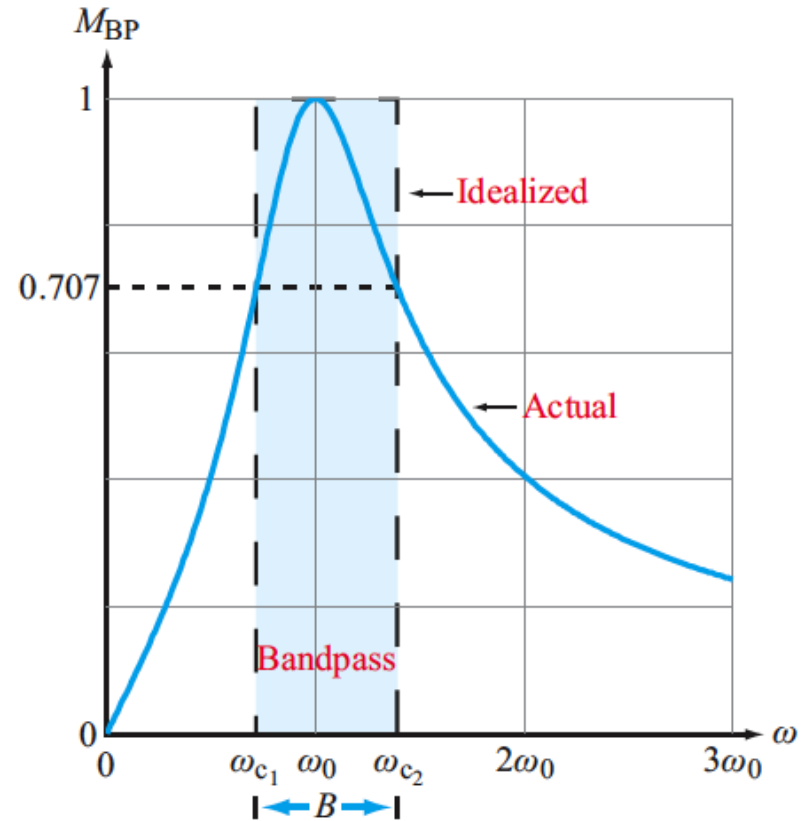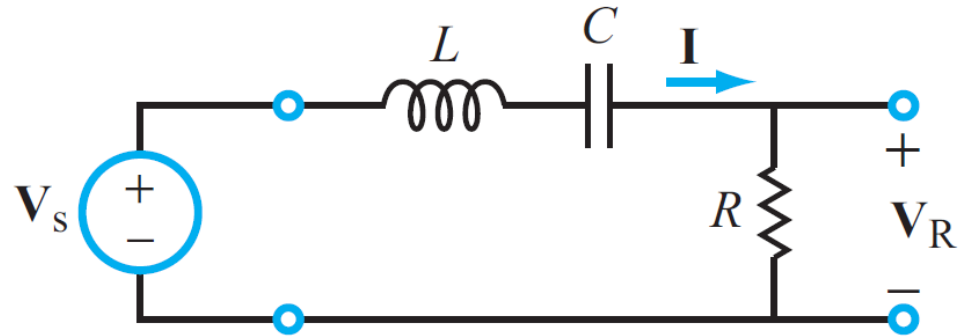
$$B = \omega_{c2} - \omega_{c1} = \frac{R}{L}$$



Bandpass RLC Filter (cont.)

$$Q = 2\pi \left(\frac{W_{\text{stor}}}{W_{\text{diss}}} \right) \Big|_{\omega=\omega_0}$$

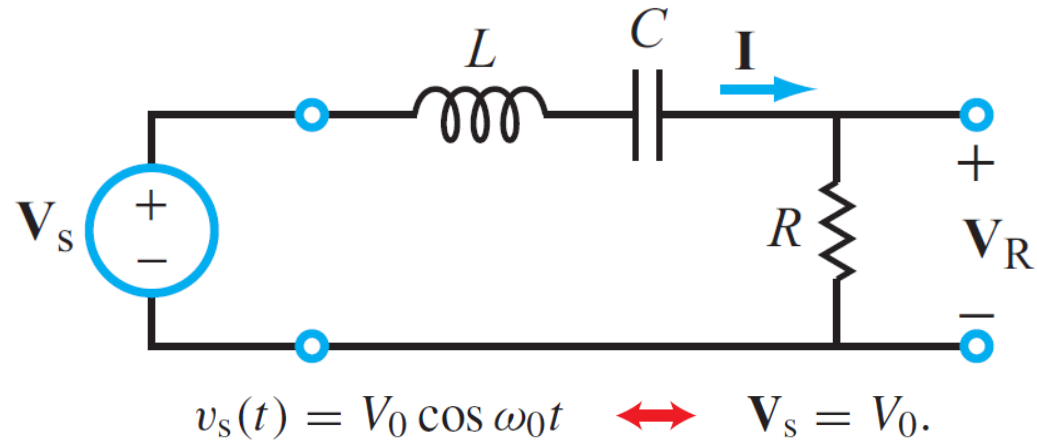- W_{stor} is the **maximum energy that can be stored** in the circuit at resonance ($\omega = \omega_0$)
- W_{diss} is the **energy dissipated** by the circuit during a single period T .



$$\begin{aligned} \mathbf{Z} &= R + j\omega_0 L - j/\omega_0 C \\ &= R \quad (@ \omega_0 = 1/\sqrt{LC}) \end{aligned}$$

and

$$\mathbf{I} = \frac{\mathbf{V}_s}{\mathbf{Z}} = \frac{\mathbf{V}_s}{R} = \frac{V_0}{R}.$$

The time-domain current then is given by

$$i(t) = \Re \left[\frac{V_0}{R} e^{j\omega_0 t} \right] = \frac{V_0}{R} \cos \omega_0 t.$$

Bandpass RLC Filter (cont.)

Derivation of Q

$$i(t) = \Re \left[\frac{V_0}{R} e^{j\omega_0 t} \right] = \frac{V_0}{R} \cos \omega_0 t$$

$$w_L(t) = \frac{1}{2} L i_L^2(t) = \frac{V_0^2 L}{2R^2} \cos^2 \omega_0 t \quad (\text{J})$$

$$\begin{aligned} w_C(t) &= \frac{1}{2} C v_C^2(t) = \frac{1}{2} C \left(\frac{1}{C} \int i dt \right)^2 \\ &= \frac{1}{2} C \left(\frac{V_0}{\omega_0 RC} \sin \omega_0 t \right)^2 \\ &= \frac{V_0^2 L}{2R^2} \sin^2 \omega_0 t \quad (\text{J}). \end{aligned}$$

$$\begin{aligned} W_{\text{stor}} = w_L(t) + w_C(t) &= \frac{V_0^2 L}{2R^2} [\cos^2 \omega_0 t + \sin^2 \omega_0 t] \\ &= \frac{V_0^2 L}{2R^2}. \end{aligned} \quad (9.59)$$

$$\begin{aligned} W_{\text{diss}} &= \int_0^T p_R dt = \int_0^T i^2 R dt \\ &= \int_0^{2\pi/\omega_0} \frac{V_0^2}{R} \cos^2 \omega_0 t dt = \frac{\pi V_0^2}{\omega_0 R} \end{aligned}$$


$$Q = 2\pi \left(\frac{W_{\text{stor}}}{W_{\text{diss}}} \right) \Big|_{\omega=\omega_0},$$

$$Q = \frac{\omega_0 L}{R} = \frac{\omega_0}{B},$$

Resonant frequency


Bandwidth

Bandpass Filter

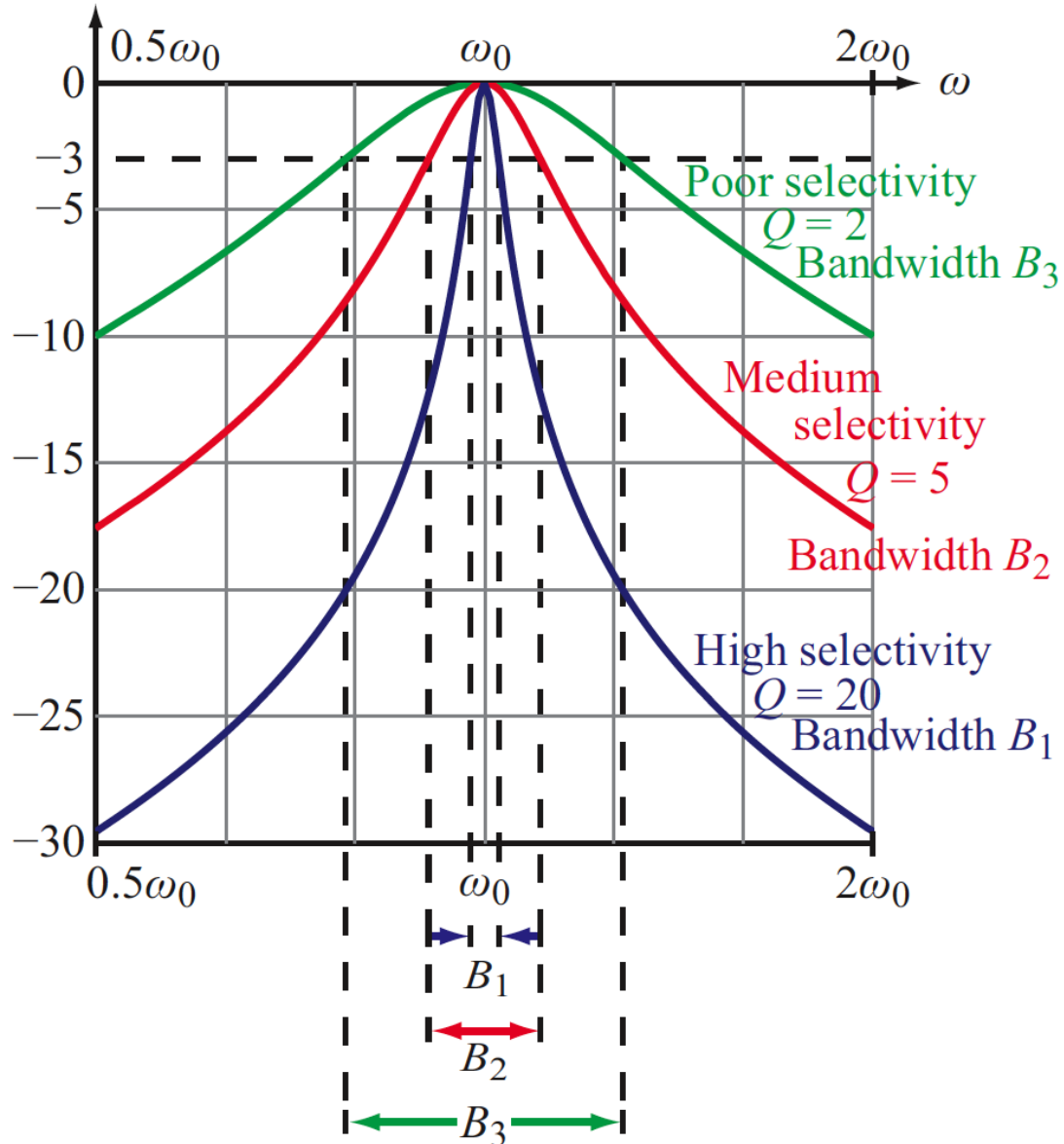

RLC Filters

RLC Circuit

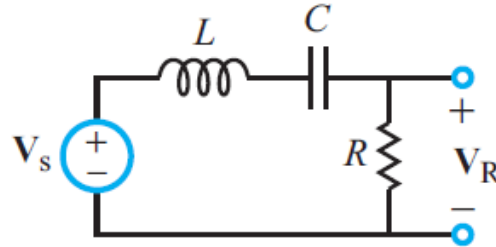

Transfer Function

$$H = \frac{V_R}{V_s}$$

Resonant Frequency, ω_0

$$\frac{1}{\sqrt{LC}}$$

Bandwidth, B

$$\frac{R}{L}$$

Quality Factor, Q


$$\frac{\omega_0}{B} = \frac{\omega_0 L}{R}$$

Lower Half-Power Frequency, ω_{c1}

$$\left[-\frac{1}{2Q} + \sqrt{1 + \frac{1}{4Q^2}} \right] \omega_0$$

Upper Half-Power Frequency, ω_{c2}
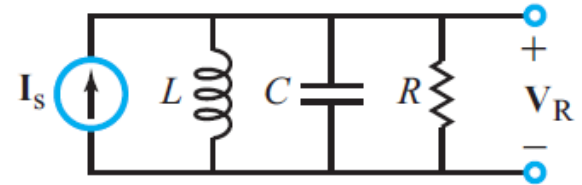
$$\left[\frac{1}{2Q} + \sqrt{1 + \frac{1}{4Q^2}} \right] \omega_0$$



$$H = \frac{V_R}{I_s}$$

$$\frac{1}{\sqrt{LC}}$$

$$\frac{1}{RC}$$

$$\frac{\omega_0}{B} = \frac{R}{\omega_0 L}$$


$$\left[-\frac{1}{2Q} + \sqrt{1 + \frac{1}{4Q^2}} \right] \omega_0$$

$$\left[\frac{1}{2Q} + \sqrt{1 + \frac{1}{4Q^2}} \right] \omega_0$$


Notes: (1) The expression for Q of the series RLC circuit is the inverse of that for Q of the parallel circuit. (2) For $Q \geq 10$, $\omega_{c1} \simeq \omega_0 - \frac{B}{2}$, and $\omega_{c2} \simeq \omega_0 + \frac{B}{2}$.

RLC Filters, con't


Highpass Filter

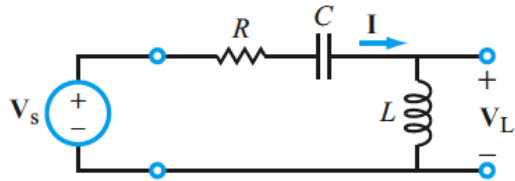


(a) $H_{HP} = V_L / V_s$

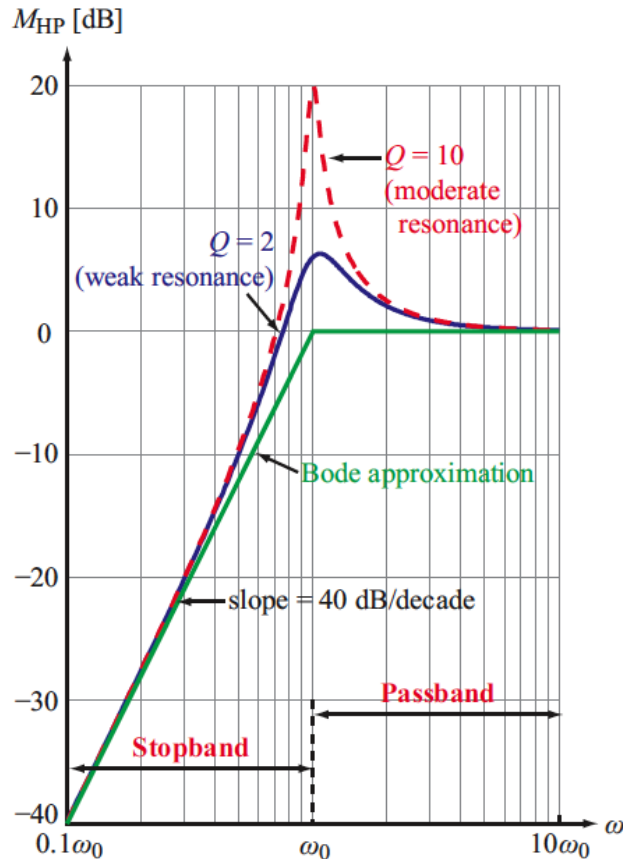

Lowpass Filter


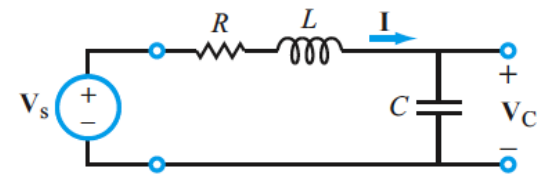


(a) $H_{LP} = V_C / V_s$

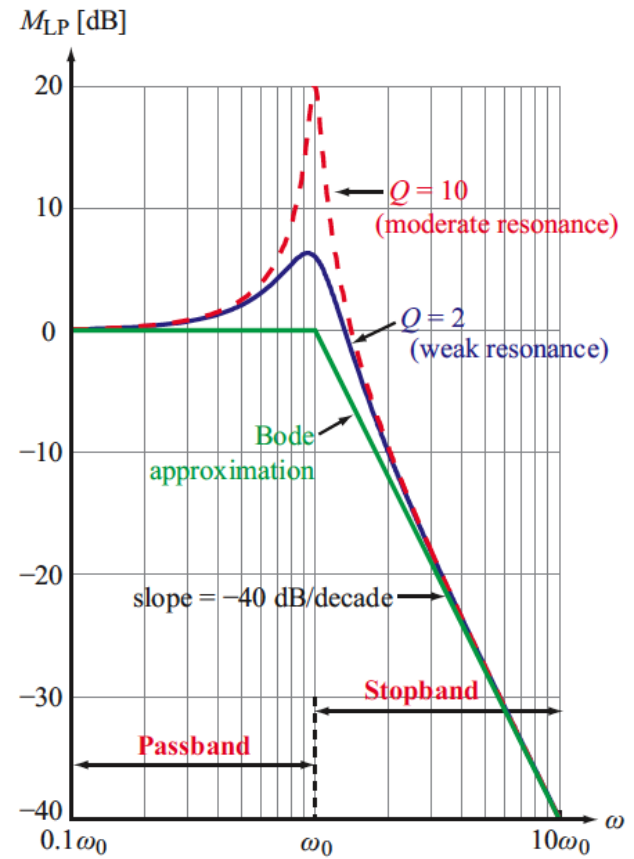


Bandreject


(a) $H_{BR} = V_{LC}/V_s$

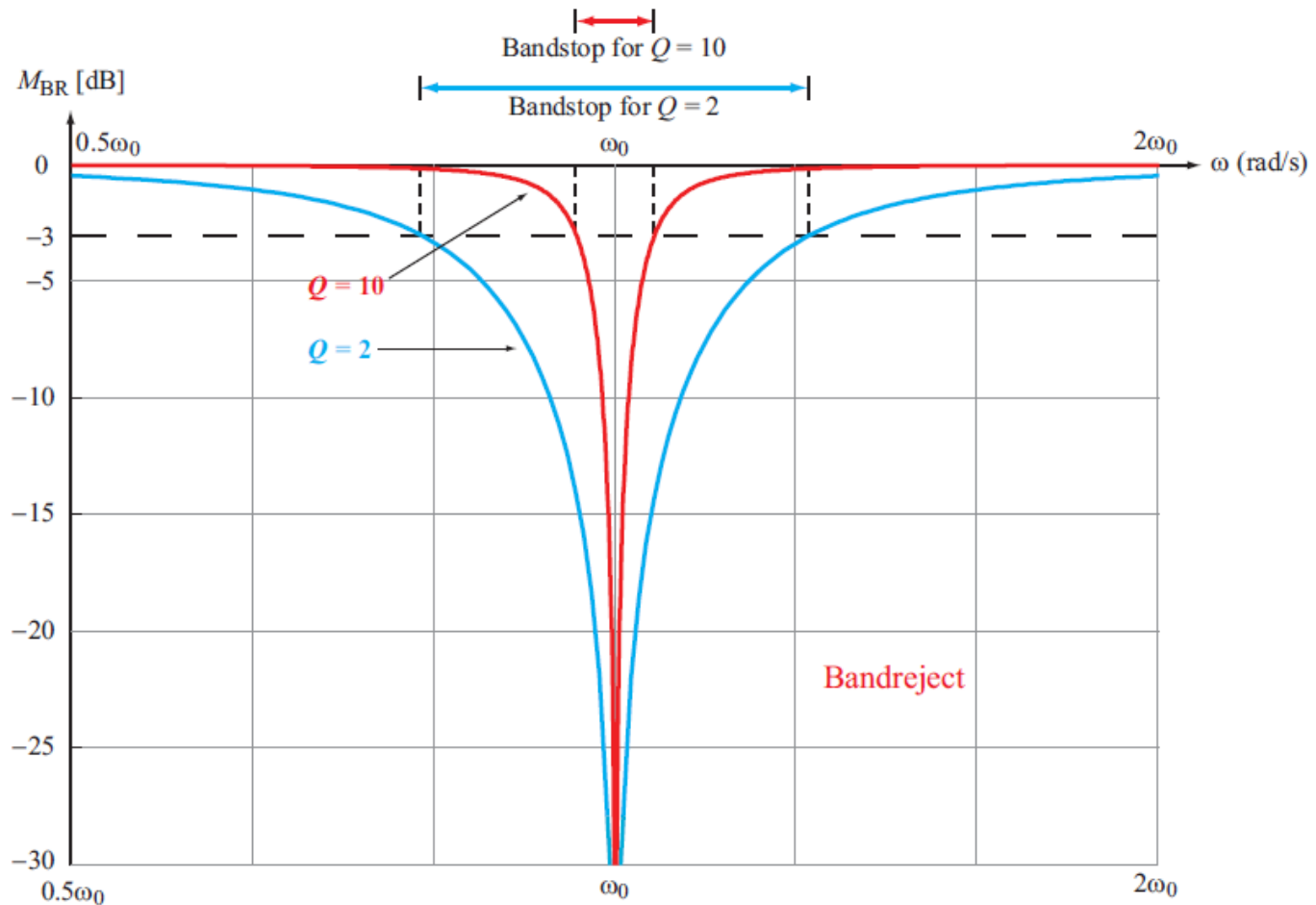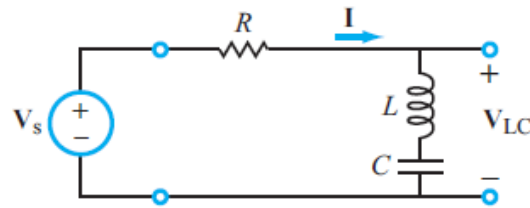


Filter Order

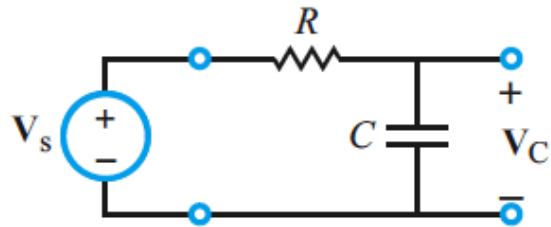


(a) First-order filter

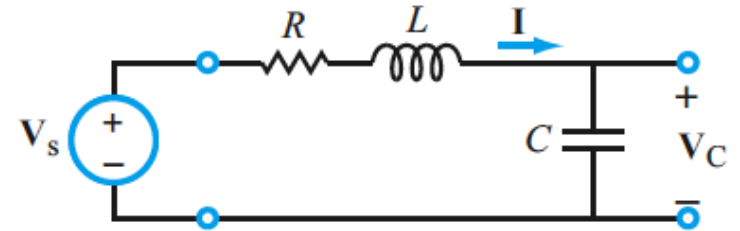

(c) Second-order filter

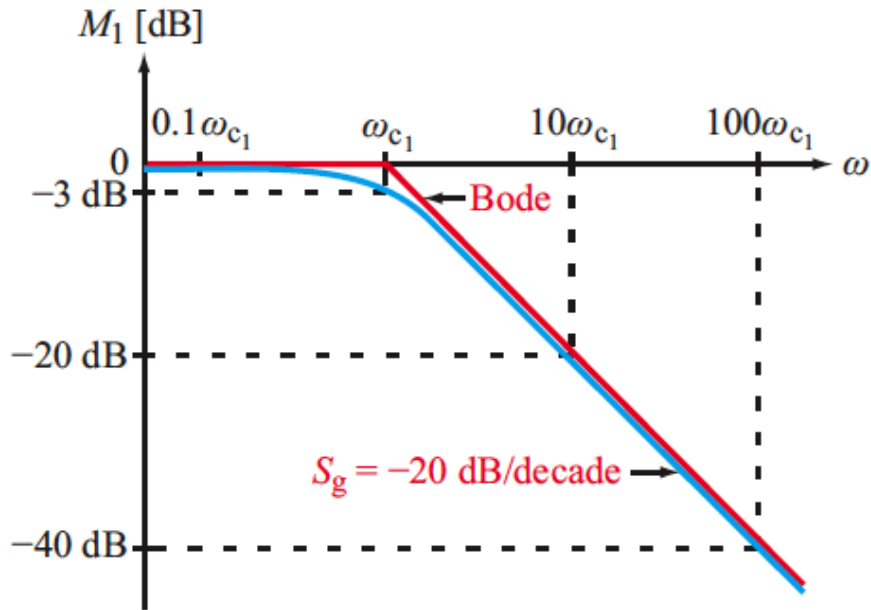

(b) Response of first-order filter

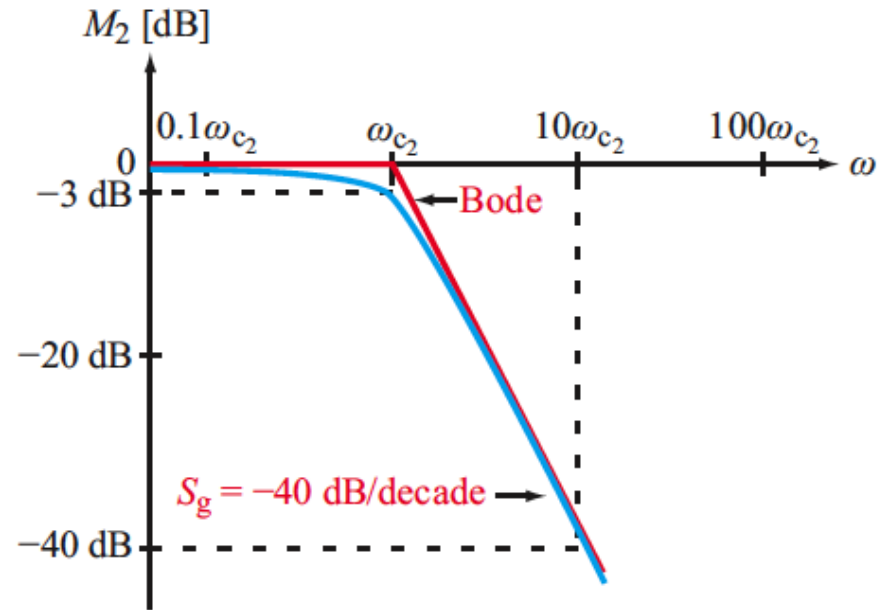

(d) Response of second-order filter