
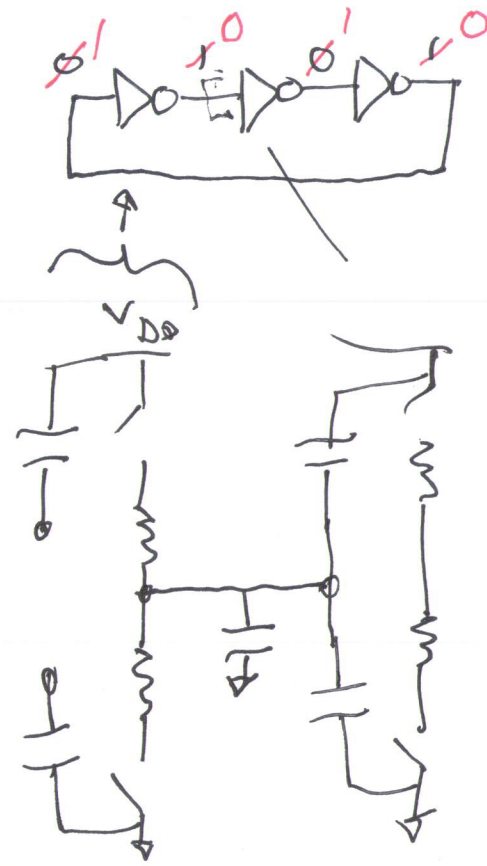
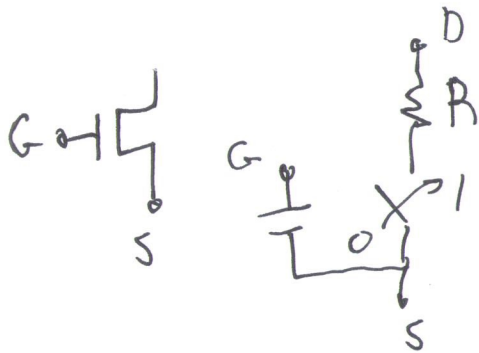
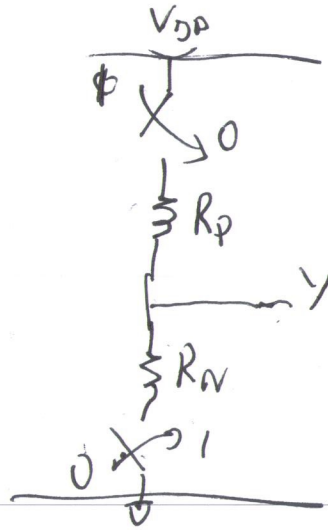
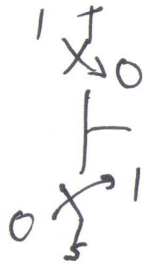



OH Tuesday 12:30 - 1:30 144MA Cory

HW parties

my office 2⁹ Cory

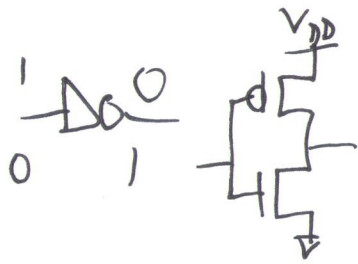


Ring Oscillator

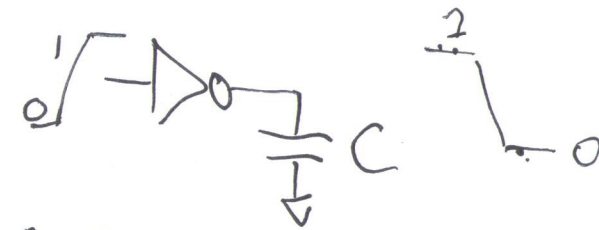

A=0





A=1

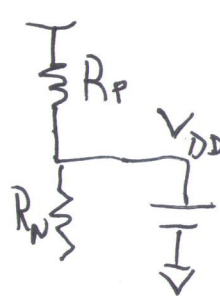


OH Tuesday 12:30 - 1:30 144MA Cory

HW parties

my office 2⁹ Cory

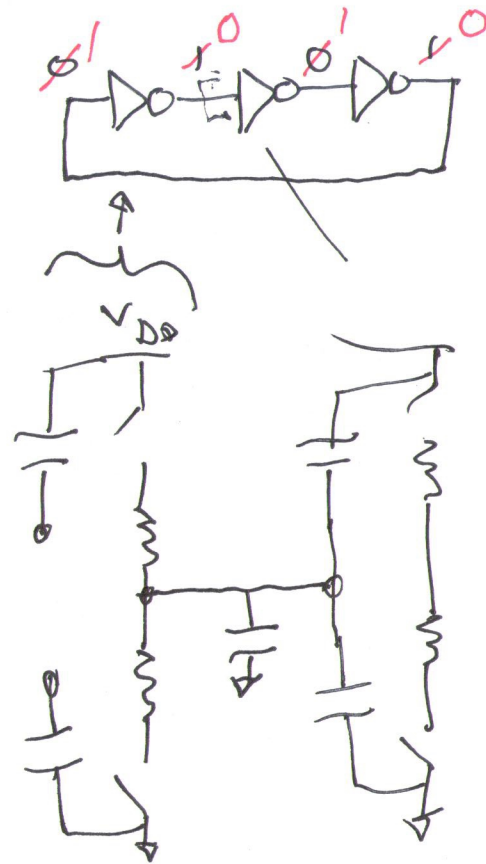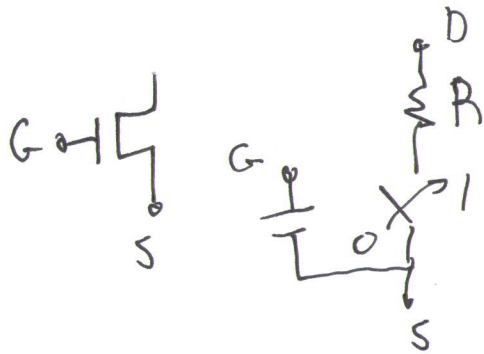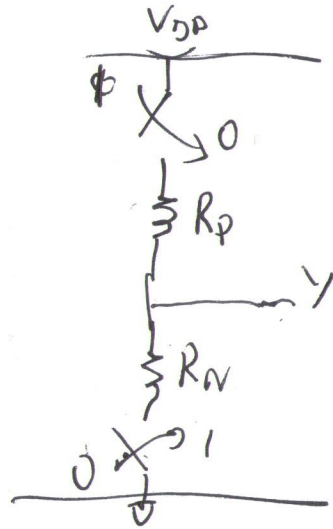
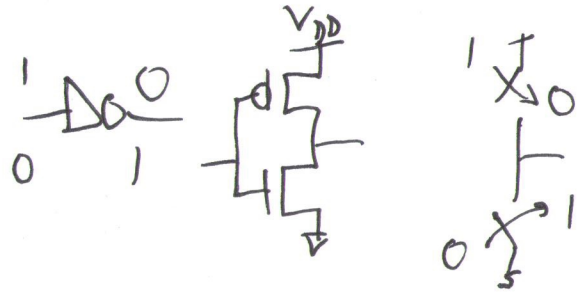



Ring Oscillator

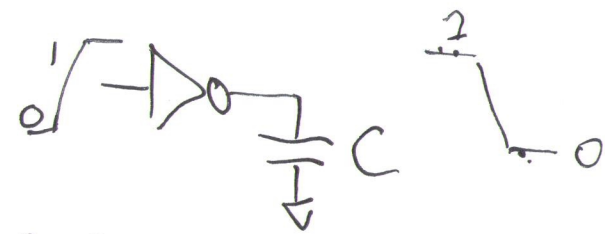


A=0

A=1

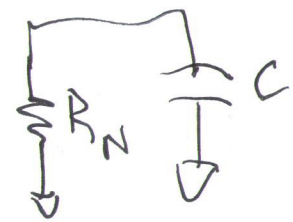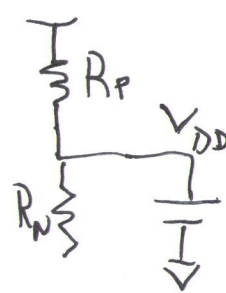

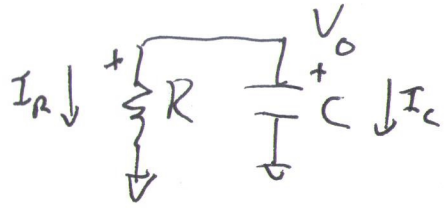

$$V_0(t=0) = V_{DD}$$

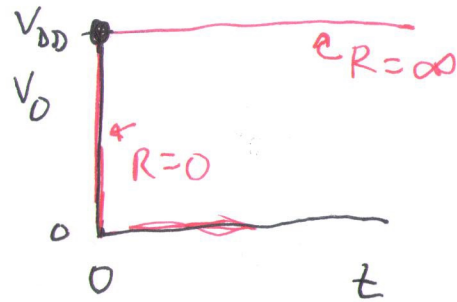

$$\frac{1}{T} \quad Q = CV$$

$$\frac{d}{dt} Q = I_C = \frac{d}{dt} (CV) = C \frac{dV}{dt}$$

$$U = \frac{1}{2} CV^2$$

$$I_C = C \frac{dV_0}{dt} = -I_R = -\frac{V_0}{R}$$

$$I_R = \frac{V_0}{R}$$


$$I_C = -I_R$$

$$\frac{dV_0}{dt} = -\frac{V_0}{RC}$$

1st order
Ordinary Diff. Egn.

$$\tau = RC \quad \text{time constant}$$

$$\frac{dV_0}{dt} = -\frac{V_0}{\tau}$$

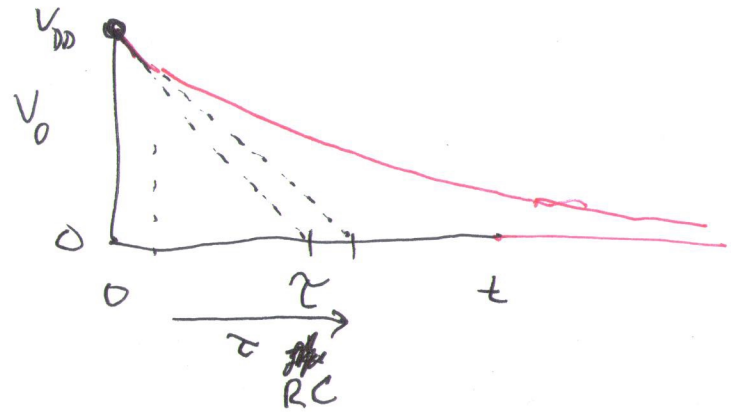

$$\frac{dV_0}{dt} = -\frac{V_0}{\tau}$$

$$\frac{d}{dt} [V_0] = \lambda [V_0]$$

differential
operator

eigen values
eigen functions


$$V_0 = K e^{-t/\tau}$$

$$V_0(t=0) = V_{DD} = K e^{-0/\tau} = K$$

$$V_0 = K e^{at}$$




$$V_0 = V_{DD} e^{at}$$

$$V_0(t) = K e^{-t/\tau}$$

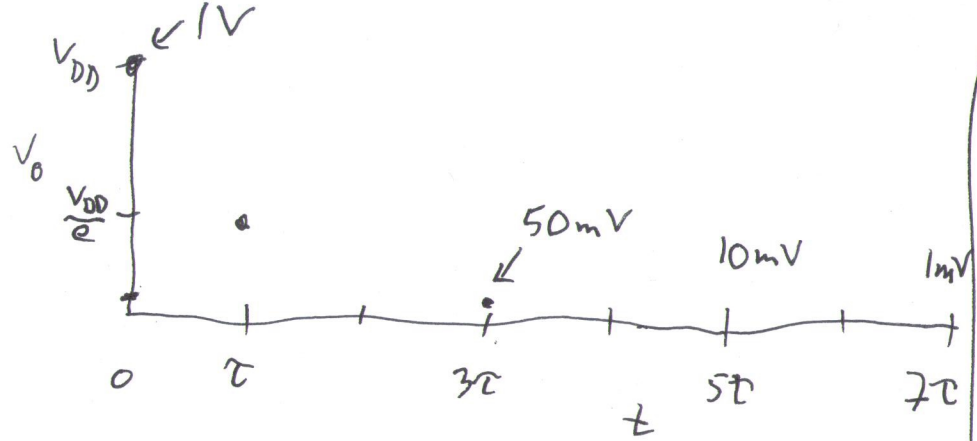

t	$e^{-t/\tau}$
τ	0.37
3τ	0.05
5τ	0.01
7τ	0.001

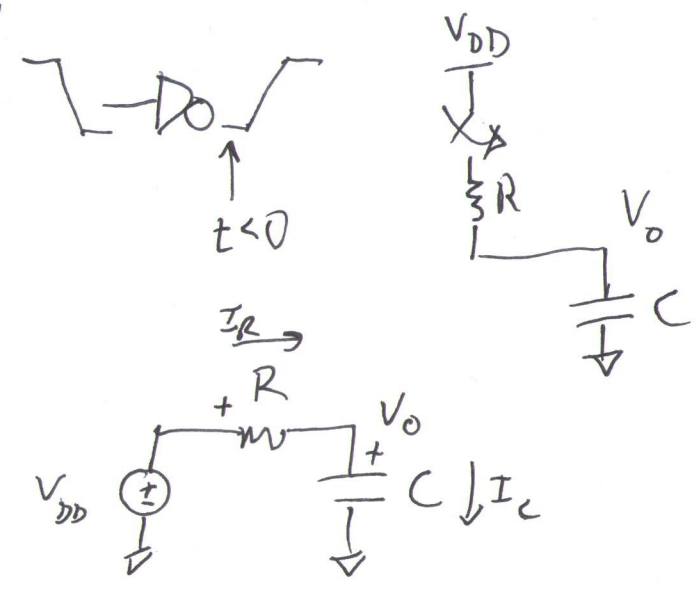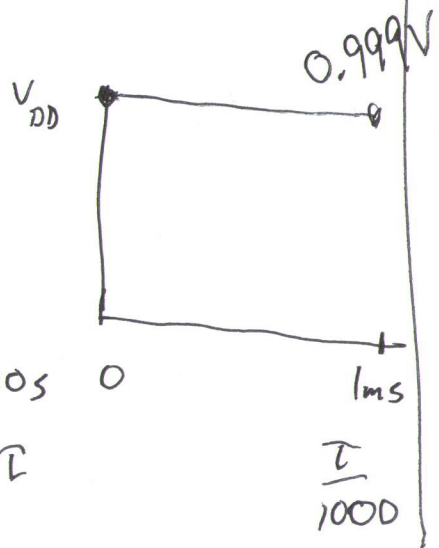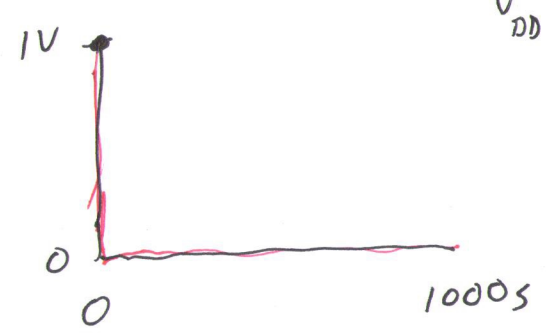EX: $R = 1\Omega$ $C = 1F$ $V_{DD} = 1V$
 $\tau = RC = 1s$




$$I_c = C \frac{dV_o}{dt}$$

$$I_R = \frac{V_{DD} - V_o}{R}$$

$$I_c = I_R$$

$$C \frac{dV_o}{dt} = \frac{V_{DD} - V_o}{R}$$
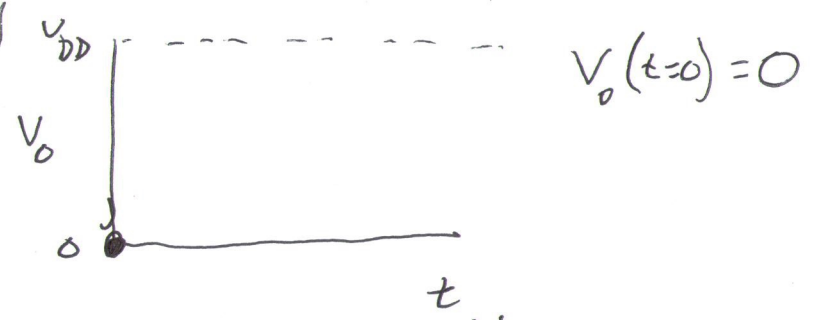
$$\frac{dV_o}{dt} = -\frac{V_o}{RC} + \frac{V_{DD}}{RC}$$





$$V_o(t) = V_{final} + V_{transient}$$


$$= V_{DD} + V_{transient}(t)$$

$$V_o(0) = 0 = V_{DD} + V_{transient}(0)$$

What about pull-up?

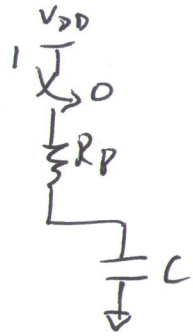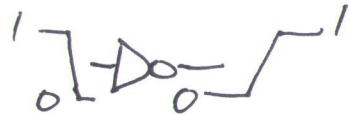

$$V_0(t=0) = 0$$

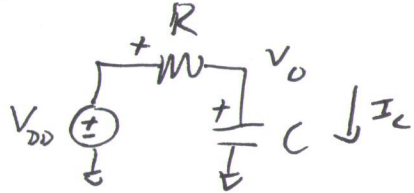

$$I_C = C \frac{dV_0}{dt}$$

$$I_R = \frac{V_{DD} - V_0}{R} = I_C = C \frac{dV_0}{dt}$$

$$\frac{dV_0}{dt} = -\frac{V_0}{RC} + \frac{V_{DD}}{RC} \quad \text{non-homogeneous ODE}$$

Assume $V_0 = V_{final} + V_{transient} = V_{DD} + V_{transient}$
 (where $V_{final} = V_{DD}$)

$$\frac{dV_0}{dt} = \frac{d}{dt} V_{transient}$$




$$\begin{aligned} \frac{d}{dt} V_{transient} &= -\frac{(V_{DD} + V_{transient})}{RC} + \frac{V_{DD}}{RC} \\ &= -\frac{V_{transient}}{RC} \end{aligned}$$


$$V_{transient}(t) = K e^{-t/RC}$$

$$V_{transient}(0) = -V_{DD} = K e^0$$

$$V_{transient} = -V_{DD} e^{-t/RC}$$
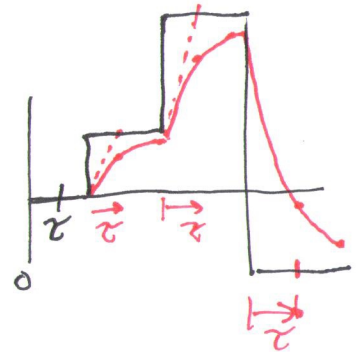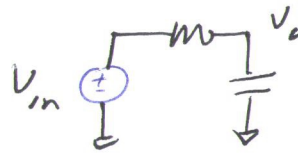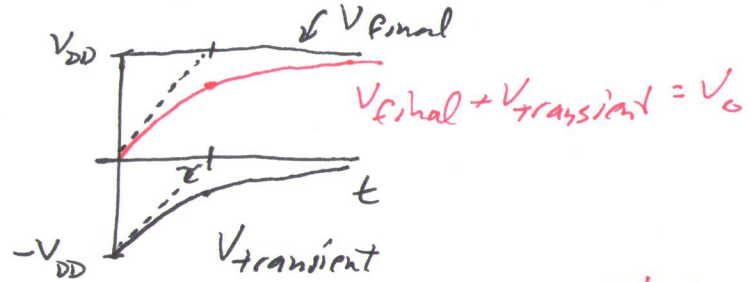
$$\begin{aligned} V_0 &= V_{DD} + V_{transient} = V_{DD} - V_{DD} e^{-t/RC} \\ &= V_{DD} (1 - e^{-t/RC}) \end{aligned}$$



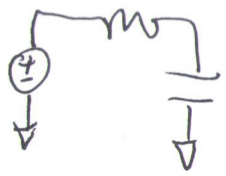


$$\frac{dV_o}{dt} = \frac{-V_o}{RC} + \frac{V_{DD}}{RC} \quad \text{circuit analysis}$$

$$V_o(t) = V_{DD} + V_{\text{transient}}(t)$$

$$V_{\text{transient}}(0) = -V_{DD}$$

$$\frac{dV_o}{dt} = \frac{dV_{DD}}{dt} + \frac{dV_{\text{transient}}}{dt}$$
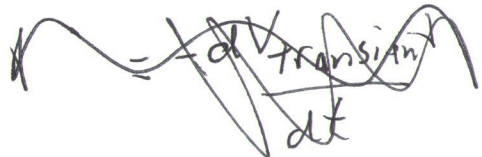
$$\frac{dV_{\text{transient}}}{dt} = -\frac{(V_{DD} + V_{\text{transient}})}{RC} + \frac{V_{DD}}{RC}$$




$$\frac{dV_{\text{transient}}}{dt} = -\frac{V_{\text{transient}}}{RC}$$




$$V_{\text{transient}} = K e^{-at}$$

$$a = \frac{1}{RC}$$

$$K = -V_{DD}$$

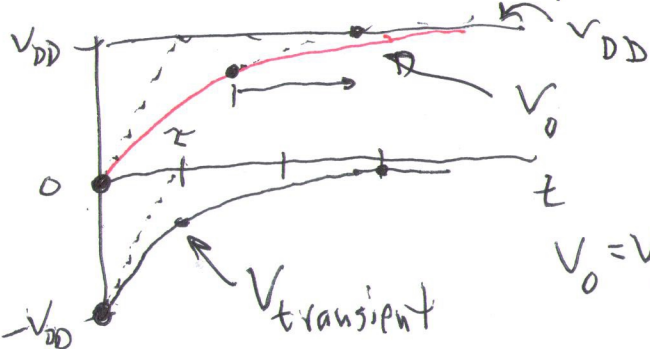


$$V_o = V_{DD} + V_{\text{transient}}$$

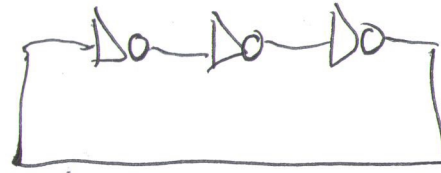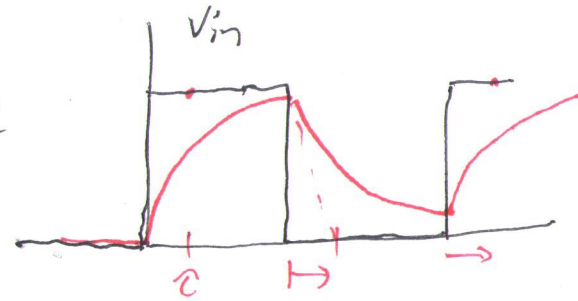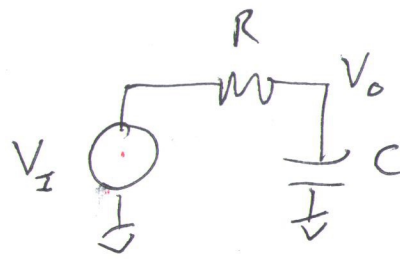


1970 $L = 20 \mu\text{m}$

2019 $L \approx 10 \text{nm}$

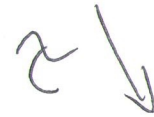


EX: 11 stage ring osc.
32 nm CMOS

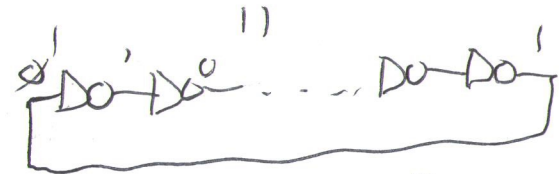

$$f_{\text{osc}} = 10 \text{ GHz} = 10^{10} \frac{\text{cycles}}{\text{sec}}$$


Capacitance/inverter $\approx 1 \text{ fF}$
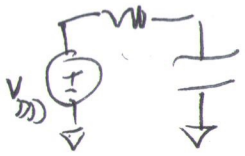
$$\text{total cap} = C_p = 10 \text{ fF}$$



$$U_c = \frac{1}{2} C V_{DD}^2$$

$$Q_c = C V_{DD}$$

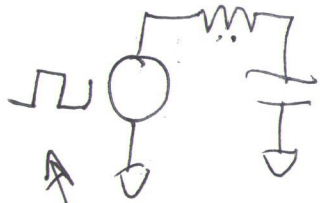


$$\Delta E_{\text{supply}} = -Q_c V_{DD}$$

$$= -C V_{DD}^2$$

f cycles
sec

$$P_{\text{dissipated}} = C V_{DD}^2 f$$

$$L = 32 \text{ nm}$$

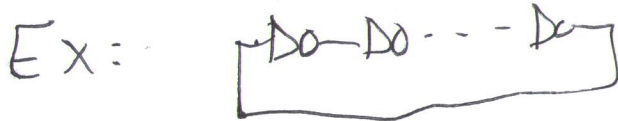

$t = 1$

$$P = C V_{DD}^2 f$$

$$= (10^{-14} \text{ F}) (1 \text{ V})^2 10^{10} \frac{1}{\text{s}}$$

$$= 10^{-4} \text{ W} = 100 \mu\text{W}$$

$$f = 10^{10} \frac{\text{cyc}}{\text{s}}$$


$$C \approx 10 \text{ fF}$$


$$V \approx 1 \text{ V}$$

$$\text{Area} = 2 \mu\text{m}^2$$

$$= 2 \times 10^{-6} \text{ mm}^2$$

Switching power

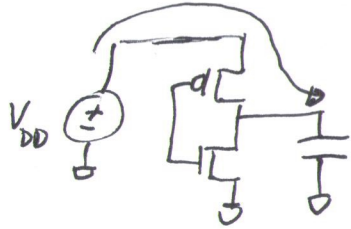
 $U_c = \frac{1}{2} C V_{DD}^2, \text{ or } 0$
 $Q_c = C V_{DD}, \text{ or } 0$



$$\begin{aligned} \Delta E_{\text{supply}} &= \Delta(QV)_{\text{supply}} \\ &= \Delta Q V_{DD} \\ &= -Q_c V_{DD} \\ &= -C V_{DD} V_{DD} \\ &= -C V_{DD}^2 \end{aligned}$$

Supply loses $C V_{DD}^2$ energy each time cap is charged.

Cap gains $\frac{1}{2} C V_{DD}^2$ " " " "

Resistor dissipates $\frac{1}{2} C V_{DD}^2$ " " " "

consumed


when switch f times per second, power is

$$P = C V_{DD}^2 f$$

CMOS

EX: 32nm 11 stage ring osc.

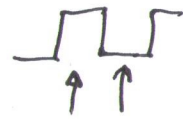$V_{DD} = 1V$
 $C = 11 (C_{inv})_{\text{total}}$
 $= 10 fF$



everyone flips once
everyone flips again

$$\begin{aligned} P &= C_{\text{total}} V_{DD}^2 f \\ &= (10^{-14} F) (1V)^2 10^{10} \\ &= 10^{-4} W \end{aligned}$$


$f = 10 \text{ GHz}$ (measured)
 ← measured
 ← measured

area $\approx 2 \mu m^2 = 2 \times 10^{-6} mm^2$

$$\begin{aligned} \frac{P}{A} &= \frac{10^{-4} W}{2 \times 10^{-6} mm^2} = \frac{1}{2} 10^2 \frac{W}{mm^2} \\ &= 50 \frac{W}{mm^2} \end{aligned}$$

> 2 x heat flux at surface of sun

Moore's law, transistor scaling

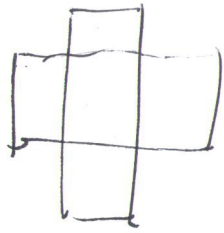

features shrink

$20\mu\text{m} \rightarrow 20\text{nm}$

capacitance decreases \sim

resistance decreases

time constant (RC) decreases

speed goes up

power per site goes down

power per area goes up

around $100\frac{\text{W}}{\text{cm}^2}$, cooling is primary problem


can make 10 GHz processors. Can't cool them!

cell phone: 6W peak (3 GHz?)

for $\approx 10\text{ms}$

average $\approx 0.8\text{W}$

Power in resistor

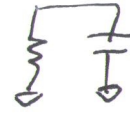

$$V_o = V_{DD} e^{-t/RC}$$

$$I_c = C \frac{dV_o}{dt} = -\frac{CV_{DD}}{RC} e^{-t/RC}$$

$$= -\frac{1}{R} V_{DD} e^{-t/RC}$$

$$I_R = \frac{V_o}{R} = \frac{V_{DD}}{R} e^{-t/RC}$$

$$= -I_c \quad \text{check } \checkmark$$

$$P_R = IV = \left(\frac{V_{DD}}{R} e^{-t/RC} \right) \left(V_{DD} e^{-t/RC} \right)$$

$$= \frac{V_{DD}^2}{R} e^{-2t/RC}$$

$$E_R = \int_0^{\infty} P_R dt = \int_0^{\infty} \frac{V_{DD}^2}{R} e^{-2t/RC} dt$$

$$= \frac{1}{\left(-\frac{2}{RC}\right)} \frac{V_{DD}^2}{R} e^{-2t/RC} \Big|_0^{\infty}$$

$$= -\frac{1}{2} CV_{DD}^2 e^{-2t/RC} \Big|_0^{\infty}$$

$$= -\left(\frac{1}{2} CV_{DD}^2\right) \left[e^{-\infty} - e^0 \right]$$

$$= \frac{1}{2} CV_{DD}^2$$

all cap energy dissipated in resistor \checkmark