

types of circuit analysis



DC analysis

transient analysis

steady state - response to sinusoidal inputs
- frequency response

inductor

frequency response

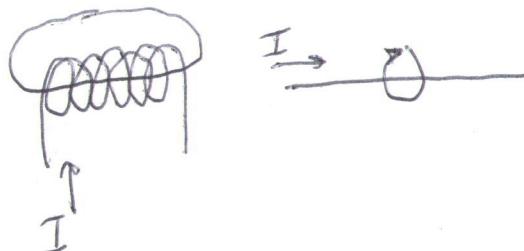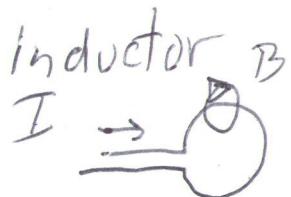

$$\phi = LI$$

$$V = \frac{d\phi}{dt} = \frac{d}{dt}(LI)$$

$$V = L \frac{dI}{dt}$$

Loop radius R
wire diameter d

$$L \approx \mu_0 R \ln\left(\frac{R}{d}\right)$$

$$4\pi \times 10^{-7} \text{ H/m}$$

$$\frac{1}{T}$$

$$Q = CV$$



$$I = C \frac{dV}{dt}$$

$$U = \frac{1}{2} LI^2$$

$$\phi = LI$$


$$V = L \frac{dI}{dt}$$

$$U = \frac{1}{2} LI^2$$

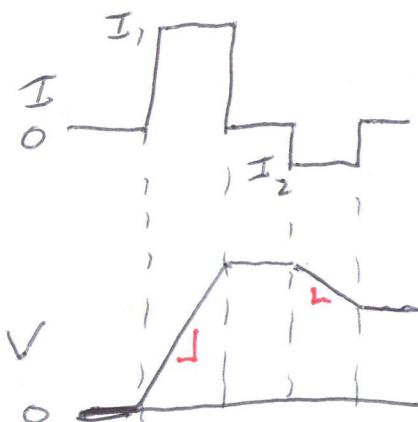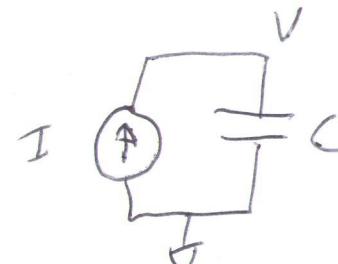

$$\frac{I_1}{C}$$

$$\frac{I_2}{C}$$

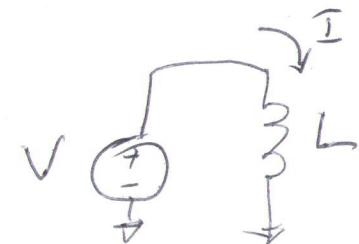


$$\frac{V_1}{L}$$

$$\frac{V_2}{L}$$

Boost

1.6V
0.8V

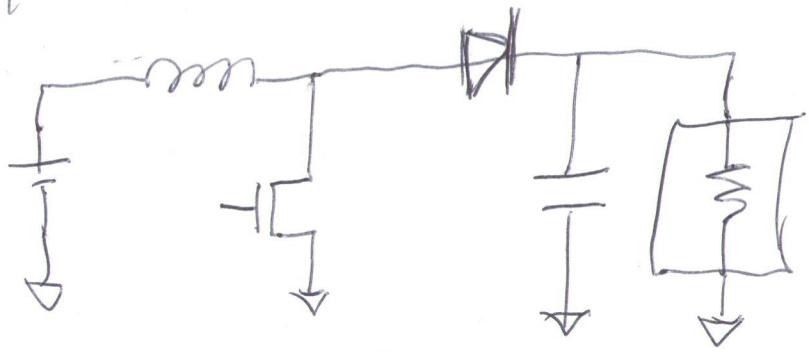

wants 5V

Ex: 2 chips : wire 1mm long


$$C = 1\text{ pF}$$

$$L = 1\text{ nH}$$

Chip 1

$$f = 60\text{ Hz}$$

$$\omega = (2\pi)(60\text{ Hz}) = 400 \frac{\text{rad}}{\text{s}}$$

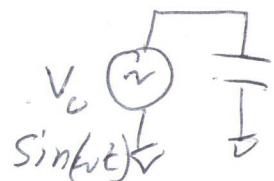

chip 2

$$3\text{ GHz}$$

$$\omega = (2\pi)(3 \times 10^9 \text{ Hz})$$

$$= 2 \times 10^{10} \frac{\text{rad}}{\text{s}}$$

$$I = C \frac{dV}{dt} = C \frac{d}{dt} (V_0 \sin \omega t)$$

$$= \omega C V_0 \cos(\omega t)$$

Resistor: $V = IR$

$$R = \frac{V}{I}$$

capacitor } $\tilde{V} = \tilde{I} Z$
inductors }

$$|Z| = \frac{|V|}{|I|}$$

$$|Z_c| = \frac{|V|}{|I|} = \frac{|V_0 \sin(\omega t)|}{|\omega C V_0 \cos(\omega t)|} = \frac{V_0}{\omega C V_0}$$

$$|Z_c| = \frac{1}{\omega C}$$

$$f = 60\text{ Hz}$$

$$\omega = 400 \frac{\text{rad}}{\text{sec}}$$

$$|Z_c| = \frac{1}{(400)(10^{-12}\text{ F})}$$

$$= 2.5 \times 10^9 \Omega$$

$$= 2.5 \text{ G}\Omega$$


$$f = 3\text{ GHz}$$

$$\omega = 2 \times 10^{10} \frac{\text{rad}}{\text{s}}$$

$$|Z_c| = \frac{1}{\omega C}$$

$$= \frac{1}{(2 \times 10^{10} \frac{\text{rad}}{\text{s}})(10^{-12}\text{ F})}$$

$$= 50 \Omega$$

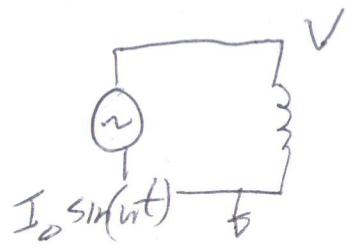

$$V = L \frac{dI}{dt}$$

$$= L \frac{d}{dt} (I_0 \sin \omega t)$$

$$= \omega L I_0 \cos(\omega t)$$

$$|Z_L| = \frac{|V|}{|I|} = \frac{|\omega L I_0 \cos(\omega t)|}{|I_0 \sin(\omega t)|} = \frac{\omega L I_0}{I_0}$$

$$|Z_L| = \omega L$$

60 Hz

$$\omega = 400$$

$$|Z_L| = \omega L$$

$$= \left(400 \frac{\pi \times 10^3}{5}\right) (10^{-9} \text{ H})$$

$$= 0.4 \mu \Omega$$

3 GHz

$$\omega = 2 \times 10^{10}$$


$$|Z_L| = \omega L$$

$$= (2 \times 10^{10})(10^{-9})$$

$$= 20 \Omega$$


$$|Z_C| = \frac{1}{\omega C}$$

$$|Z_L| = \omega L$$

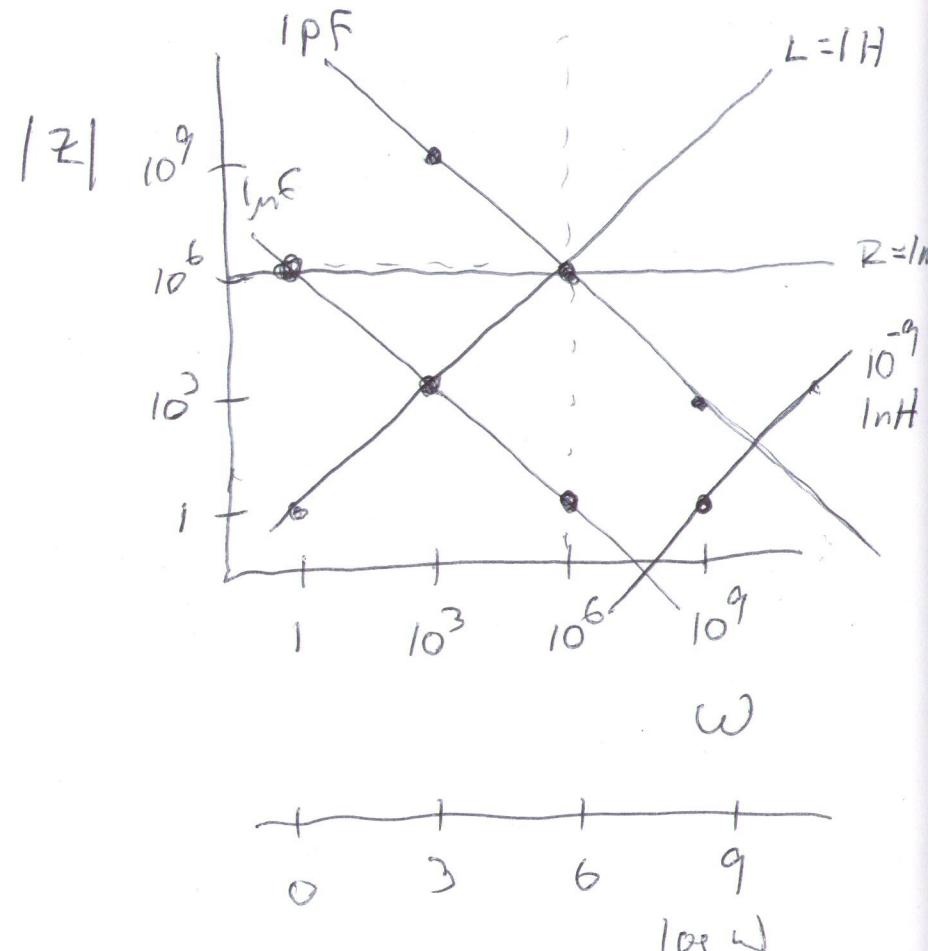

$$|Z_C| = \frac{1}{\omega C} \quad |Z_L| = \omega L$$


$\log \omega$

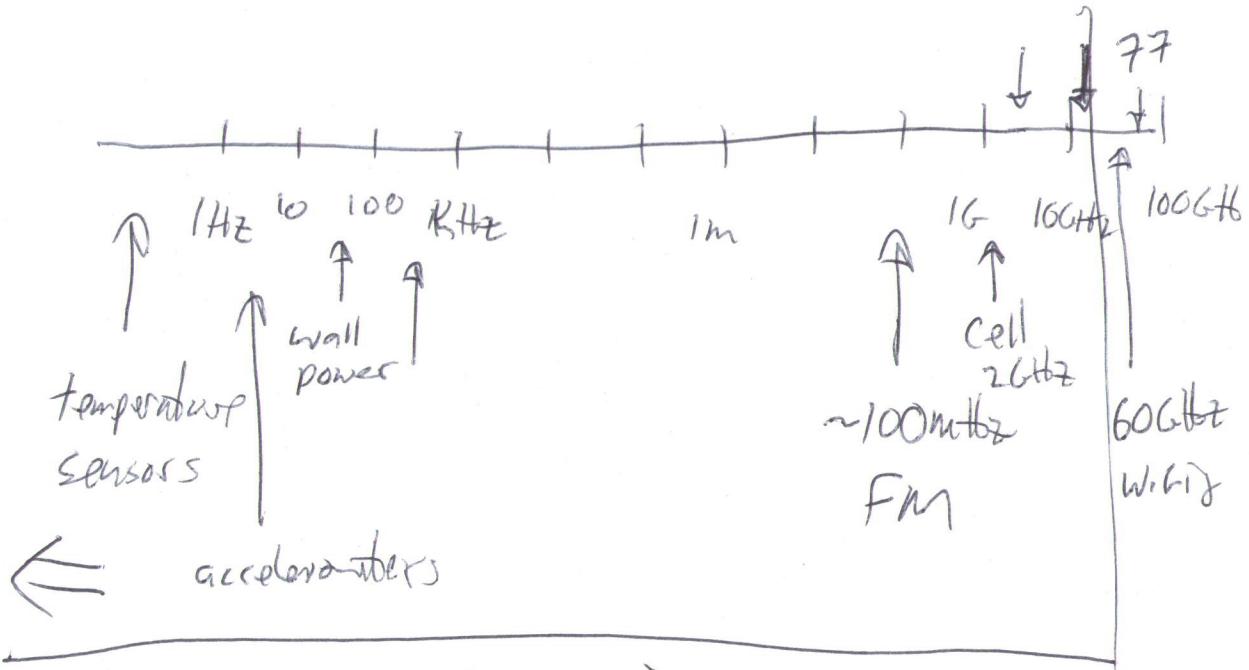

Series & parallel resistors




$$R_1 \quad R_2$$

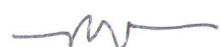


$$R_{eq}$$

$$\max(R_1, R_2)$$

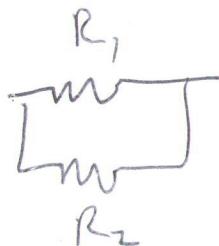


$$R_{eq}$$

$$\min(R_1, R_2)$$

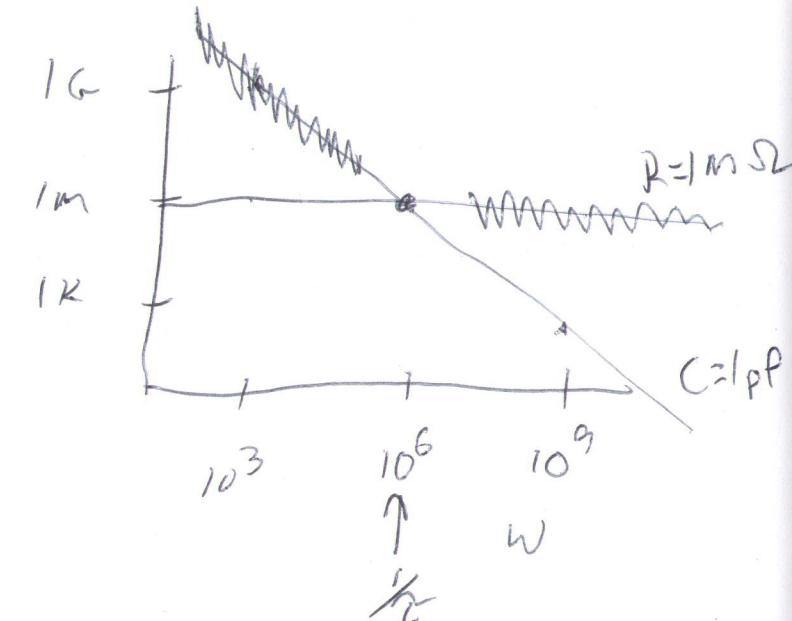

W.L.F.

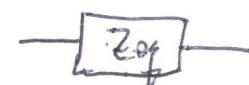


$$|Z_{eq}| = \max(R, |Z_c|)$$

$$\frac{1}{\omega C}$$

$$|Z_c| = R$$

$$\frac{1}{\omega C} = R$$


$$\omega = \frac{1}{RC} = \frac{1}{L}$$

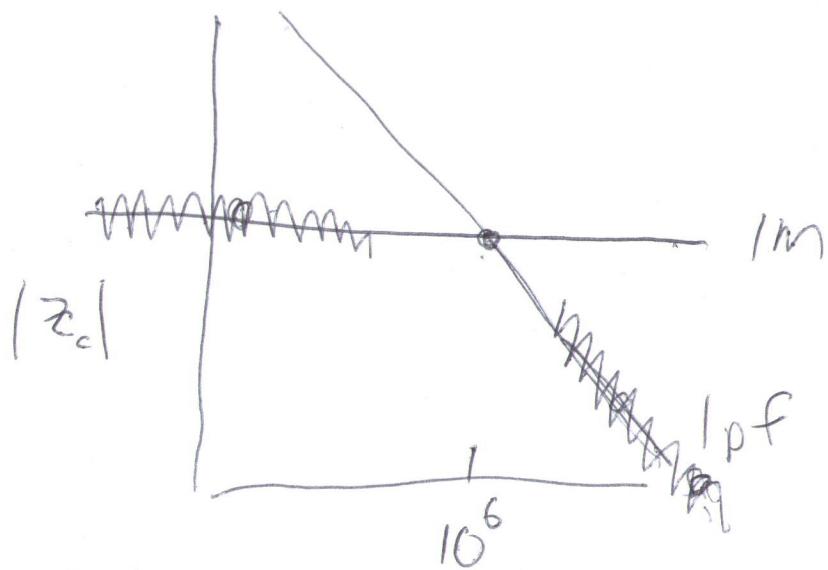

TWT

$$-\boxed{|Z_g|} \quad \min(R, |Z_d|)$$

Filters

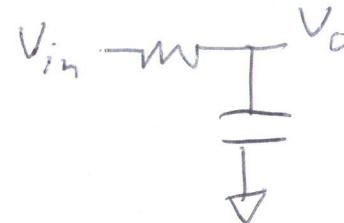


$$V_o = () V_{in}$$

$$\frac{V_o}{V_{in}} = ()$$

$$R = 1M$$

$$C = 1\text{ pF}$$

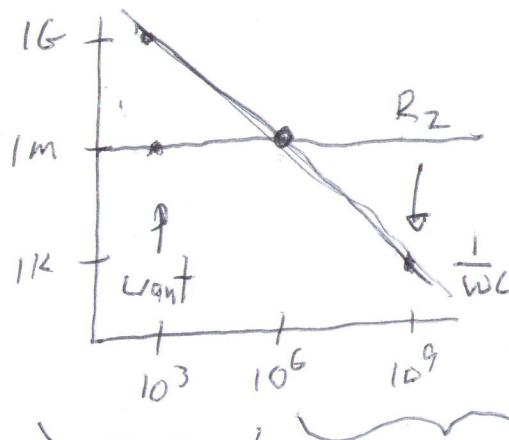


$$\text{gain} = \frac{V_o}{V_i} \approx 1$$

$$\frac{R_1}{R_2}$$

low pass
single pole

Voltage dividers

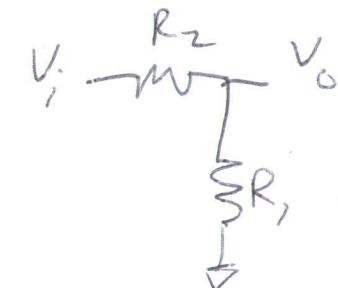

$$V_o = \left(\frac{R_2}{R_1 + R_2} \right) V_{in}$$

$$\frac{V_o}{V_{in}} = \frac{R_2}{R_1 + R_2}$$


$$\approx \begin{cases} 1 & R_1 \gg R_2 \\ \frac{R_1}{R_1 + R_2} & R_1 \ll R_2 \end{cases}$$

time domain



$$V(t) = V_0 e^{-t/\tau}$$

$$\tau = RC$$

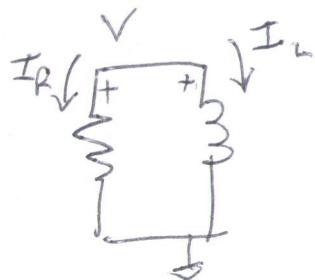

$$I(t) = I_0 e^{-t/\tau}$$

$$\tau = L/R$$

$$V = L \frac{dI_L}{dt}$$

$$V = I_L R = -I_L R$$

$$L \frac{dI_L}{dt} = -I_L R$$

$$\frac{dI_L}{dt} = -I_L \frac{R}{L}$$

$$= -\frac{1}{\tau} I_L \quad \tau = L/R$$

$$I_L(t) = I_0 e^{-t/\tau}$$