

Review




R

$$\frac{\tilde{V}}{\tilde{I}} = R$$

$$Z_C = \frac{\tilde{V}}{\tilde{I}} = \frac{1}{j\omega C}$$

$$Z_L = j\omega L$$

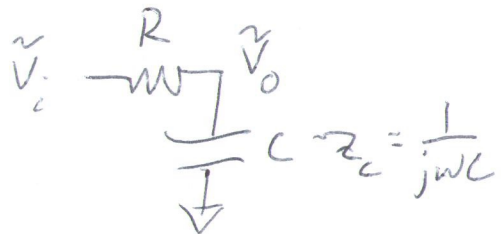

$$H(\omega) = \frac{Z_C}{Z_C + R}$$

$$= \frac{1}{j\omega C} \frac{1}{\frac{1}{j\omega C} + R}$$



$$= \frac{1}{1 + j\omega RC}$$

$$= \frac{1}{1 + j\omega \tau}$$

$$\tau = RC$$

$$\omega_p = \frac{1}{\tau}$$
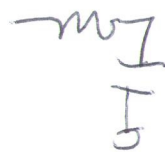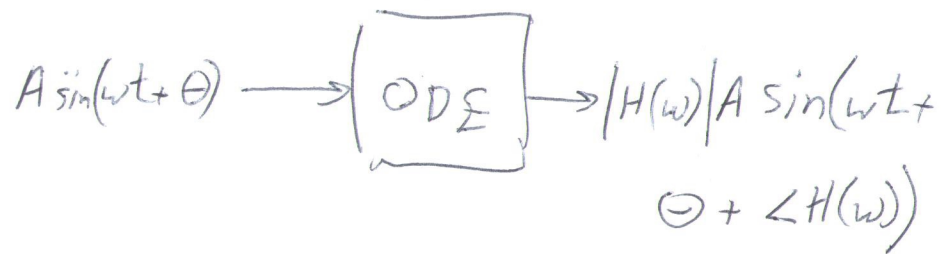
$$H(\omega) = \frac{1}{1 + j\omega/\omega_p}$$





$$H(\omega) = \frac{1}{1 + j\omega/\omega_p}$$


$$\omega_p = \frac{1}{\tau}$$

$$\tau = RC$$


low-pass filter

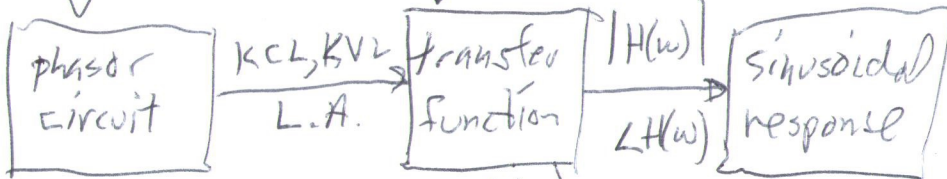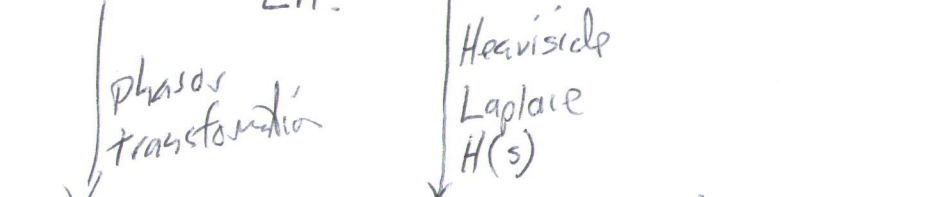

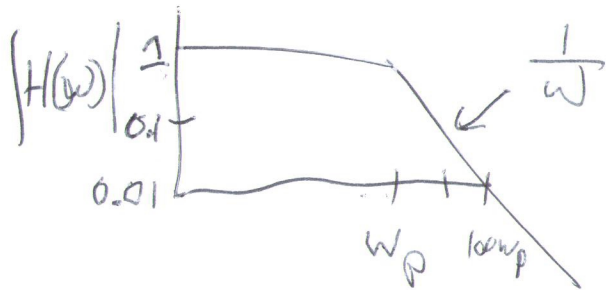
KCL, KVL voltage dividers still work w/ phasors



low-pass
f_c Hz

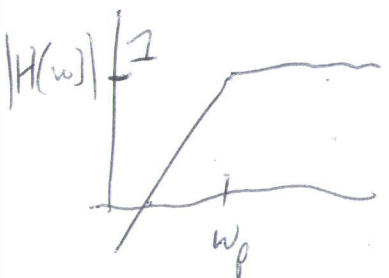


High Pass


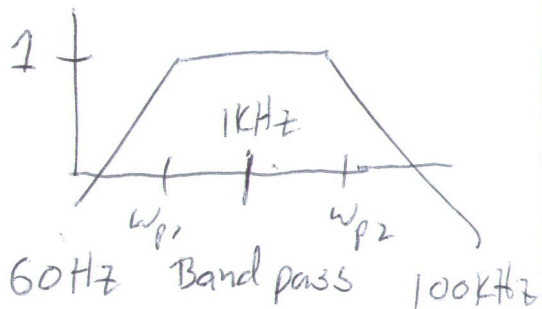


60 Hz Band pass 100 kHz


EX: sensor

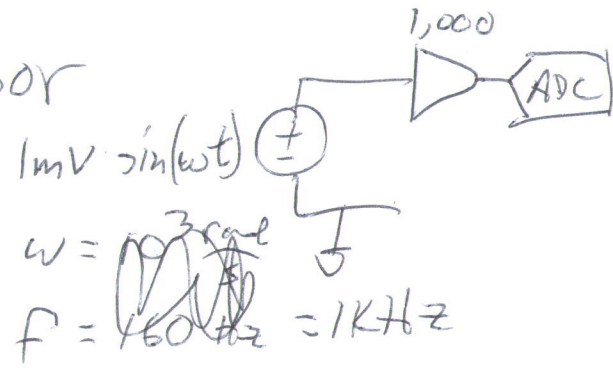

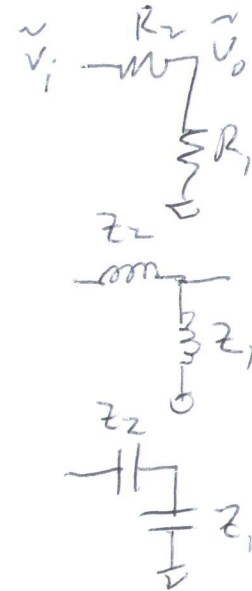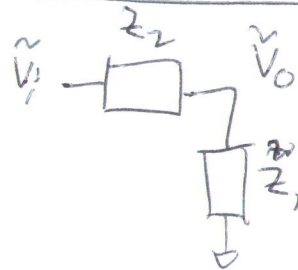
60 Hz noise $(20\text{mV})\sin(2\pi 60t)$
~~100 kHz~~ noise $(50\text{mV})\sin(\text{~~10^5~~ } t)$
~~100 kHz~~
~~100 kHz~~
 Sec



$$H(\omega) = \frac{R_1}{R_1 + R_2}$$

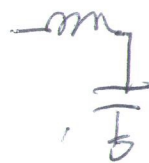


Thursday

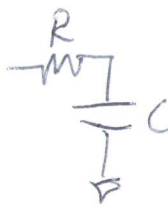

$\tau = RC$
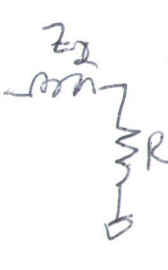
$$H(\omega) = \frac{1}{1 + j\omega/\omega_p} = \frac{1}{1 + j\omega\tau}$$




$\tau = \frac{L}{R}$

$$H(\omega) = \frac{R}{R + j\omega L} = \frac{1}{1 + j\omega \frac{L}{R}}$$

$\omega_p = \frac{1}{\tau}$

$$= \frac{1}{1 + j\omega\tau} = \frac{1}{1 + j\omega/\omega_p}$$




$\tau = RC$

$$H(\omega) = \frac{R}{R + \frac{1}{j\omega C}} = \frac{j\omega RC}{1 + j\omega RC} = \frac{j\omega\tau}{1 + j\omega\tau}$$

$\omega_p = \frac{1}{\tau}$
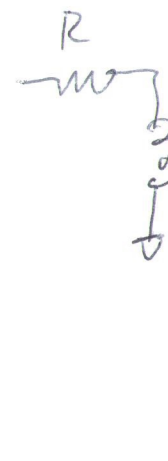
$$H(\omega) = \frac{j\omega/\omega_p}{1 + j\omega/\omega_p}$$



$\tau = \frac{L}{R}$

$$H(\omega) = \frac{j\omega L}{j\omega L + R} = \frac{j\omega L/R}{1 + j\omega L/R} = \frac{j\omega\tau}{1 + j\omega\tau}$$



$\omega_p = \frac{1}{\tau}$

$$H(\omega) = \frac{j\omega/\omega_p}{1 + j\omega/\omega_p}$$

$$H(\omega) = \frac{1}{1 + j\omega/\omega_p} = \frac{r_p e^{j\theta_p}}{r_p e^{j\theta_p}} = \frac{1 e^{j0}}{r_p e^{j\theta_p}}$$

$$= |H(\omega)| e^{j\angle H(\omega)} = \frac{1}{r_p} e^{j(0 - \theta_p)}$$
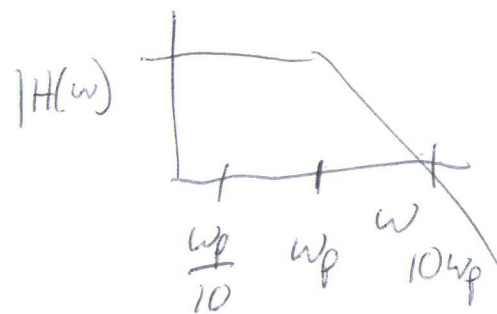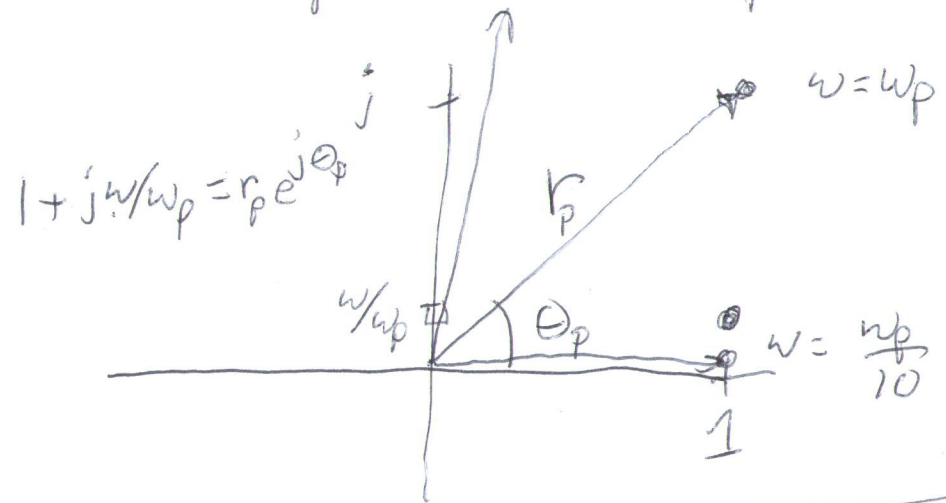
$$H(\omega) = \frac{1}{r_p} \quad \angle H(\omega) = -\theta_p \quad \omega = 10\omega_p$$




$$\omega = \omega_p$$

$$r_p = \sqrt{2}$$

$$\theta_p = \frac{\pi}{4}, 45^\circ$$

$$\omega = \frac{\omega_p}{10}$$

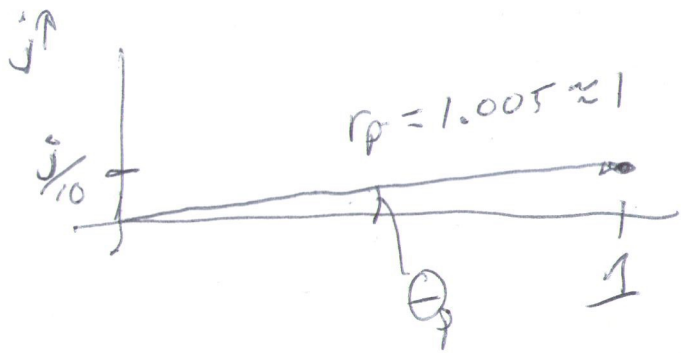

$$1 + \frac{j\omega}{\omega_p}$$

$$1 + \frac{j}{10}$$


$$\theta_p \approx \frac{\omega/\omega_p}{1} = 0.1 \text{ rad}$$

$$6^\circ$$

$$\omega = 10\omega_p$$

$$1 + \frac{j\omega}{\omega_p}$$

$$1 + 10j$$

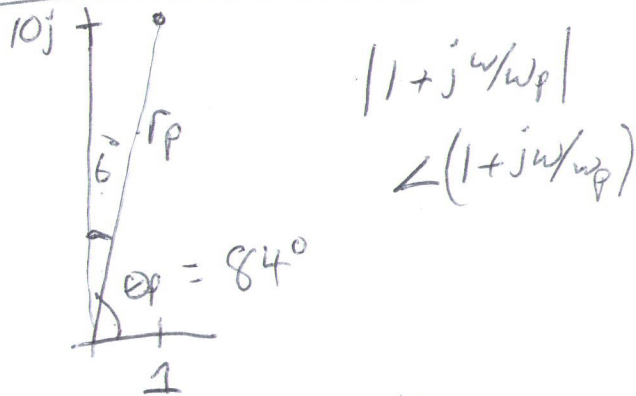

$$\frac{1}{r_p}$$

$$\angle(1 + j\omega/\omega_p)$$

~~$\omega = \omega_p$~~ $\omega = \frac{\omega_p}{10}$

$$\omega = \omega_p$$

$$\omega = 10\omega_p$$

$$\omega = \frac{\omega_p}{10}$$

$$\omega = \omega_p$$

$$\omega = 10\omega_p$$

$$|H(\omega)| \approx \begin{cases} 1 \\ \frac{1}{\sqrt{2}} \\ 0.1 \end{cases}$$


$$\frac{1}{r_p}$$

$$\angle H(\omega) = \begin{cases} -6^\circ \\ -45^\circ \\ -84^\circ \end{cases}$$

$$-\theta_p$$

$$H(\omega) = \frac{1}{1 + j\omega/\omega_p}$$






$$|H(\omega)|$$

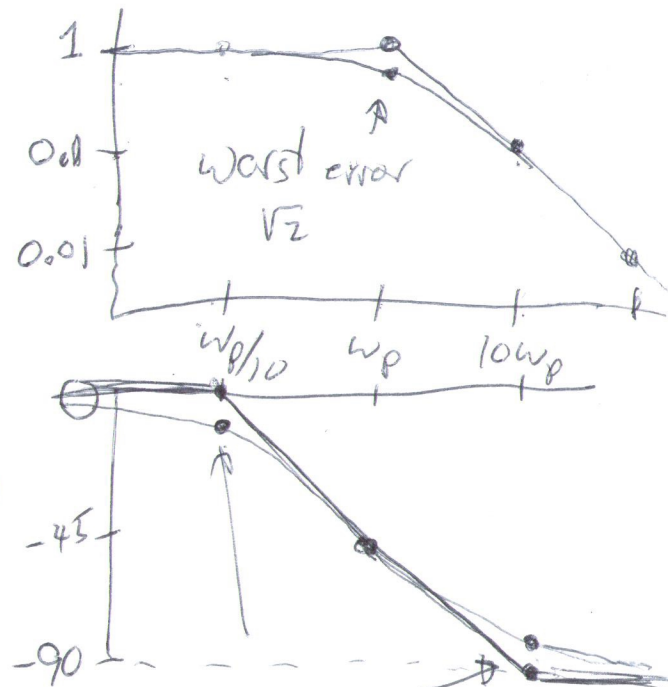

$$\text{worst error}$$

$$\pm 6^\circ$$

Waveforms (transient)

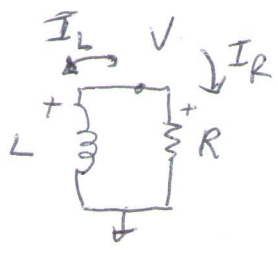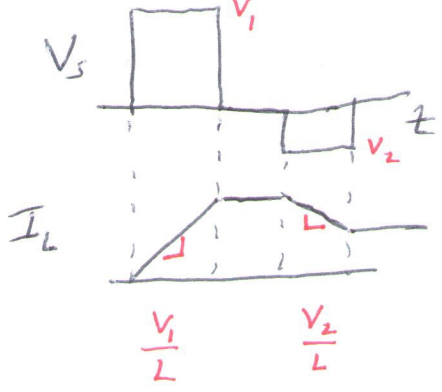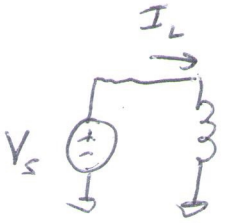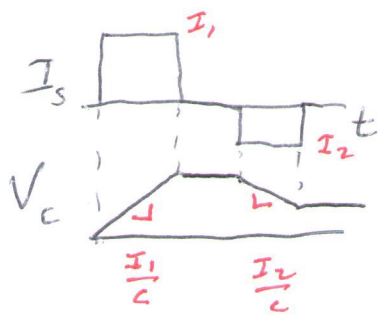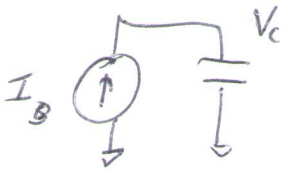

$$V = L \frac{dI_L}{dt}$$

$$V = I_R R = -I_L R$$

$$L \frac{dI_L}{dt} = -I_L R$$

$$\frac{d}{dt} I_L = -\frac{R}{L} I_L$$


$$\tau = \frac{L}{R} \quad \frac{d}{dt} I_L = -\frac{I_L}{\tau}$$

$$I(t) = I_0 e^{-t/\tau} \quad \tau = \frac{L}{R}$$

Recall


$$V(t) = V_0 e^{-t/\tau} \quad \tau = RC$$

Boost Converter

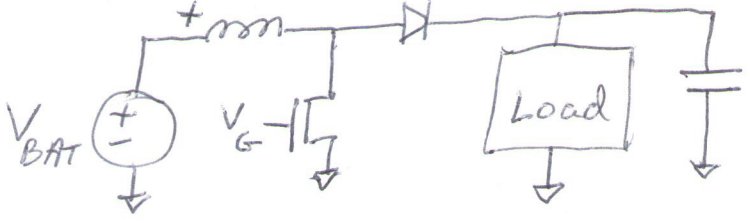

0.8-1.6V

wants 5V (say)

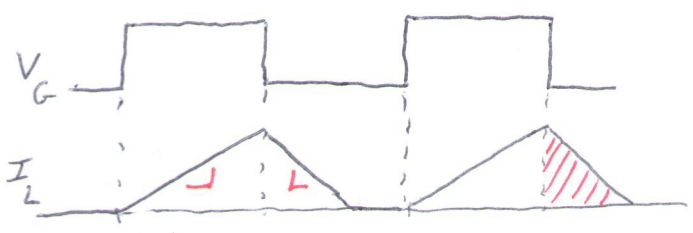

$$\frac{V_{BAT}}{L}$$

$$\frac{V_{BAT} - V_{LOAD}}{L}$$

Energy delivered to load

DC analysis - sources are constant
I, V constant

$$I = C \frac{dV}{dt} = 0 \quad I = 0 \Rightarrow \text{open}$$

$$V = L \frac{dI}{dt} = 0 \quad V = 0 \Rightarrow \text{short}$$

transient - anything goes, find $V(t)$
 $I(t)$

steady state - sinusoidal inputs

find sinusoidal response after any non-sinusoidal transients