
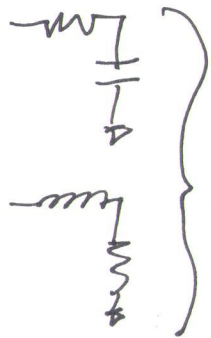


Bode Plots

Filters

LC


16B 185P W3L2 3B

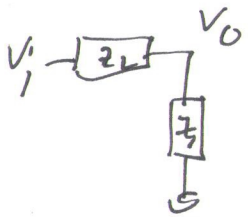

$$H(\omega) = \frac{1}{(1 + j\omega/\omega_p)}$$


$$H(\omega) \approx \begin{cases} 1 & \omega \ll \omega_p \\ \frac{1}{1+j} & \omega = \omega_p \\ \frac{\omega_p}{j\omega} & \omega \gg \omega_p \end{cases}$$

$|H(\omega)|$

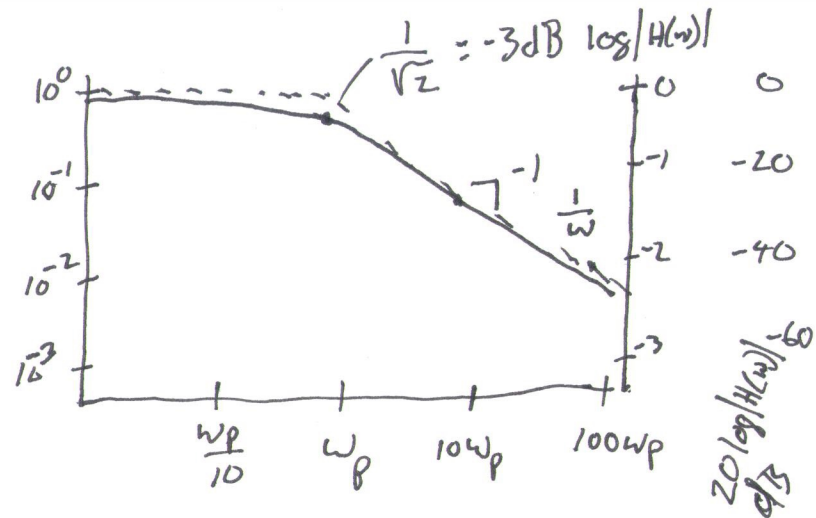


$\angle H(\omega)$



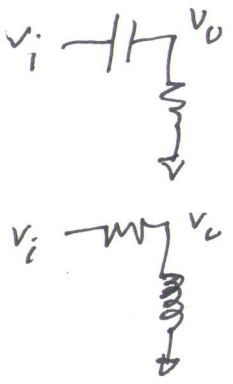


$$H(\omega) = \frac{j\omega/\omega_p}{1 + j\omega/\omega_p}$$
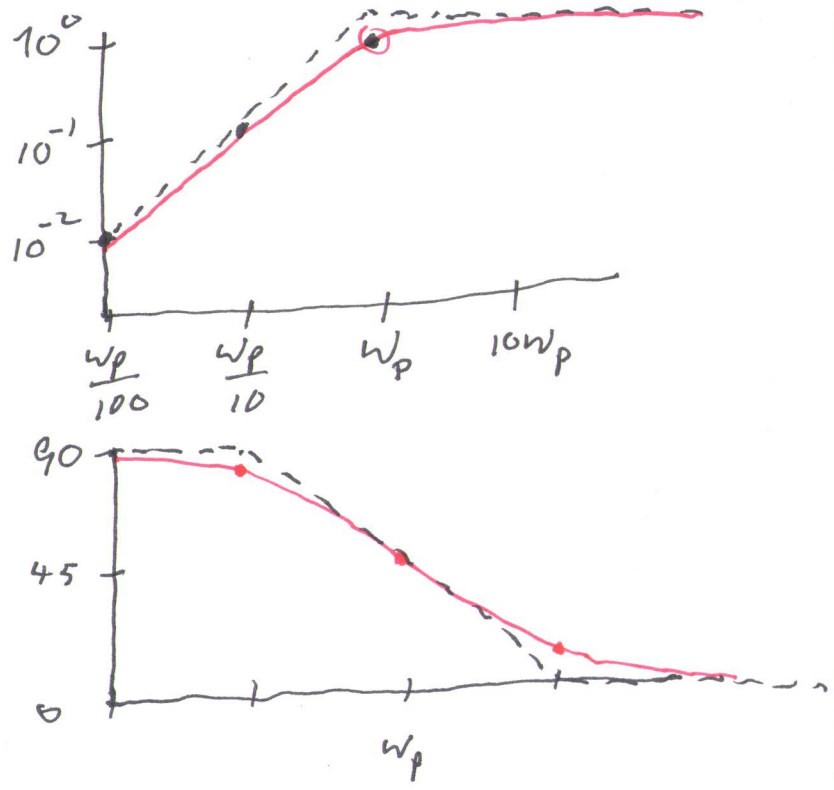
$$H(\omega) = \begin{cases} \frac{j\omega}{\omega_p} & \omega \ll \omega_p \\ \frac{j}{1+j} & \omega = \omega_p \\ 1 & \omega \gg \omega_p \end{cases}$$



Composing Filters

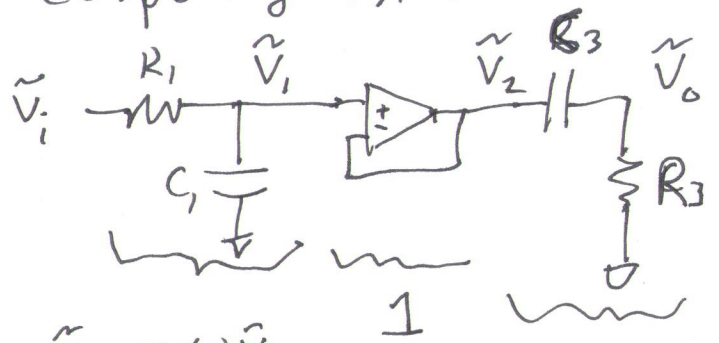

$$\tilde{V}_1 = H_1(\omega) \tilde{V}_i$$

$$\tilde{V}_2 = 1 \tilde{V}_1$$

$$\tilde{V}_o = H_2(\omega) \tilde{V}_2$$

$$= H_2 \tilde{V}_1$$

$$= H_2 H_1 \tilde{V}_i$$

$$= H \tilde{V}_i$$

$$H(\omega) = \frac{\tilde{V}_o}{\tilde{V}_i} = H_1 H_2$$

$$|H(\omega)| = |H_1 H_2| = |H_1(\omega)| |H_2(\omega)|$$

$$\angle H(\omega) = \angle H_1 H_2 = \angle (|H_1| e^{j\angle H_1} |H_2| e^{j\angle H_2}) = \angle H_1 + \angle H_2$$




$$R_1 = 1\text{K}\Omega \quad C_1 = 0.1\mu\text{F} \quad \tau_1 = R_1 C_1 = 10^3 \cdot 10^{-7} = 10^{-4}\text{s}$$

$$R_3 = 200\Omega \quad C_3 = 1\mu\text{F}$$



$$\tau_3 = R_3 C_3 = (200) \cdot 10^{-6} = 2 \times 10^{-4}\text{s}$$

$$\omega_{p1} = \frac{1}{\tau_1} = 10^4 \frac{\text{rad}}{\text{s}}$$
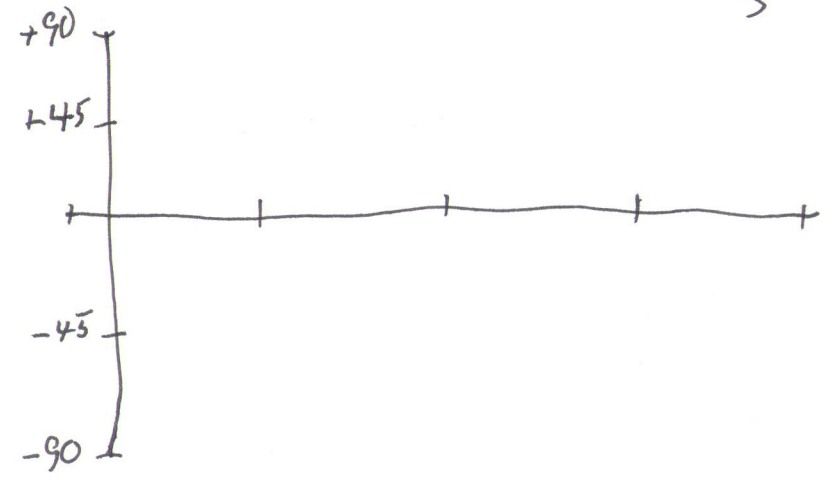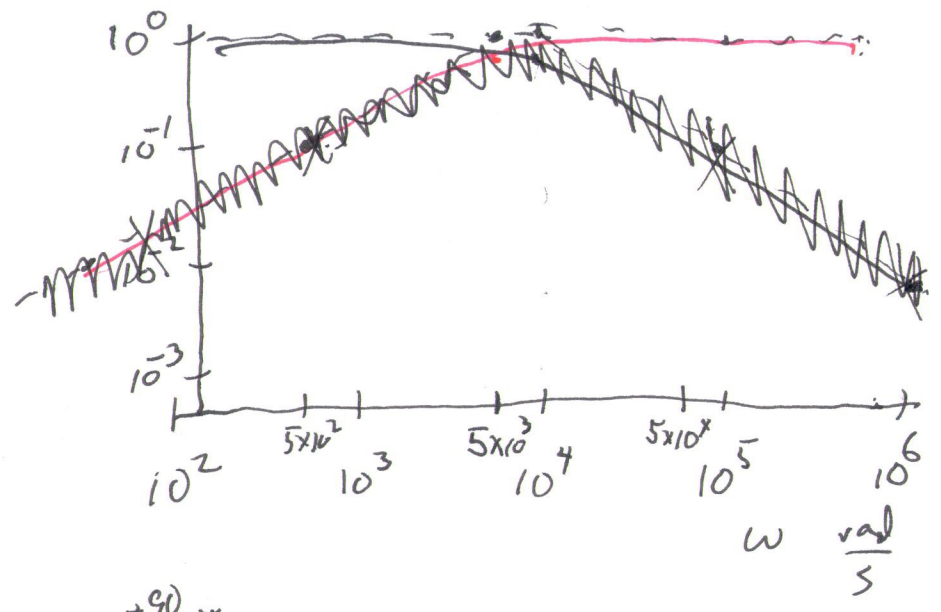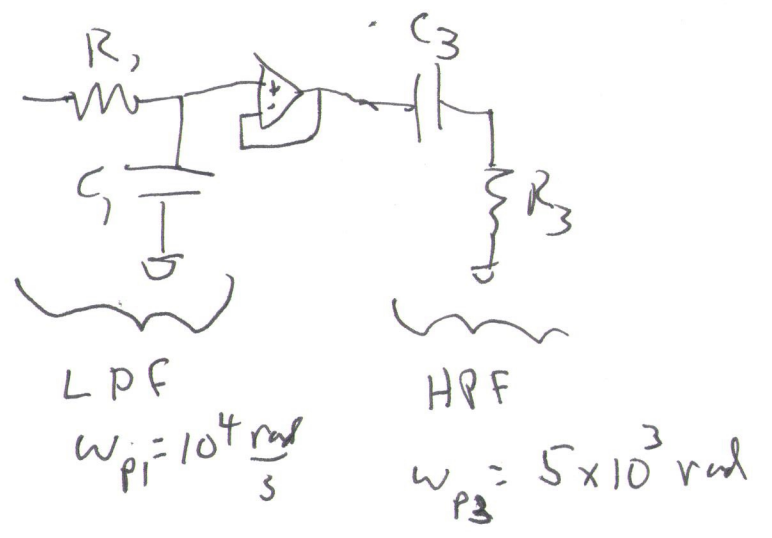
$$\omega_{p3} = \frac{1}{\tau_3} = \frac{1}{2 \times 10^{-4}} = 5 \times 10^3 \frac{\text{rad}}{\text{s}}$$



Buffers?

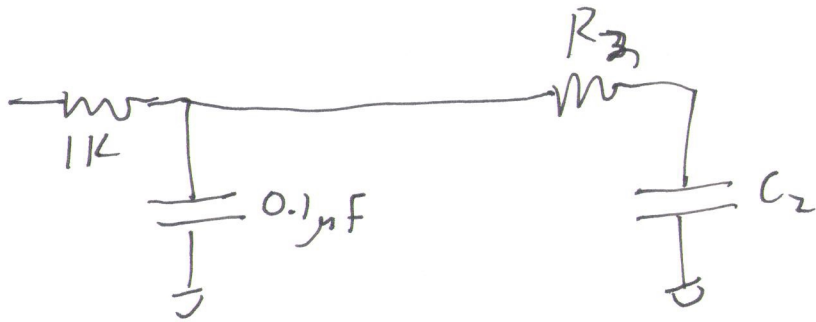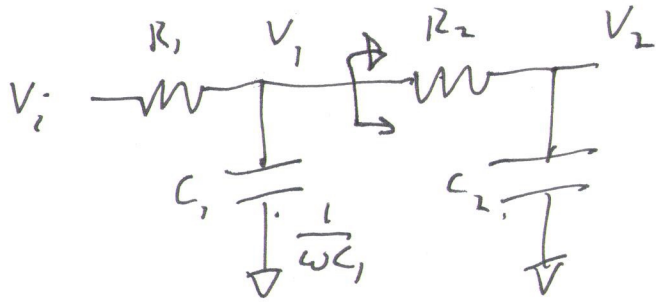

~~R2 >> R1~~



$$\left| R_2 + \frac{1}{\omega C_2} \right| \gg \frac{1}{\omega C_1}$$

$$C_2 = \frac{C_1}{100}$$

want $\omega_{p1} = \omega_{p2}$

$$R_1 C_1 = R_2 C_2$$

$$R_2 = 100 R_1$$

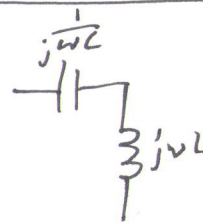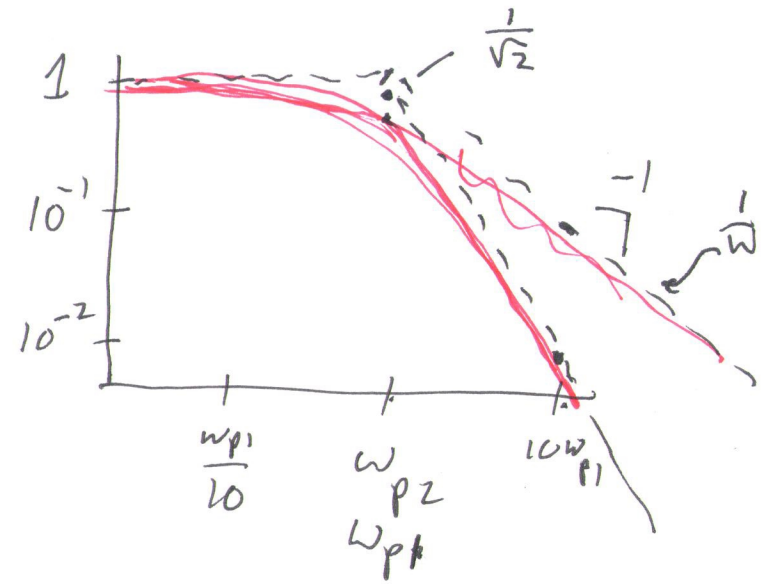





$$H(\omega) = \frac{j\omega L}{j\omega L + \frac{1}{j\omega C}}$$

$$= \frac{(j\omega L)(j\omega C)}{(j\omega L)(j\omega C) + 1}$$

$$= \frac{-\omega^2 LC}{1 - \omega^2 LC}$$

$$\omega_n = \frac{1}{\sqrt{LC}}$$
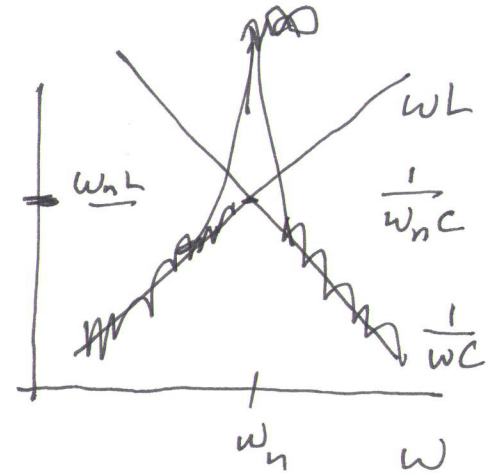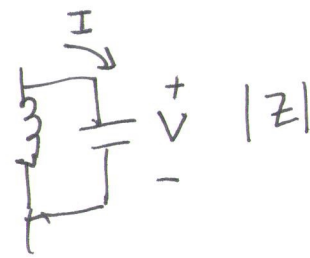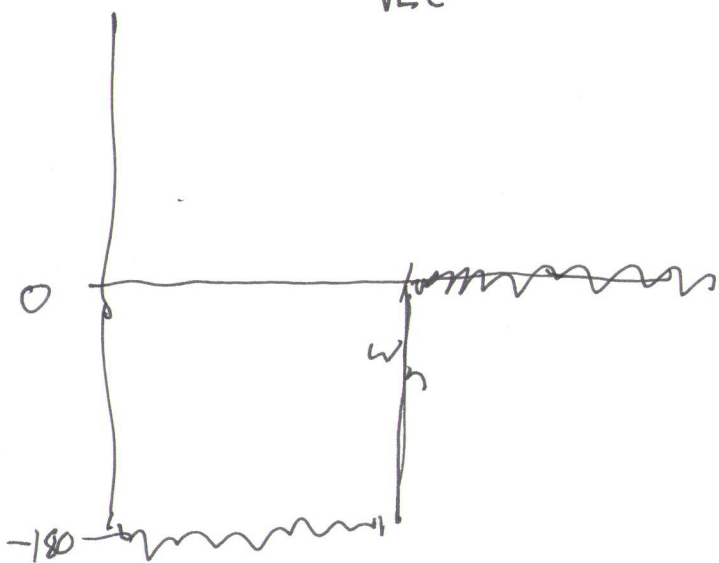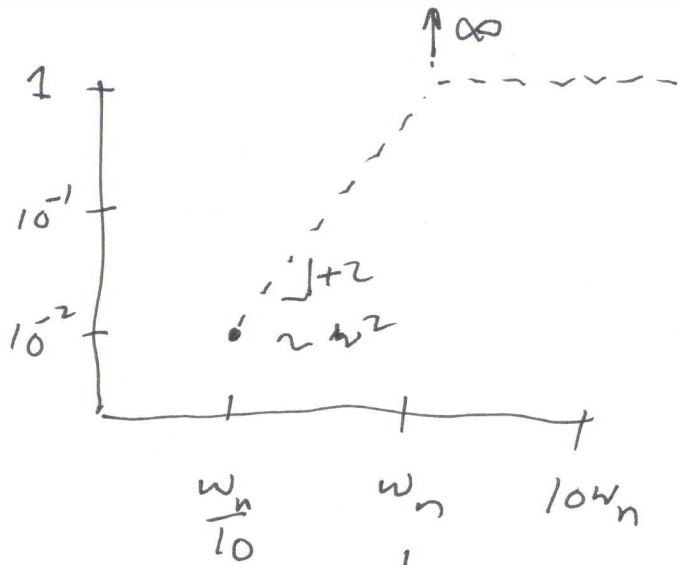
$$H(\omega) = \begin{cases} -\omega^2 LC = -\frac{\omega^2}{\omega_n^2} & \omega \ll \omega_n \\ \infty & \omega = \omega_n \\ 1 & \omega \gg \omega_n \end{cases}$$



$$Z = \frac{j\omega L \frac{1}{j\omega C}}{j\omega L + \frac{1}{j\omega C}}$$

$$= \frac{j\omega L}{(j\omega L)(j\omega C) + 1}$$

$$Z(\omega_n = \frac{1}{\sqrt{LC}}) = \infty$$

$$I = C \frac{dV}{dt}$$

$$V = L \frac{d}{dt} I_L$$

$$I_L = -I$$

$$V = L \frac{d}{dt} \left(-C \frac{dV}{dt} \right)$$

$$= -LC \frac{d^2 V}{dt^2}$$

$$LC \frac{d^2 V}{dt^2} + V = 0$$

$$V(t) = V_0 \cos(\omega t + \phi)$$


$$\frac{dV}{dt} = -\omega V_0 \sin(\omega t + \phi)$$

$$\frac{d^2 V}{dt^2} = -\omega^2 V_0 \cos(\omega t + \phi)$$


$$LC(-\omega^2 V_0 \cos(\omega t + \phi)) + V_0 \cos(\omega t + \phi) = 0$$

$$-LC\omega^2 + 1 = 0$$

$$\omega_n = \frac{1}{\sqrt{LC}}$$

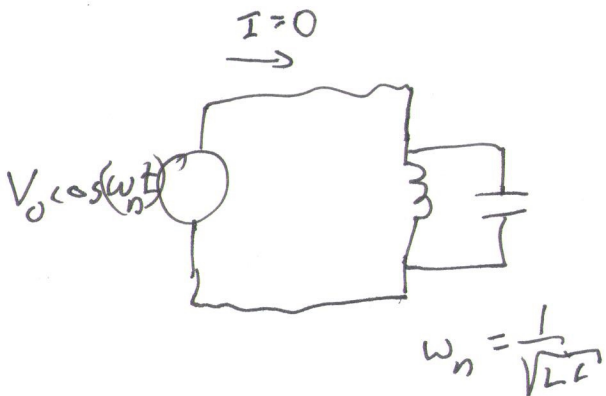

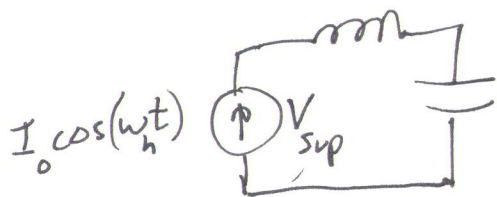
$$Z_{\text{par}} = \frac{\hat{V}_0}{\hat{I}} = \infty$$




$$\omega_n = \frac{1}{\sqrt{LC}}$$
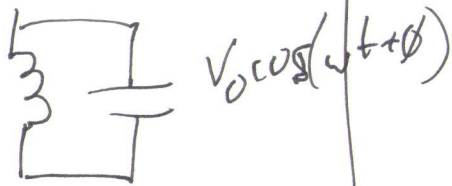
$$Z_{\text{series}} = \frac{\hat{V}_{\text{sup}}}{\hat{I}_0} = 0$$




Real inductors

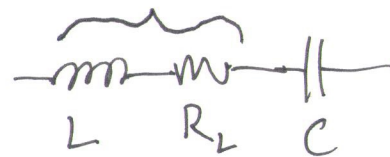

$$Z = j\omega L + R_L + \frac{1}{j\omega C}$$

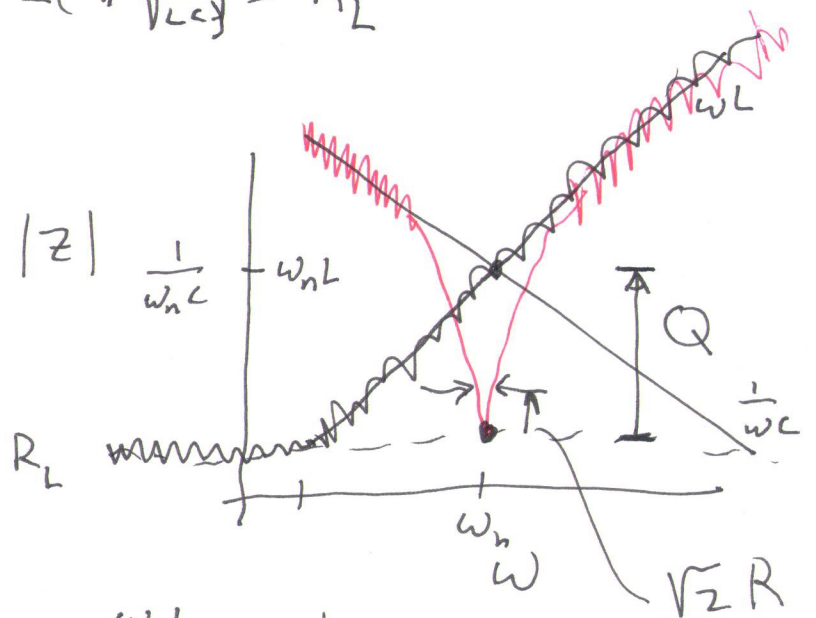
$$Z(\omega_n = \frac{1}{\sqrt{LC}}) = R_L$$







$$Q = \frac{\omega_n L}{R_L} = \frac{1}{\omega_n RC}$$

$$\rightarrow \kappa$$

$$B = \frac{\omega_n}{Q}$$

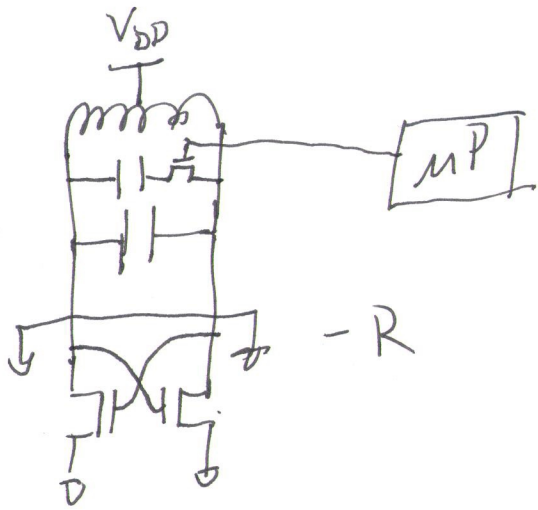


$|Z|$

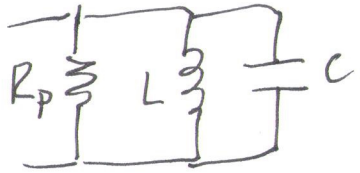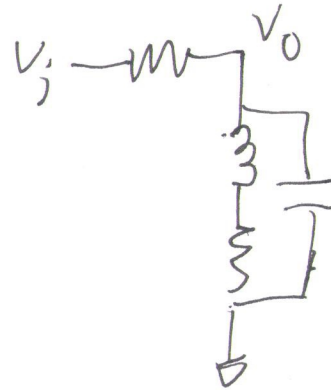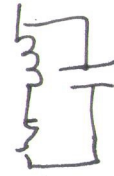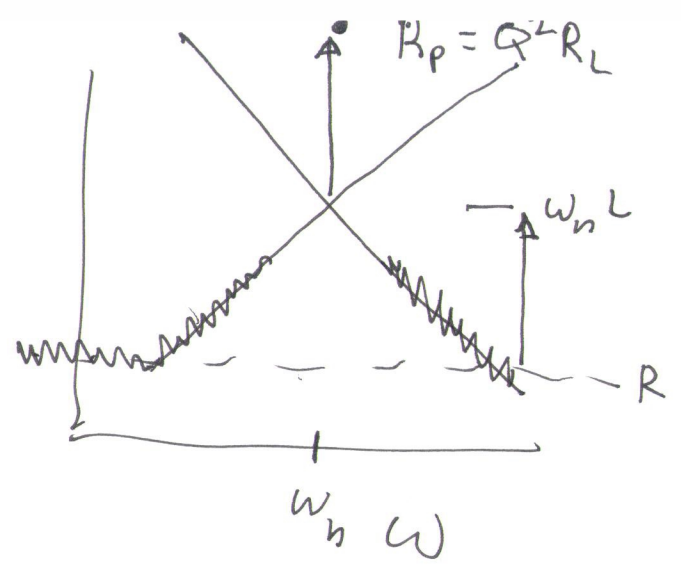

$$Z = R_p \parallel [LC \text{ tank}]$$
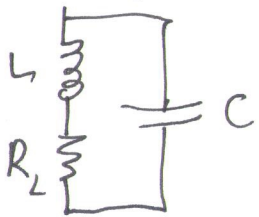
$$Z(\omega_n = \frac{1}{\sqrt{LC}}) = R_p$$



$$j\omega L + R_L \parallel \frac{1}{j\omega C}$$

$$Z_{eq} = \frac{(j\omega L + R_L)}{j\omega C} \frac{1}{j\omega L + R_L + \frac{1}{j\omega C}}$$