

ANNOUNCEMENTS



- NEW SECTIONS: 1-2, and 2-3 ← SEE PIAZZA FOR LOCATIONS (NOFFITT)
- DSP ACCOMODATION LETTERS: PLEASE REQUEST THEM FROM THE DSP OFFICE.

→ RECAP


→ CIRCUIT ANALYSIS

→ DC ANALYSIS ← 16A
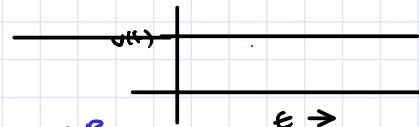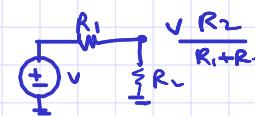
$$\rightarrow \text{EQNS: } i = \frac{v}{R}$$



$e \Rightarrow$

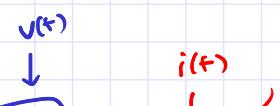


$i(t)$

→ TRANSIENT ANALYSIS

$$\rightarrow i(t), v(t)$$

→ EQNS: DIFFERENTIAL EQNS.
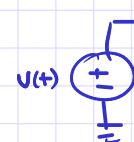
$$\rightarrow i(t) = C \frac{dv(t)}{dt},$$



$$C \frac{dx}{dt} = \frac{v(t) - x(t)}{R}$$

$$\Rightarrow \frac{dx}{dt} = \frac{v(t) - x(t)}{RC}$$


$$\text{if } v(t) \equiv 0$$

$$\frac{dx}{dt} = -\frac{x(t)}{RC}$$

$$c(1) : \lambda = -\frac{1}{RC}$$

$$\rightarrow \boxed{x(t) = x_0 e^{\lambda t}}$$

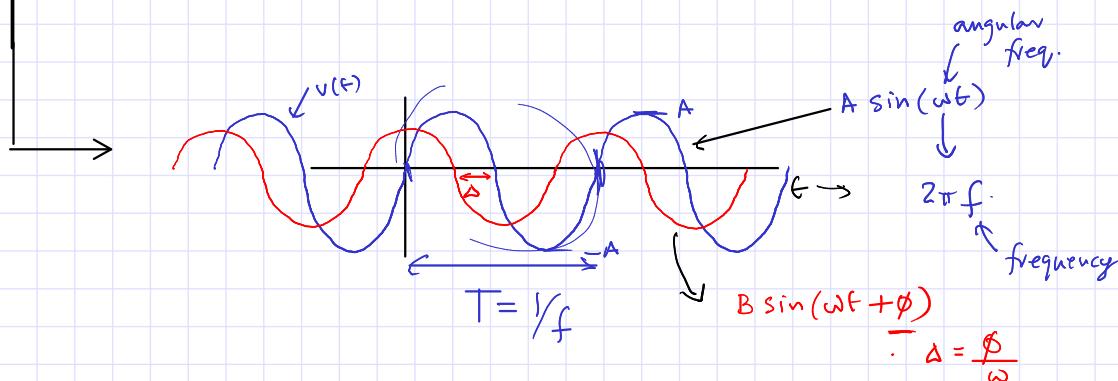→ KRIS: Showed that this solves
→ HW: SHOWED THAT ONLY this solves




→ DEMO: AUDIO CAN BE SPLIT INTO A SUM OF SINUSOIDS
→ OF DIFFERENT FREQS.


→ WITH ALL SINUSOIDS: MUCH EASIER TO SOLVE

THE CIRCUIT → NO DIFF. EQN. SOLNS.
NEEDED, INSTEAD: LIKE DC

→ LAST CLASS :

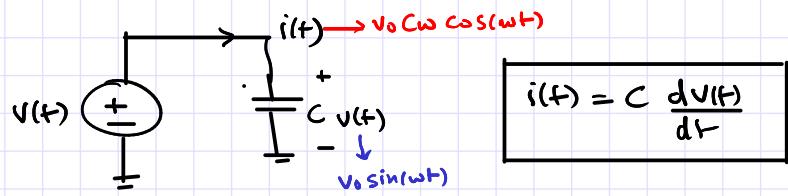
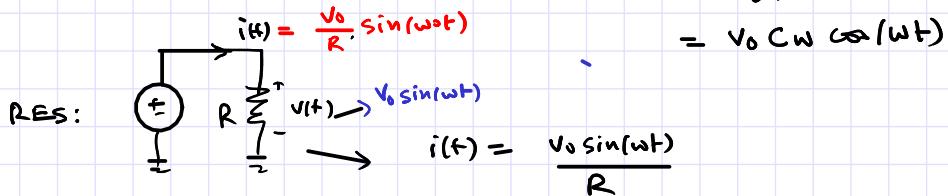
$$\rightarrow V(t) = V_0 \sin(\omega t) \Rightarrow i(t) = C \frac{d}{dt} (V_0 \sin(\omega t))$$



Using Ohm's Law: $\boxed{i(t) = \frac{V(t)}{R}}$ $\Rightarrow R = \frac{V(t)}{i(t)}$; CHECK: $\frac{V_0 \sin(\omega t)}{\cancel{\frac{V_0}{R} \sin(\omega t)}} = R$ ✓

→ WHAT IS $\frac{V(t)}{i(t)}$ FOR THE CAP?

$$\cancel{\frac{V_0 \sin(\omega t)}{V_0 C \omega \cos(\omega t)}} = \frac{1}{\omega C} \frac{\tan(\omega t)}{\cos(\omega t)} \leftarrow ???$$

STRANGE / ∞/0 VALUES

→ KEY TO A BETTER ANALYSIS: EXPRESS $\sin()$ / $\cos()$ USING COMPLEX NUMBERS

→ QUICK COMPLEX NUMBER TUT:

$$\rightarrow j = \sqrt{-1}, \quad j^2 = -1 \quad j \text{ is imaginary}$$

$$\rightarrow \text{complex: } a = ar + j ai$$

\uparrow \uparrow
 real part imag. part

→ same arithmetic rules as real numbers

$$\rightarrow \text{eg: } a+b = (ar+jai) + (br+jbi) = (ar+br) + j(ai+bi)$$

→ CONJUGATE OF A COMPLEX NUMBER:

$$\rightarrow a = ar + jai, \quad \bar{a} \triangleq ar - jai \quad (\text{change sign of imag. part})$$

$$\rightarrow a + \bar{a} = (ar + jai) + (ar - jai) = 2ar \leftarrow \text{always real} \leftarrow \text{IMPORTANT}$$


$$\rightarrow a - \bar{a} = (ar + jai) - (ar - jai) = 2jai \leftarrow " \text{ imag.}$$

→ RELATIONSHIP w/ $\sin()$ / $\cos()$.


→ de Moivre's Theorem (dMT):

$$\boxed{e^{j\theta} = \cos(\theta) + j \sin(\theta)}$$
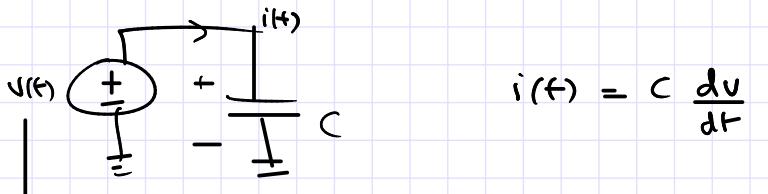
$$\begin{aligned}
 e^{j\theta} &= \cos(\theta) + j \sin(\theta) \\
 -e^{-j\theta} &= \cos(-\theta) - j \sin(-\theta) \\
 \underline{e^{j\theta} + e^{-j\theta}} &= 2 \cos(\theta) \Rightarrow \boxed{\cos(\theta) = \frac{e^{j\theta} + e^{-j\theta}}{2}} \\
 \underline{e^{j\theta} - e^{-j\theta}} &= 2j \sin(\theta) \\
 \Rightarrow \sin(\theta) &= \frac{e^{j\theta} - e^{-j\theta}}{2j}
 \end{aligned}$$


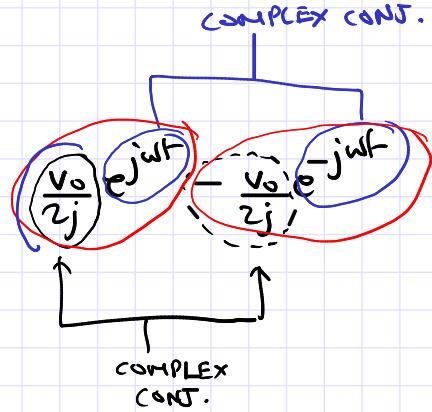
$$V(t) = V_0 \sin(\omega t) = \frac{V_0}{2j} [e^{j\omega t} - e^{-j\omega t}]$$



$$\begin{aligned}
 e^{j\omega t} &= \cos(\omega t) + j \sin(\omega t) \\
 e^{-j\omega t} &= \cos(-\omega t) - j \sin(-\omega t)
 \end{aligned}$$

$$i(t) = C \frac{d}{dt} \left[\frac{V_0}{2j} [e^{j\omega t} - e^{-j\omega t}] \right] = \frac{V_0 C}{2j} [j\omega e^{j\omega t} - (-j\omega) e^{-j\omega t}]$$

$$= \frac{V_0 C j\omega}{2j} [e^{j\omega t} + e^{-j\omega t}]$$

$$= \frac{V_0 C \omega}{2} \frac{e^{j\omega t} + e^{-j\omega t}}{2}$$

$$V(t) = \frac{V_0}{2j} \underline{e^{j\omega t}} + \underline{\left(\frac{V_0}{2j} \right)} e^{-j\omega t}$$

CC

PITASOR = coeff. of $e^{j\omega t}$ term.


$$i(t) = \frac{V_0 C \omega}{2} e^{j\omega t} + c.c. \text{ term.}$$

$$\rightarrow \text{TRY: } \frac{\tilde{V}}{\tilde{I}} = \frac{\frac{V_0}{2j}}{\frac{V_0 C \omega}{2}} = \boxed{\frac{1}{j\omega C}}$$

$$\tilde{I} = \frac{\tilde{V}_x}{\left(\frac{1}{j\omega C} \right)} \leftarrow Z_C$$

IMPEDANCE

→ CIRCUITS CAN BE ANALYZED IN PHASORS!

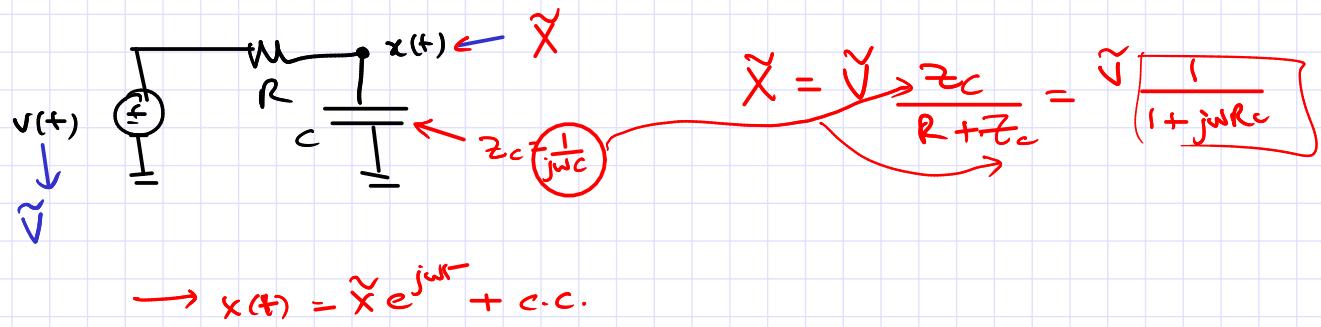

→ TODAY

→ DEMO: AUDIO = SUM OF MANY SINUSOIDS

→ SINUSOIDS: WROTE USING COMPLEX NUMBERS
→ PHASOR: COEFF. OF $e^{j\omega t}$

→ CAP "LOOKS LIKE" RES IN "PHASOR DOMAIN": IMPEDANCE

→ CIRCUITS, CAN BE SOLVED EASILY USING PHASORS.
including CAPS