

→ WHAT WE DID LAST TIME

→ CIRCUIT ANALYSIS w SINUSOIDAL voltages / currents:


→ write sinusoids using complex number + conjugate

$$\text{PHASOR} \leftarrow \underline{x} e^{j\omega t} + \overline{\underline{x}} e^{-j\omega t}$$

→ PHASORS make CAPS look like resistors  $\underline{i} = \frac{\underline{v}}{Z_c} \rightarrow (1/j\omega C)$

→ PHASORS GREATLY SIMPLIFY CIRCUIT ANALYSIS (IF ALL ARE SINUSOIDAL)

→ STARTED LOOKING AT

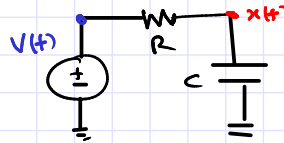

→ TODAY:

→ CONTINUE WITH  $\nearrow$  IN MORE DETAIL

→ TRANSFER FUNCTIONS: nice way of capturing how  $x(t)$  &  $v(t)$  are related.

→ PLOTTING PHASORS and TRANSFER FUNCTIONS

↳ LOG-LOG PLOTS look VERY NICE → WHY?

↳ BODE PLOTS

→ COMPLEX NUMBER / u-TVT CONTD.


→ MAGNITUDE (OR ABSOLUTE VALUE) OF COMPLEX NUMBER:

→  $a = a_r + ja_i$

$|a| = \sqrt{a_r^2 + a_i^2}$   
 ↑  
 MAG. of a

→ NOTE:  $|a|^2 = a\bar{a}$

→ GRAPHICAL DEPICTION OF COMPLEX NO:

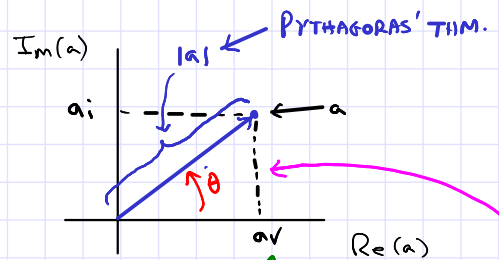

→  $\theta = \text{"angle of } a \text{"} = \angle a$

→  $\tan \theta = \frac{a_i}{a_r} \Rightarrow \theta = \tan^{-1} \left( \frac{a_i}{a_r} \right)$

→ also:  $\sin(\theta) = \frac{a_i}{|a|}, \cos(\theta) = \frac{a_r}{|a|}$


→ NOTE:

$a = |a| e^{j\theta}$

← POLAR REPRESENTATION


$= |a| \cos(\theta) + j|a| \sin(\theta)$

$\rightarrow a = a_r + j a_i = M e^{j\theta} \leftarrow \text{phase} = \angle a$   
 $\uparrow$   
 CARTESIAN REPR.  
 $\uparrow$   
 magnitude =  $|a|$   
 $\uparrow$   
 POLAR REPR.

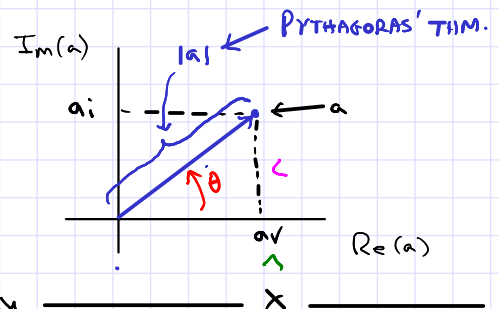

$\rightarrow \text{NOTE: } (M e^{j\theta}) = M e^{-j\theta}$

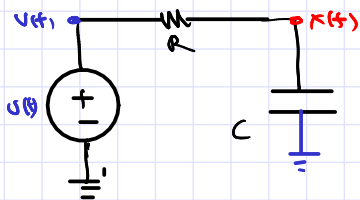
$\rightarrow$  SIMPLE RC CKT: PHASOR ANALYSIS



$v(t) = \tilde{V} e^{j\omega t} + \text{c.c. term}$   
 $\uparrow$   
 known (eg:  $\tilde{V} = \frac{1}{\sqrt{2}}$  if  $v(t) = \sin(\omega t)$ )

$\rightarrow$  ASSUME  $x(t) = \text{sinusoid} = \tilde{X} e^{j\omega t} + \text{c.c.t.}$

$\uparrow$   
 unknown: want to find.

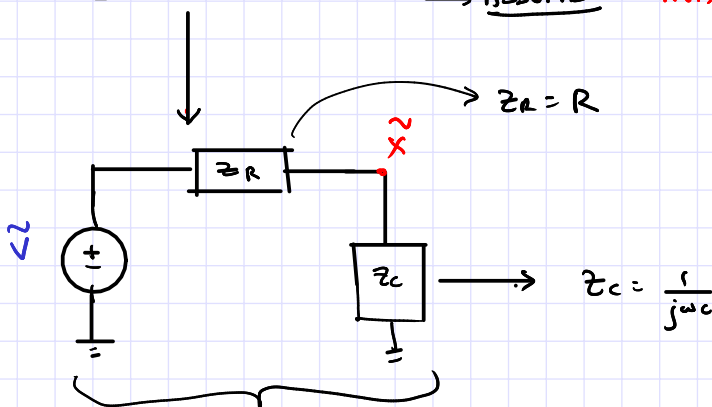


$\rightarrow$  THIS IS A CKT DIAGRAM IN TERMS OF PHASORS ("PHASOR DOMAIN")  
 $\rightarrow$  MAKES SENSE BECAUSE PHASORS OBEY KCL & KVL

$\rightarrow$  DISCUSSION Problem 4

$\rightarrow$  SOLVING THE CIRCUIT:

$\rightarrow$  KCL @ x:  $\frac{\tilde{X}}{Z_C} = \frac{\tilde{V} - \tilde{X}}{Z_R} \Rightarrow \tilde{X}(Z_C + Z_R) = \tilde{V} Z_C \Rightarrow \tilde{X} = \tilde{V} \frac{Z_C}{Z_C + Z_R}$

$\rightarrow$  Series impedance of

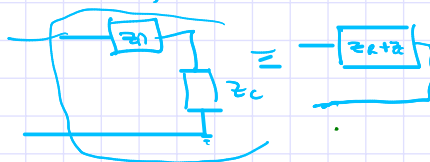

$\uparrow$  IMPEDANCE DIVIDER FORMULA


$\rightarrow \tilde{X} = \tilde{V} \frac{Z_C}{Z_C + Z_R} = \tilde{V} \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R} = \frac{\tilde{V}}{1 + j\omega RC}$

$\tilde{X} = \tilde{V} \frac{1}{1 + j\omega RC}$

$\rightarrow$  call it  $H(\omega)$

FREQ. DOMAIN TRANSFER FUNCTION  
 (from  $\tilde{V}$  to  $\tilde{X}$ )

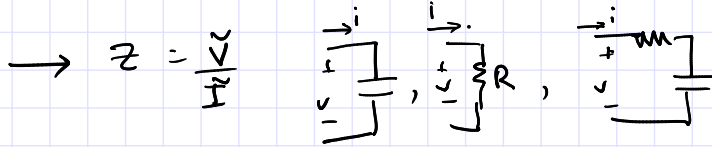→ TRANSFER FUNCTION: GENERALIZATION OF IMPEDANCE / RESISTANCE:




(PHASORS OF)





→ RATIO OF ANY TWO CRT QUANTITIES

→ voltages / currents (change, f(x), ...)

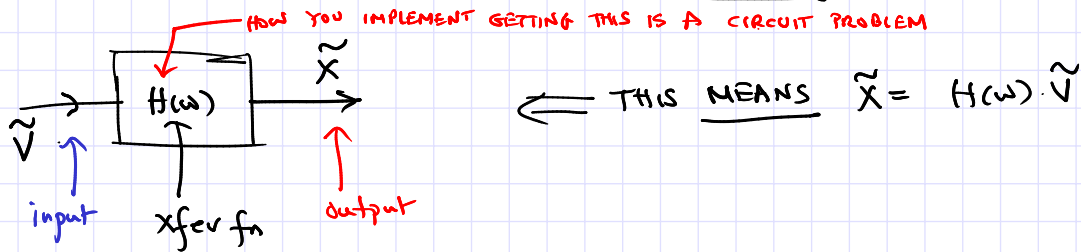→ HELPS YOU LOOK AT A CIRCUIT AS A SYSTEM:



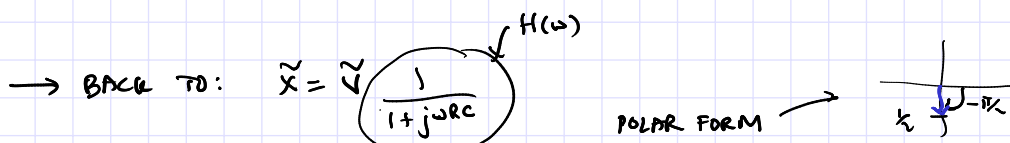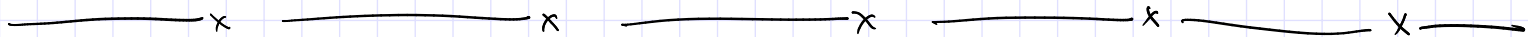→ NOW YOU SEE THAT: IMPEDANCES ARE ALSO A SPECIAL CASE OF TRANSFER FNS..



→ Q: Suppose  $\tilde{V} = \frac{1}{2j} = \frac{-j}{2} = \frac{1}{2} e^{-j\pi/2}$  (ie.,  $v(t) = \sin(\omega t)$ ), what is  $x(t)$ ?

→  $x(t) = \tilde{X} e^{j\omega t} + \text{c.c. term}$ , where  $\tilde{X} = \frac{1}{2} e^{-j\pi/2} \times \frac{1}{1+j\omega RC} \rightarrow H(\omega)$

Let's write  $H(\omega)$  in POLAR FORM:  $H(\omega) = M(\omega) e^{j\theta(\omega)}$

→  $M(\omega) = |H(\omega)|$ ,  $\theta(\omega) = \angle H(\omega)$

⇒  $x(t) = \frac{1}{2} e^{-j\pi/2} M(\omega) e^{j(\omega t + \theta(\omega))} + \text{c.c. term}$

$= \frac{1}{2} M(\omega) e^{j(\omega t + \theta(\omega) - \pi/2)} + \text{c.c. term}$

↑  
real and  $\geq 0$

→  $\frac{1}{2} M(\omega) e^{-j(\omega t + \theta(\omega) - \pi/2)}$

$\cos(\phi - \pi/2) = \cos(\pi/2 - \phi) = \sin(\phi)$

$x(t) = M(\omega) \cos(\omega t + \theta(\omega) - \pi/2)$



→  $x(t) = \frac{M(\omega) \sin(\omega t + \theta(\omega))$

↑ amplitude      ↑ phase shift

$M(\omega) = \left| \frac{1}{1+j\omega RC} \right| = \frac{1}{\sqrt{1+\omega^2 R^2 C^2}}$


$\theta(\omega) = \angle \frac{1}{1+j\omega RC} = \angle \frac{-j\omega RC}{1+\omega^2 R^2 C^2} = -\tan^{-1}(\omega RC)$

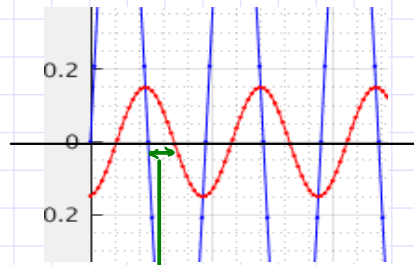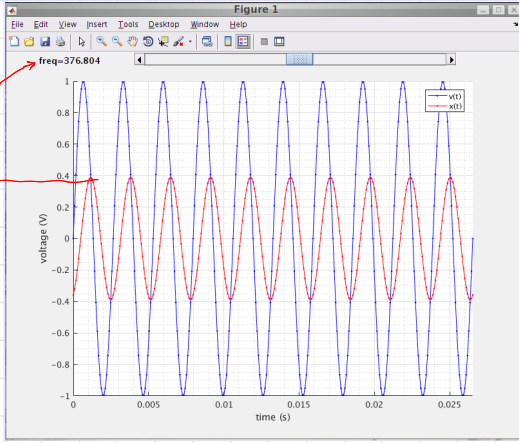→ DEMO:  $v(t)$  vs.  $x(t)$  as  $f$  changes ( $\omega = 2\pi f$ )



$$\theta(\omega) = -\tan^{-1}(\omega RC)$$

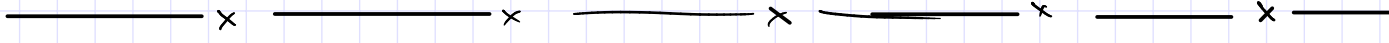→ 0 at  $\omega \rightarrow 0$   
 →  $-90^\circ = -\pi/2$  radians at  $\omega \rightarrow \infty$





→ VERY CLEAR THAT  $M(\omega)$  &  $\theta(\omega)$  TOTALLY DESCRIBE  $x(t)$

→ WHY NOT PLOT THEM VS  $f$ , TO VISUALLY APPRECIATE HOW THEY CHANGE?


→ TRANSFER FN PLOT DEMO

BODE PLOT of  $H(2\pi f)$

LINEAR  
-LINEAR  
PLOT

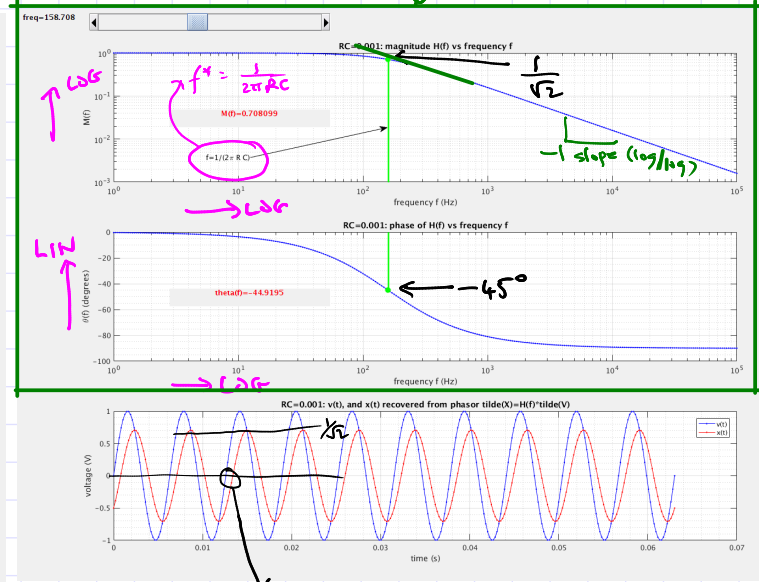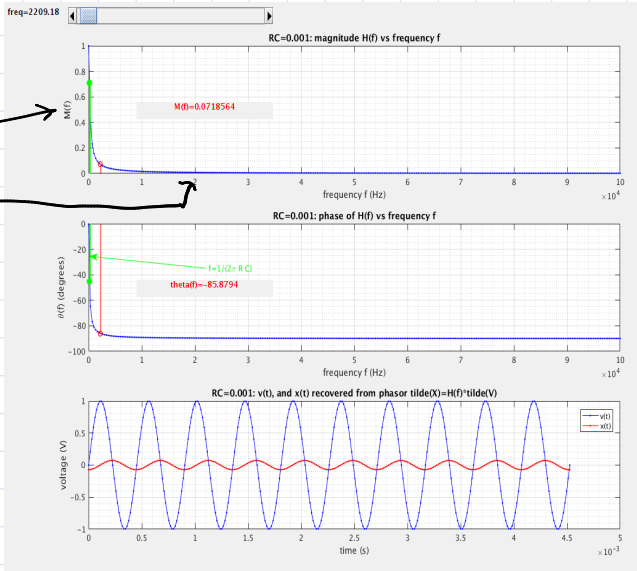

→ WHY IS THE MAGNITUDE PLOT SO NICE?

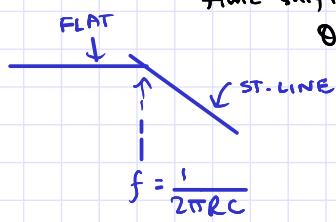

→ CAN WE UNDERSTAND THIS?

time shift corresponding to  $\theta = -45^\circ$

→ Recall:  $H(\omega) = \frac{1}{1+j\omega RC} = \frac{1}{1+j2\pi f RC}$


→  $M = |H(\omega)| = \frac{1}{\sqrt{1+4\pi^2 f^2 R^2 C^2}} = (1+4\pi^2 f^2 R^2 C^2)^{-1/2}$

→ what is  $\log(M)$ ?  $\log(M) = -\frac{1}{2} \log(1+4\pi^2 f^2 R^2 C^2)$

→ consider values of  $f$  s.t.  $1 \gg 4\pi^2 f^2 R^2 C^2 \Leftrightarrow \boxed{f \ll \frac{1}{2\pi RC}}$

→ then:  $1+4\pi^2 f^2 R^2 C^2 \approx 1$

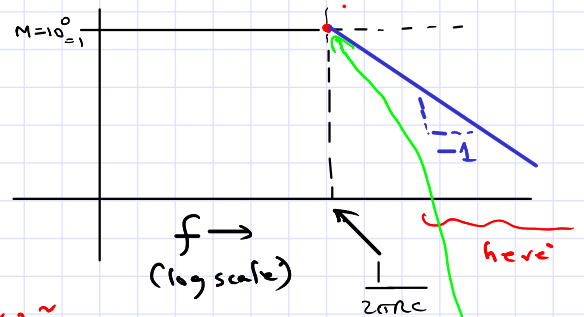→  $\log(M) \approx -\frac{1}{2} \log(1) = 0$



→ now, try  $f$  s.t.  $1 \ll 4\pi^2 f^2 R^2 C^2$

⇒  $f \gg \frac{1}{2\pi RC}$

→ IN THIS REGIME:  $1+4\pi^2 f^2 R^2 C^2 \approx 4\pi^2 f^2 R^2 C^2$

⇒  $\log(M) \approx -\frac{1}{2} \log((2\pi f RC)^2)$

$= -1 \times \log(2\pi f RC) = -\log(2\pi RC) - \log(f)$

$= +\log\left(\frac{1}{2\pi RC}\right) - \log(f)$

→ at  $f = \frac{1}{2\pi RC}$ , this is 0.

→ thereafter, falls with a slope of -1


→ THE ABOVE ARE APPROXIMATIONS, VALID for  $f \ll \frac{1}{2\pi RC}$  and  $f \gg \frac{1}{2\pi RC}$

→ WHAT IS  $|H(2\pi f)|$  EXACTLY at  $f = \frac{1}{2\pi RC}$ ?

$$M = \frac{1}{\sqrt{1+(2\pi RC)^2 f^2}} = \frac{1}{\sqrt{1+(2\pi RC)^2 \times \frac{1}{(2\pi RC)^2}}} = \frac{1}{\sqrt{1+1}} = \frac{1}{\sqrt{2}} \approx 0.707!$$

$\theta = -\tan^{-1}(\omega RC) = -\tan^{-1}(2\pi RC f) = -\tan^{-1}(1) = -45^\circ!$

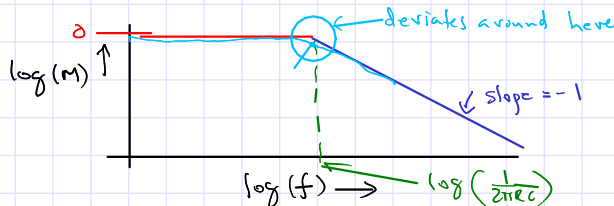→ IF YOU WANTED TO QUICKLY SKETCH THE BODE PLOT OF  $H(2\pi f) = \frac{1}{1+j\omega RC}$ .



→ SUMMARY (PHASORS + TRANSFER FNS. + BODE PLOTS):

→ PHASORS: EASY CKT ANALYSIS FOR SINUSOIDAL SIGNALS!


→ RATIO OF ANY 2 CKT QUANTITIES: TRANSFER FUNCTION  
 → USUALLY denoted as  $H(\omega) = H(2\pi f)$

→ YOU CAN RECOVER TIME-DOMAIN WAVEFORMS EASILY FROM MAG(PHASE of  $H(2\pi f)$ )

→ PLOT MAG/PHASE of  $H(2\pi f)$  ON LOG-LOG AND LOG-LIN SCALE:  
 → BODE PLOT.

→ MAG APPROXIMATED WELL WITH FLAT and -1 slope STRAIGHT LINE SEGMENTS.  
 $= \frac{1}{\sqrt{2}}$  at  $f = \frac{1}{2\pi RC}$

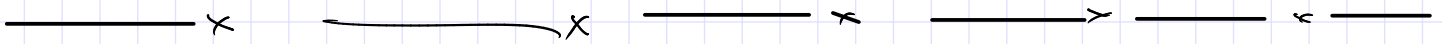
→ PHASE =  $-45^\circ$  at  $f = \frac{1}{2\pi RC}$ ,  $0$  at  $f \rightarrow 0$ ,  $\rightarrow -90^\circ$  as  $f \rightarrow \infty$



→ FROM PHASORS TO TIME-DOMAIN: GEOMETRICAL VIEW


$$\begin{aligned} \rightarrow x(t) &= \tilde{X} e^{j\omega t} + \text{c.c. term} \\ &= M e^{j\theta} e^{j\omega t} + \text{c.c. term} \\ &= M e^{j(\omega t + \theta)} + \text{c.c. term} \\ &\quad \tilde{Y}(t) \end{aligned}$$
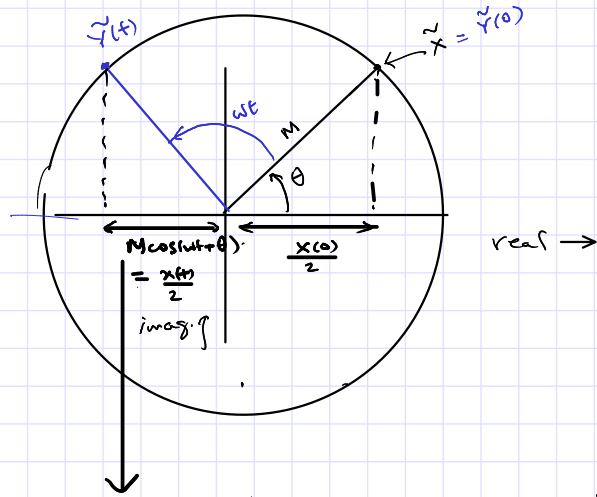
$$\begin{aligned} \rightarrow x(t) &= M e^{j(\omega t + \theta)} + M e^{-j(\omega t + \theta)} \\ &= \underline{2M \cos(\omega t + \theta)} \end{aligned}$$





→ PROJECT  $\tilde{Y}(t)$  onto horizontal axis  
 → MULTIPLY BY 2  
 → you've got  $x(t)$ !

→ SLIDER DEMO:


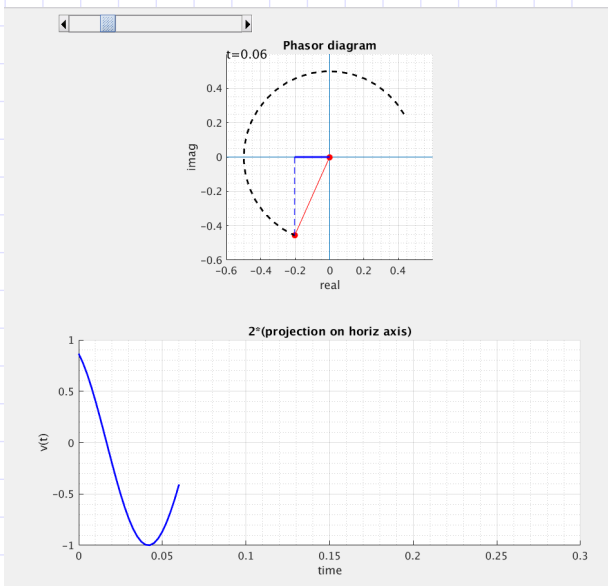


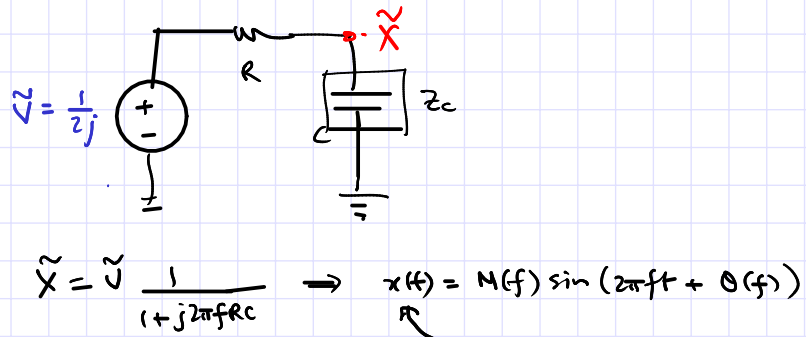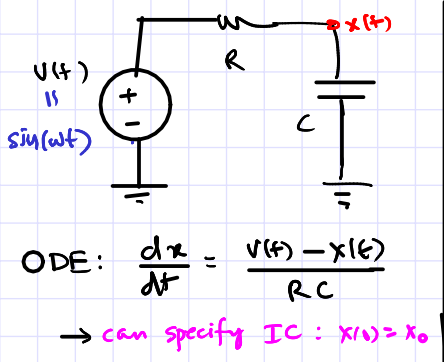→ PHASOR SOLUTIONS vs DIFFERENTIAL EQN SOLUTIONS:



→ THE QUESTION IS: IS  $x(t)$  from solving the ODE the same as ??

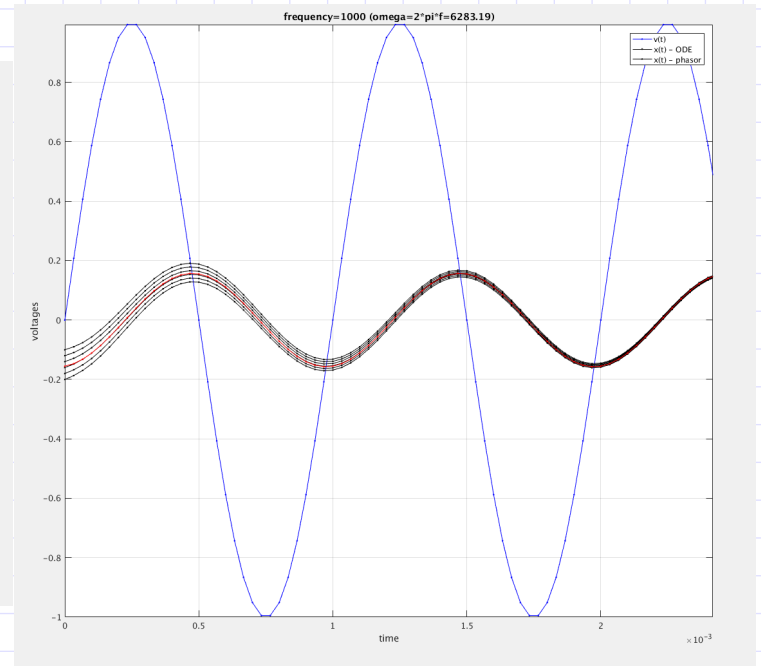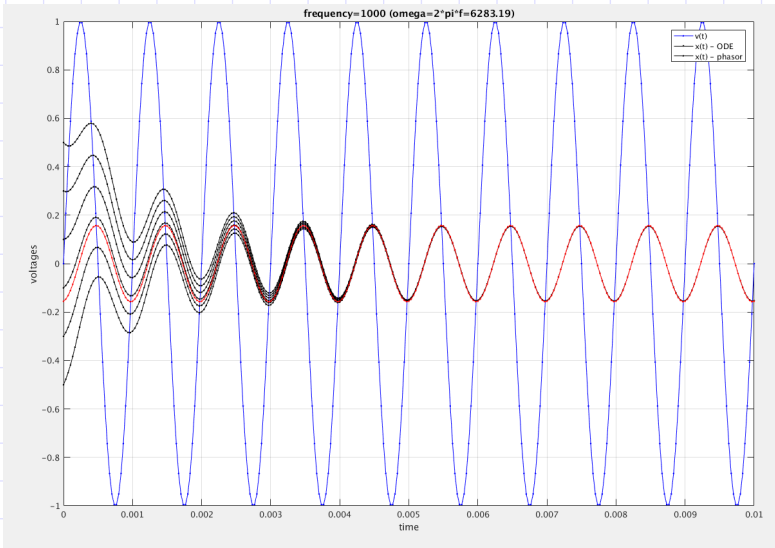→ DEMO: ODE NUMERICAL SOLN vs PHASOR-derived solution.  
 ↳ with various ICs.



→ PHASOR ANALYSIS AUTOMATICALLY FINDS THE IC THAT  
MAKES THE ODE SOLUTION A PERFECT SINE WAVE → NO "STARTUP TRANSIENTS"



STEINMETZ



BODE