
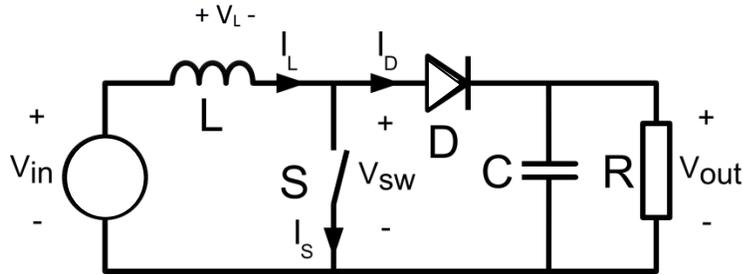


Boost Converter (draft 2/27/2015)

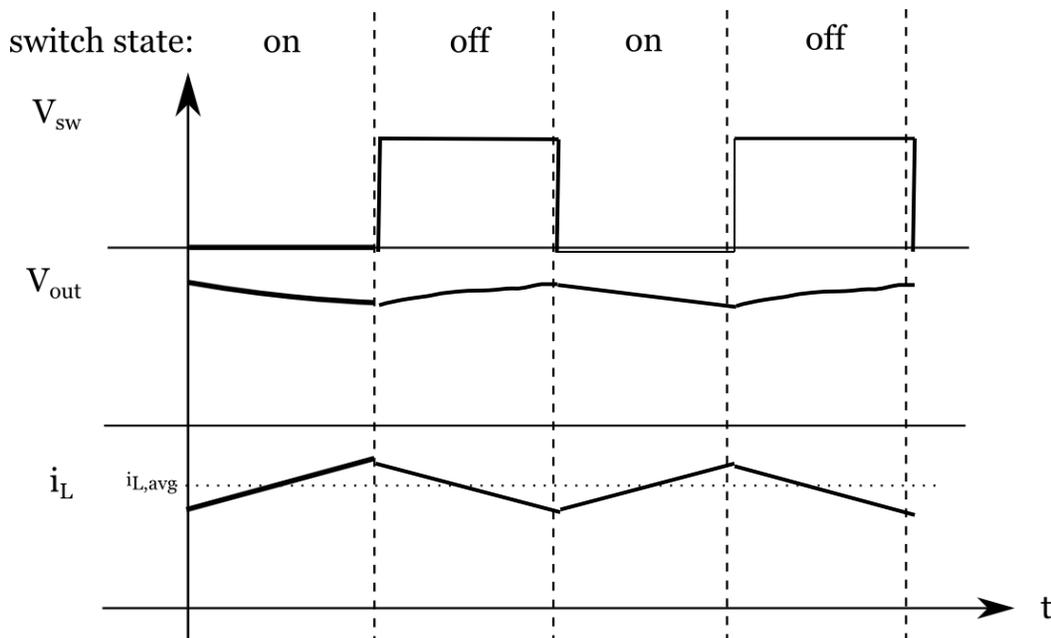- Switching type DC-DC converter
- Output voltage is greater than input voltage



1. Fill in the plots for two periods of the boost converter's operation.



For simplicity, assume i_L goes from i_{\max} to i_{\min} in a linear fashion in time T_{off} , with a change of $\Delta i = i_{\min} - i_{\max} (<0)$. Also assume V_{out} is approximately constant. During T_{off} the instantaneous power delivered to the capacitor and load from the inductor in series with V_{in} is $p(t) = i_L(t) (-V_L(t) + V_{\text{in}})$.

The inductor voltage during T_{off} is assumed constant: $V_L(t) = L \Delta i / T_{\text{off}}$, where V_{in} is boosted by V_L .

The work delivered per cycle from battery and inductor (when switch is open) is:

$$W = i_L (-V_L + V_{\text{in}}) T_{\text{off}} = i_L (-L \Delta i / T_{\text{off}} + V_{\text{in}}) T_{\text{off}} = i_L (-L \Delta i + V_{\text{in}} T_{\text{off}})$$

The time average power delivered to the load (through the diode) is $W/T =$

$$P_{\text{ave}} = i_L (-L \Delta i + V_{\text{in}} T_{\text{off}}) / (T_{\text{on}} + T_{\text{off}}) = (L (i_{\max}^2 - i_{\min}^2) / 2 + i_L V_{\text{in}} T_{\text{off}}) / (T_{\text{on}} + T_{\text{off}})$$

Note that there is a contribution from energy stored in the inductor and the power provided by battery.

The average power in the load should equal delivered power to load so

$$P_{\text{ave}} = (L (i_{\max}^2 - i_{\min}^2) / 2 + i_L V_{\text{in}} T_{\text{off}}) / (T_{\text{on}} + T_{\text{off}}) = V_{\text{out}}^2 / R$$

Note that the current may instead oscillate around an average current value, delivering more power to load.