
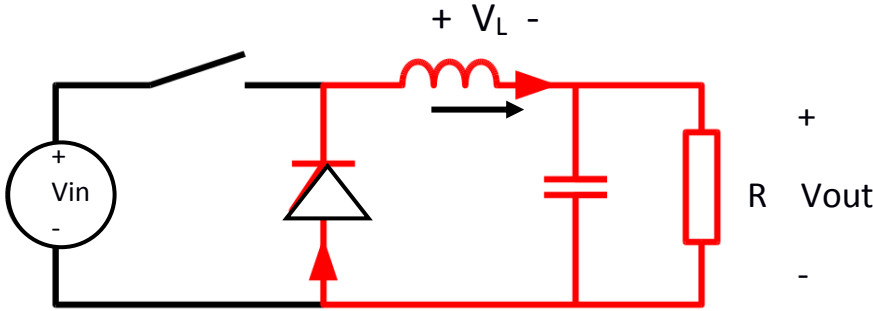


## Buck Converter (draft 2/20/2017) v2

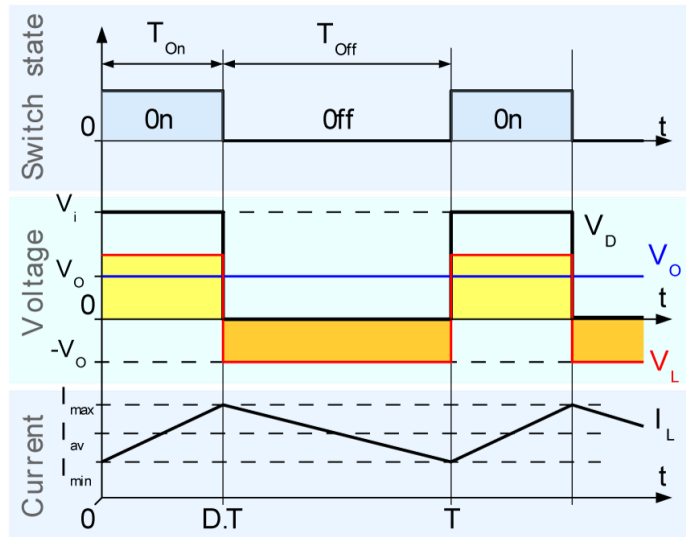

- Output voltage is less than input voltage



For simplicity, assume  $i_L$  goes from  $i_{max}$  to  $i_{min}$  in a linear fashion in time  $T_{off}$ , with a change of  $\Delta i = i_{max} - i_{min} (>0)$ . Also assume  $V_{out}$  is approximately constant. During  $T_{off}$  the instantaneous power delivered to the capacitor and load from the inductor in series with  $V_{in}$  is  $p(t) = -i_L(t)V_L(t)$ . (Note  $V_L$  is negative during off, so  $-V_L = V_{out}$ , for ideal diode.) The inductor voltage during  $T_{off}$  is assumed constant:  $V_L(t) = -L \Delta i / T_{off}$ . Also  $i_{av} \sim V_{out} / R$ .

When switch is open, the work delivered per cycle from inductor to load is (assuming  $i_L = i_{av}$ ), and  $V_L < 0$ :

$$W_{off} = -i_L V_L T_{off} = -i_L (L \Delta i / T_{off}) T_{off} = i_L L \Delta i$$

When switch is closed,  $\Delta i = i_{max} - i_{min} (>0)$ , and  $V_L > 0$  the work delivered through inductor per cycle is:

$$W_{on} = i_L (V_{in} - V_L) T_{on} = i_L (V_{in} - \Delta i L / T_{on}) T_{on} = -i_L L \Delta i + i_L V_{in} T_{on}$$

The time average power delivered to the load (through the inductor) is  $W/T =$

$$P_{ave} = (W_{off} + W_{on}) / (T_{on} + T_{off}) = i_L (L \Delta i - L \Delta i + V_{in} T_{on}) / (T_{on} + T_{off}) = i_L V_{in} T_{on} / (T_{on} + T_{off}) = V_{out}^2 / R$$

Note that there is a contribution from energy stored in the inductor and the power provided by battery.

Note that L is chosen based frequency. Consider  $V_{in} = 10V$ ,  $V_{out} = 2V$ ,  $R = 1 \text{ ohm}$ . Then  $i_{av} = 2 \text{ amps}$ , and  $V_L = 8V$  with switch on and  $V_L = -2V$  with switch off. Thus  $4T_{on} = T_{off}$ . For switching period  $T = T_{on} + T_{off} = 4 \text{ us}$  (LM2678), we might choose  $L = 33 \text{ uH}$  (bigger L means smaller di/dt). Then  $\Delta i = T_{on} (8V) / L = 0.2 \text{ amps}$ . Thus  $i_{max} = 2.1 \text{ amps}$  and  $i_{min} = 1.9 \text{ amps}$ .