

EECS192 Lecture 5

Feb. 14, 2017


Notes:

1. Check off-
 - 2/19: Motor drive/stall, steering servo from battery, schematics due (+ part location rats nest- no copper)
 - PCB design due (Gerbers) Tues 2/21 midnight
2. 2/21 Quiz 3: switch mode power supply and regulator
3. CalDay Sat. April 22 @ UCB

Topics

- Wiring
- Battery cell balancing
- Power supplies
- Linear regulator
- Buck converter
- *Boost converter- switch mode power supply*

Power supply wiring- Star is better!

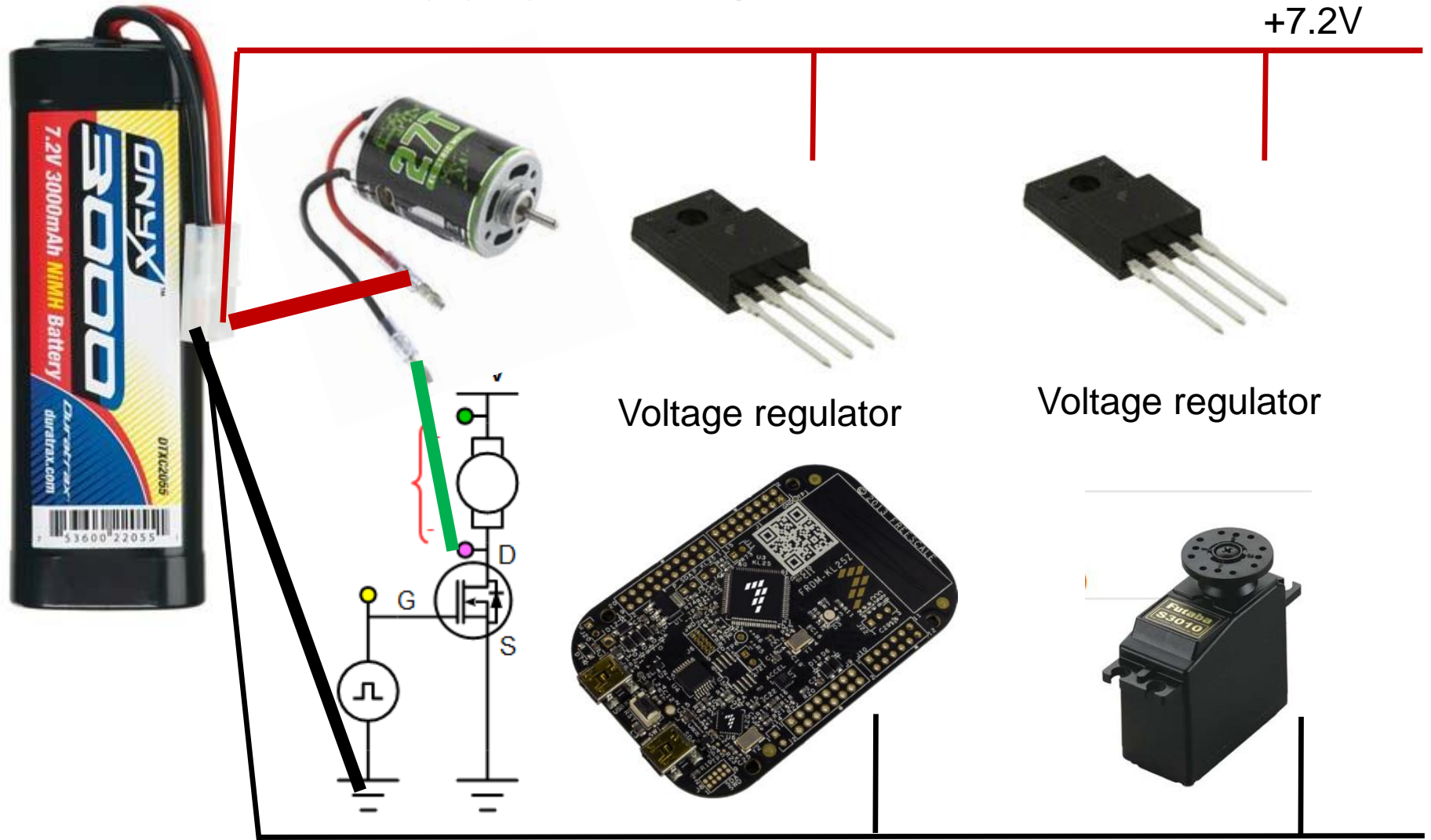

+7.2V



Voltage regulator

Voltage regulator



Low power ground

On board: what does this look like electrically (as a schematic)?

Which is ``Star'' config?

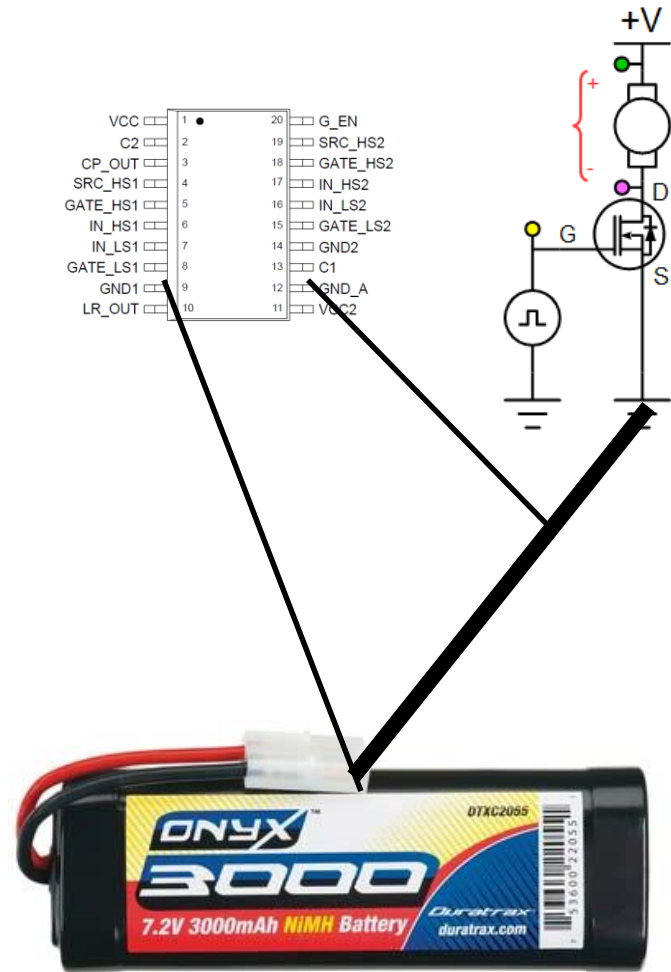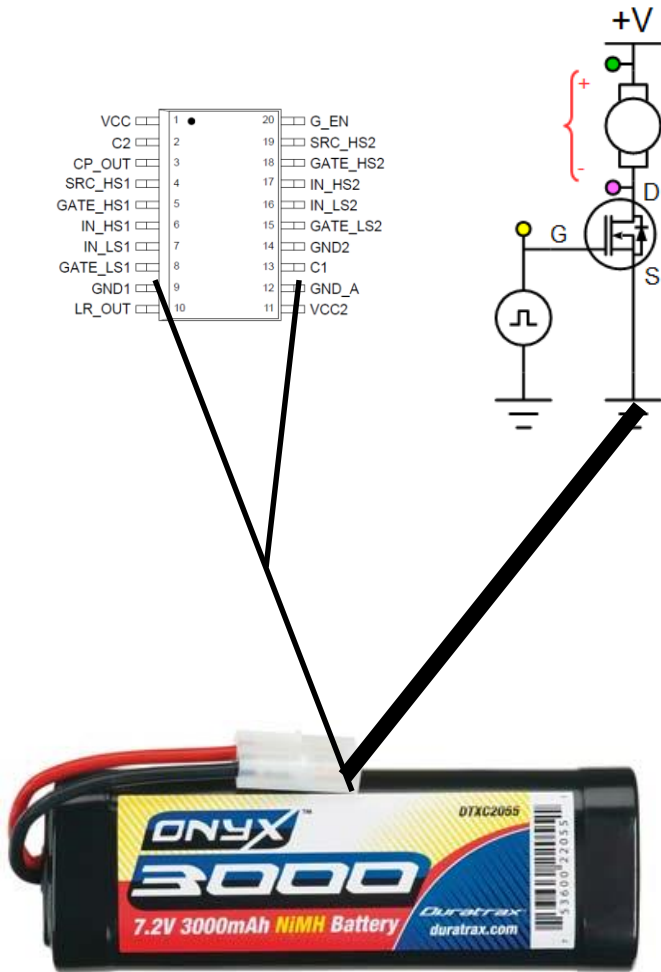


Which is "Star" config?

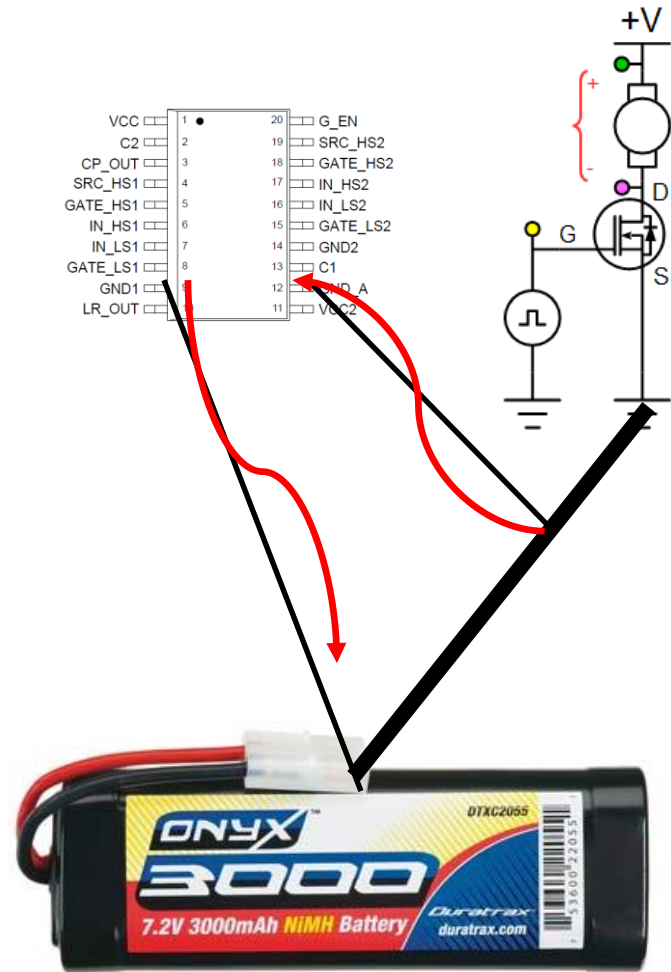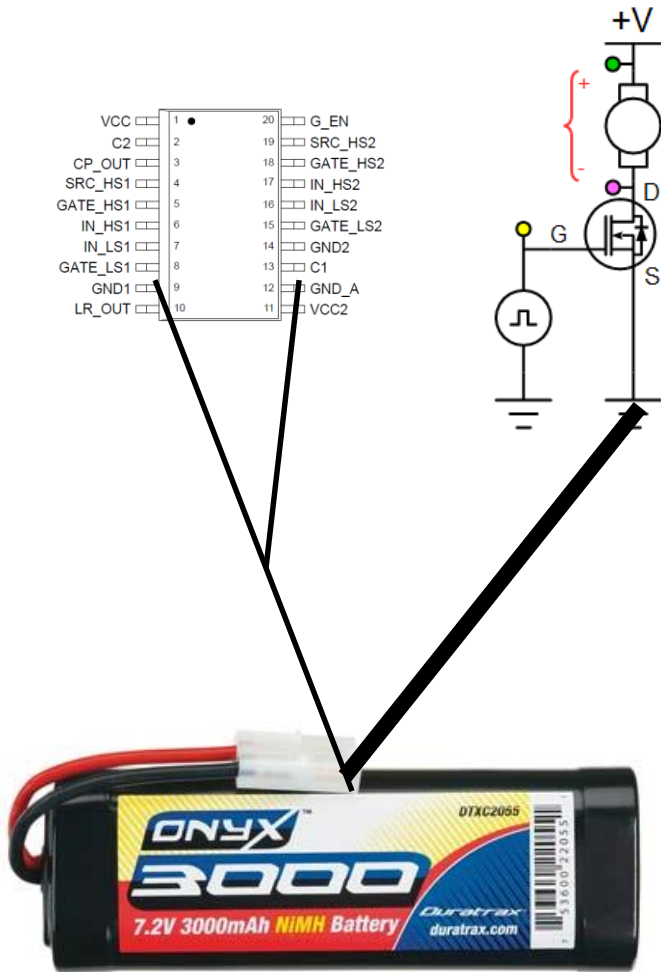


➔ supply waveforms with motor PWM

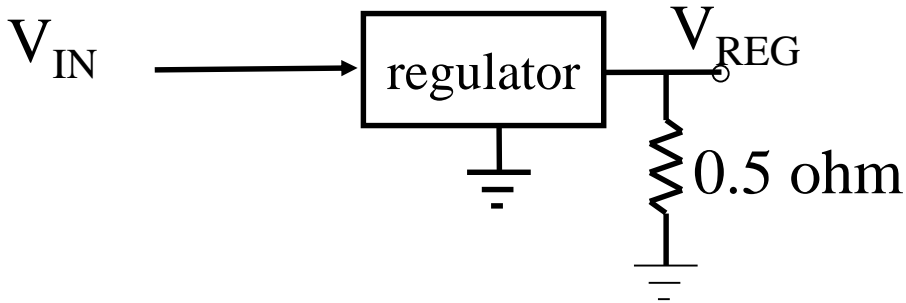
- Battery model
- Waveforms on board
- Wiring to reduce voltage resistance effects of wiring




Linear Regulator $V_{IN} > V_{REG}$

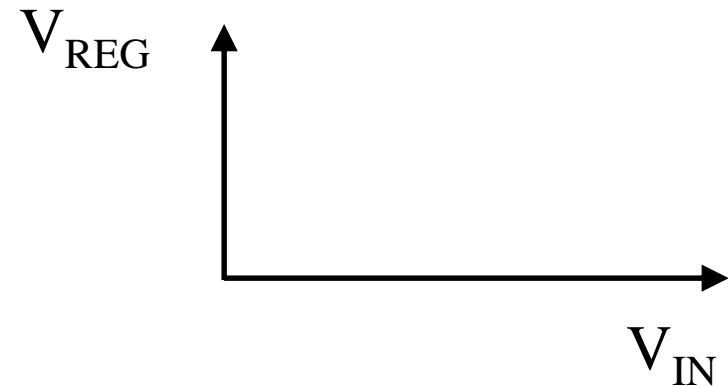



Boost Converter $V_{IN} < V_{REG}$

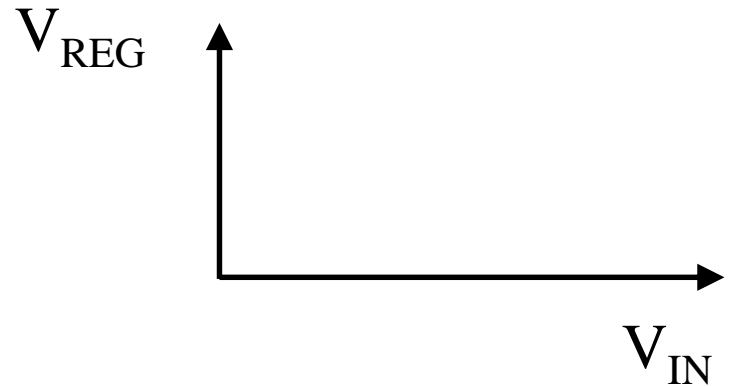

Buck Converter $V_{IN} < V_{REG}$

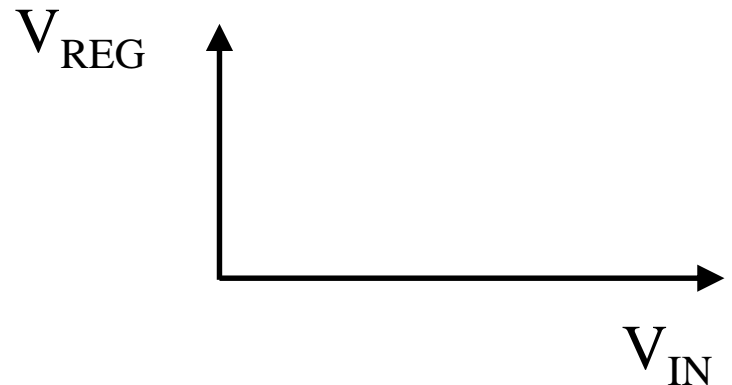


Linear Regulator, e.g. KA378R05

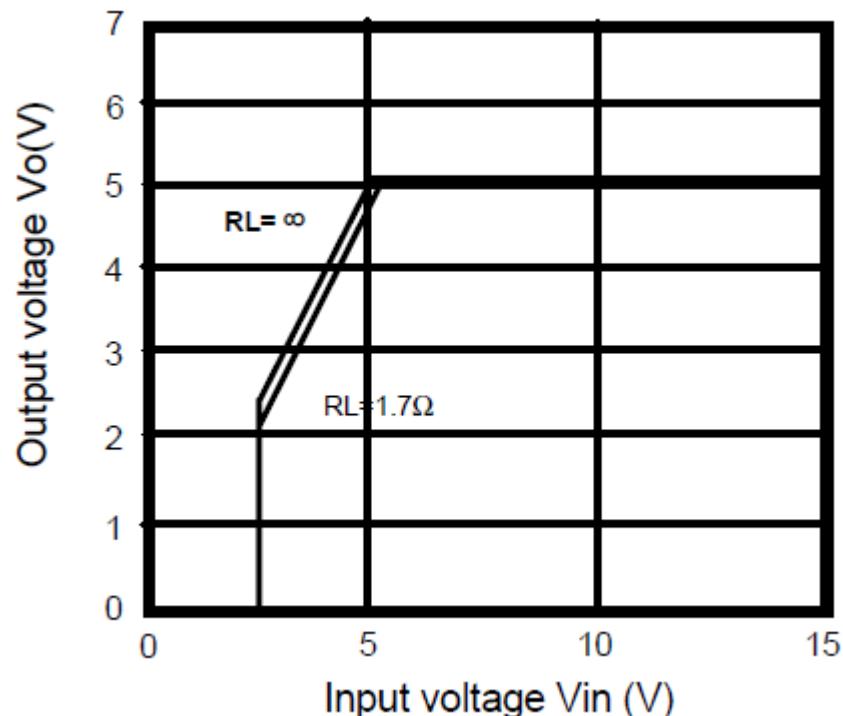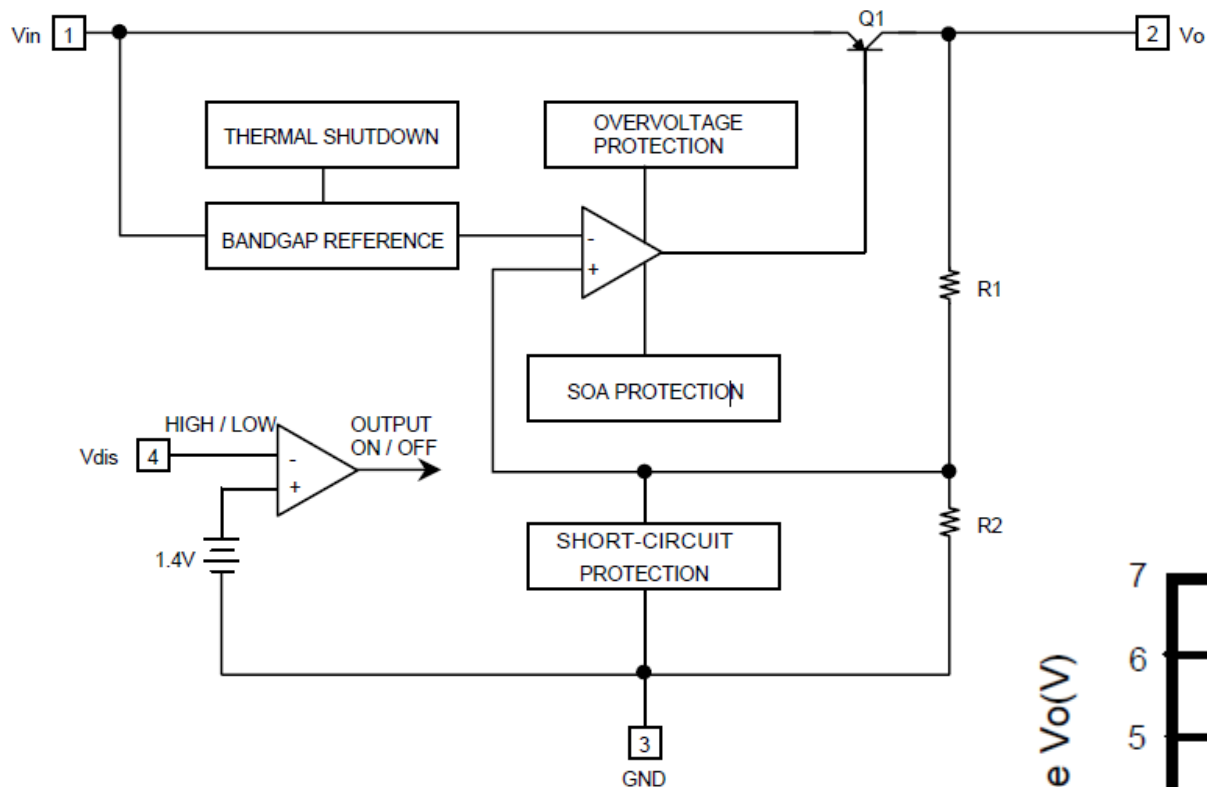

LDO = low drop out
Caution: not all are low drop out

LDO linear regulator LM2940



Typical Application

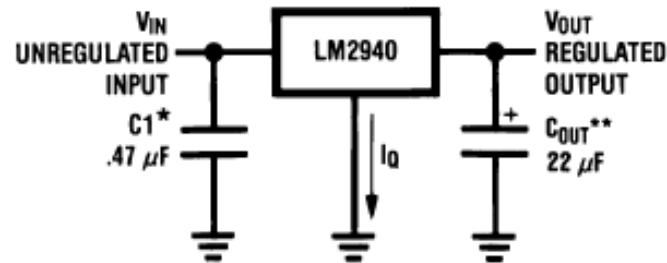

00882203


*Required if regulator is located far from power supply filter.

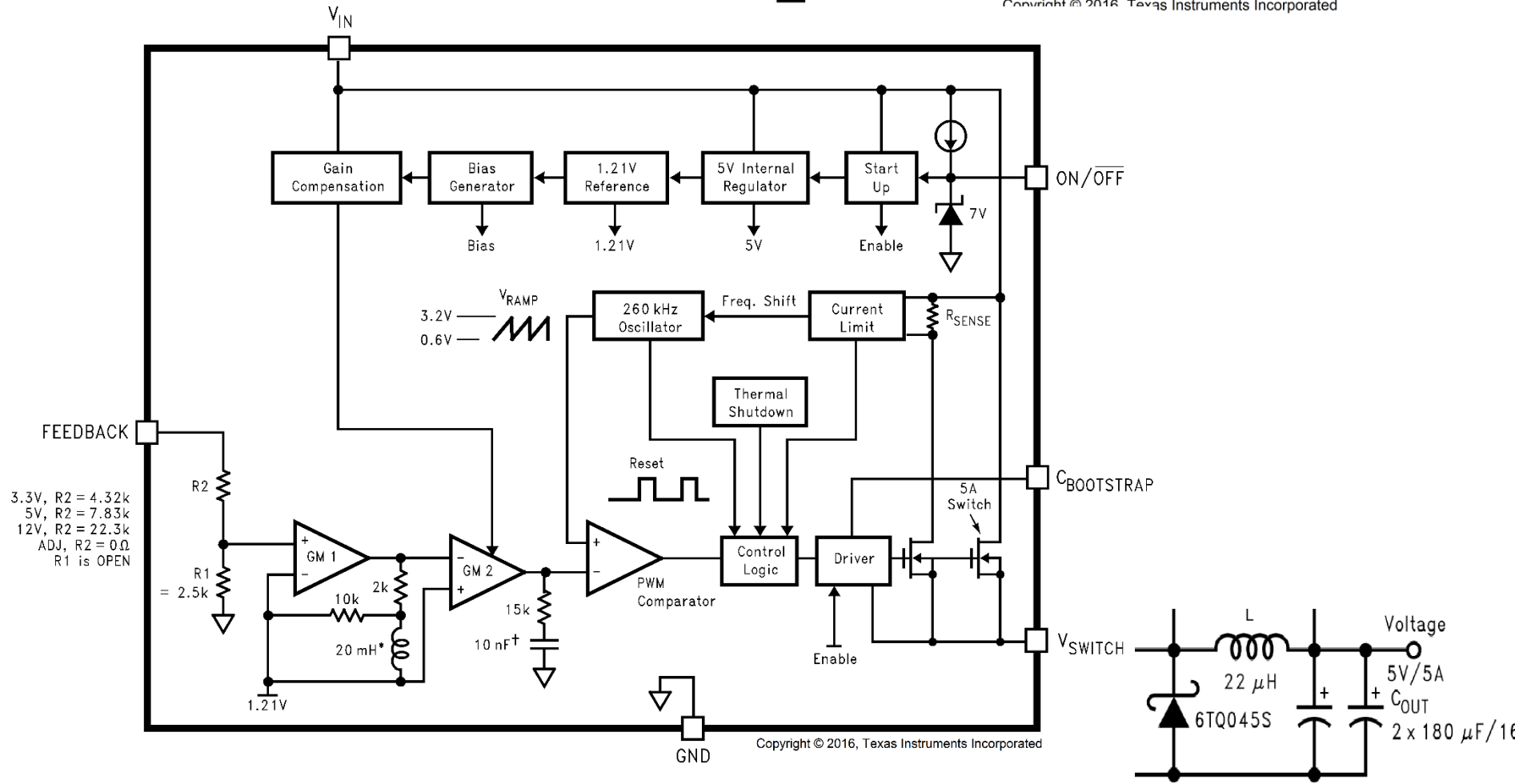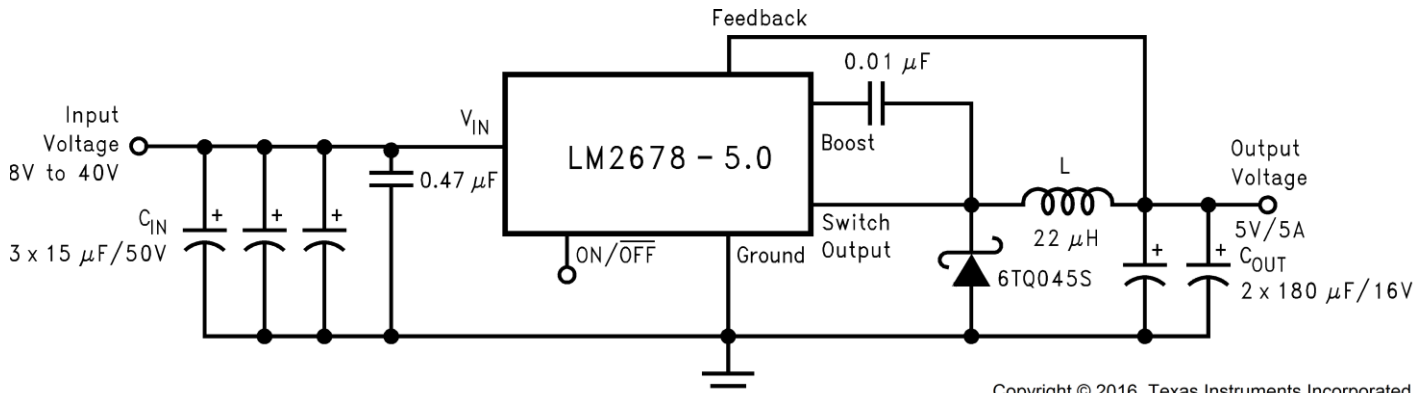** C_{OUT} must be at least $22 \mu F$ to maintain stability. May be increased without bound to maintain regulation during transients. Locate as close as possible to the regulator. This capacitor must be rated over the same operating temperature range as the regulator and the ESR is critical; see curve.





Buck Converter




On-State

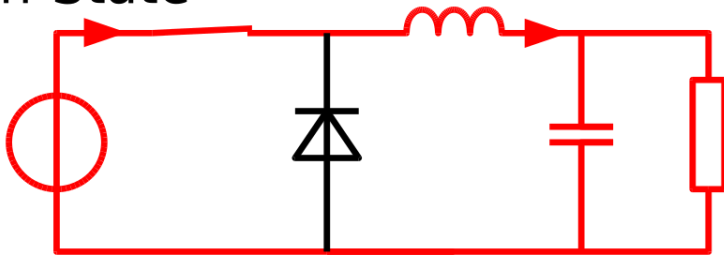

Off-State

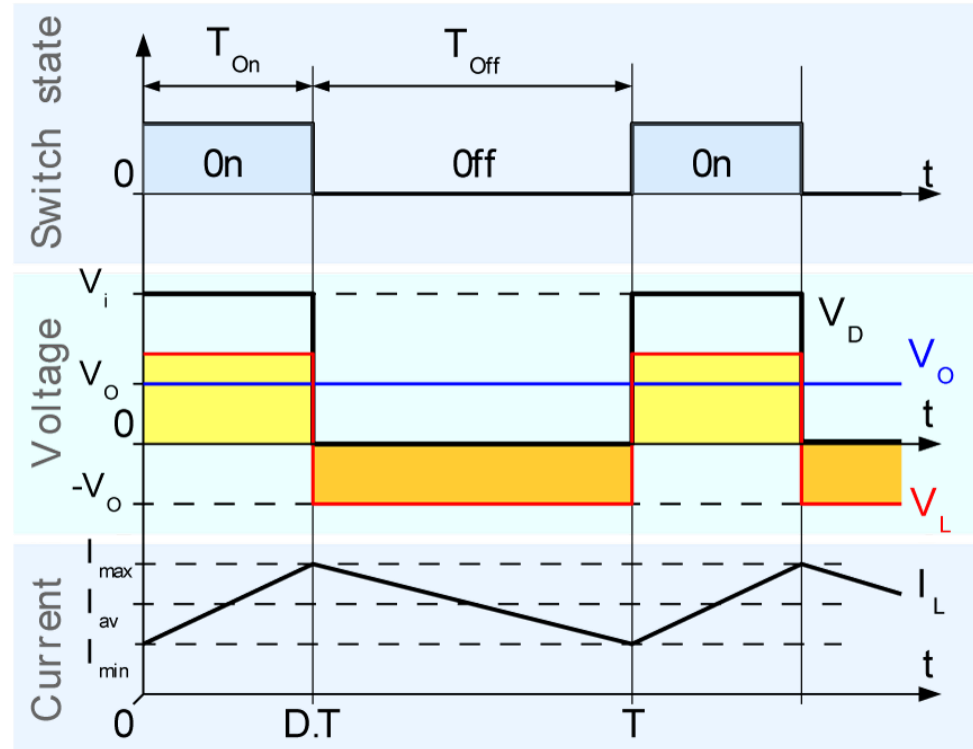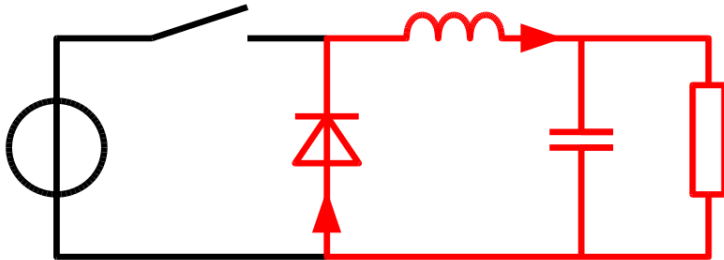

Buck Converter LM2678

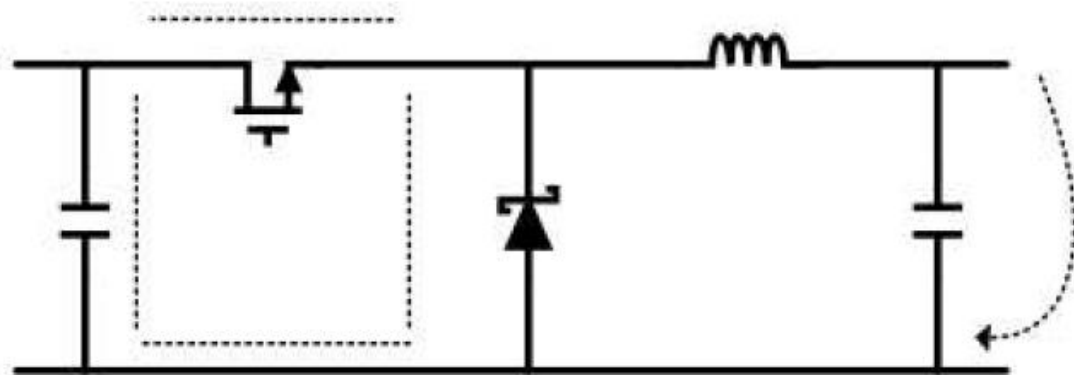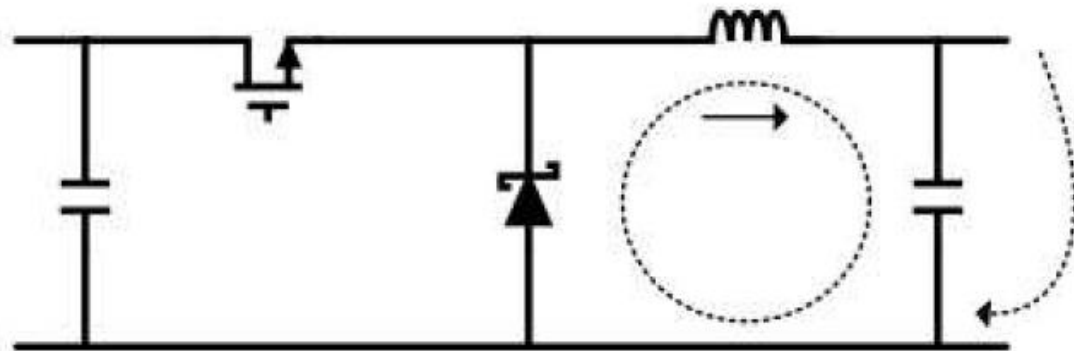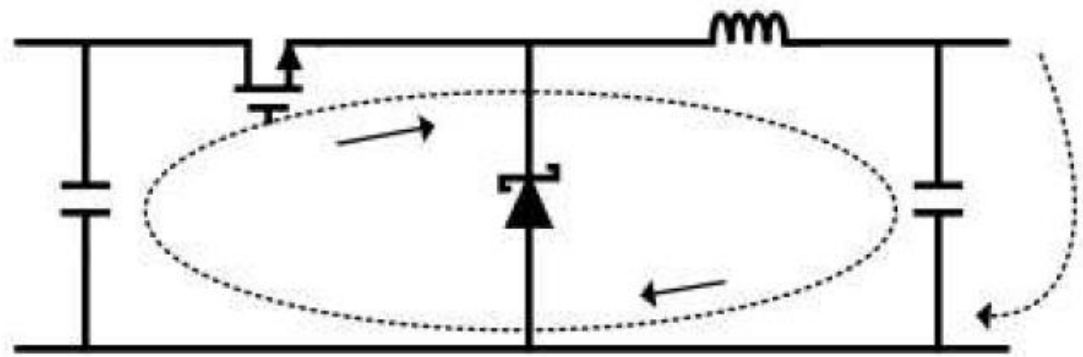

DC-DC Gotchas

- Switch stuck on → 11V LiPo burns out everything
- High peak currents → big conductors, short leads
- 200 kHz radiation into sensor circuits or A/D
- Filter caps: low ESR, low inductance
- Feedback disconnect, noise on feedback line


Lin Reg Gotchas

- Inefficient: need heat sink
- Filter caps: low ESR, low inductance possible instability!


Boost Converter- LT1370

LT1370

BLOCK DIAGRAM

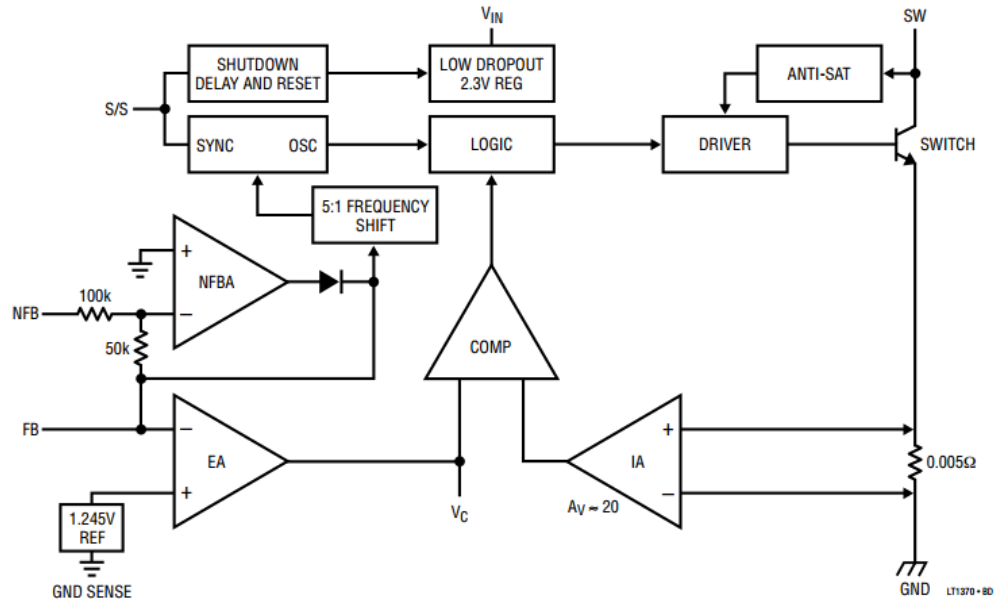


5V to 12V Boost Converter

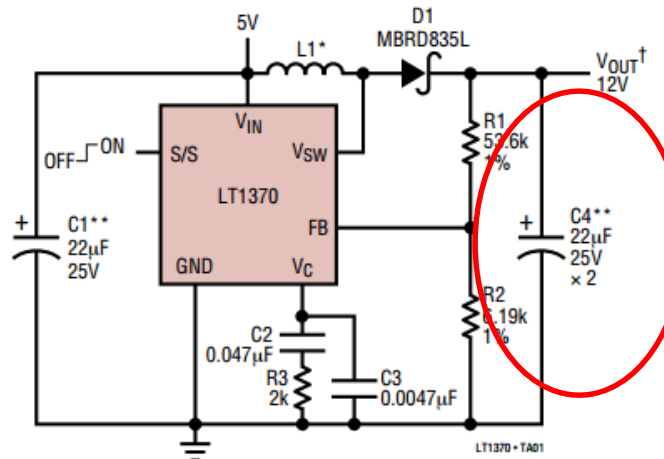

Caution: ESR!
Need special cap

Boost Converter

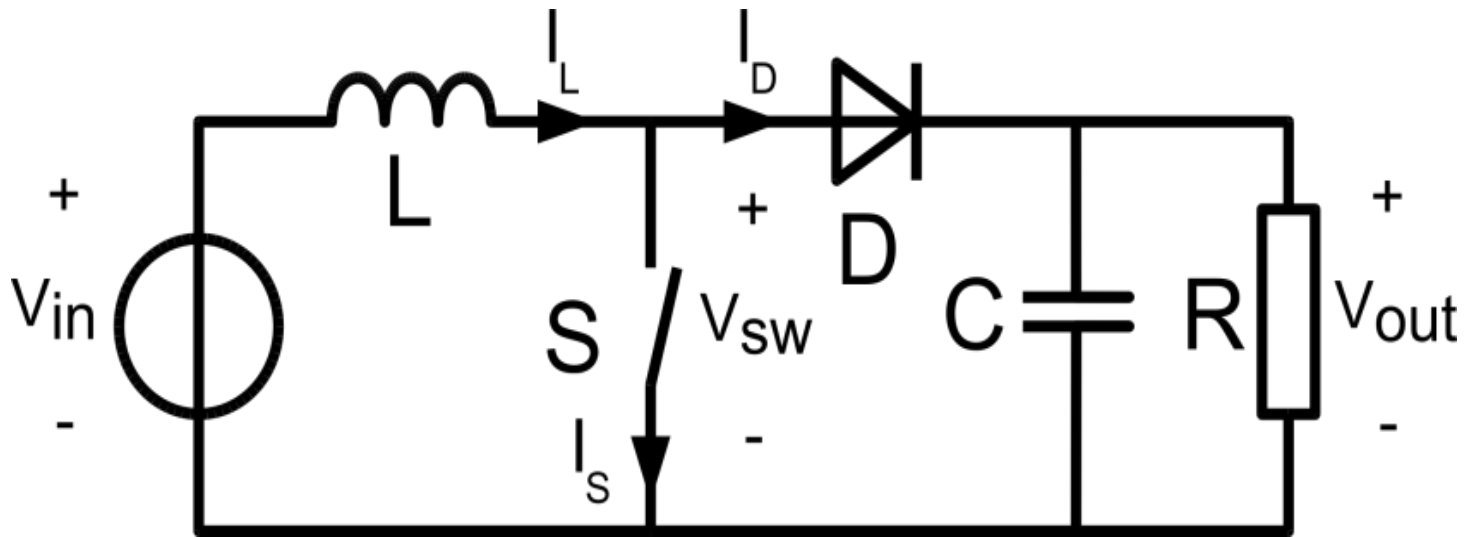

Waveforms on board
(also see boost
converter notes)