

EECS 192: Mechatronics Design Lab

Discussion 4: Power Systems

written by: Richard "Ducky" Lin 📧 Spring 2015


8 & 9 Feb 2017 (Week 4)

- SMPS Recap
- Practical Application
- Summary

Switching Power Supply Recap

Boost Converter Circuit

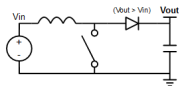
- ▶ DC-to-DC switching power supply generating output voltage higher than input
- ▶ Uses inductor as storage element
- ▶ Efficient, no losses in ideal case
 - ▶ Non-idealities: wire resistance, diode and transistor losses
- ▶ Capacitive filter to smooth output voltage



Boost Converter

Boost Converter Operation

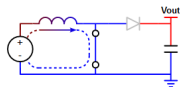
- ▶ Inductor charges when switch is closed
 - ▶ Energy stored in inductor by magnetic field, current through inductor increases
 - ▶ Diode prevents higher output voltage from flowing back to source



Switch Closed

Boost Converter Operation


- ▶ Inductor charges when switch is closed
 - ▶ Energy stored in inductor by magnetic field, current through inductor increases
 - ▶ Diode prevents higher output voltage from flowing back to source
- ▶ Inductor discharges when switch is open
 - ▶ Magnetic field dissipates, current through inductor decreases
 - ▶ Inductor voltage polarity reversed, generating voltage over input
 - ▶ Current flows through diode, output capacitor charged

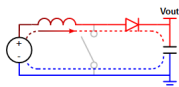


Switch Open

Boost Converter Control

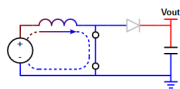- ▶ If switch cycled fast enough, inductor does not fully discharge
- ▶ Can do a lot of math, but output voltage is function of duty cycle D
 - ▶ $V_{out} = \frac{1}{1-D} V_{in}$




Inductor charging

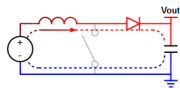

Inductor discharging

Check your Understanding (Live Demo Edition!)

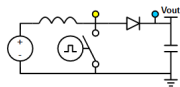
- ▶ So I've got a boost converter set up...
 - ▶ One probe on the switch
 - ▶ Another probe on the output
- ▶ It's running at steady-state



Boost Circuit

Check your Understanding (Live Demo Edition!)

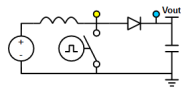
- ▶ So I've got a boost converter set up...
 - ▶ One probe on the switch
 - ▶ Another probe on the output
- ▶ It's running at steady-state
- ▶ Which scope waveform is the switch?



Boost Circuit

Check your Understanding (Live Demo Edition!)

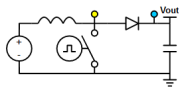
- ▶ So I've got a boost converter set up...
 - ▶ One probe on the switch
 - ▶ Another probe on the output
- ▶ It's running at steady-state
- ▶ Which scope waveform is the switch?
- ▶ Is the output waveform what you expect?



Boost Circuit

Check your Understanding (Live Demo Edition!)

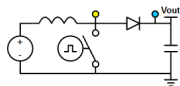
- ▶ So I've got a boost converter set up...
 - ▶ One probe on the switch
 - ▶ Another probe on the output
- ▶ It's running at steady-state
- ▶ Which scope waveform is the switch?
- ▶ Is the output waveform what you expect?
- ▶ On the switch waveform...
 - ▶ Which part is the switch closed?



Boost Circuit

Check your Understanding (Live Demo Edition!)

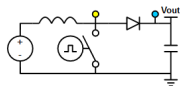
- ▶ So I've got a boost converter set up...
 - ▶ One probe on the switch
 - ▶ Another probe on the output
- ▶ It's running at steady-state
- ▶ Which scope waveform is the switch?
- ▶ Is the output waveform what you expect?
- ▶ On the switch waveform...
 - ▶ Which part is the switch closed?
 - ▶ Which part is the switch opened?



Boost Circuit

Check your Understanding (Live Demo Edition!)

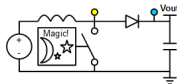
- ▶ So I've got a boost converter set up...
 - ▶ One probe on the switch
 - ▶ Another probe on the output
- ▶ A magic chip regulates the output to 12v
 - ▶ Duty cycle is adjusted to maintain voltage
 - ▶ Remember: $V_{out} = \frac{1}{1-D} V_{in}$
- ▶ What happens if I...



Boost Circuit

Check your Understanding (Live Demo Edition!)

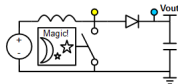
- ▶ So I've got a boost converter set up...
 - ▶ One probe on the switch
 - ▶ Another probe on the output
- ▶ A magic chip regulates the output to 12v
 - ▶ Duty cycle is adjusted to maintain voltage
 - ▶ Remember: $V_{out} = \frac{1}{1-D} V_{in}$
- ▶ What happens if I...
 - ▶ Increase the input voltage?



Boost Circuit

Check your Understanding (Live Demo Edition!)

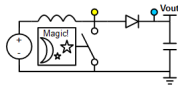
- ▶ So I've got a boost converter set up...
 - ▶ One probe on the switch
 - ▶ Another probe on the output
- ▶ A magic chip regulates the output to 12v
 - ▶ Duty cycle is adjusted to maintain voltage
 - ▶ Remember: $V_{out} = \frac{1}{1-D} V_{in}$
- ▶ What happens if I...
 - ▶ Increase the input voltage?
 - ▶ Duty cycle decreases, current decreases



Boost Circuit

Check your Understanding (Live Demo Edition!)

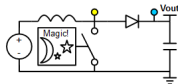
- ▶ So I've got a boost converter set up...
 - ▶ One probe on the switch
 - ▶ Another probe on the output
- ▶ A magic chip regulates the output to 12v
 - ▶ Duty cycle is adjusted to maintain voltage
 - ▶ Remember: $V_{out} = \frac{1}{1-D} V_{in}$
- ▶ What happens if I...
 - ▶ Increase the input voltage?
 - ▶ Duty cycle decreases, current decreases
 - ▶ Decrease the input voltage?



Boost Circuit

Check your Understanding (Live Demo Edition!)


- ▶ So I've got a boost converter set up...
 - ▶ One probe on the switch
 - ▶ Another probe on the output
- ▶ A magic chip regulates the output to 12v
 - ▶ Duty cycle is adjusted to maintain voltage
 - ▶ Remember: $V_{out} = \frac{1}{1-D} V_{in}$
- ▶ What happens if I...
 - ▶ Increase the input voltage?
 - ▶ Duty cycle decreases, current decreases
 - ▶ Decrease the input voltage?
 - ▶ Duty cycle increases, current increases

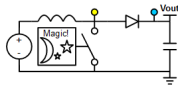

Boost Circuit

Buck Converter Circuit (for your reference)

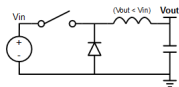- ▶ DC-to-DC switching power supply generating output voltage *lower* than input
- ▶ Similar principle to boost converter
 - ▶ $V_{out} = DV_{in}$
- ▶ Also exists buck-boost converters, where output can be greater than, equal to, or less than the input



Buck Converter

Questions?

got it?

power supply pros, right?


Practical Application

Automatic Feedback Control


- ▶ So, what is the switch-controlling magic?
- ▶ Feedback control: chip has logic to regulate the voltage on the feedback pin to an internal 1.245v reference
- ▶ Pop quiz: what resistor divider do I use to regulate the output to 7.2v?
 - ▶ Use $8.2\text{k}\Omega$ for the lower resistor

LT1370

BLOCK DIAGRAM

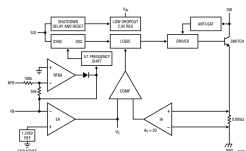

LT1370 Block Diagram

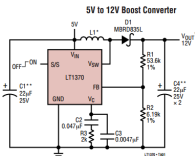

Application circuit


source: datasheet, Linear Technology

Automatic Feedback Control


- ▶ So, what is the switch-controlling magic?
- ▶ Feedback control: chip has logic to regulate the voltage on the feedback pin to an internal 1.245v reference
- ▶ Pop quiz: what resistor divider do I use to regulate the output to 7.2v?
 - ▶ Use $8.2\text{k}\Omega$ for the lower resistor
 - ▶ ... and $39\text{k}\Omega$ For the higher resistor
 - ▶ Why these numbers? Preferred numbers!

LT1370

BLOCK DIAGRAM

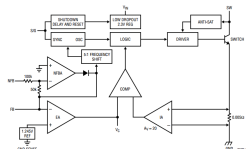

LT1370 Block Diagram

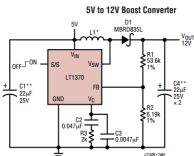


Application circuit

source: datasheet, Linear Technology

Noise (Live Demo Edition!)

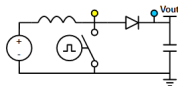
- ▶ Let's take a closer look at the output
 - ▶ Specifically, note the ripple near the switch toggling
- ▶ What issues might this cause?
- ▶ What do you think are some ways to reduce noise?



Boost Circuit

Capacitors at High Frequencies (Live Demo Edition!)

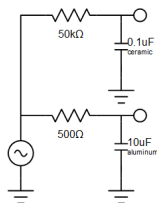
- ▶ Output smoothing is critical for proper operation, depends on output capacitors
- ▶ Not all capacitors are created equal
 - ▶ Ceramic, tantalum, aluminum, ...
- ▶ Live demo
 - ▶ Expect both filters to behave the same:
 $Gain = \frac{1}{\sqrt{1+(\omega RC)^2}}$, $\phi = atan(-\omega RC)$
(gain and phase dependent on only RC)



RC filter demo circuit

Capacitors at High Frequencies (Live Demo Edition!)

- ▶ Output smoothing is critical for proper operation, depends on output capacitors
- ▶ Not all capacitors are created equal
 - ▶ Ceramic, tantalum, aluminum, ...
- ▶ Live demo
 - ▶ Expect both filters to behave the same:
$$\text{Gain} = \frac{1}{\sqrt{1+(\omega RC)^2}}, \phi = \text{atan}(-\omega RC)$$
(gain and phase dependent on only RC)
 - ▶ As frequency increases, behavior diverges
 - ▶ Capacitors become inductive - no longer a good filter

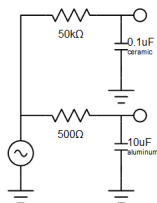

RC filter demo circuit

Layout Guidelines

- ▶ Switching power supplies are layout sensitive
 - ▶ Part placement and routing matters!
- ▶ Tips from the datasheet:
 - ▶ Keep output diode, switch pin, output capacitor as short as possible
 - ▶ Minimize length and area of switch pin
 - ▶ Minimize high frequency current path (switch, diode, capacitor)
- ▶ Read the datasheet!

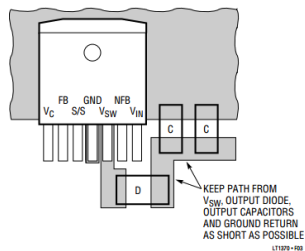


Figure 3. Layout Considerations—R Package

Recommended layout
(uses surface-mount components)

source: datasheet, Linear Technology

Summary

Summary

- ▶ Boost converters step up a DC voltage to a higher DC voltage
- ▶ LT1370 uses feedback control to do voltage regulation
- ▶ Follow recommended layout guidelines during PCB design

Parts Handout

- ▶ Get a battery and charger!
 - ▶ Please, keep explosions and flames to a minimum

Office hours for the rest of the section

- ▶ PCB deadline coming up in a week! Need help? Get it now!
- ▶ Need tips on mechanical fabrication? Get some here!