

Worksheet 1 Solution.

2/6/2015



$$e = k_e \dot{\theta}_m$$


$$\tau = k_z i_m$$

$$k_e = 0.01 \frac{V \cdot s}{\text{rad}}, \quad k_z = 0.1 \frac{N \cdot m}{A}$$

1. unloaded, $\tau = 0, i_m = 0 \Rightarrow e = V_{bat}$
 $k_e \dot{\theta}_m = 6V, \quad \dot{\theta}_m = 600 \text{ rad/sec}$




2. $\dot{\theta}_m = 0, \frac{V_{BAT}}{2\Omega} = 3 \text{ amps} = i_m, \tau = 0.3 \text{ Nm}$
 $V_e = 0$



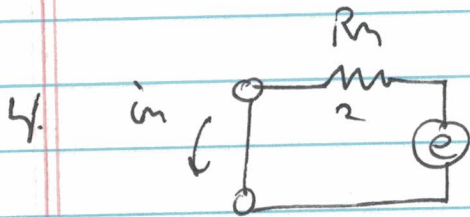
3. $5000 \text{ rpm} = 524 \text{ rad/sec}$, open circuit $V_m = k_e \dot{\theta}_m = 5.24V$



$$i_m = \frac{-5.24V}{2} = -2.62 \text{ amps}$$
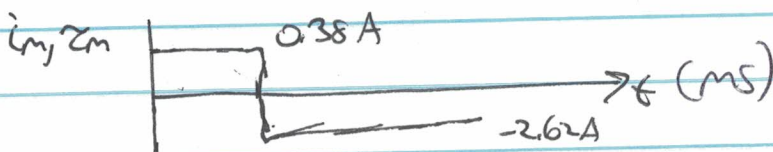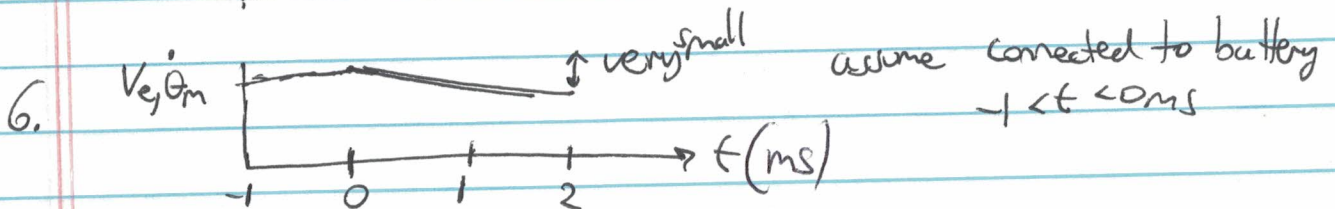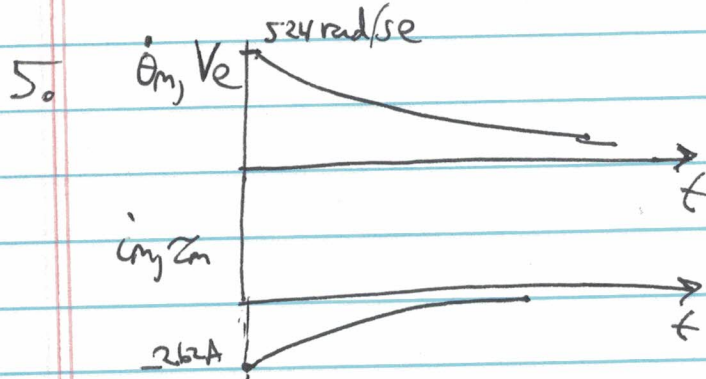
$$\tau = -0.26 \text{ Nm (not braking)}$$



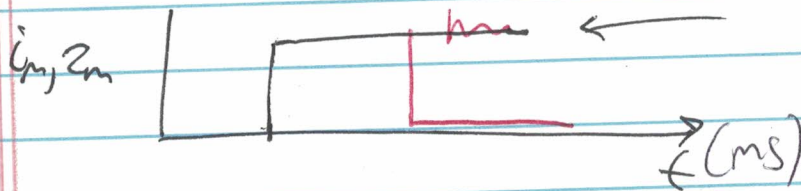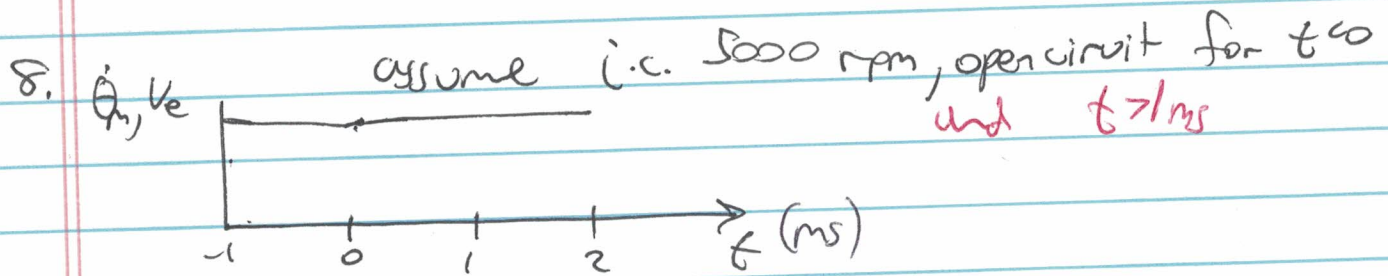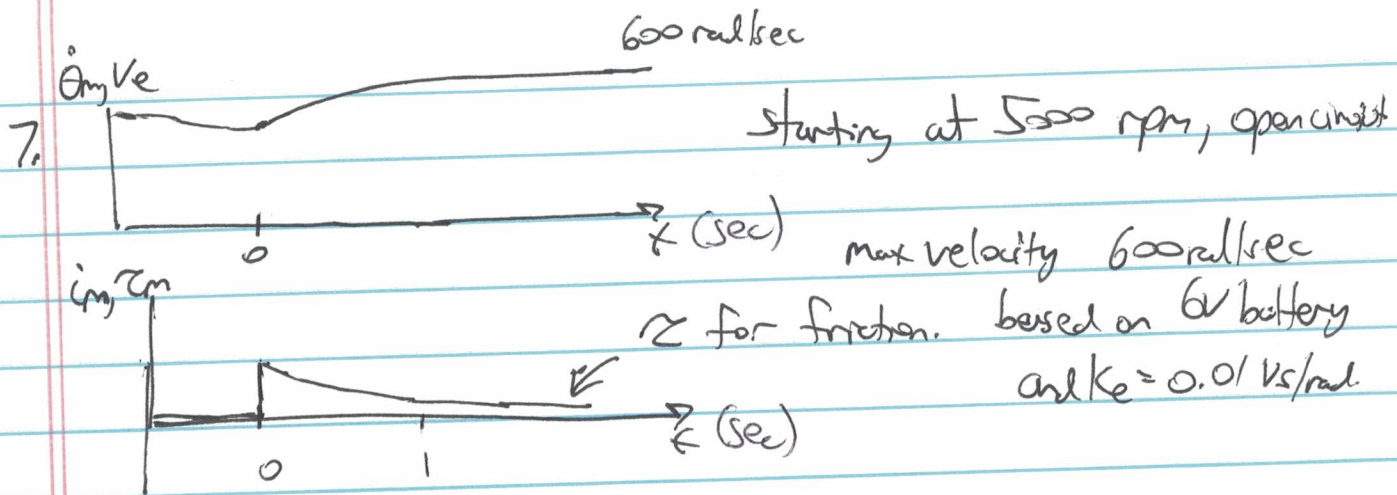

$$i_m = \frac{6V - k_e \dot{\theta}_m}{R_m} = \frac{6V - 5.24V}{2} = 0.38 \text{ amps}$$

$$\tau = 0.038 \text{ N-m}$$