

# EE241B : Advanced Digital Circuits

## Lecture 11 – Flip-Flops

**Borivoje Nikolić**



**February 25, 2020, NY Times: Should robots have a face?**

As automation comes to retail industries, companies are giving machines more humanlike features in order to make them liked, not feared.

# Announcements

- Response to project abstracts sent
  - Please let me know if you didn't receive it
  - Team web pages
  - Be careful not to leak proprietary info (interface tools via Hammer)
- Assignment 2 posted



# Outline

- **Module 3**
  - Design of latches and flip-flops






## 3. Design for Performance

### 3.D Latch Design

# MUX







- 2-input MUX

   

$$g_A = 1.5$$
$$g_{Sel} = 1.5$$


# Transmission Gates

$g_{sel} \Rightarrow$

   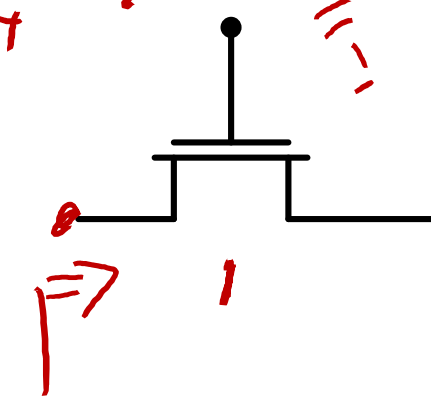  


$R || 2R = \frac{2}{3} R$

# Latch vs. Flip-Flop

 


# Latches


Transmission-Gate Latch

 

Usually without contention

 


C<sup>2</sup>MOS Latch

 




# Latches

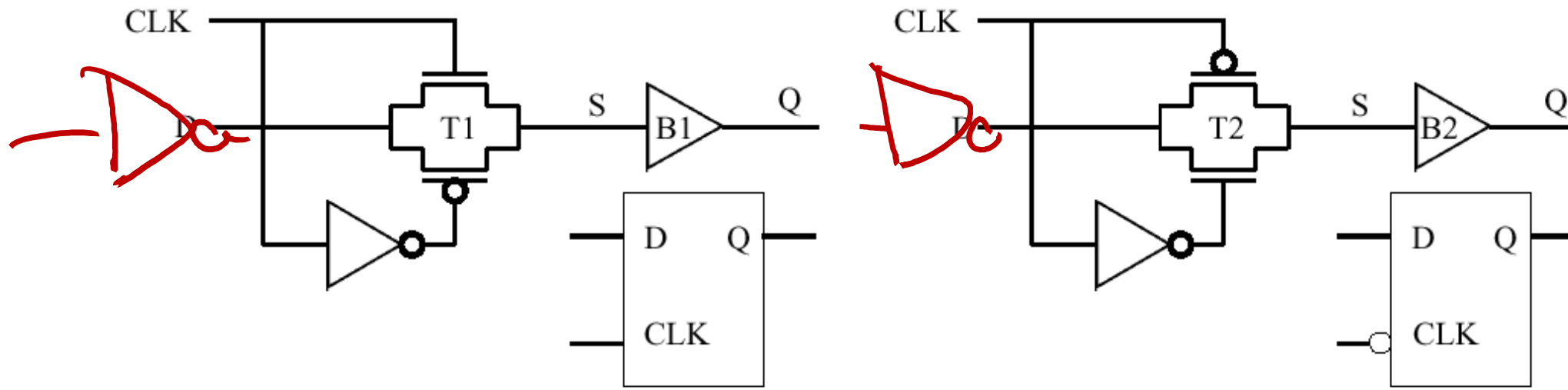

(a) The transparent high latch (THL)

(b) The transparent low latch (TLL)

 


(c) Timing waveforms for the THL
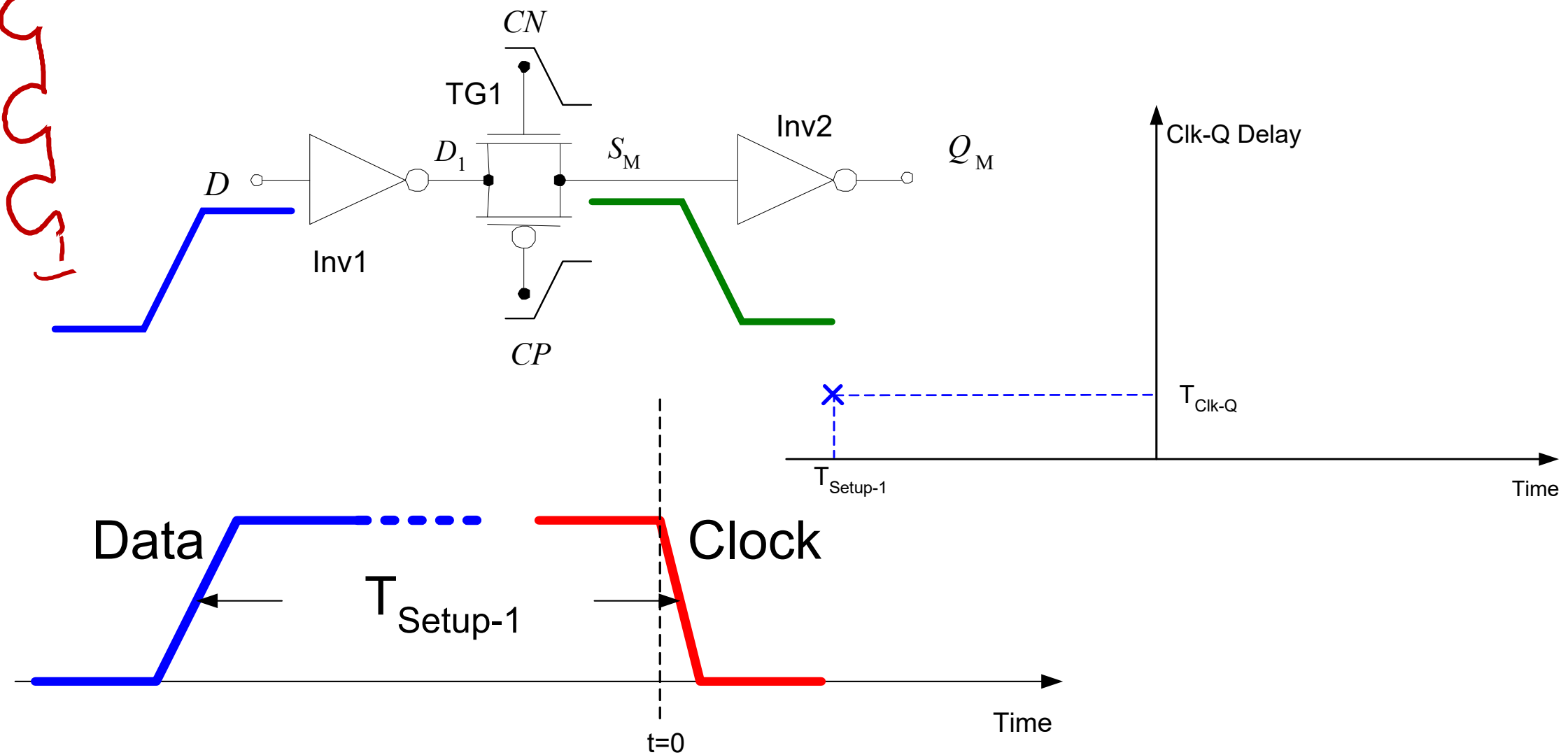
# Setup-Hold Time Illustrations


Setup-1

Circuit before clock arrival (Setup-1 case)




# Setup-Hold Time Illustrations
 
## Circuit before clock arrival (Setup-1 case)




# Setup-Hold Time Illustrations
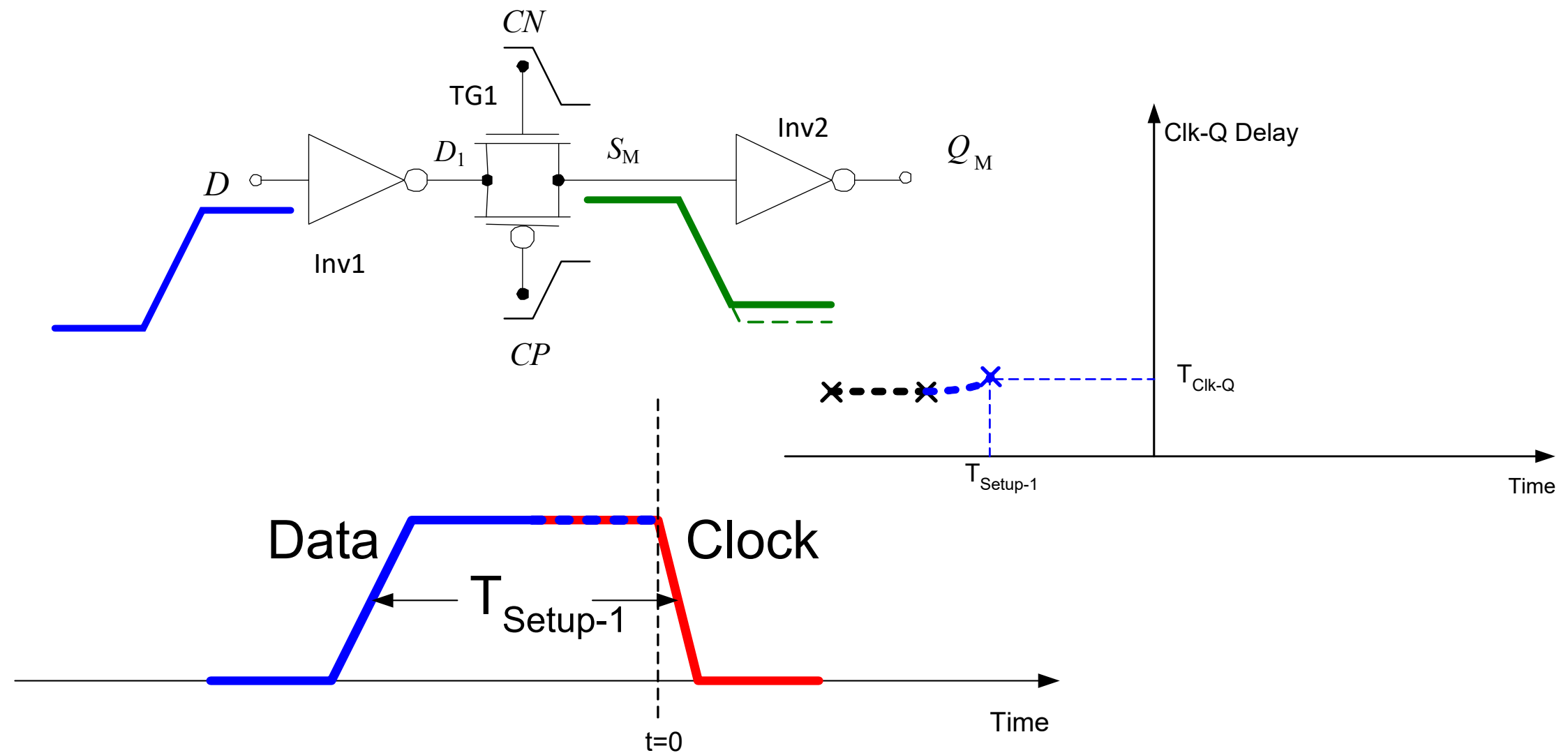
## Circuit before clock arrival (Setup-1 case)




# Setup-Hold Time Illustrations
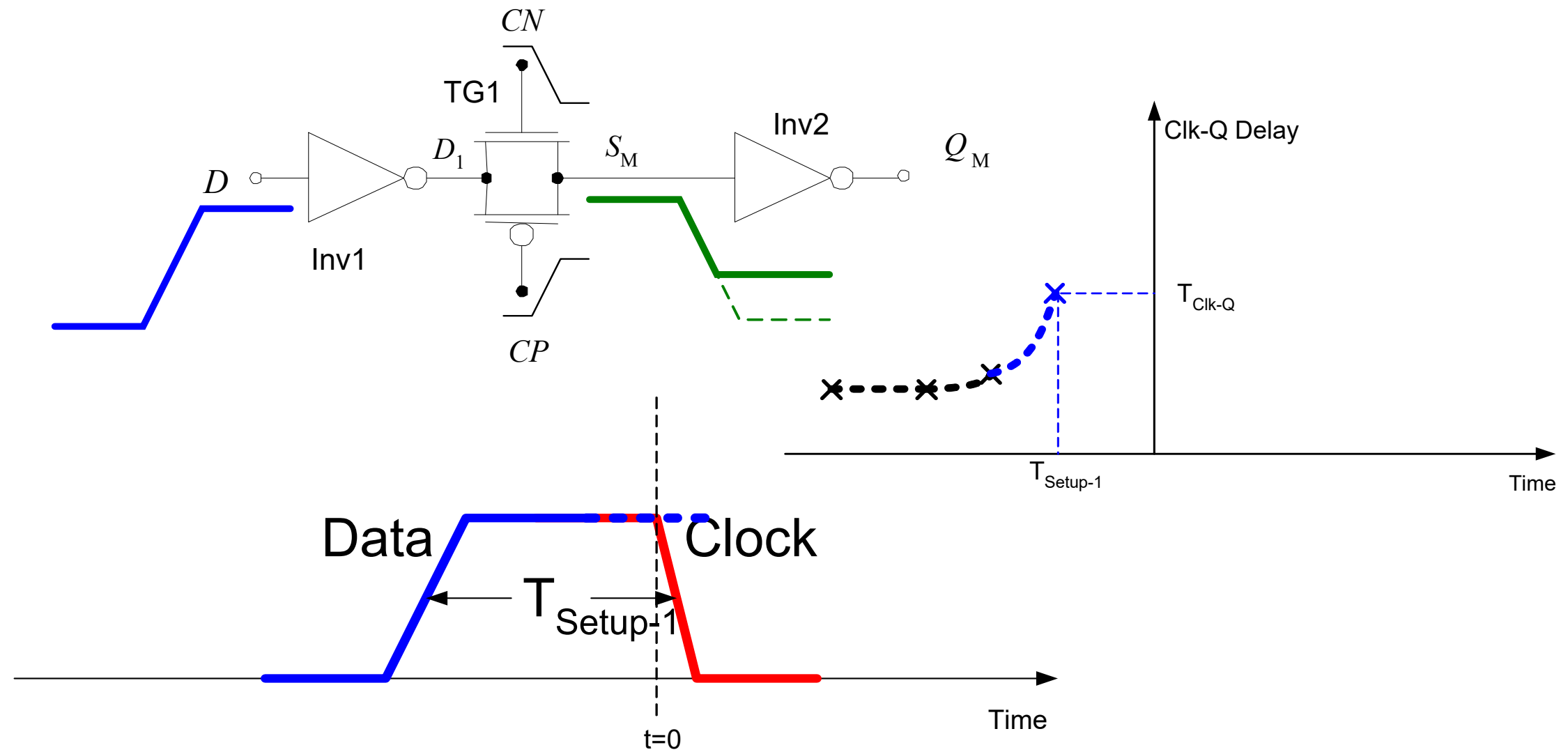
## Circuit before clock arrival (Setup-1 case)




# Setup-Hold Time Illustrations
 
## Circuit before clock arrival (Setup-1 case)




# Setup-Hold Time Illustrations

## Hold-1 case

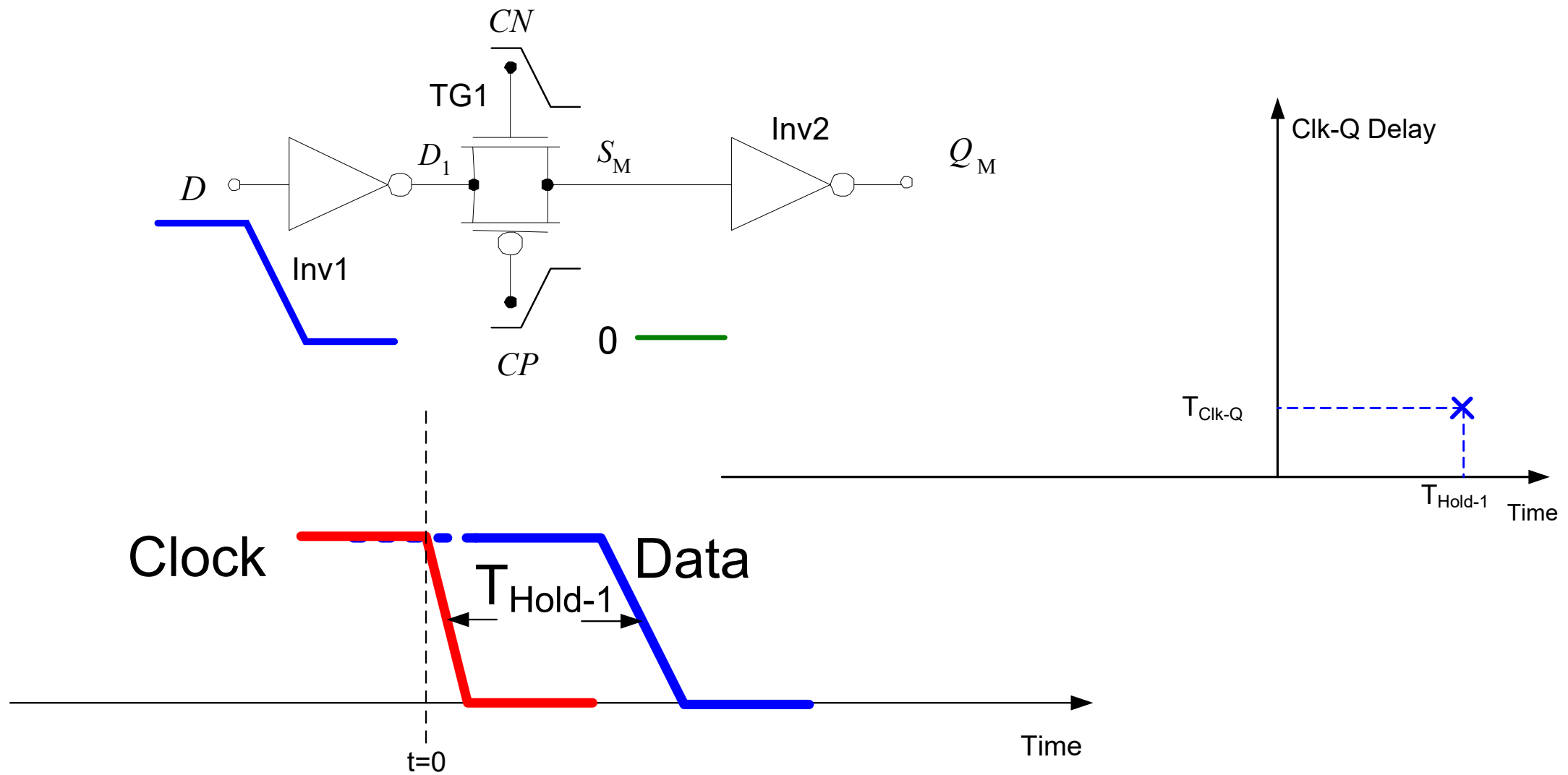

# Setup-Hold Time Illustrations




## Hold-1 case

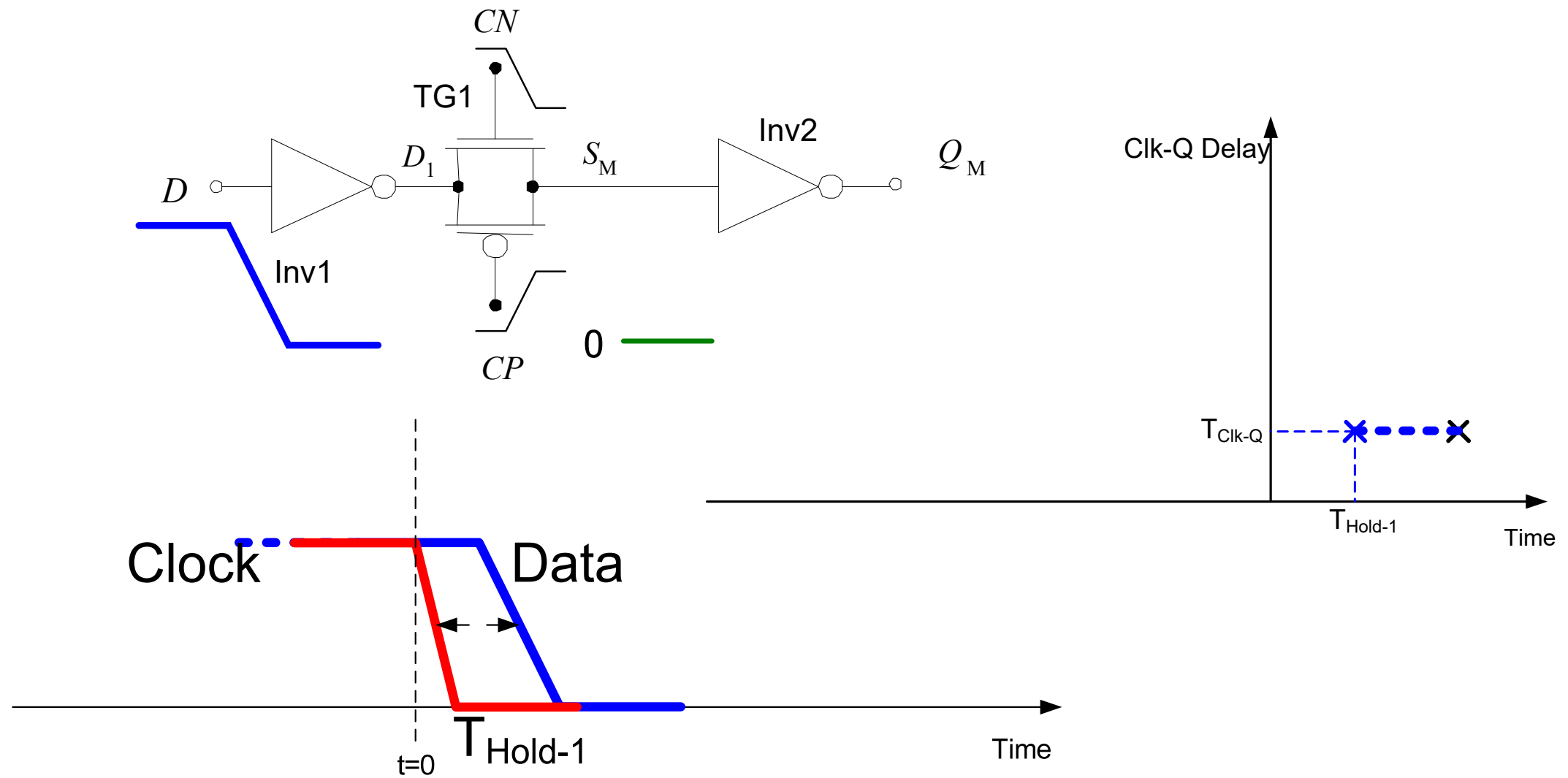




# Setup-Hold Time Illustrations

## Hold-1 case

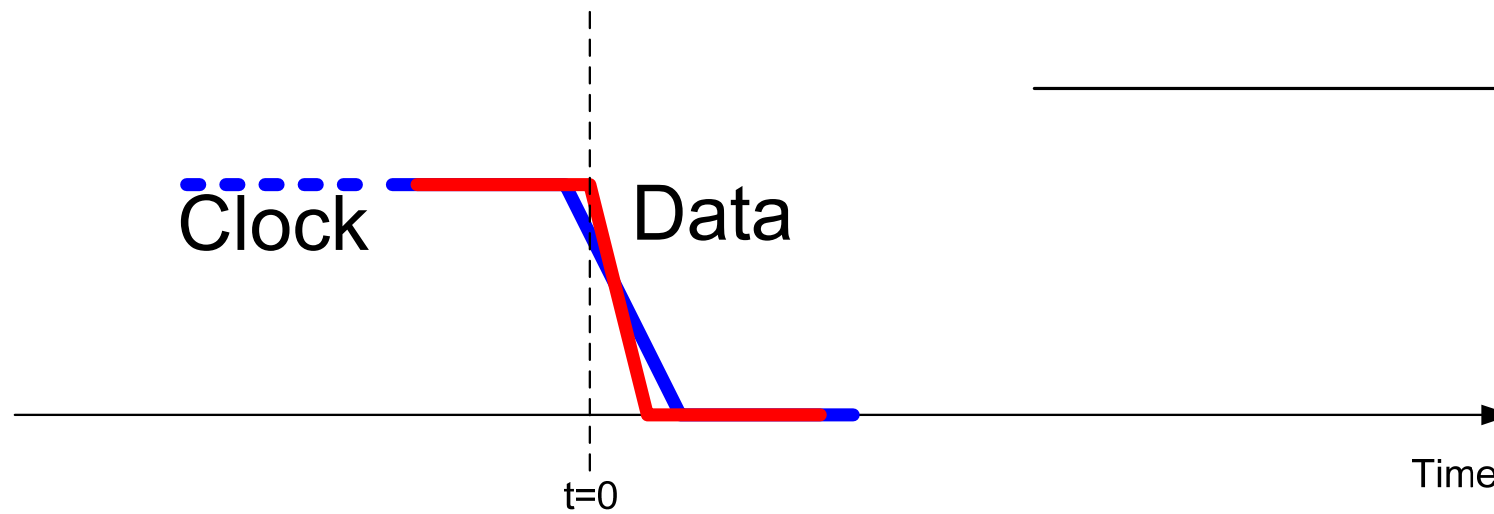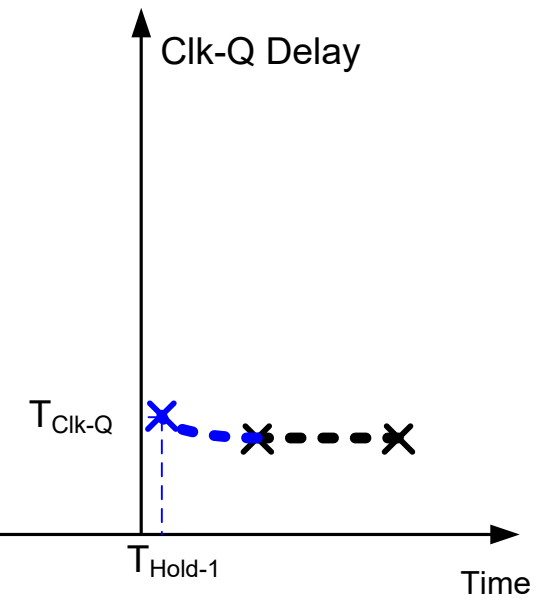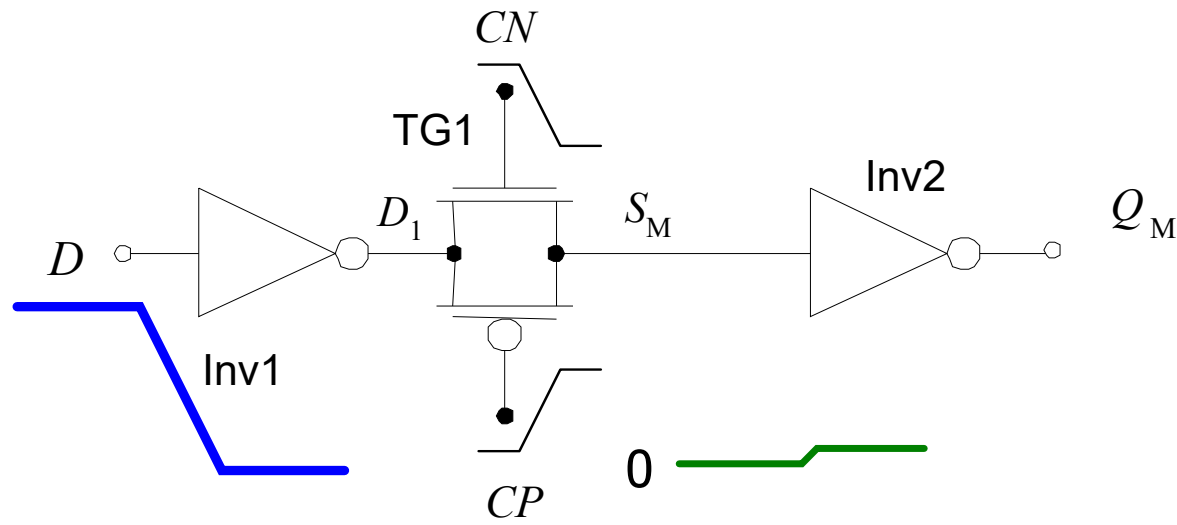


# Setup-Hold Time Illustrations

## Hold-1 case


 


# Setup-Hold Time Illustrations


## Hold-1 case

 


# More Precise Setup Time

  

# Generating Complementary Clocks

 


# Latch $t_{D-Q}$ and $t_{CLK-Q}$

 

$$GF = g_1 \cdot g_2 \cdot g_3 \cdot g_4 = 1.5$$

$$g_A = \sqrt{GF} = \sqrt{1.5} = 1.2$$


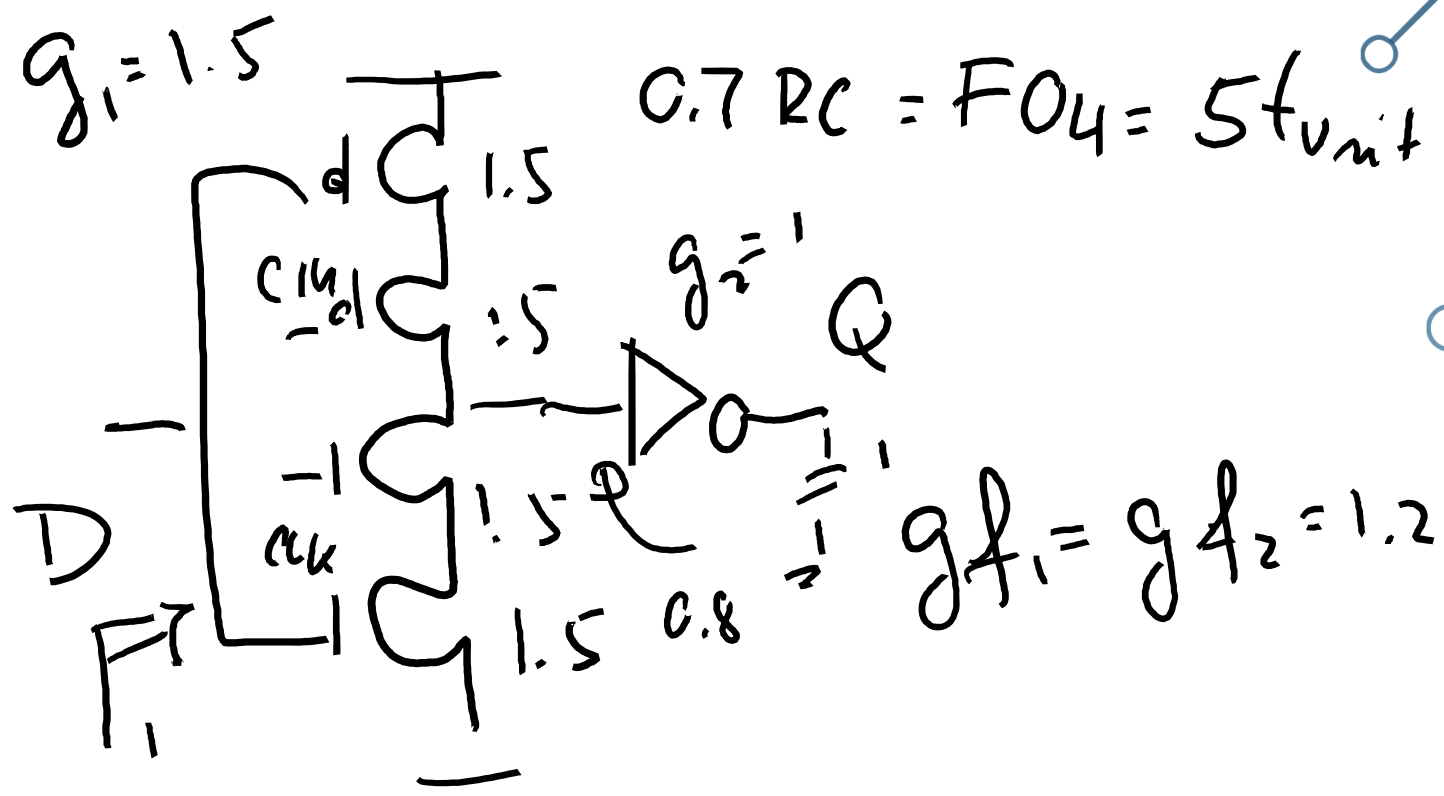


$$t_p = (g_1 \cdot f_1 + g_2 \cdot f_2 + p_1 + p_2) t_{unit}$$

$$= (1.2 + 1.2 + 1.5 + 1) t_{unit}$$

$$= 4.9 t_{unit} = 1 FO4$$

$t_{setup}$

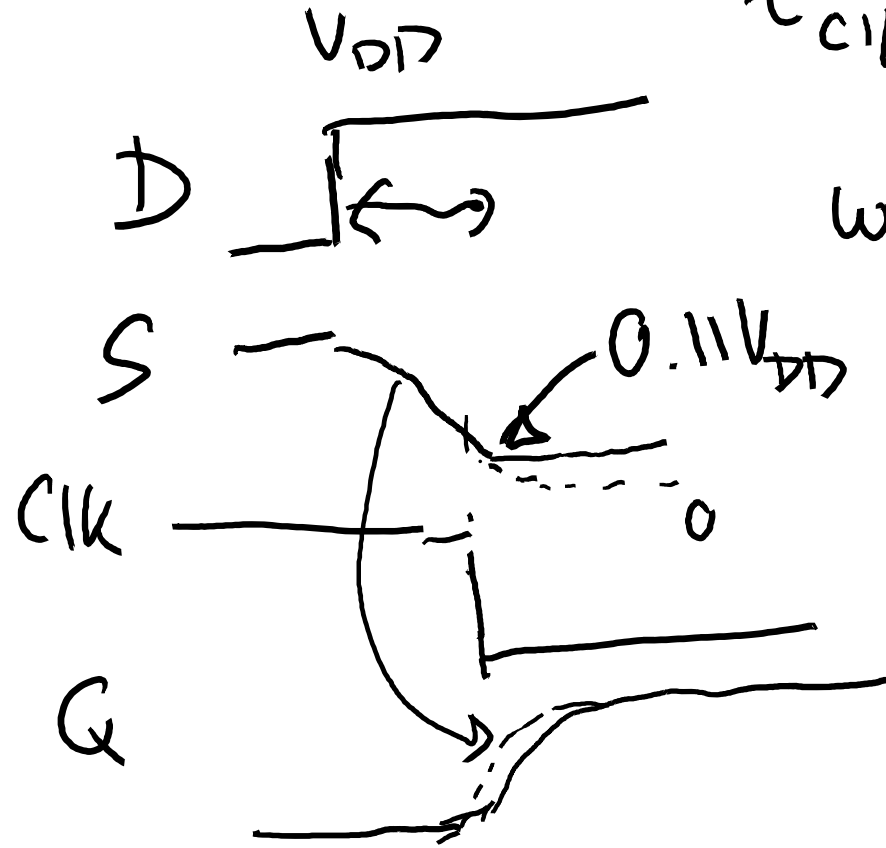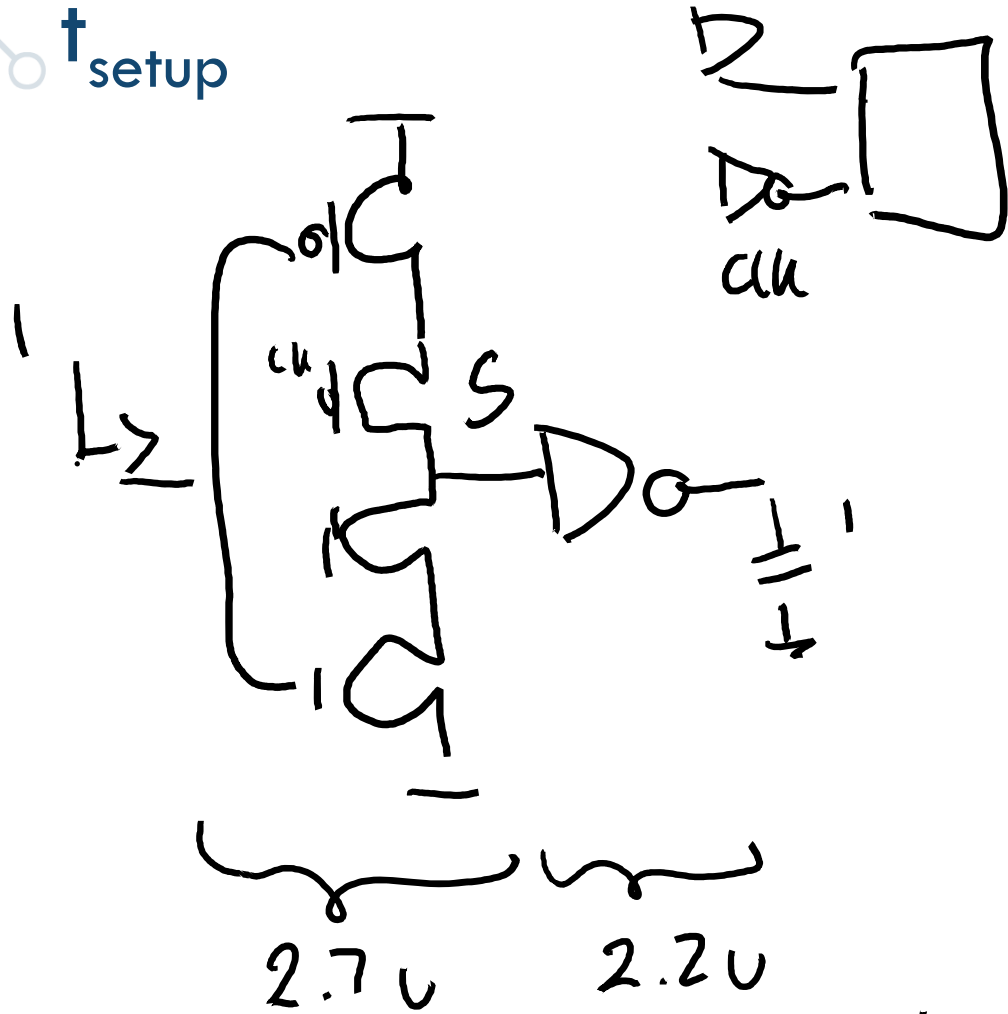

$t_{clk-Q, nom} = 1 FO4$

what  $t_{D-CLK}$  causes

$t_{clk-Q} \rightarrow 1.05 FO4$

$1.05 \times 1 FO4$

$\rightarrow 2.45v$

$t_p, c^2 MOS, 0.5 \rightarrow 0.89 = 2.1 RC = \frac{2.1}{0.7} t_p = 3.2.2 t_v = 1.3 FO4$

$t_{su} = 1.3 FO4$

$t_{DC} = t_{clk-Q} = 1.0 FO4$

## Key Point

- Two ways to design a flip-flop
  - Latch pair
  - Pulsed latch






## 3. Design for Performance

### 3.E Flip-Flop Design

# Latch vs. Flip-Flop

 

# Flip-Flops

- Performance metrics
- Delay metrics
  - Insertion delay
  - Inherent race immunity
  - ‘Softness’ (Clock skew absorption)
  - Inclusion of logic
  - Small (+constant) clock load
- Power/Energy Metrics
  - Power/energy
- Design robustness
  - Noise immunity

$$t_{SU} + t_{CK-Q}$$
$$t_{CK-Q} - t_H$$

# Scan Test

