

EE241B : Advanced Digital Circuits

Lecture 15 – SRAM 3

Borivoje Nikolić



March 11, 2020, EE Times

Startup Ampere Attacks Intel's Strength: Startup Ampere Computing said it is shipping an Arm-based, 80-core processor, a chip it is positioning as the world's first "cloud-native" processor. Called the Altra, it was designed to process the workloads that are typically handled in the cloud, while also drawing significantly less power than the average CPU.

Announcements

- Quiz 2 today
- Project midterm reports due next Thursday (March 19)
- Assignment 3 due next week
- Reading - comprehensive (and optional)
 - Horiguchi, Itoh, *Nanoscale Memory Repair*, Springer, 2011.
 - Itoh, Horiguchi, Tanaka, *Ultra-Low Voltage Nano-Scale Memories*, Springer 2007.

Outline


- **Module 4**
 - SRAM assist techniques
 - Sense amps



 
4.F SRAM Assist Circuits

Basic Ideas

- Dynamically change voltages
- Negative BL helps with writing
- Lower VDD (V_{CELL}) helps with writing
- Higher WL helps with writing, lower hurts
- Lower WL helps with read, higher hurts
- Half-select condition: WL selected for write, but write operation is masked (BLs stay high)



Dynamic V_{DD} Implementation

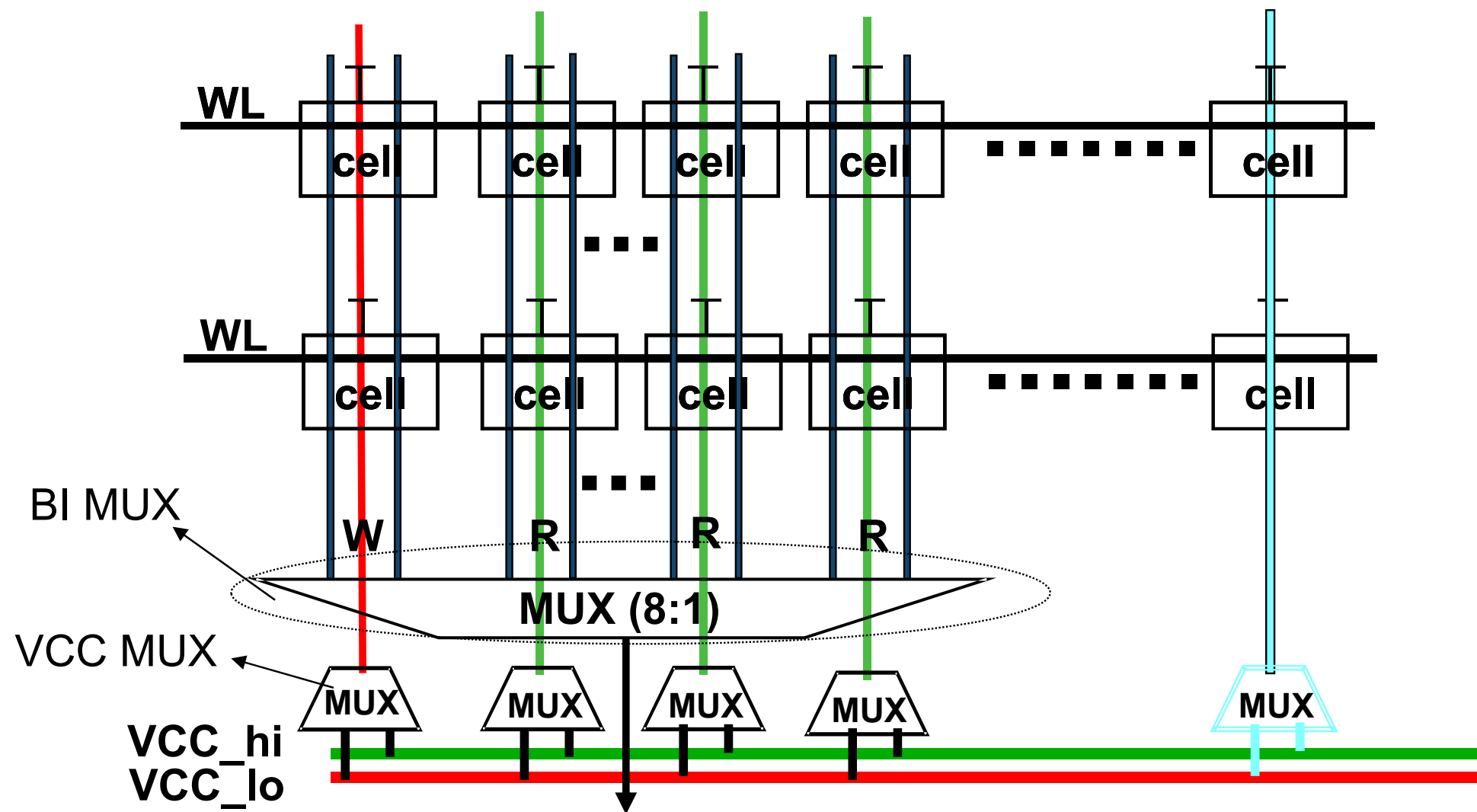


- VCC selection is along column direction to decouple the read & write


Zhang, ISSCC'05

Floating VDD Technique


- W/o second supply

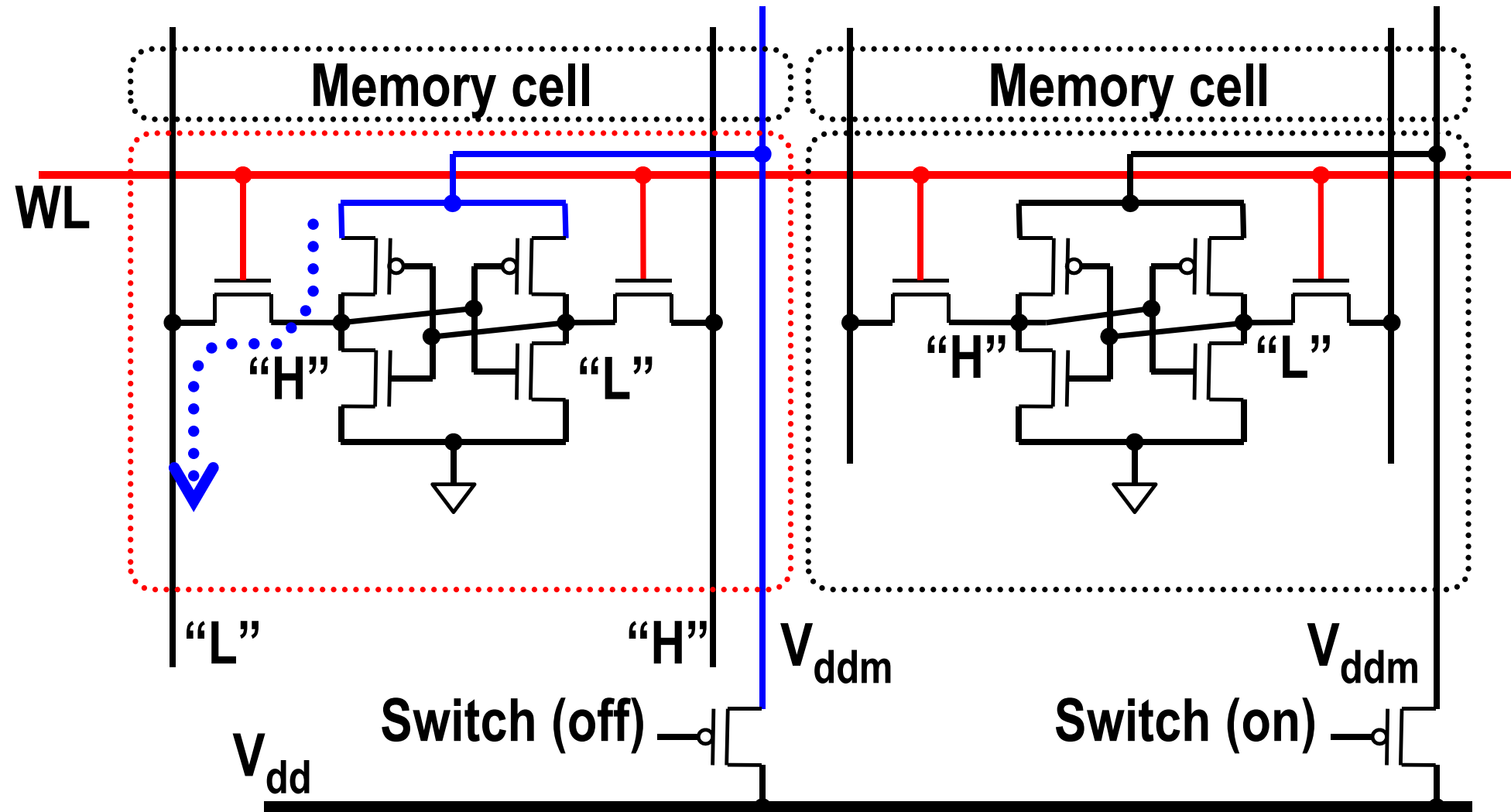


Collapsing V_{DD} Technique

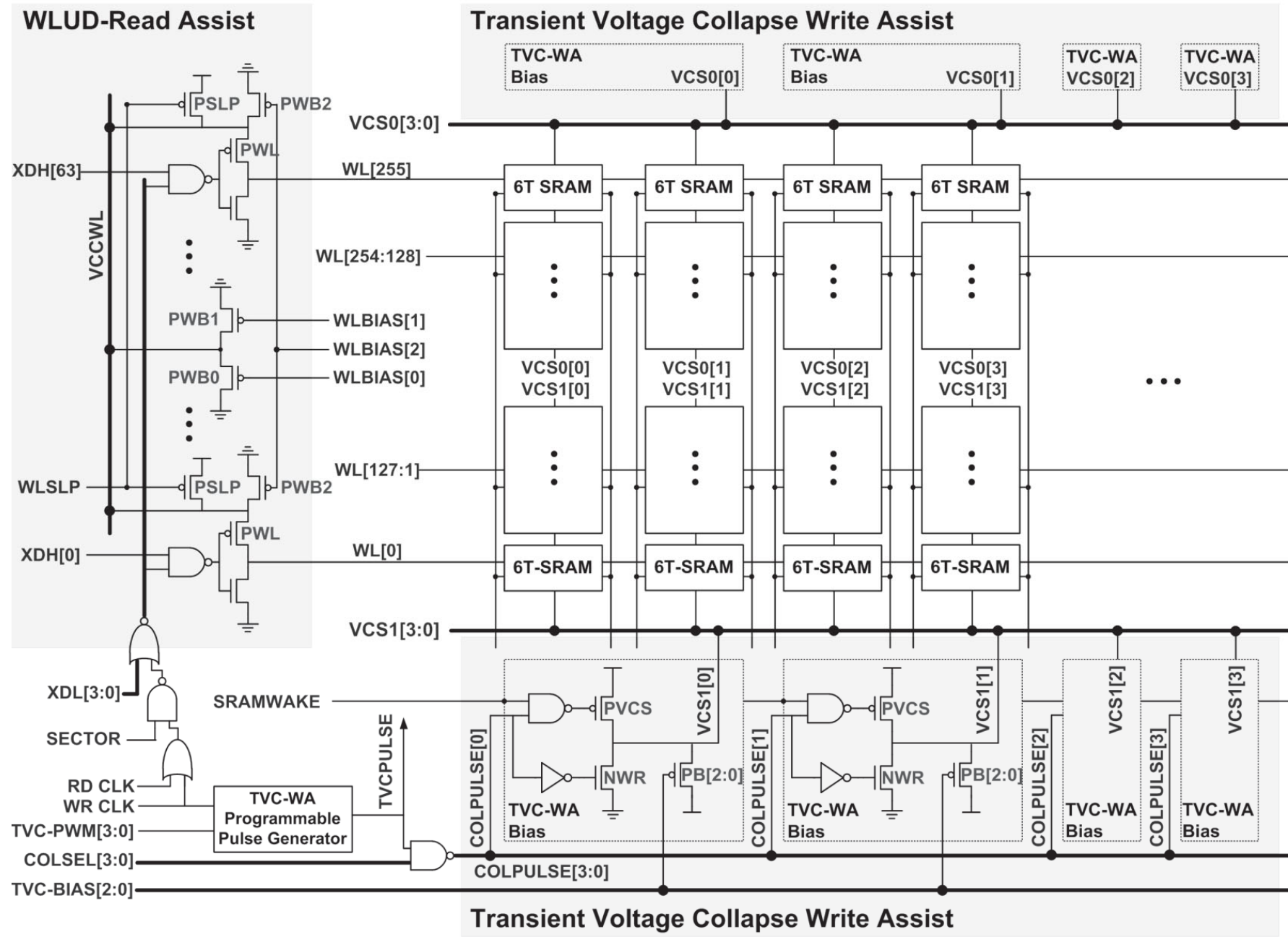

Collapsing V_{DD} Technique


 


Negative BL

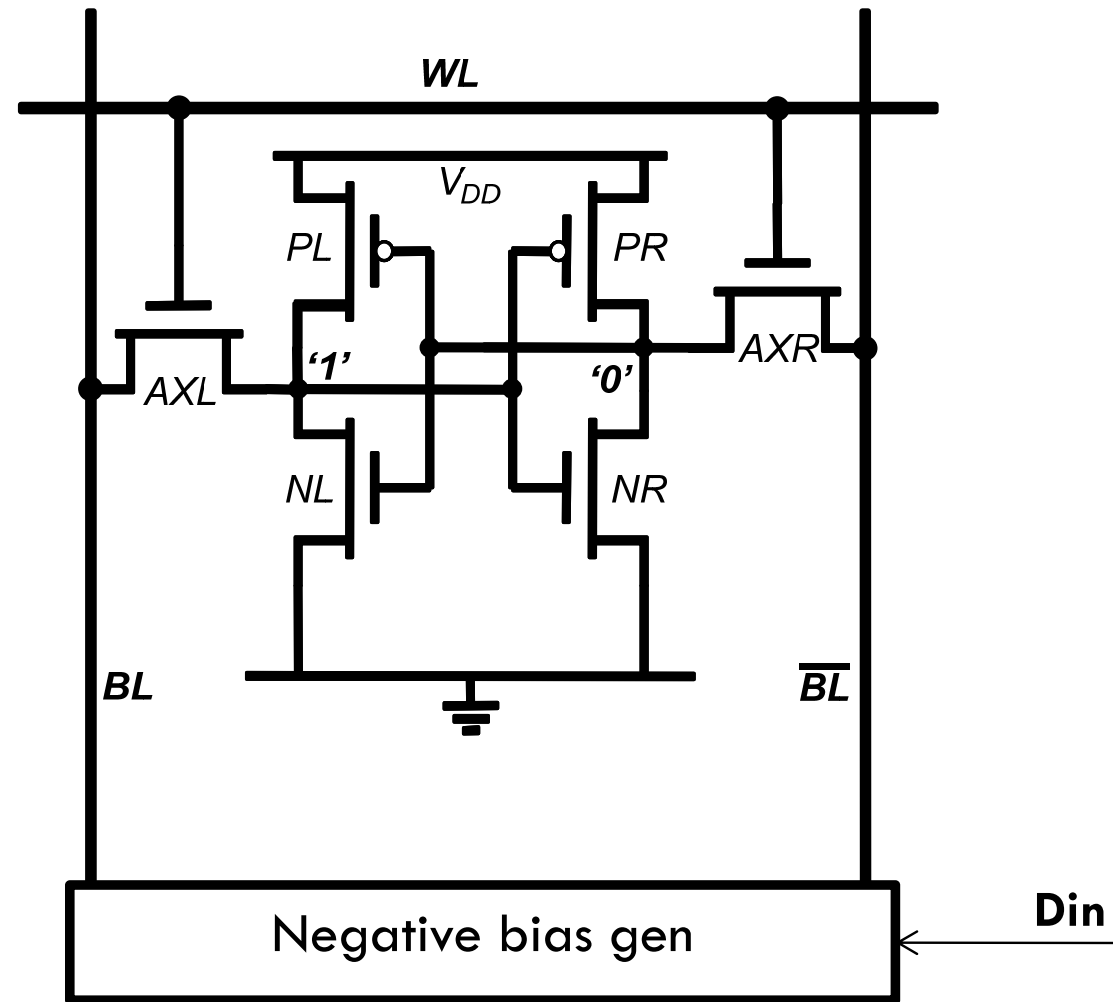

Nii, VLSI'08


Negative BL

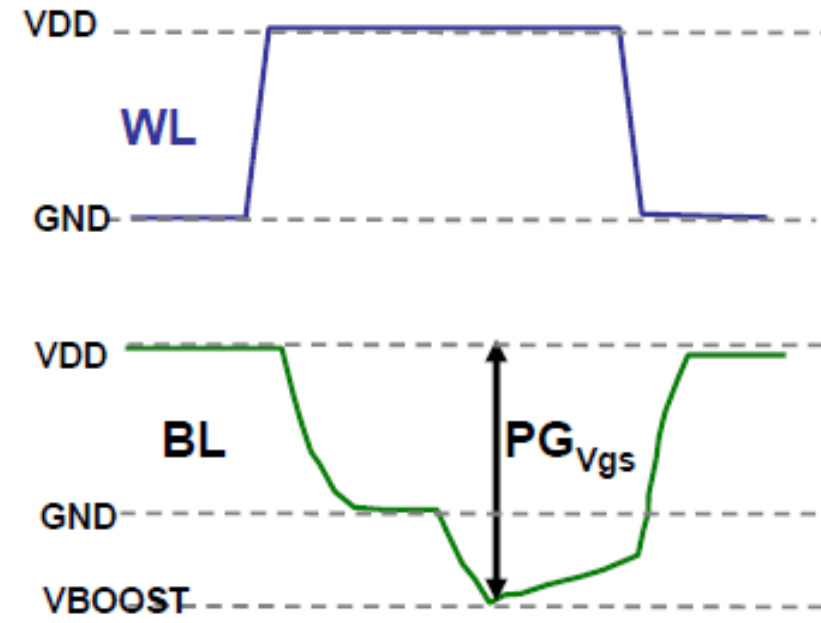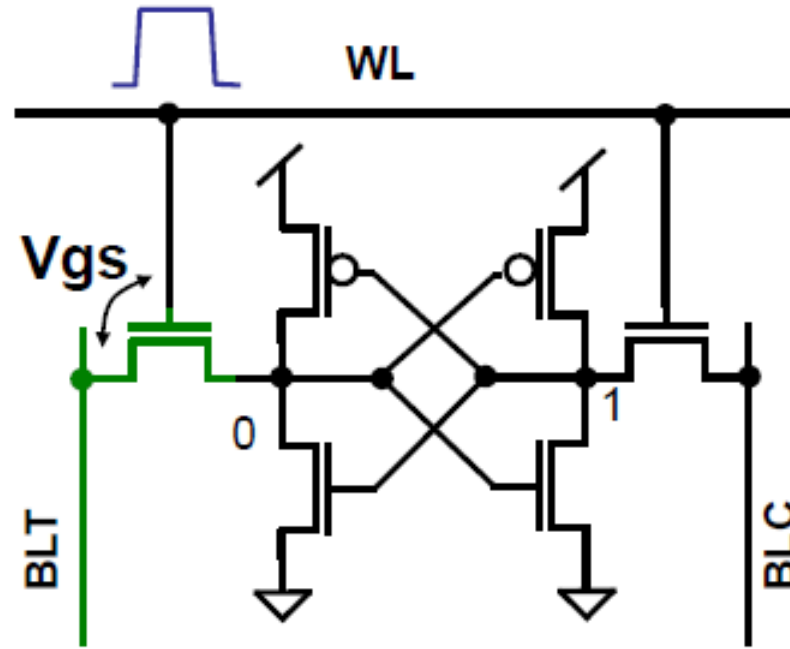


- Arsovski, ISSCC'11

WL Underdrive

- Sensing appropriate WL voltage

 


Carlson, CICC'08

 

Nho, ISSCC'10


Capacitive Write Assist + WL Underdrive

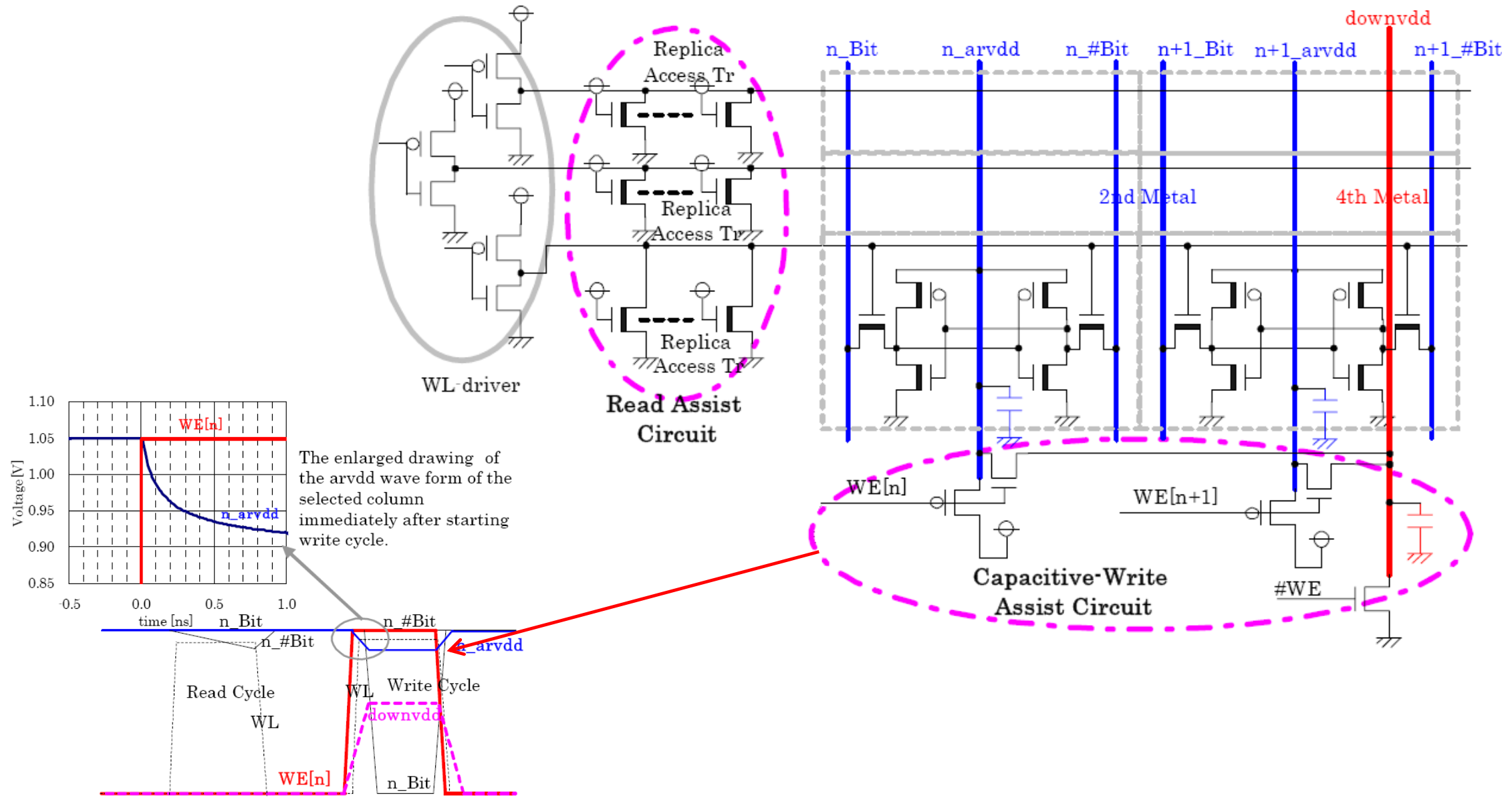

S. Ohbayashi, VLSI 2006

Capacitive Write Assist (ISSCC'20)

- 5nm SRAM [J. Chang, ISSCC'20]

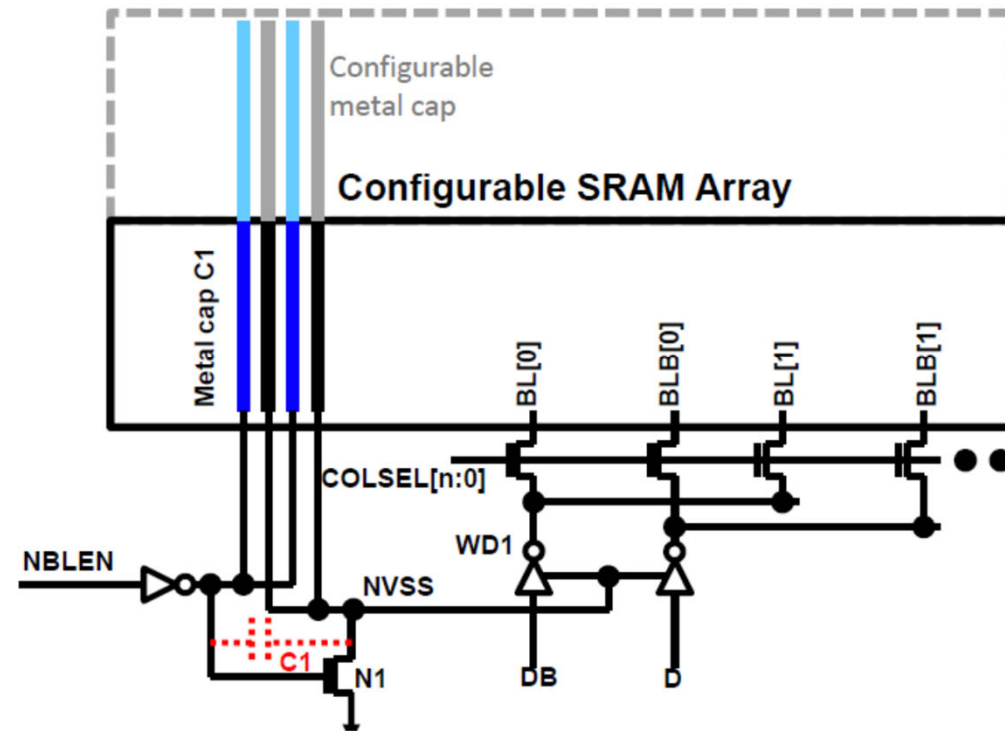

Pulsed WL/BL


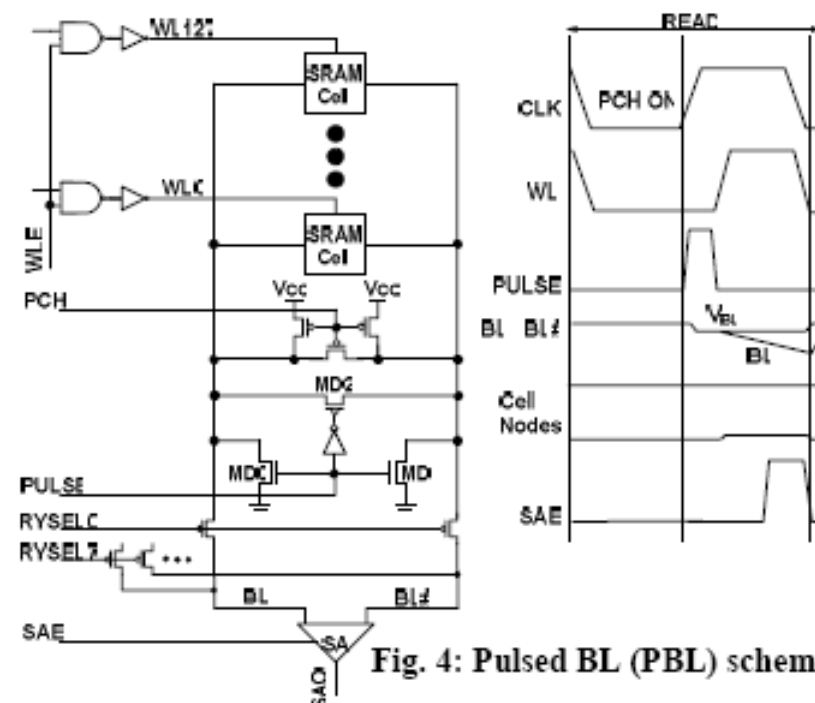
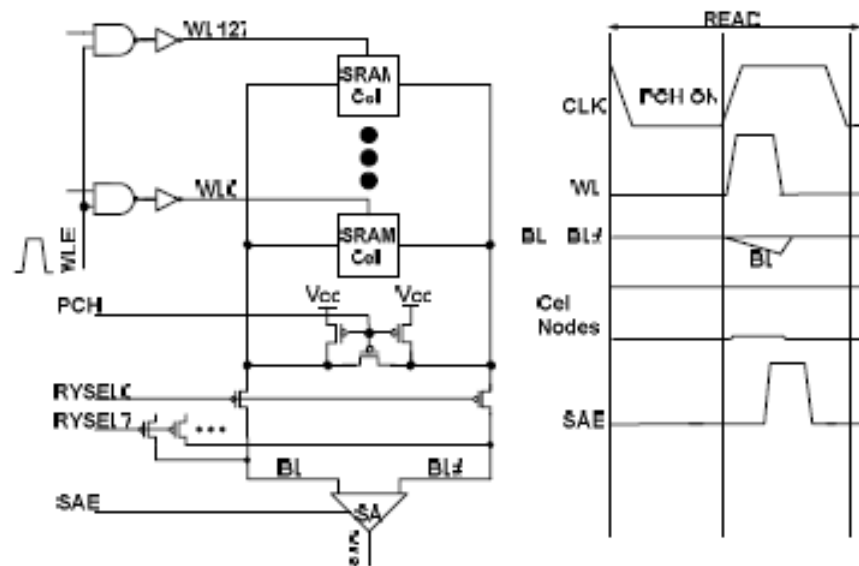




Fig. 4: Pulsed BL (PBL) scheme

Pulsing WL

Wordline pulse shape

 


Generating boost

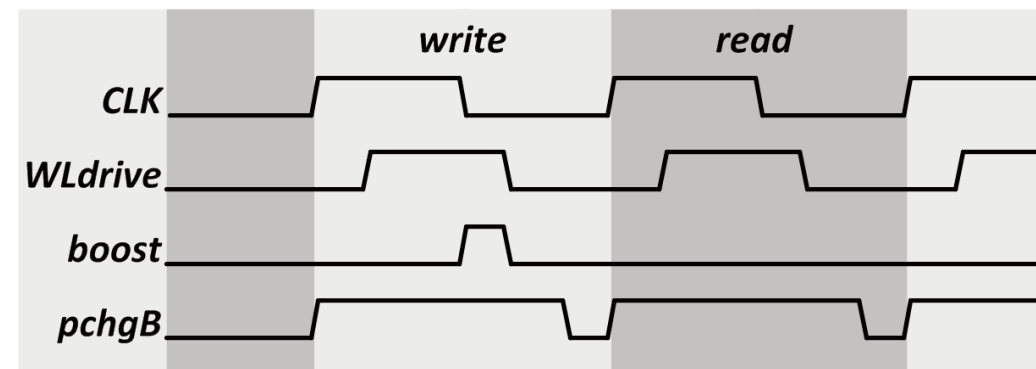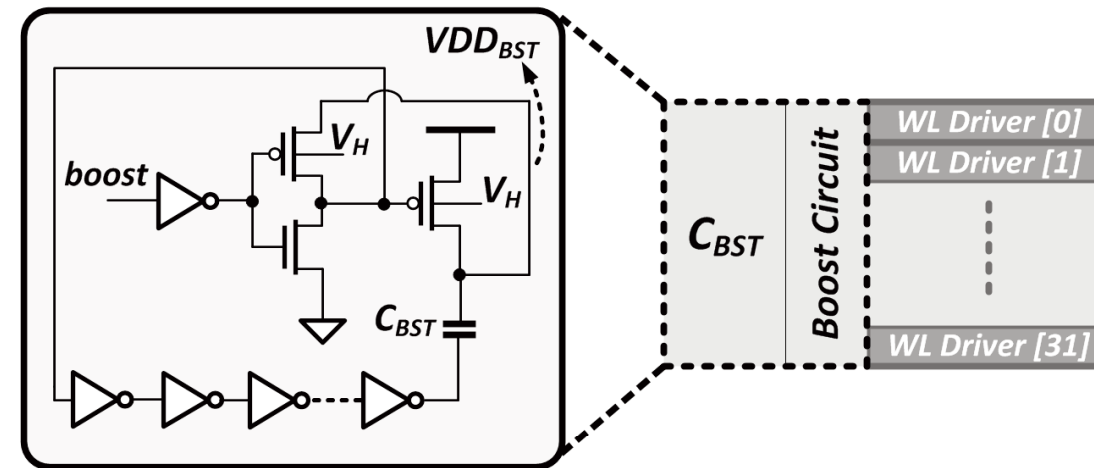


- Sinangil, ISSCC'2011

Write Assist Techniques

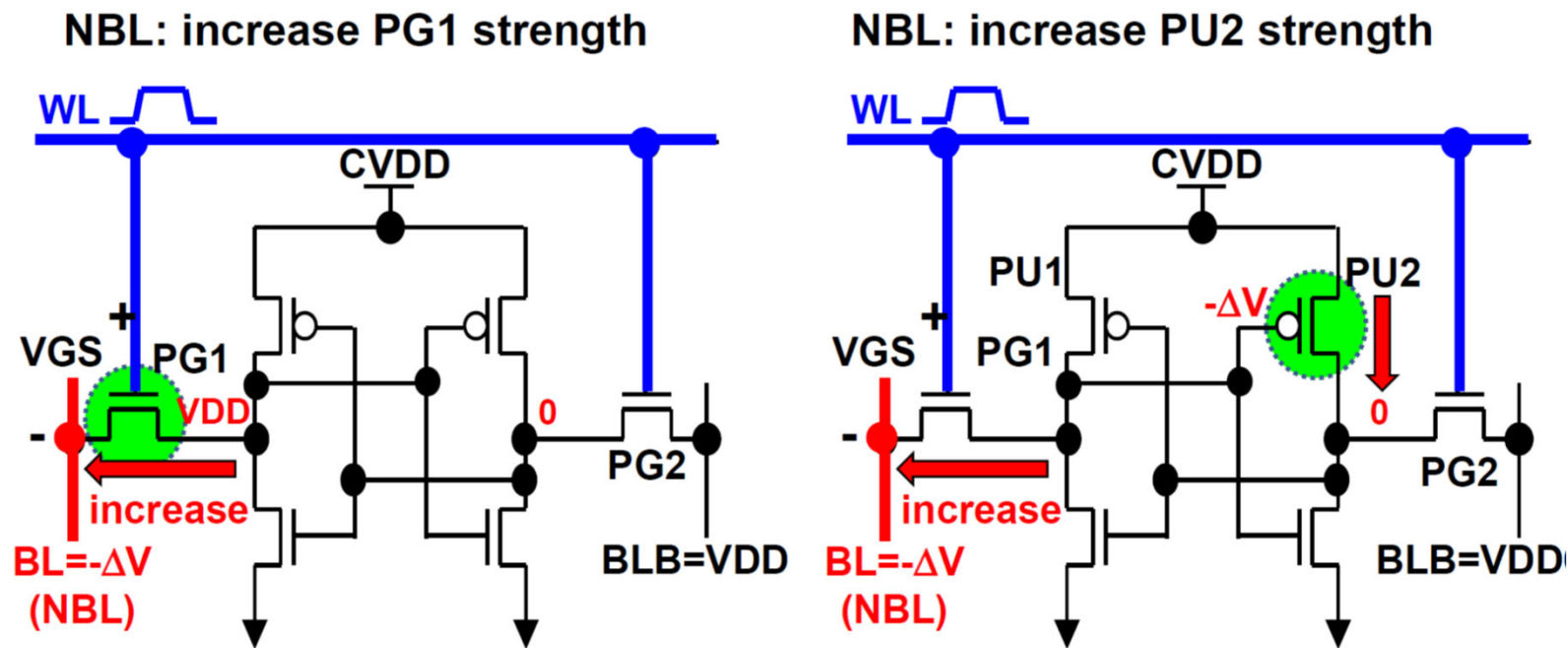- Negative Bit-Line (NBL):
 - increase PG1 and PU2 strength
- Improve both contention and recovery




NBL Scheme

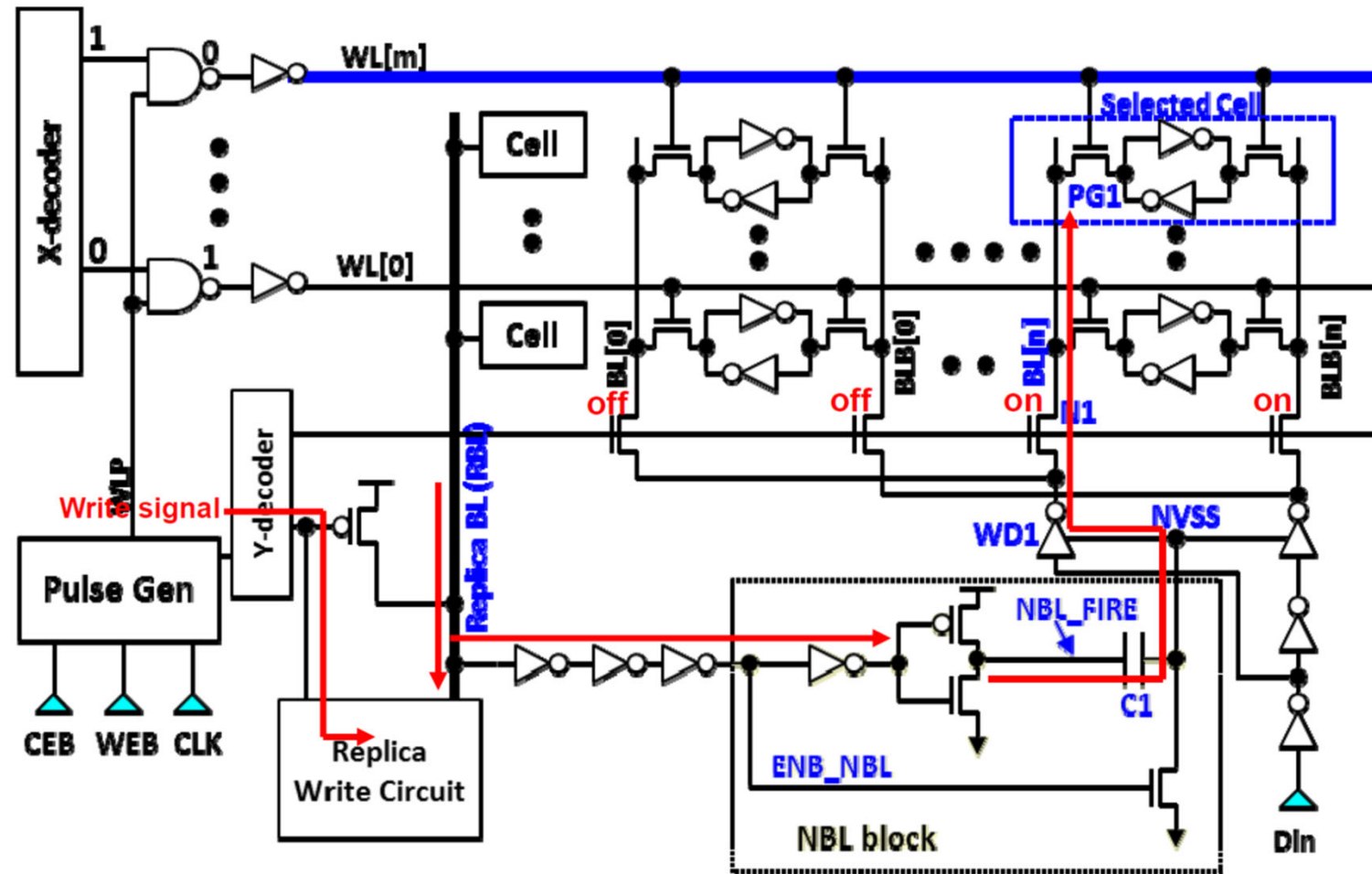

ISSCC'18 - 10nm Read Assist


- Wordline underdrive

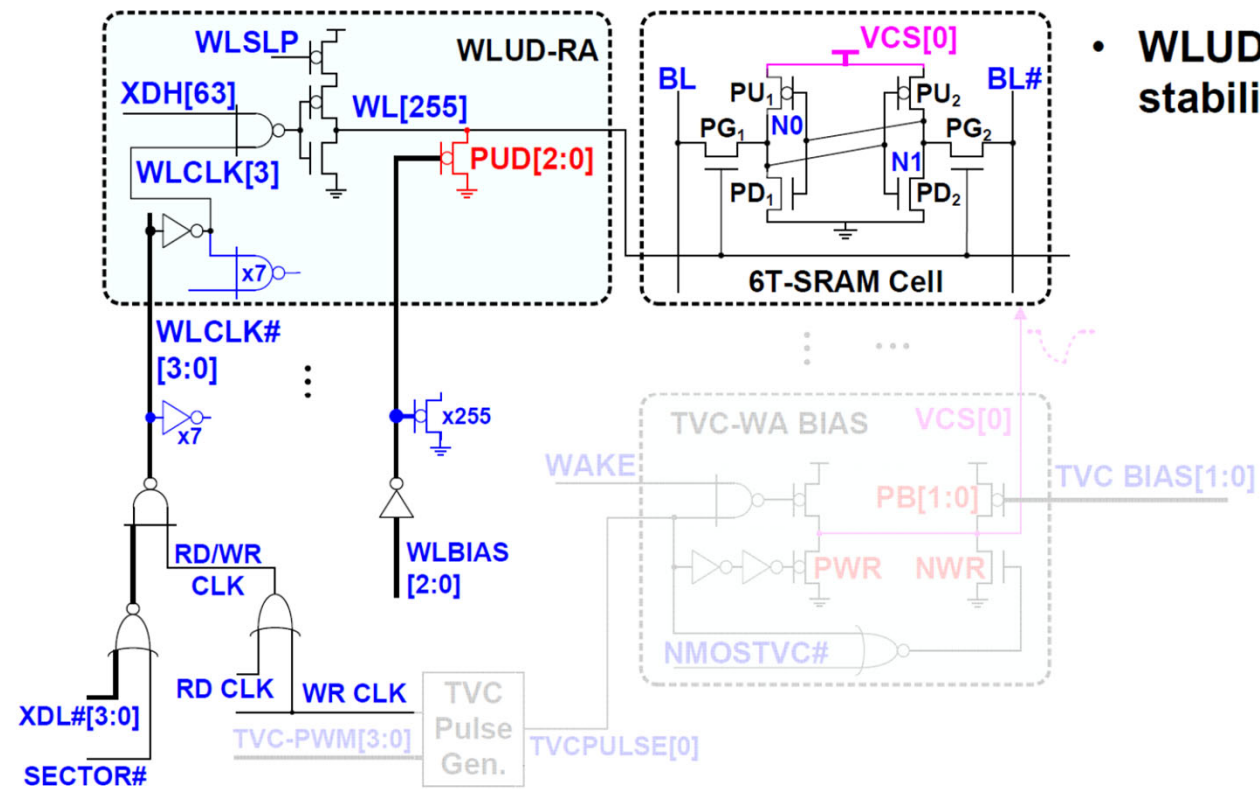

- WLUD-RA for improved stability margin (1.5% area)


ISSCC'18 - 10nm SRAM

- Transient voltage collapse

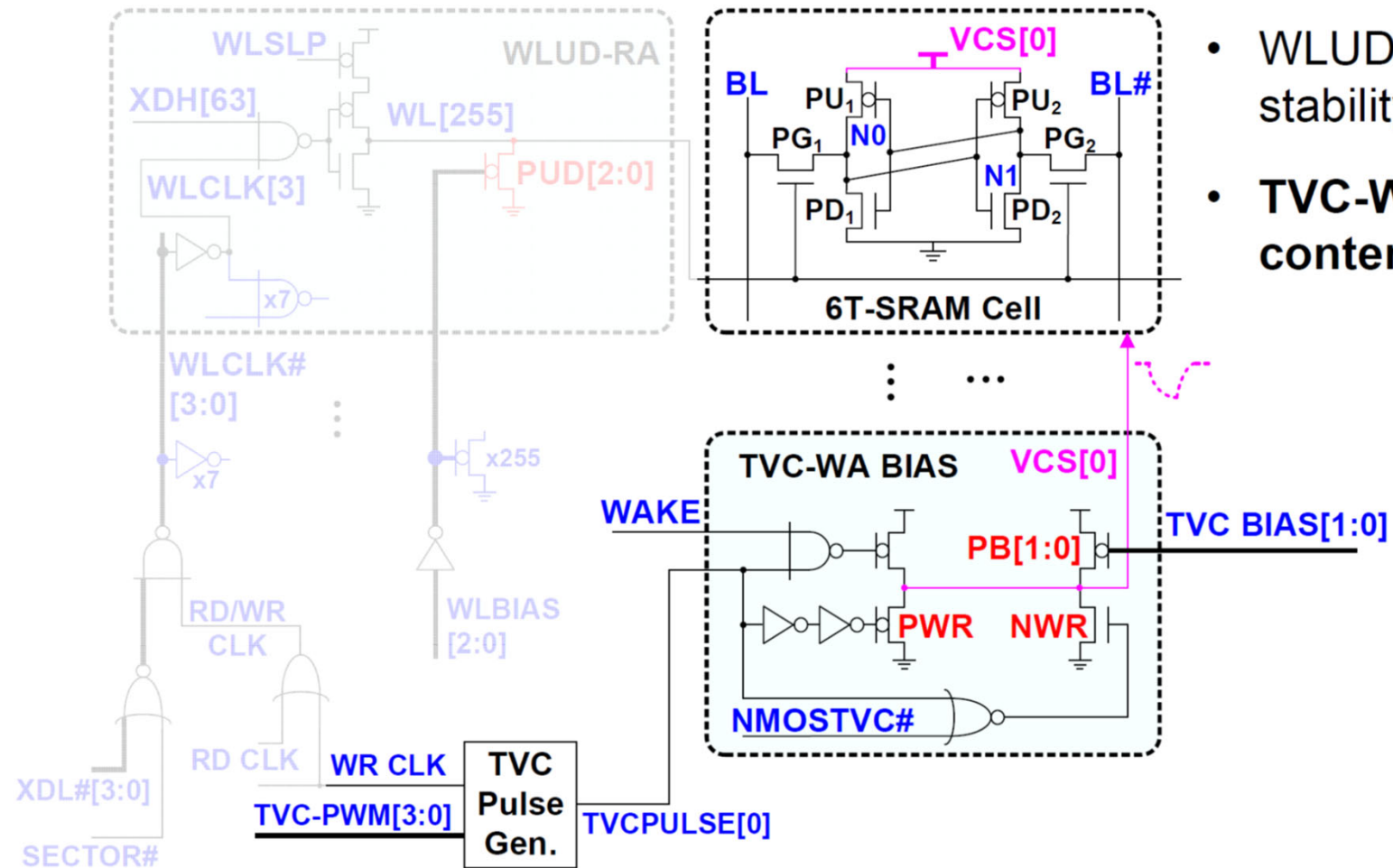


- WLUD-RA for improved stability margin (1.5% area)
- TVC-WA to reduce PU:PG contention (3.3% area)

SRAM Failure Rates

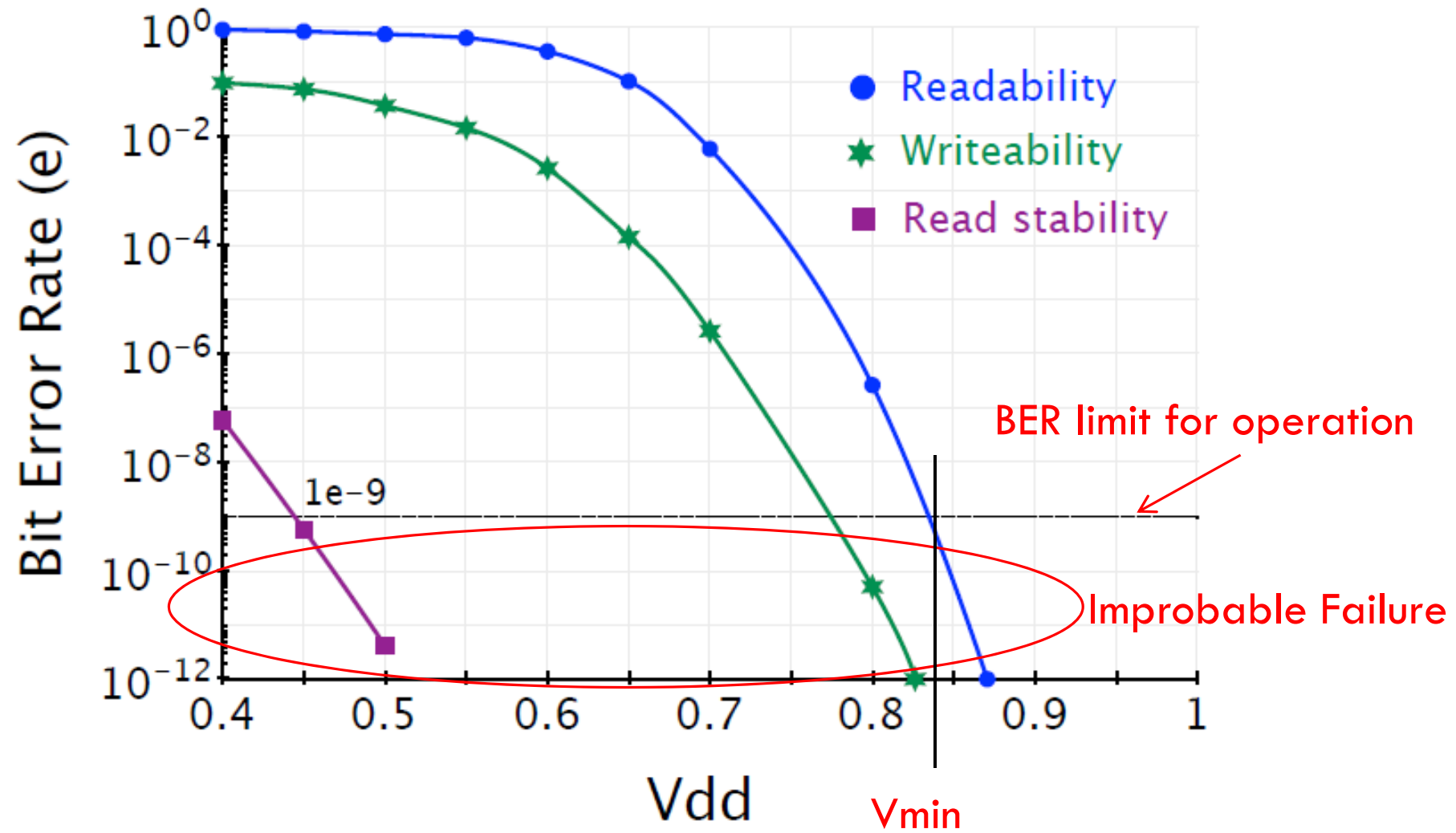


Readability, writeability, and read-stability failure rates for a 28nm 6T SRAM bitcell


Effect of bitline capacitance

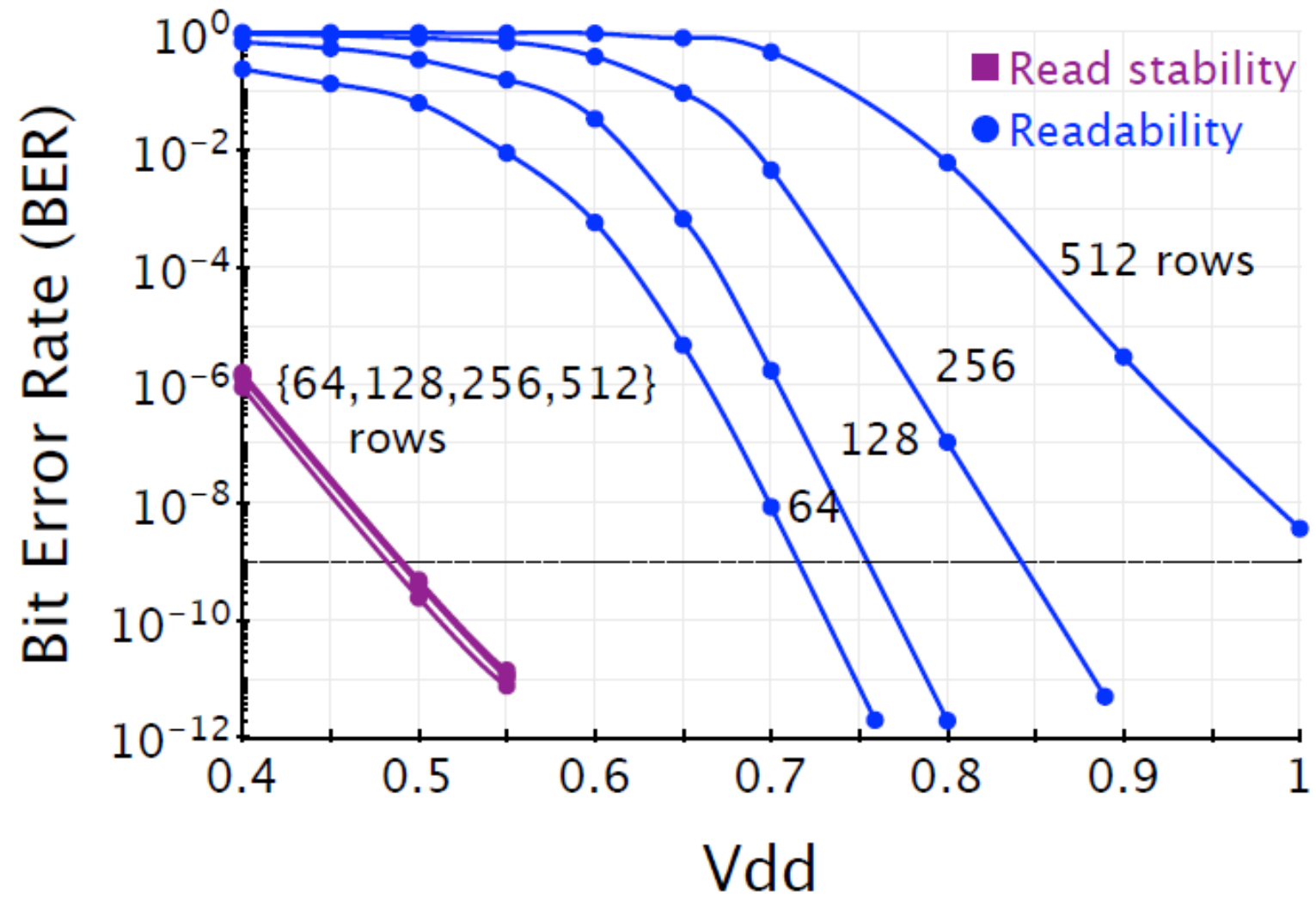

Effect of clock period


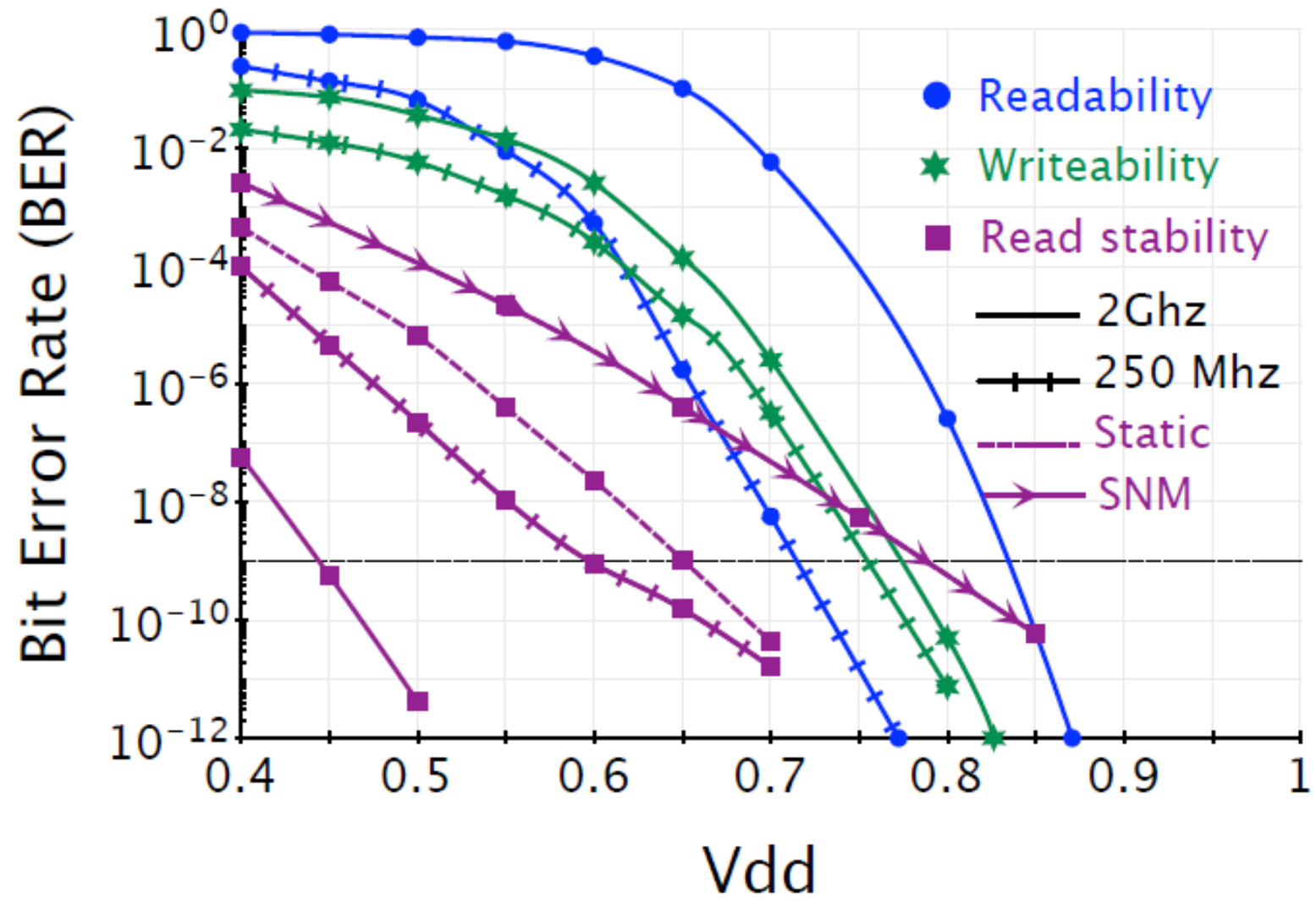


Effect of Assist Techniques

 


How Do They Stack Up?

- 28nm bulk CMOS

  

SRAM In Practice



- 7nm AMD Zen2 (Singh, ISSCC'20)

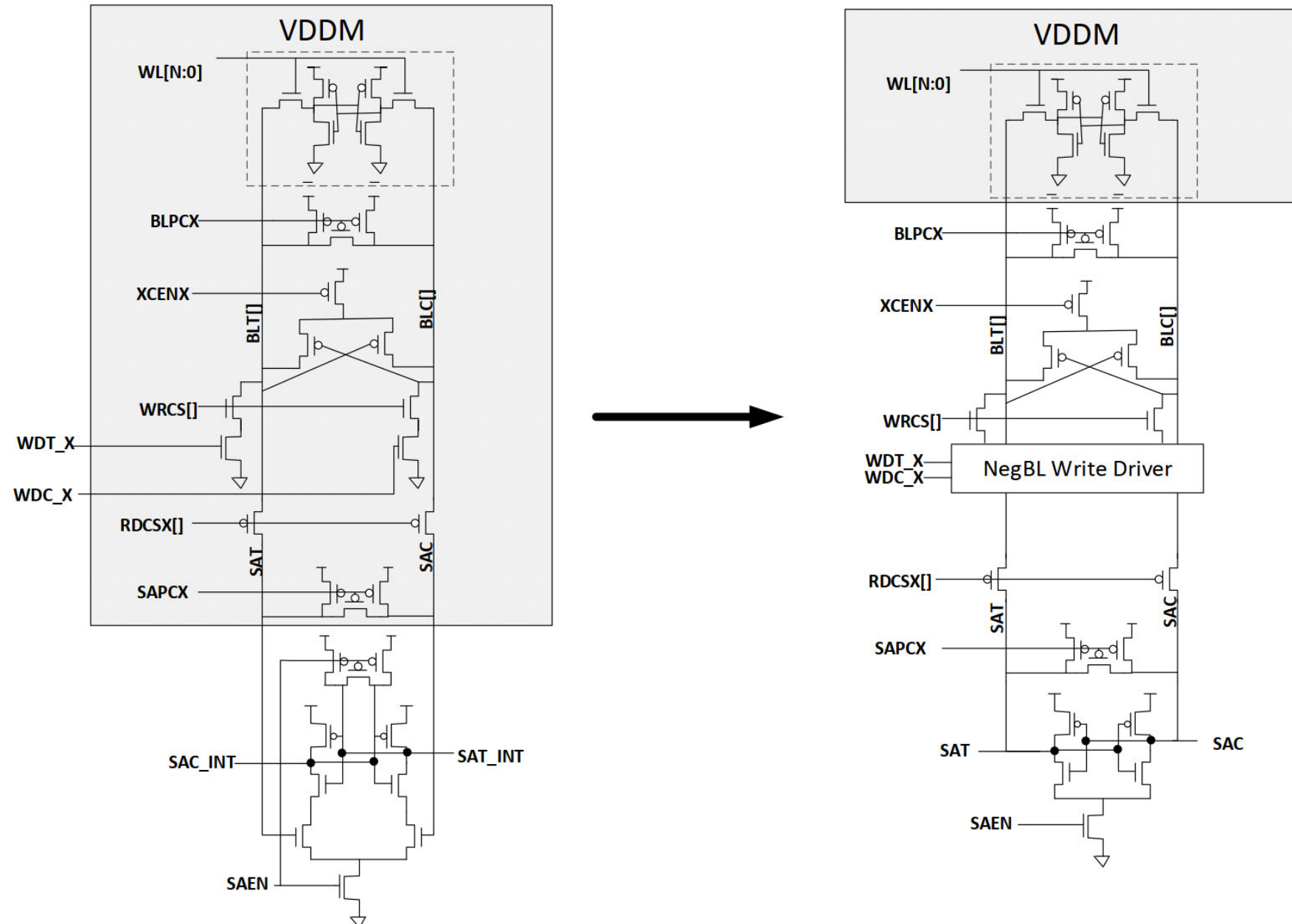

SRAM In Practice

- 7nm AMD Zen2 (Singh, ISSCC'20)

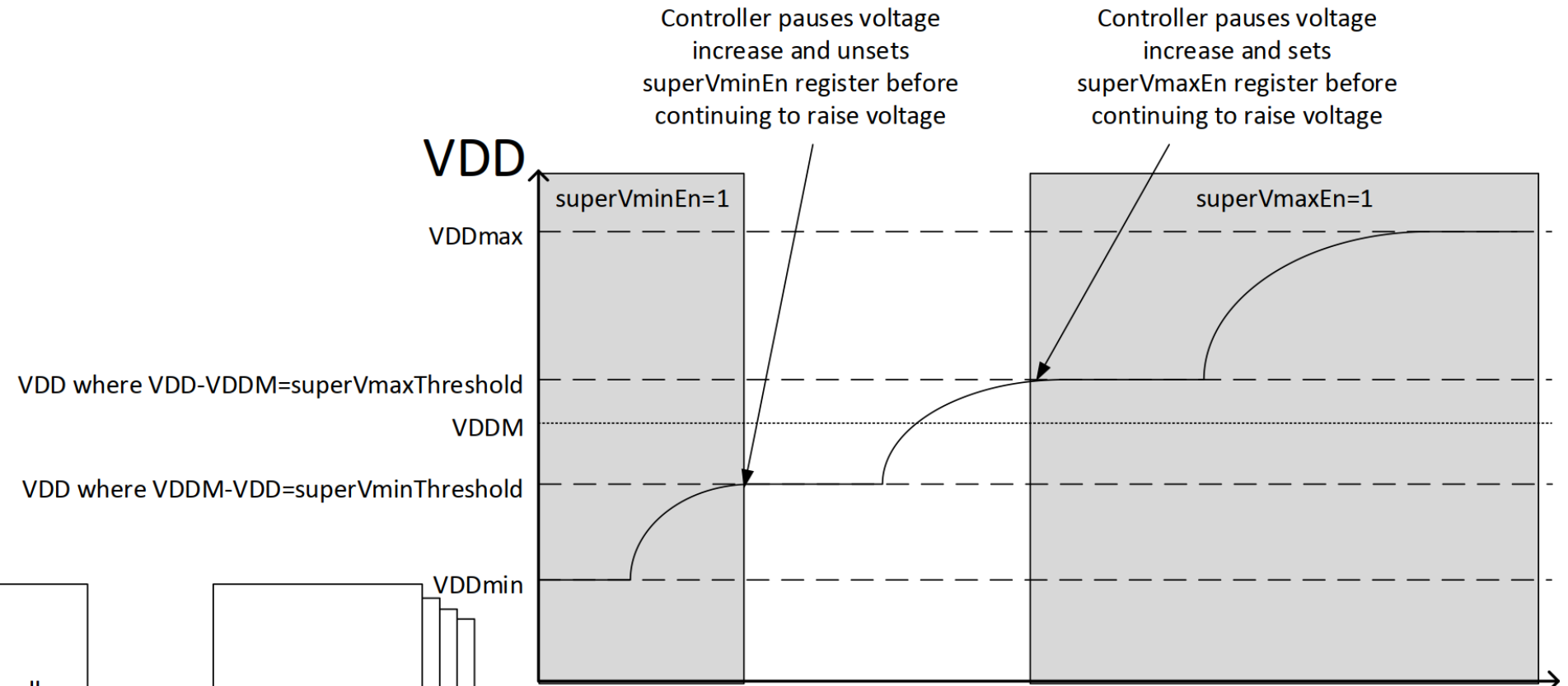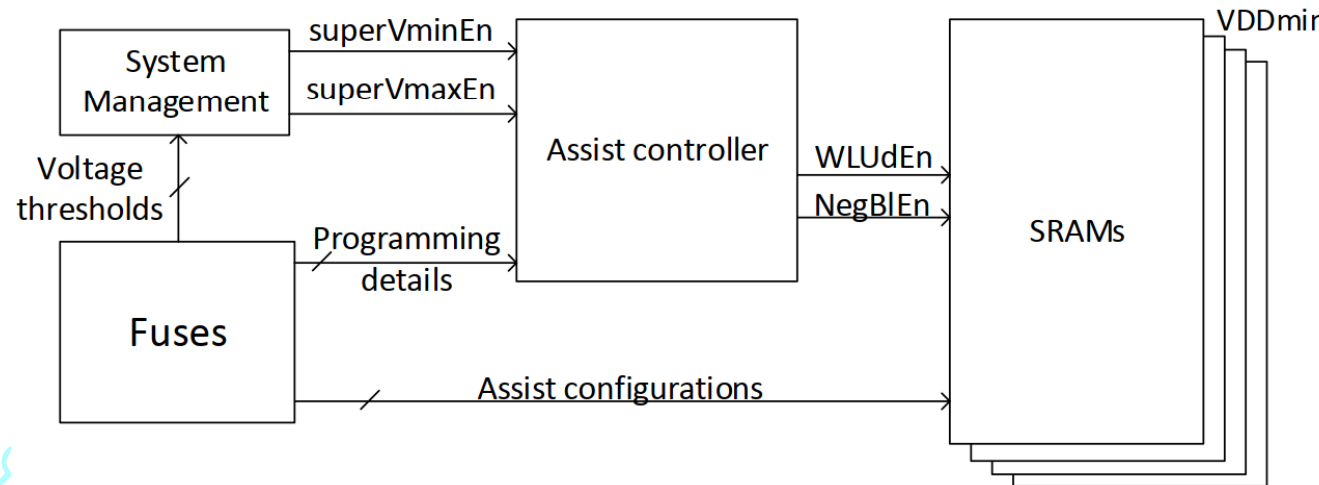- Moving bitline precharge to VDD creates both bitcell stability and writeability challenges
- High level of configurability allows for silicon flexibility







4.G Sense Amps

SRAM Periphery Design

- SRAM periphery:
 - Decoders (covered in EECS251A)
 - Bitline design and sense-amps




Sense-Amp Triggering

- Some older techniques

  


Sense-Amp Triggering

- Replica bitline

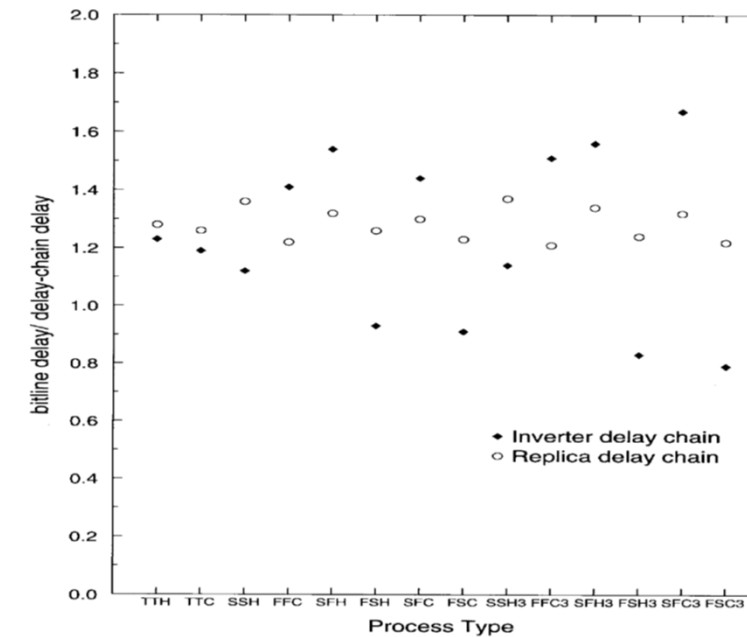 
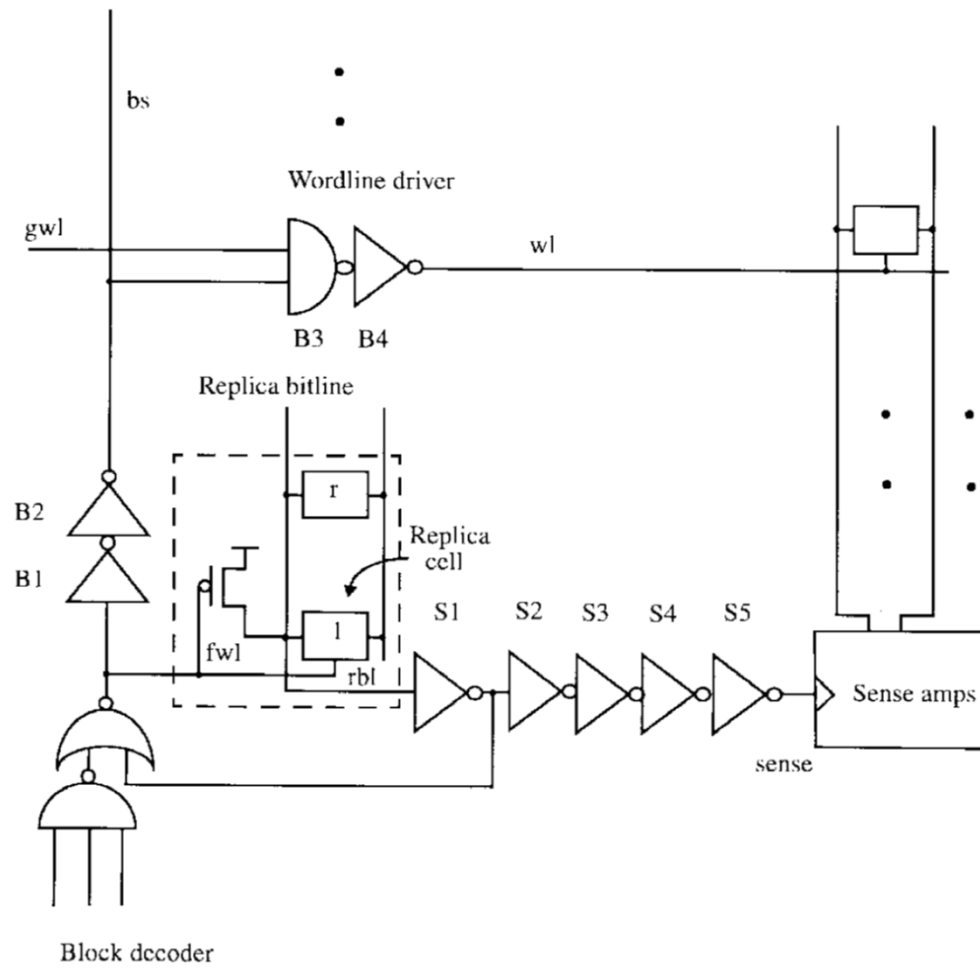


Multiplicative Replica Bitline

- Conventional replica

 

- Multiplicative replica

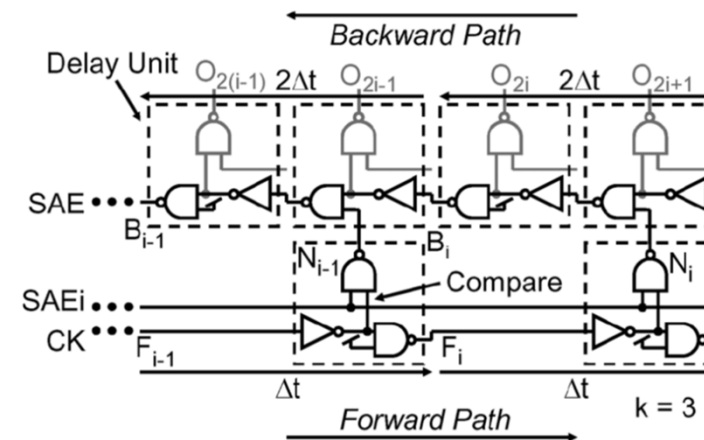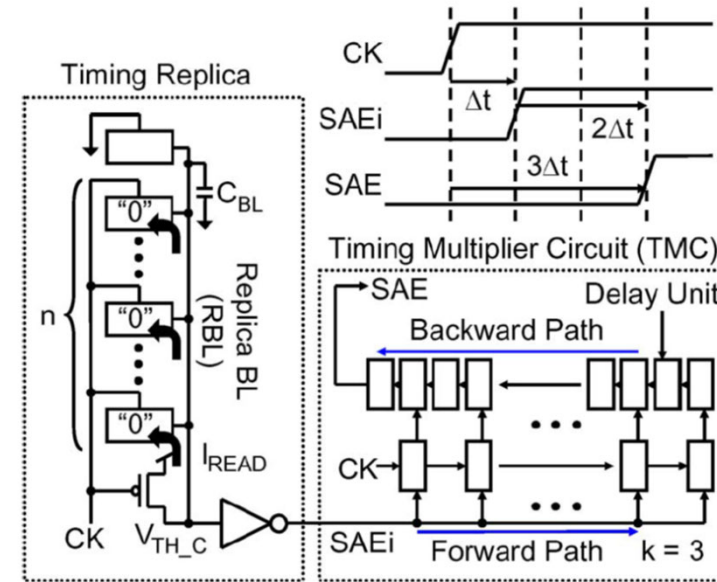

Next Lecture

- Redundancy, ECC
- Alternatives to 6T SRAM