

# EE241B : Advanced Digital Circuits

## Lecture 15 – SRAM 3

Borivoje Nikolić



March 11, 2020, EE Times

**Startup Ampere Attacks Intel's Strength:** Startup Ampere Computing said it is shipping an Arm-based, 80-core processor, a chip it is positioning as the world's first "cloud-native" processor. Called the Altra, it was designed to process the workloads that are typically handled in the cloud, while also drawing significantly less power than the average CPU.

Cal  
EECS241B L15 SRAM III

### Announcements

- Quiz 2 today
- Project midterm reports due next Thursday (March 19)
- Assignment 3 due next week

### • Reading - comprehensive (and optional)


- Horiguchi, Itoh, *Nanoscale Memory Repair*, Springer, 2011.
- Itoh, Horiguchi, Tanaka, *Ultra-Low Voltage Nano-Scale Memories*, Springer 2007.

### Outline


- Module 4
  - SRAM assist techniques
  - Sense amps
 
### Basic Ideas

- Dynamically change voltages
- Negative BL helps with writing
- Lower VDD ( $V_{CELL}$ ) helps with writing
- Higher WL helps with writing, lower hurts
- Lower WL helps with read, higher hurts
- Half-select condition: WL selected for write, but write operation is masked (BLs stay high)



### Dynamic $V_{DD}$ Implementation

 


- VCC selection is along column direction to decouple the read & write

Zhang, ISSCC'05


### Floating VDD Technique

- W/o second supply

 


Yamaoka, ISSCC'04

### Collapsing $V_{DD}$ Technique

 


E. Karl, ISSCC'12

## Collapsing $V_{DD}$ Technique

 


E. Karl, ISSCC'12

## Negative BL

 


Nii, VLSI'08

## Negative BL

 

Arsovski, ISSCC'11

 
## Capacitive Write Assist + WL Underdrive




S. Ohbayashi, VLSI 2006

## WL Underdrive

- Sensing appropriate WL voltage

 


Carlson, CICC'08

 

Nho, ISSCC'10

## Pulsed WL/BL

 


M.Khellah, VLSI 2006

## Pulsing WL

### Wordline pulse shape




### Generating boost

 


Sinangil, ISSCC'2011
 
### Write Assist Techniques


- Negative Bit-Line (NBL):
  - increase PG1 and PU2 strength
- Improve both contention and recovery








### NBL Scheme

 

- Wordline underdrive

 


- Transient voltage collapse

     



## How Do They Stack Up?

- 28nm bulk CMOS

 

## SRAM In Practice



- 7nm AMD Zen2 (Singh, ISSCC'20)

  
  
## SRAM In Practice

- 7nm AMD Zen2 (Singh, ISSCC'20)

- Moving bitline precharge to VDD creates both bitcell stability and writeability challenges
- High level of configurability allows for silicon flexibility



## 4.G Sense Amps



## SRAM Periphery Design

- SRAM periphery:

- Decoders (covered in EECS251A)
- Bitline design and sense-amps


## Sense-Amp Triggering

- Some older techniques

  


## Sense-Amp Triggering

- Replica bitline

 


## Multiplicative Replica Bitline

- Conventional replica

 

- Multiplicative replica

 

Niki, JSSC'11



## Next Lecture

- Redundancy, ECC
- Alternatives to 6T SRAM



EECS241B L15 SRAM II



33