

EE241B : Advanced Digital Circuits

Lecture 18 – Power-Performance Tradeoffs 2

Borivoje Nikolić



MarketWatch, March 28: Opinion: There's no returning to regular schooling as online learning goes mainstream, by Alex Hicks



When in-person education resumes, online learning tools and methods will be entrenched in the system

Announcements

- Project midterm reports due today, March 31
 - Please e-mail me the link to your web page
- Assignment 3 due Thursday, April 2.
 - Quiz next Tuesday
- Reading – req'd
 - Rabaey et al, LPDE, Ch. 4

Outline

- Module 5
 - Power-performance tradeoffs

5.B Power-Performance Tradeoffs



Know Your Enemy

- Where does power go in CMOS?
 - Switching (dynamic) power
 - Charging capacitors
 - Leakage power
 - Transistors are imperfect switches
 - Short-circuit power
 - Both pull-up and pull-down on during transition
 - Static currents
 - Biasing currents

Summary of Power Dissipation Sources


$$P \sim \alpha \cdot (C_L + C_{CS}) \cdot V_{swing} \cdot V_{DD} \cdot f + (I_{DC} + I_{Leak}) \cdot V_{DD}$$

- α – switching activity
- C_L – load capacitance
- C_{CS} – short-circuit "capacitance"
- V_{swing} – voltage swing
- f – frequency
- I_{DC} – static current
- I_{Leak} – leakage current


$$P = \frac{\text{energy}}{\text{operation}} \times \text{rate} + \text{static power}$$

CMOS Performance Optimization

 - Reminder - sizing: Optimal performance with equal fanout per stage




 - Extendable to general logic cone through 'logical effort'
- Equal effective fanouts ($g_i C_{i+1} / C_i$) per stage
- Optimal fanout is around 4




[Ref: I. Sutherland, Morgan-Kaufman'98]

Performance Optimization

 


Performance Optimization

 

IECS2418 L18 POWER-PERFORMANCE II

The Design Abstraction Stack

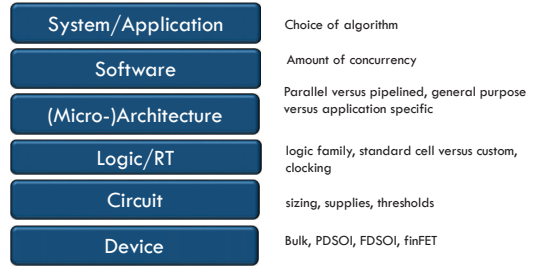A very rich set of design parameters to consider!
It helps to consider options in relation to their abstraction layer




9

IECS2418 L18 POWER-PERFORMANCE II

10


Power-Performance Optimization

 

Achieve the highest performance under the power cap

IECS2418 L18 POWER-PERFORMANCE II

Power-Performance Optimization

 


Achieve the highest performance under the power cap

11

IECS2418 L18 POWER-PERFORMANCE II

12


Power-Performance Optimization

 

Achieve the highest performance under the power cap

IECS2418 L18 POWER-PERFORMANCE II

Power-Performance Optimization

 


How far away are we from the optimal solution?

13

IECS2418 L18 POWER-PERFORMANCE II

14


Power-Performance Optimization

 

Global optimum – best performance

IECS2418 L18 POWER-PERFORMANCE II

Power-Performance Optimization

 

Maximize throughput for given energy or
Minimize energy for given throughput


15

IECS2418 L18 POWER-PERFORMANCE II

16


Power-Performance Optimization

 - There are many sets of parameters to adjust
 - Tuning variables
 - Circuit (sizing, supply, threshold)
 - Logic style (std. cells, custom, ...)
 - Block topology (adder: CLA, CSA, ...)
 - Micro-architecture (parallel, pipelined)




Power-Performance Optimization

 - There are many sets of parameters to adjust
 - Tuning variables
 - Circuit (sizing, supply, threshold)
 - Logic style (std. cells, custom, ...)
 - Block topology (adder: CLA, CSA, ...)
 - Micro-architecture (parallel, pipelined)




Globally optimal power-performance curve for a given function

Energy-Delay Sensitivity

 

$$S_A = \left. \frac{\partial E / \partial A}{\partial D / \partial A} \right|_{A=A_0}$$

Solution: Equal Sensitivities

 

At the solution point all sensitivities should be equal

5. C Architectural Optimization



Optimal Processors

- Processors used to be optimized for performance
 - Optimal logic depth was found to be 8-11 FO4 delays in superscalar processors
 - 1.8-3 FO4 in sequentials, rest in combinatorial
 - Kunkel, Smith, ISCA'86
 - Hrishesh, Jouppi, Farkas, Burger, Keckler, Shivakumar, ISCA'02
 - Harstein, Puzak, ISCA'02
 - Sprangle, Carmean, ISCA'02
- But those designs are have very high power dissipation
 - Need to optimize for both performance and power/energy

From System View: What is the Optimum?

- How do sensitivities relate to more traditional metrics:
 - Power per operation (MIPS/W, GOPS/W, TOPS/W)
 - Energy per operation (Joules per op)
 - Energy-delay product
- Can be reformatted as a goal of optimizing power x delayⁿ
 - n = 0 – minimize power per operation
 - n = 1 – minimize energy per operation
 - n = 2 – minimize energy-delay product
 - n = 3 – minimize energy-(delay)² product

Optimization Problem


- Set up optimization problem:
 - Maximize performance under energy constraints
 - Minimize energy under performance constraints
- Or minimize a composite function of $E^n D^m$
 - What are the right n and m?
- n = 1, m = 1 is EDP – improves at lower V_{DD}
- n = 1, m = 2 is invariant to V_{DD}
 - $E \sim CV_{DD}^2$
 - $D \sim 1/V_{DD}$

Hardware Intensity

- Introduced by Zyuban and Strenski in 2002.
- Measures where is the design on the Energy-Delay curve
- Parameter in cost function optimization


$$F_c = (E/E_0)(D/D_0)^\eta \quad 0 \leq \eta < +\infty,$$

$$\eta = - \frac{D \partial E}{E \partial D} \Big|_x$$

 

Slope of the optimal E-D curve at the chosen design point

Optimum Across Hierarchy Layers

 


Optimal logic depth in pipelined processors is ~18FO4
Relatively flat in the 16-22FO4 range

Zyuban et al, TComp'04



5.D Circuit-Level Tradeoffs

Alpha-Power Based Delay Model

 

$$t_{pi} = \frac{K_d V_{DD}}{(V_{DD} - V_{Th})^\alpha} \left(1 + \frac{C_{L,i}}{C_{in,i}} \right)$$

$$D = \sum t_{pi} = \sum \frac{K_d V_{DD}}{(V_{DD} - V_{Th})^\alpha} \left(1 + \frac{W_{L,i}}{W_{in,i}} \right)$$

Energy Models

Switching

$$E_{Sw} = \alpha_{0 \rightarrow 1} (C_{L,i} + C_{int,i}) V_{DD}^2$$




Leakage

$$E_{Lk} = W_{in} I_0 e^{\frac{-(V_{Th} - \gamma V_{DD})}{n V_T}} V_{DD} D$$

Sizing, Supply, Threshold Optimization

- Transistor sizing can yield large power savings with small delay penalties
 - Gate sizing
 - Beta-ratio adjustments $\beta = W_p/W_n$
 - (Stack resizing)
- Supply voltage affects both active and leakage energy
- Threshold voltage affects primarily the leakage

Apply to Sizing of an Inverter Chain

 

Unconstrained energy: find $\min D = \sum t_{pi}$

$$C_{gin,j} = \sqrt{C_{gin,j-1} C_{gin,j+1}} \quad W_j = \sqrt{W_{j-1} W_{j+1}}$$

Constrained energy: find $\min D$, under $E < E_{max}$
Where $E = \sum e_i$

Constrained Optimization

- Find $\min(D)$ subject to $E = E_{max}$
 - Constrained function minimization
 - E.g. Lagrange multipliers

Or dual:


$$\Lambda(x) = D(x) + \lambda(E(x) - E_{max}) \quad K(x) = E(x) + \lambda(D - D_{max})$$

$$\frac{\partial \Lambda}{\partial x} = 0$$

- Can solve analytically for $x = W_i, V_{DD}, V_{Th}$

Inverter Chain: Sizing Optimization

Inverter Chain: Sizing Optimization

 

$$W_j = \sqrt{\frac{W_{j-1}W_{j+1}}{1 + \lambda W_{j-1}}}$$

[Ma, Franzon, IEEE JSSC, 9/94]

$$\lambda = -\frac{2KV_{DD}^2}{\tau_{nom}S_W}$$

$$S_W \propto \frac{\theta_j}{f_j - f_{j-1}}$$

θ_j – energy per stage
 f_j – fanout per stage

Stojanovic, ICCAD'02

- Variable taper achieves minimum energy
- Reduce number of stages at large d_{inc}

Sensitivity to Sizing and Supply

- Gate sizing (W_j)


$$-\frac{\partial E_{sw}}{\partial D} \frac{\partial D}{\partial W_j} = \frac{\theta_j}{\tau_{nom}(f_j - f_{j-1})}$$

∞ for equal f_{eff}
(D_{min})

- Supply voltage (V_{dd})

$$-\frac{\partial E_{sw}}{\partial D} \frac{\partial D}{\partial V_{DD}} = \frac{E_{sw}}{D} 2 \frac{1 - x_v}{\alpha - 1 + x_v}$$
 
$$x_v = (V_{th} + \Delta V_{th}) / V_{dd}$$




Sensitivity to V_{th}

- Threshold voltage (V_{th})

$$-\frac{\partial E}{\partial D} \frac{\partial D}{\partial \Delta V_{th}} = P_{Lk} \left(\frac{V_{DD} - V_{th} - \Delta V_{th}}{\alpha n V_t} - 1 \right)$$

 Low initial leakage
 \Rightarrow speedup comes for “free”



Next Lecture

- Low-power design
 - Lowering supply voltage

