

EE241B : Advanced Digital Circuits

Lecture 18 – Power-Performance Tradeoffs 2

Borivoje Nikolić



MarketWatch, March 28: Opinion: There's no returning to regular schooling as online learning goes mainstream, by Alex Hicks



When in-person education resumes, online learning tools and methods will be entrenched in the system

Announcements

- Project midterm reports due today, March 31
 - Please e-mail me the link to your web page
- Assignment 3 due Thursday, April 2.
 - Quiz next Tuesday
- Reading – req'd
 - Rabaey et al, LPDE, Ch. 4, 5

Outline

- **Module 5**
 - Power-performance tradeoffs



5.B Power-Performance Tradeoffs


Know Your Enemy

- Where does power go in CMOS?
- Switching (dynamic) power
 - Charging capacitors
- Leakage power
 - Transistors are imperfect switches
- Short-circuit power
 - Both pull-up and pull-down on during transition
- Static currents
 - Biasing currents



2/3

1/3

 

LSI

(PLLs, SRAM, references)

Summary of Power Dissipation Sources

$$P \sim \underbrace{\alpha \cdot (C_L + C_{CS}) \cdot V_{swing} \cdot V_{DD} \cdot f}_E + (I_{DC} + I_{Leak}) \cdot V_{DD}$$


short cut

- α – switching activity
- C_L – load capacitance
- C_{CS} – short-circuit “capacitance”
- V_{swing} – voltage swing
- f – frequency
- I_{DC} – static current
- I_{leak} – leakage current


$$P = \underbrace{\frac{\text{energy}}{\text{operation}} \times \text{rate}}_{P_{act}} + \text{static power}$$

CMOS Performance Optimization

 
- Reminder - sizing: Optimal performance with equal fanout per stage



 
- Extendable to general logic cone through 'logical effort'
- Equal effective fanouts ($g_i C_{i+1} / C_i$) per stage
- Optimal fanout is around 4



Performance Optimization

 

Energy

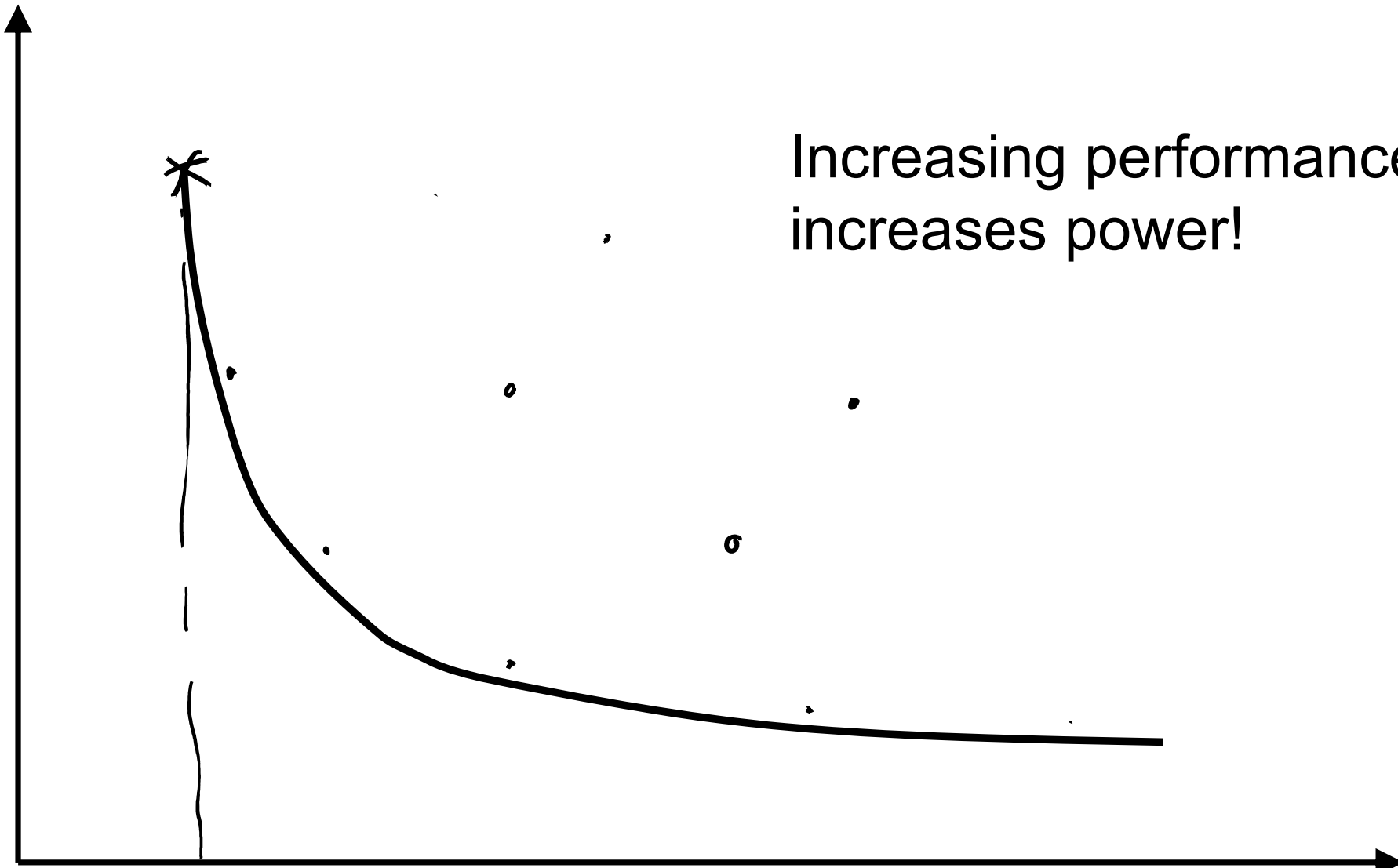


Increasing performance increases power!

LE

Delay = 1/Performance

Performance Optimization

Energy

 


Delay = $1/\text{Performance}$


The Design Abstraction Stack

A very **rich set of design parameters** to consider!

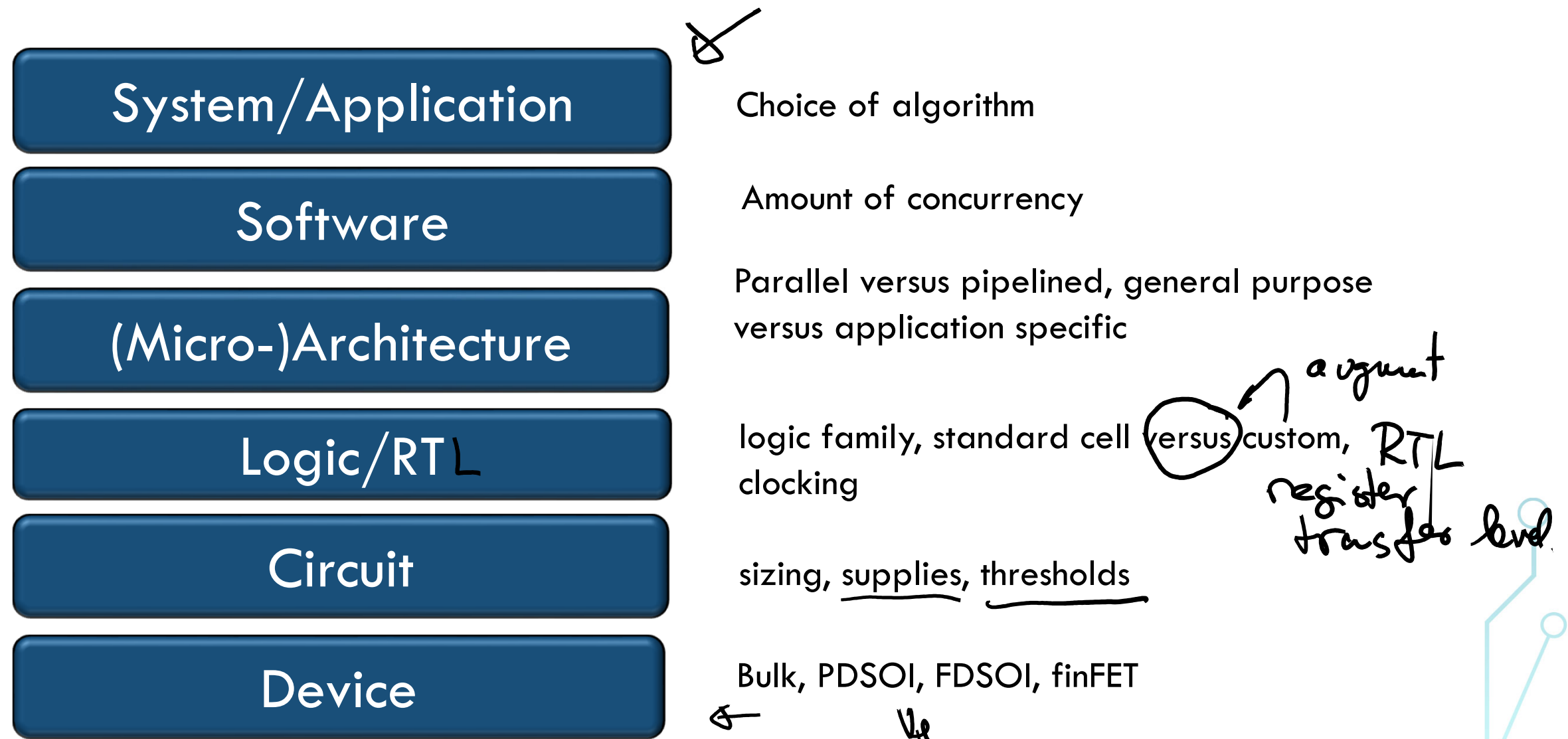It helps to consider options in relation to their abstraction layer




Power-Performance Optimization

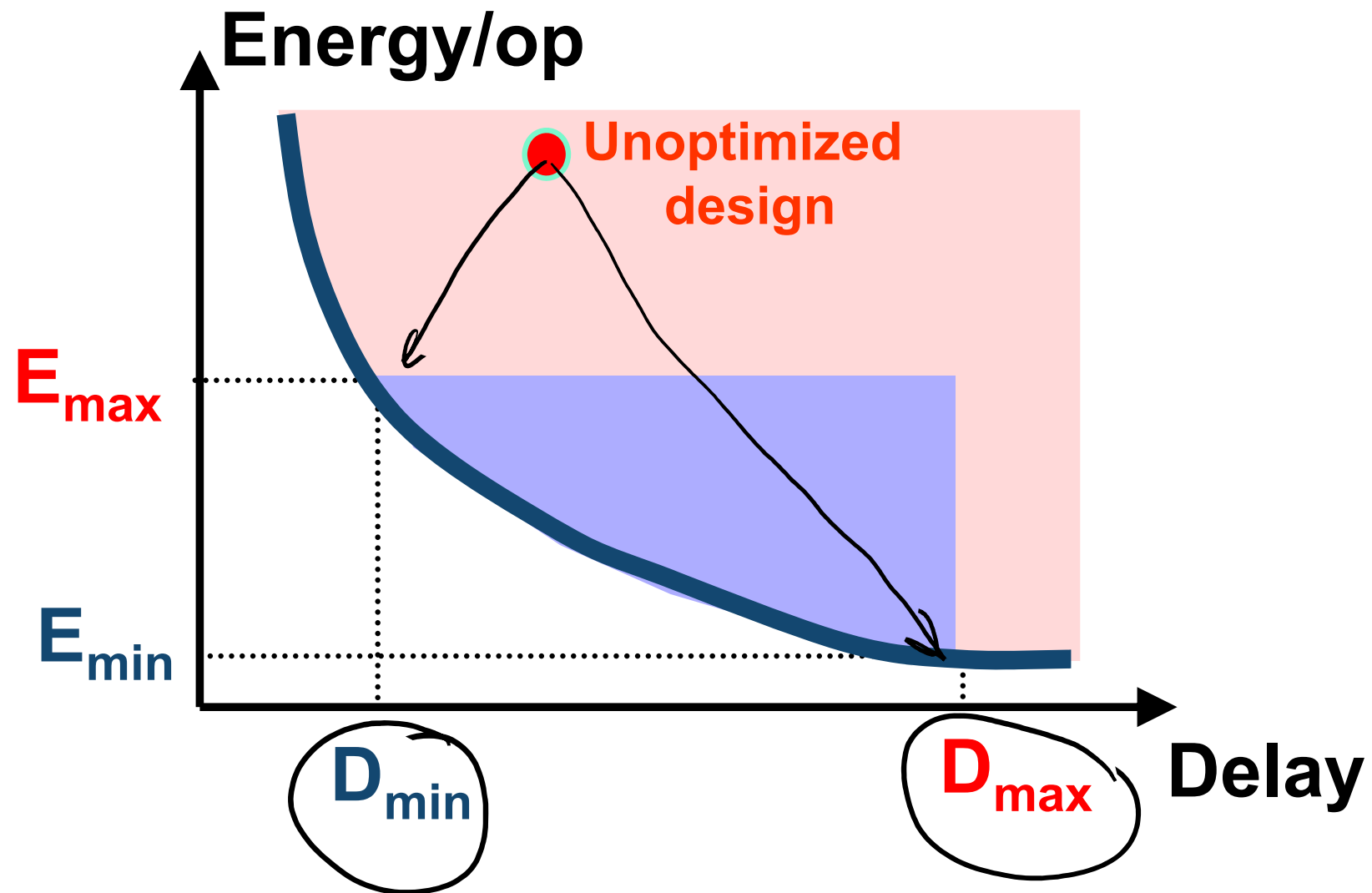


**Achieve the highest performance
under the power cap**

Power-Performance Optimization

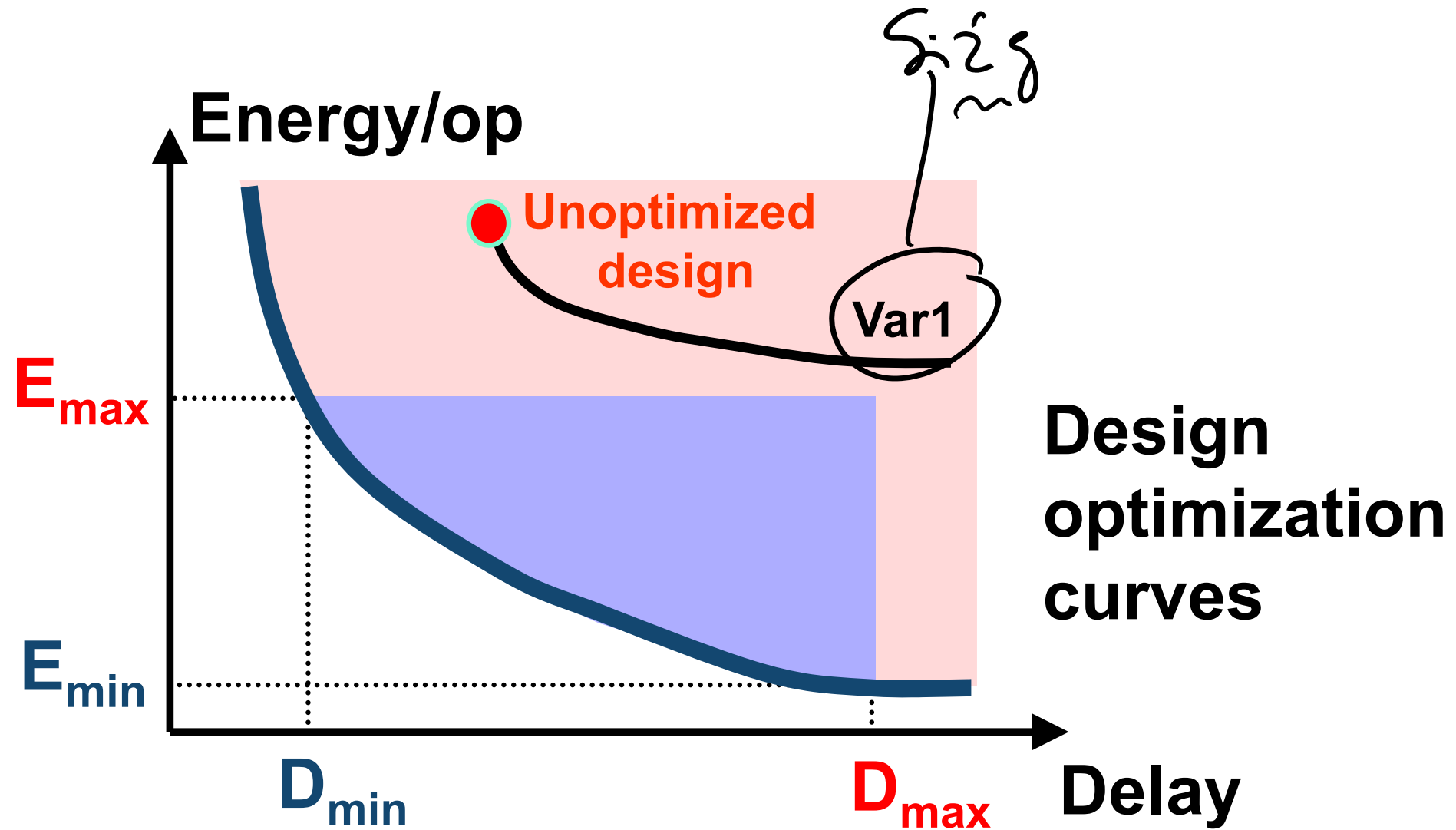

**Achieve the highest performance
under the power cap**


Power-Performance Optimization

 

Design optimization curves


Achieve the highest performance under the power cap

Power-Performance Optimization

 


How far away are we from the optimal solution?

Power-Performance Optimization

 


Power-Performance Optimization

 

Maximize throughput for given energy or
Minimize energy for given throughput


Power-Performance Optimization

 - There are many sets of parameters to adjust
 - Tuning variables
 - Circuit
(sizing, supply, threshold)
 - Logic style
(std. cells, custom , ...)
 - Block topology
(adder: CLA, CSA, ...)
 - Micro-architecture
(parallel, pipelined)



Power-Performance Optimization

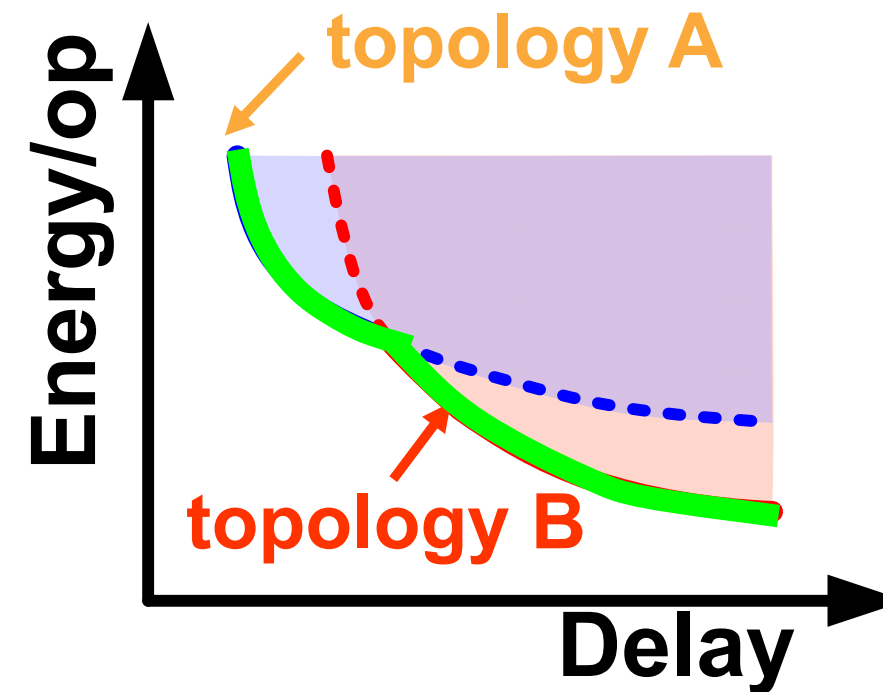
- There are many sets of parameters to adjust
 - Tuning variables
 - Circuit
(sizing, supply, threshold)
 - Logic style
(std. cells, custom , ...)
 - Block topology
(adder: CLA, CSA, ...)
 - Micro-architecture
(parallel, pipelined)



Globally optimal power-performance curve for a given function

Energy-Delay Sensitivity

$$S_A = \left. \frac{\partial E / \partial A}{\partial D / \partial A} \right|_{A=A_0}$$

 


$V_A = V_{DD}$
Absolute

$$\frac{\partial E / \partial V_{DD}}{\partial D / \partial V_{DD}} = \frac{2\%}{1\%} = 2\%$$

Relative

Solution: Equal Sensitivities
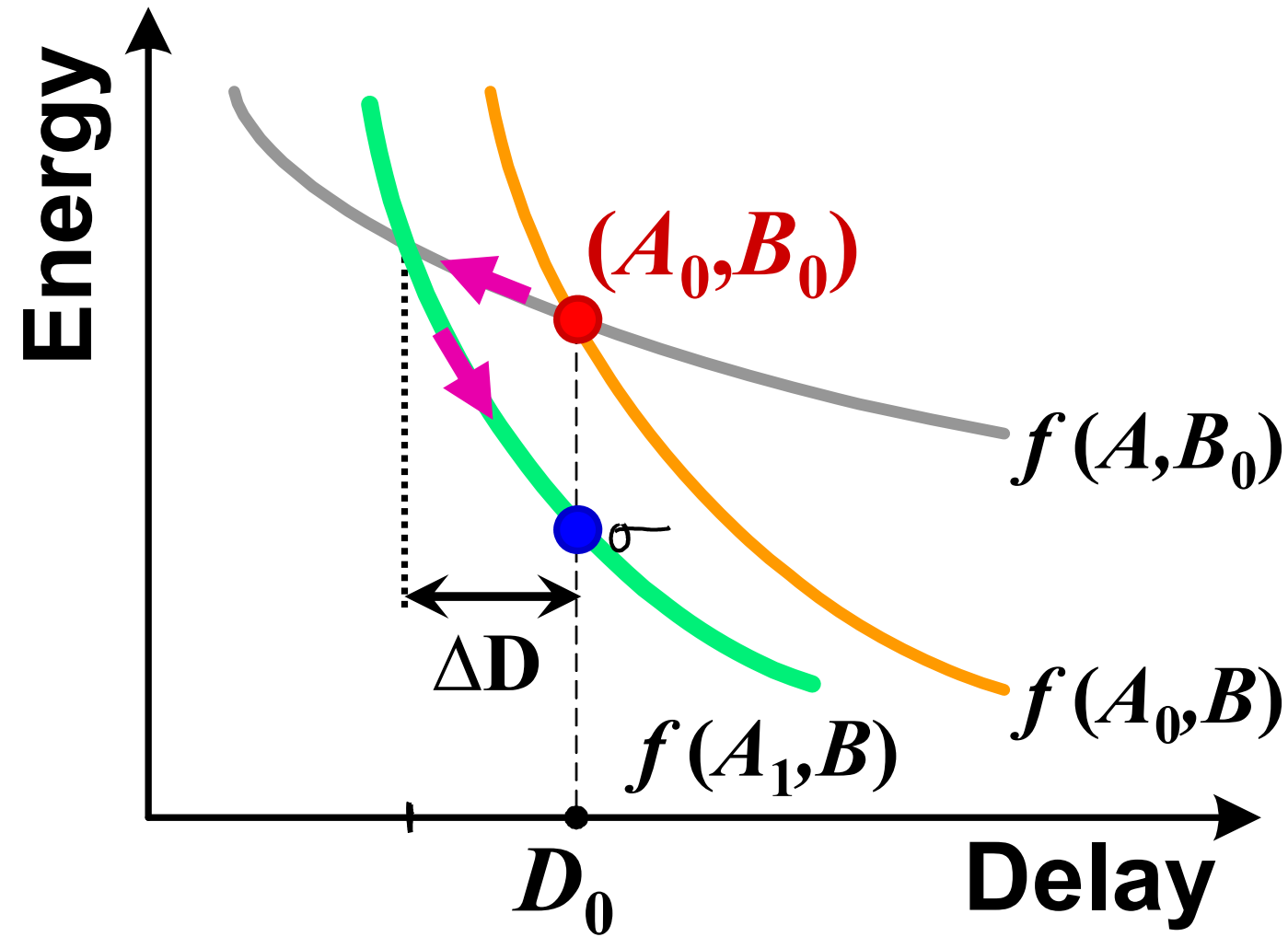
$$\Delta E = S_A \cdot (-\Delta D) + S_B \cdot \Delta D$$



(or are at limit)

At the solution point all sensitivities should be equal (slopes)



5. C Architectural Optimization

Optimal Processors

- Processors used to be optimized for performance
 - Optimal logic depth was found to be 8-11 FO4 delays in superscalar processors
 - 1.8-3 FO4 in sequentials, rest in combinatorial
 - Kunkel, Smith, ISCA'86
 - Hrishesh, Jouppi, Farkas, Burger, Keckler, Shivakumar, ISCA'02
 - Harstein, Puzak, ISCA'02
 - Sprangle, Carmean, ISCA'02
- But those designs are have very high power dissipation
 - Need to optimize for both performance and power/energy

From System View: What is the Optimum?

- How do sensitivities relate to more traditional metrics:
 - Power per operation (MIPS/W, GOPS/W, TOPS/W)
 - Energy per operation (Joules per op)
 - Energy-delay product

$$P \cdot D^n$$

- Can be reformatted as a goal of optimizing power x delayⁿ
 - $n = 0$ – minimize power per operation
 - $n = 1$ – minimize energy per operation
 - $n = 2$ – minimize energy-delay product \leftarrow improves with $V_{DD} \downarrow$
 - $n = 3$ – minimize energy-(delay)² product \leftarrow invariant to V_{DD} (@ μ_{Cen} V_{DD})
 - $n = 4$...

Optimization Problem

- Set up optimization problem:
 - Maximize performance under energy constraints
 - Minimize energy under performance constraints
- Or minimize a composite function of $\underline{E^n D^m}$
 - What are the right n and m ?
- $n = 1, m = 1$ is EDP – improves at lower V_{DD}
- $n = 1, m = 2$ is invariant to V_{DD}
 - $E \sim CV_{DD}^2$
 - $D \sim 1/V_{DD}$


Hardware Intensity

- Introduced by Zyuban and Strenski in 2002.
- Measures where is the design on the Energy-Delay curve
- Parameter in cost function optimization


$$F_c = (E/E_0)(D/D_0)^\eta \quad 0 \leq \eta < +\infty,$$

$$\eta = - \frac{D \partial E}{E \partial D} \Big|_v$$

 Slope of the optimal E-D curve at the chosen design point



Optimum Across Hierarchy Layers

 

Optimal logic depth in pipelined processors is ~18FO4

Relatively flat in the 16-22FO4 range