

# EE241B : Advanced Digital Circuits

## Lecture 19 – Supply Voltage

**Borivoje Nikolić**



**April 2, AnandTech: Intel Details 10th Gen Comet Lake-H for 45 W Notebooks: Up to 5.3 GHz\***



\*This CPU can hit this frequency on two cores, when the system is both within its secondary power limits but also Intel's Thermal Velocity Boost is enabled, which means there has to be additional thermal headroom in the system (and it has to be enabled by the OEM). This allows the CPU to go from 5.1 GHz to 5.3 GHz. Every Intel Thermal Velocity Boost enabled CPU requires OEM support in order to get those extra two bins on the single core frequency.

# Announcements

- **Assignment 3 due today, April 2.**
  - Quiz next Tuesday, end of class



# Outline

- **Module 5**
  - Circuit-level power-performance tradeoffs
  - Reducing supply voltage

# Architectural Tradeoffs


- H, Mair, ISSCC'20





## 5.D Circuit-Level Tradeoffs

# Alpha-Power Based Delay Model

 


$$t_{pi} = \frac{K_d V_{DD}}{(V_{DD} - V_{Th})^\alpha} \left( 1 + \frac{C_{L,i}}{C_{in,i}} \right)$$

$$D = \sum t_{pi} = \sum \frac{K_d V_{DD}}{(V_{DD} - V_{Th})^\alpha} \left( 1 + \frac{W_{L,i}}{W_{in,i}} \right)$$

# Energy Models
 
## ◆ Switching

$$E_{Sw} = \alpha_{0 \rightarrow 1} (C_{L,i} + C_{int,i}) V_{DD}^2$$



## ◆ Leakage

$$E_{Lk} = W_{ln} I_0 e^{\frac{-(V_{Th} - \gamma V_{DD})}{nV_t}} V_{DD} D$$


# Sizing, Supply, Threshold Optimization

- Transistor sizing can yield large power savings with small delay penalties
  - Gate sizing
  - Beta-ratio adjustments
  - (Stack resizing)
- Supply voltage affects both active and leakage energy
- Threshold voltage affects primarily the leakage

$$\beta = W_p/W_n$$



# Apply to Sizing of an Inverter Chain

 

*Unconstrained energy: find min  $D = \sum t_{pi}$*

$$C_{gin,j} = \sqrt{C_{gin,j-1} C_{gin,j+1}}$$

$$W_j = \sqrt{W_{j-1} W_{j+1}}$$

*Constrained energy: find min  $D$ , under  $E < E_{max}$*

*Where  $E = \sum e_j$*

# Constrained Optimization

- Find  $\min(D)$  subject to  $E = E_{max}$ 
  - *Constrained function minimization*
- E.g. Lagrange multipliers

$$\Lambda(x) = D(x) + \lambda(E(x) - E_{max})$$

$$\frac{\partial \Lambda}{\partial x} = 0$$


- Can solve analytically for  $x = W_i, V_{DD}, V_{Th}$

Or dual:

$$K(x) = E(x) + \lambda(D - D_{max})$$

# Inverter Chain: Sizing Optimization

# Inverter Chain: Sizing Optimization

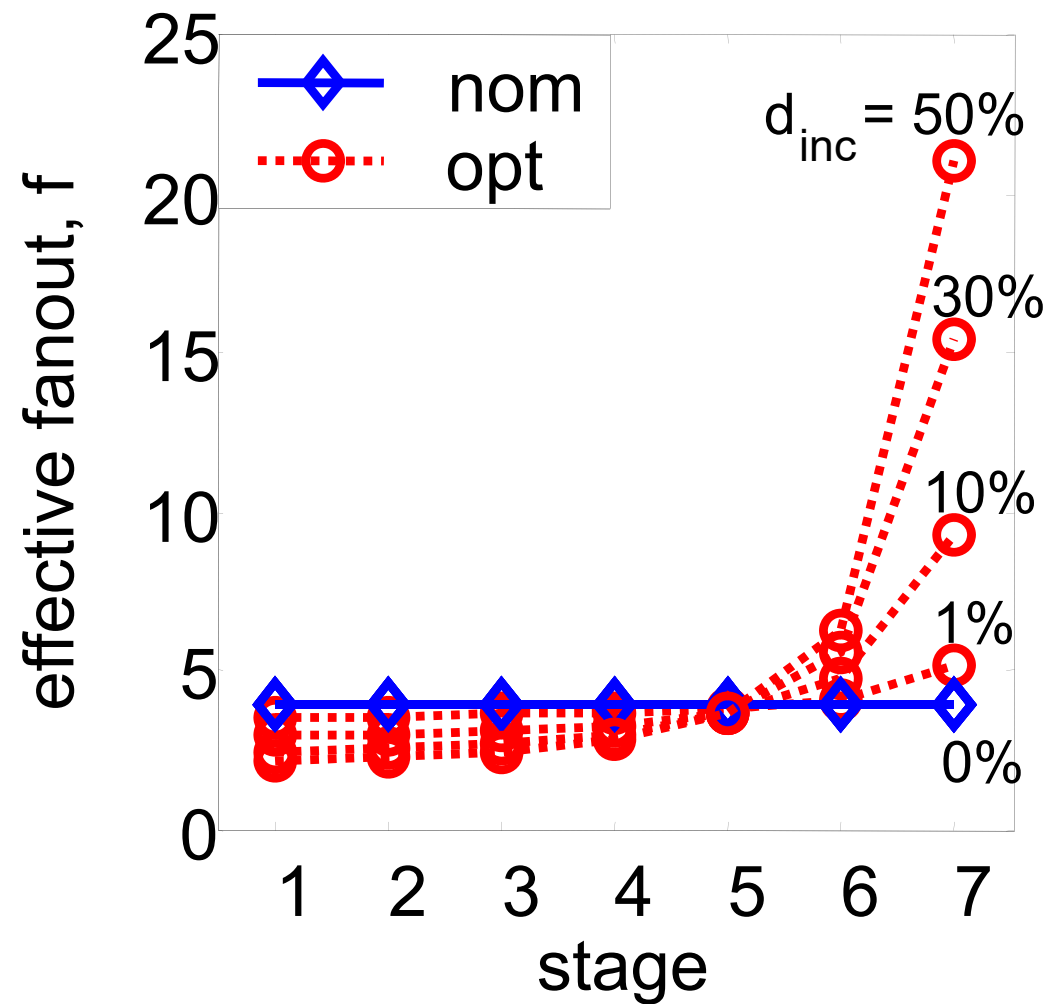

$$W_j = \sqrt{\frac{W_{j-1}W_{j+1}}{1 + \lambda W_{j-1}}}$$

[Ma, Franzon, *IEEE JSSC*, 9/94]

$$\lambda = -\frac{2KV_{DD}^2}{\tau_{nom} S_W}$$

$$S_W \propto \frac{e_j}{f_j - f_{j-1}}$$

$e_j$  – energy per stage  
 $f_j$  – fanout per stage

Stojanovic, ICCAD'02

- **Variable taper achieves minimum energy**
- **Reduce number of stages at large  $d_{inc}$**

# Sensitivity to Sizing and Supply

- Gate sizing ( $W_i$ )


$$-\frac{\partial E_{sw} / \partial W_j}{\partial D / \partial W_j} = \frac{e_j}{\tau_{nom} (f_j - f_{j-1})}$$

$\infty$  for equal  $f_{eff}$   
( $D_{min}$ )

- Supply voltage ( $V_{dd}$ )

$$-\frac{\partial E_{sw} / \partial V_{DD}}{\partial D / \partial V_{DD}} = \frac{E_{sw}}{D} 2 \frac{1 - x_v}{\alpha - 1 + x_v}$$
 
$$x_v = (V_{Th} + \Delta V_{Th}) / V_{dd}$$




## Sensitivity to $V_{th}$

- Threshold voltage ( $V_{th}$ )

$$-\frac{\frac{\partial E}{\partial \Delta V_{Th}}}{\frac{\partial D}{\partial \Delta V_{th}}} = P_{Lk} \left( \frac{V_{DD} - V_{Th} - \Delta V_{Th}}{\alpha n V_t} - 1 \right)$$

**Low initial leakage**

**⇒ speedup comes for “free”**

 

# Power /Energy Optimization Space

	Constant Throughput/Latency	Variable Throughput/Latency	
Energy	Design Time	Sleep Mode	
Active	Logic design Scaled $V_{DD}$ Trans. sizing Multi- $V_{DD}$	Clock gating	
Leakage	Stack effects Trans sizing Scaling $V_{DD}$ + Multi- $V_{Th}$	Sleep T's Multi- $V_{DD}$ Variable $V_{Th}$ + Input control	DVS Variable $V_{Th}$
			Run Time

# Energy-Performance Tradeoffs

<b>Enable Time/ Perf. Impact</b>	<b>Design Time</b>	<b>Run Time</b>
<b>Near-zero perf. penalty</b>	<b>Clock gating Architectural switching reduction Multi-<math>V_{Th}</math></b>	<b>Dynamic <math>V_{DD}</math> Dynamic <math>V_{Th}</math></b>
<b>True tradeoffs</b>	<b>Fine-granularity clock gating <math>V_{DD}</math>, <math>V_{Th}</math> adjustments Multi-<math>V_{DD}</math> Sizing, logic styles Stack forcing</b>	<b>Power gating</b>





## 5.E Scaling Supplies


# Power /Energy Optimization Space

	Constant Throughput/Latency	Variable Throughput/Latency	
Energy	Design Time	Sleep Mode	Run Time
<b>Active</b>	Logic design <b>Scaled <math>V_{DD}</math></b> Trans. sizing Multi- $V_{DD}$	Clock gating	DFS, DVS
<b>Leakage</b>	Stack effects Trans sizing Scaling $V_{DD}$ + Multi- $V_{Th}$	Sleep T's Multi- $V_{DD}$ Variable $V_{Th}$ + Input control	DVS Variable $V_{Th}$

# Supply Voltage Adjustment

- How to maintain throughput under reduced supply?
- Introducing more parallelism/pipelining
  - Area increase
  - Cost/power tradeoff
- Multiple voltage domains
  - Separate supply voltages for different blocks
  - Lower VDD for slower blocks
  - Cost of DC-DC converters
- Dynamic voltage scaling – with variable throughput
- Reducing  $V_{TH}$  to improve speed
  - Leakage issues

# Reducing $V_{dd}$

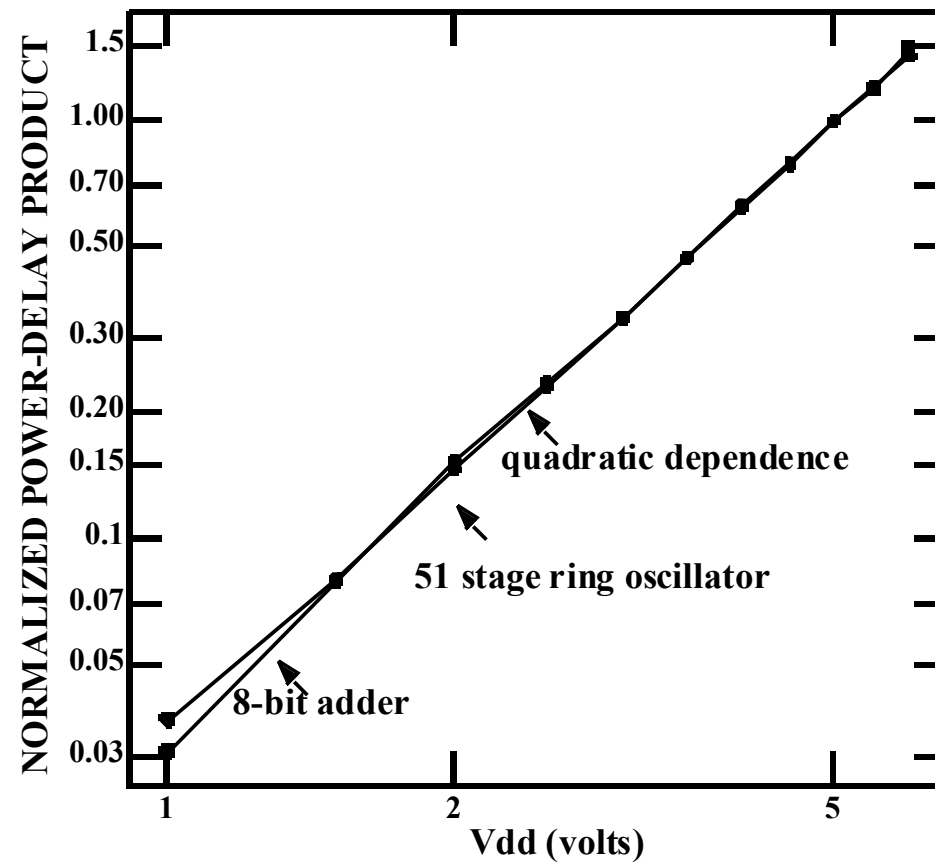

$$P \times t_d = E_t = C_L * V_{dd}^2$$


$$\frac{E_{(V_{dd}=2)}}{E_{(V_{dd}=5)}} = \frac{(C_L) * (2)^2}{(C_L) * (5)^2}$$

$$E_{(V_{dd}=2)} \approx 0.16 E_{(V_{dd}=5)}$$


- Strong function of voltage ( $V^2$  dependence).
- Relatively independent of logic function and style.
- Power Delay Product Improves with lowering  $V_{DD}$ .

# Reducing $V_{DD}$

32nm process

 

# Lower $V_{DD}$ Increases Delay

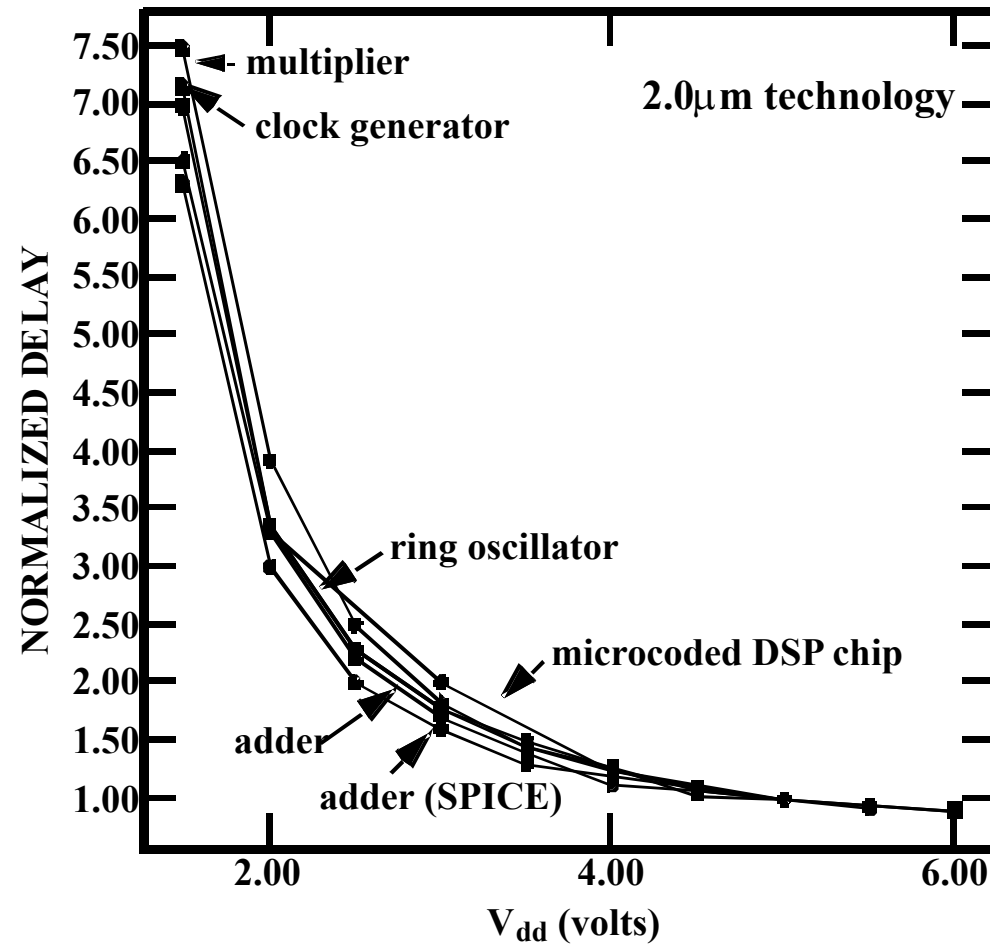


$$T_d = \frac{C_L * V_{dd}}{I}$$

$$I \sim (V_{dd} - V_t)^2$$

$$\frac{T_d(V_{dd}=2)}{T_d(V_{dd}=5)} = \frac{(2) * (5 - 0.7)^2}{(5) * (2 - 0.7)^2} \approx 4$$

- Relatively independent of logic function and style.

# Trade-off Between Power and Delay

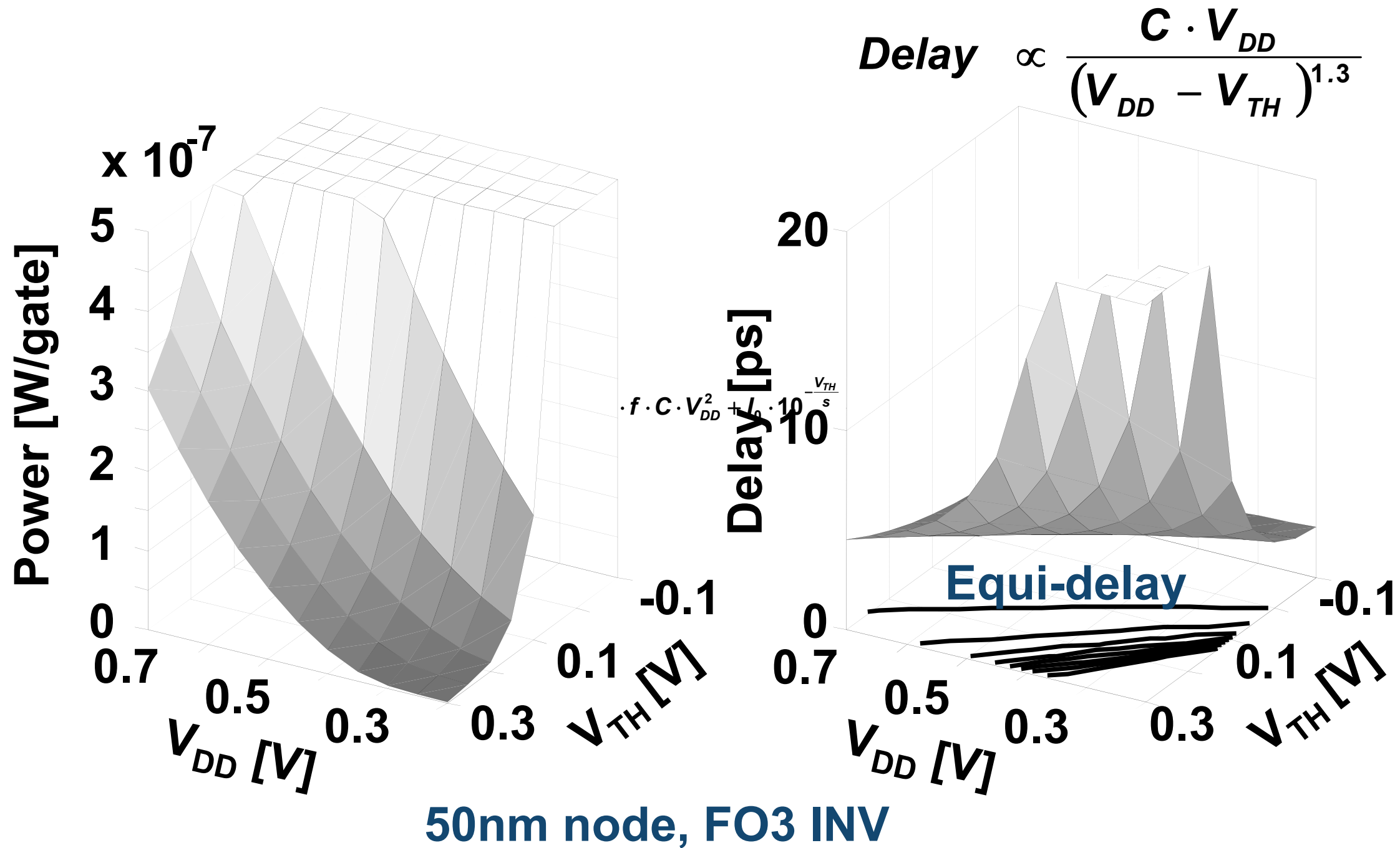


# Two Types of Processing

- Fixed-rate processing (e.g. signal processing for multimedia or communications)
  - Stream-based computation
  - No advantage in obtaining throughput in excess of the real-time constraint
- Variable-rate or burst-mode computation (e.g. general purpose computation)
  - Mostly idle (or low-load) with bursts of computation
  - Faster is better



# Architecture Trade-off for Fixed-rate Processing



## Reference Datapath

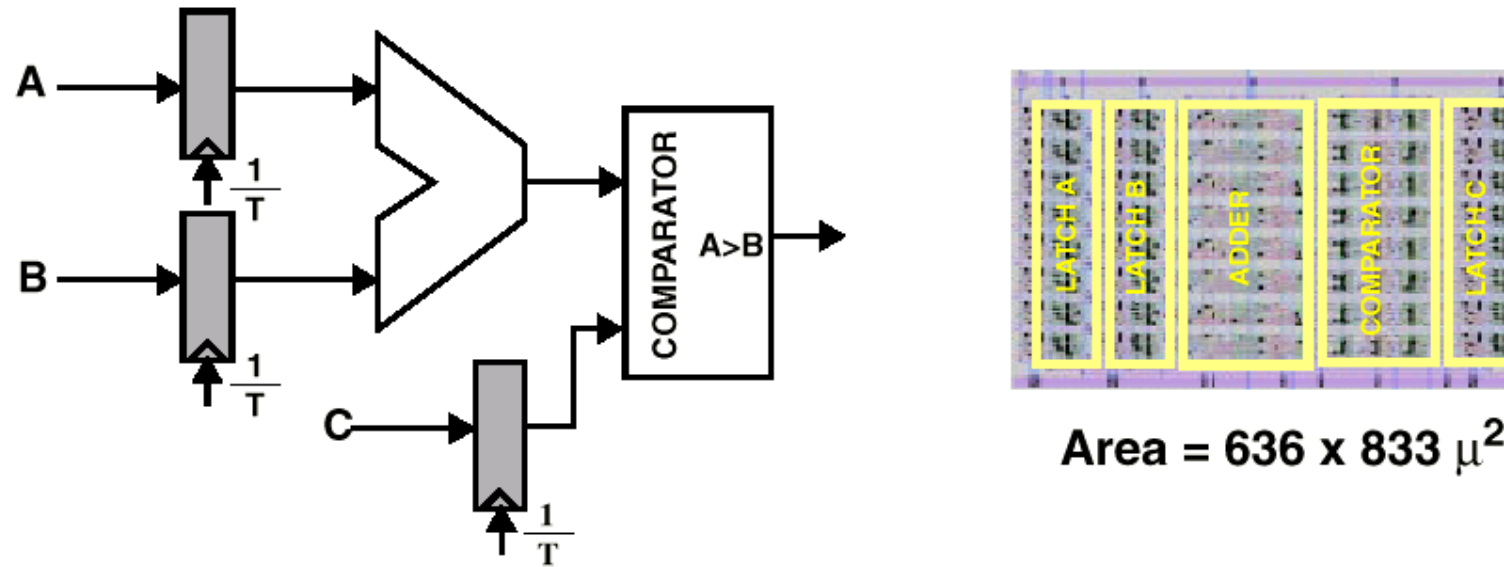

- Critical path delay  $\Rightarrow T_{\text{adder}} + T_{\text{comparator}} (= 25\text{ns})$   
 $\Rightarrow f_{\text{ref}} = 40\text{Mhz}$
- Total capacitance being switched =  $C_{\text{ref}}$
- $V_{\text{dd}} = V_{\text{ref}} = 5\text{V}$
- Power for reference datapath =  $P_{\text{ref}} = C_{\text{ref}} V_{\text{ref}}^2 f_{\text{ref}}$

from [Chandrakasan92] (*IEEE JSSC*)


# Parallel Datapath

  

Area = 1476 x 1219  $\mu^2$

- The clock rate can be reduced by half with the same throughput  $\Rightarrow f_{\text{par}} = f_{\text{ref}} / 2$
- $V_{\text{par}} = V_{\text{ref}} / 1.7$ ,  $C_{\text{par}} = 2.15C_{\text{ref}}$
- $P_{\text{par}} = (2.15C_{\text{ref}}) (V_{\text{ref}}/1.7)^2 (f_{\text{ref}}/2) \approx 0.36 P_{\text{ref}}$

# Pipelined Datapath

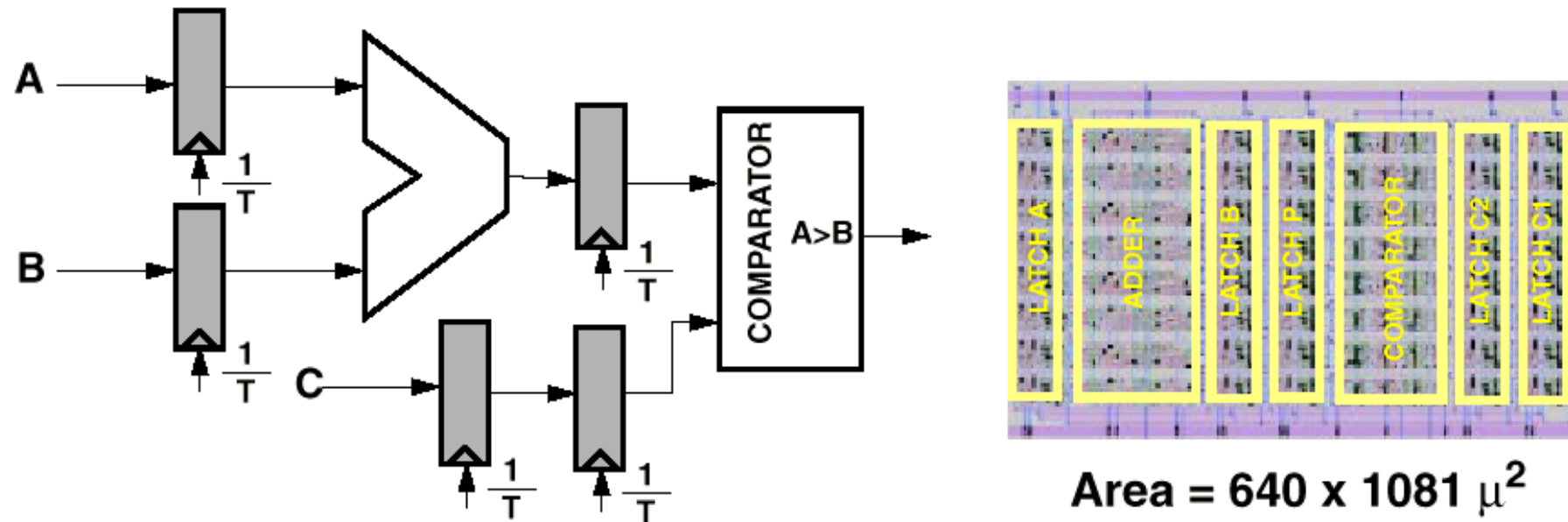

- Critical path delay is less  $\Rightarrow \max [T_{\text{adder}}, T_{\text{comparator}}]$
- Keeping clock rate constant:  $f_{\text{pipe}} = f_{\text{ref}}$   
Voltage can be dropped  $\Rightarrow V_{\text{pipe}} = V_{\text{ref}} / 1.7$
- Capacitance slightly higher:  $C_{\text{pipe}} = 1.15C_{\text{ref}}$
- $P_{\text{pipe}} = (1.15C_{\text{ref}}) (V_{\text{ref}}/1.7)^2 f_{\text{ref}} \approx 0.39 P_{\text{ref}}$

# A Simple Datapath: Summary

Architecture type	Voltage	Area	Power
Simple datapath (no pipelining or parallelism)	5V	1	<b>1</b>
Pipelined datapath	2.9V	1.3	0.39
Parallel datapath	2.9V	3.4	0.36
Pipeline-Parallel	2.0V	3.7	<b>0.2</b>

# Next Lecture

- Low-power design
  - Multiple supplies
  - Dynamic voltage scaling