 


EE241B : Advanced Digital Circuits

Lecture 24 – DTS, Clock

Borivoje Nikolić



The Promise and Pitfalls of Neuromorphic Computers, by Sunny Bains, EE Times, April 22, 2020.

<https://www.eetimes.com>

Announcements

- Assignment 4 due on Friday.
 - Quiz on Tuesday
- Last lecture on Tuesday
- Final on Thursday, April 30
- Project presentations on Monday, May 4
- Reading: Wong, JSSC, 2006


Outline

- Module 5
 - Dynamic threshold scaling
 - Optimal thresholds and supplies
- Module 6
 - Clock generation




5.M Dynamic Threshold Scaling

Dynamic Body Bias (Bulk)

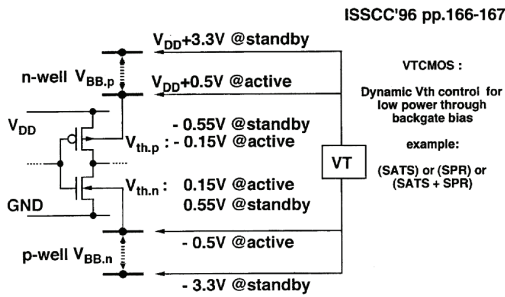


Switches between active and sleep

Dynamic Body Bias (Bulk)

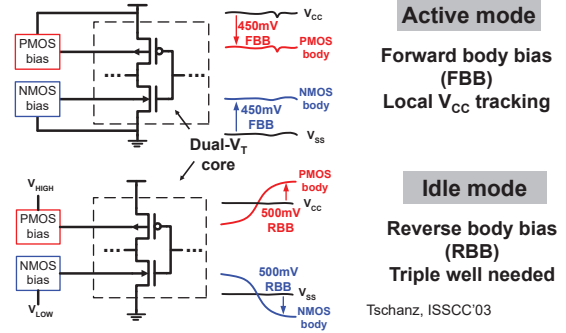


Body Bias Layout

 


Total Active Power Savings

(Fixed activity: $\alpha = 0.05$)

 

Generating Back-Bias

 
- Tradeoff – speed of charging and discharging well caps
- Often measure V_{BB} indirectly (leakage)
- Challenge: Generating $-V_{SS}$
- 28nm FDSOI implementation



 D. Jacquet, VLSI 2013

Generating Back Bias


- Fast and wide voltage range back-bias in FDSOI



M. Blagojevic, VLSI 2016

Switched capacitors generate negative bias and pump substrate

Supply/Process Compensation

 

- Able to track ~200mV supply droops and maintain constant frequency (measured by a replica) by back-bias adjustments

5.N Dynamic Threshold Scaling and Variations




Body Biasing and Variations

- Body biasing with a local control loop can be used to lower the impact of process variations
- Used to limit die-to-die and within-die variations

Self-Adjusting Threshold-Voltage Scheme (SATS)

 
- Older bulk technologies had stronger body effect



CICC'94, pp.271-274


low V_{th} → large leakage → SSB ON → deep V_{BB} → high V_{th}
 high V_{th} → little leakage → SSB OFF → shallow V_{BB} → low V_{th}
 • control V_{th} to adjust leakage current
 • compensate V_{th} fluctuation

Dynamic Frequency Loop in FDSOI

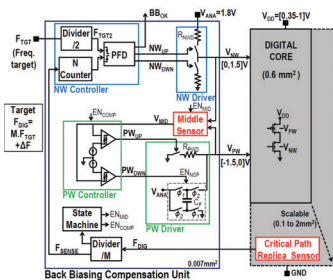

Quelen, ISSCC'18

Techniques Summary (around 130nm node)

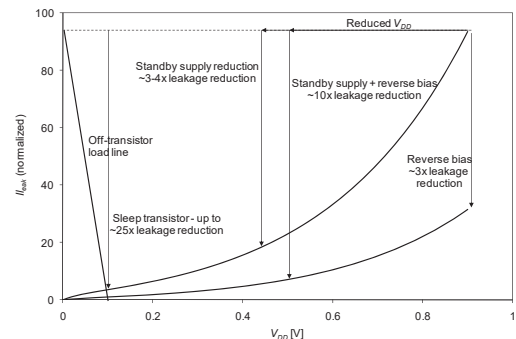


Power /Energy Optimization Space

	Constant Throughput/Latency		Variable Throughput/Latency
Energy	Design Time	Sleep Mode	Run Time
Active	Logic design Scaled V_{DD} Trans. sizing Multi- V_{DD}	Clock gating	DFS, DVS
Leakage	Stack effects Trans sizing Scaling V_{DD} + Multi- V_{Th}	Sleep T's Multi- V_{DD} Variable V_{Th} + Input control	+ Variable V_{Th}




5.0 Optimal V_{DD} , V_{Th}

Dynamic Voltage Scaled Microprocessor

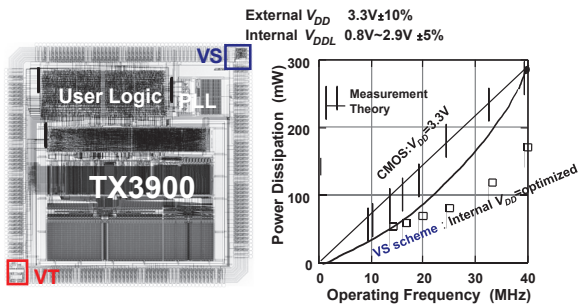


Adapting V_{DD} and V_{Th}

 

- Adapting both V_{DD} and V_{Th} during runtime
- V_{Th} is much less sensitive

Miyazaki, ISSCC'02

Adapting V_{DD} and V_{Th}

 


Miyazaki, ISSCC'02

Optimal V_{DD} , V_{Th}

- Adjusting V_{DD} , V_{Th} trades of energy and delay
- We studied energy-limited design
 - And alternate ways for optimizing energy and delay together
 - E.g. energy-delay product (EDP)
 - Or $E^m D^n$, $n, m > 1$

Optimal EDP Contours

 - Plot of EDP curves in V_{DD} , V_{Th} plane




Gonzalez, JSSC 8/97

Sizing, Supply, Threshold Optimization


Reference Design:	Topology	Inverter	Adder	Decoder
$D^{ref} (V_{dd}^{max}, V_{th}^{ref})$	$(E_L/E_{Sw})^{ref}$	0.1%	1%	10%

 Large variation in optimal circuit parameters V_{dd}^{opt} , V_{th}^{opt} , w^{opt}



Technology parameters (V_{dd}^{max} , V_{th}^{ref}) rarely optimal

Result: E-D Tradeoff in an Adder

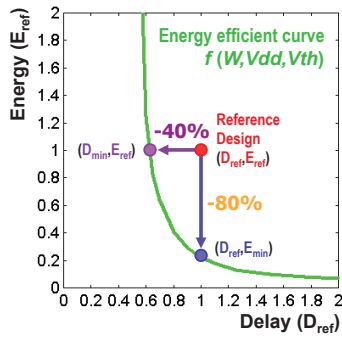

Sensitivity	W	Vdd	Vth
(D _{ref} , E _{ref})	∞	1.5	0.2
(D _{ref} , E _{min})		1	
(D _{min} , E _{ref})	22	16	22

80% of energy saved without delay penalty

40% delay improvement without energy penalty

Energy-constrained delay

- Active power

$$P_{act} = \alpha f C V_{DD}^2$$

$$f = 1/L_D t_p$$


- Leakage power

$$P_{leak} = I_0 e^{\frac{-V_{Th} - \gamma V_{DD}}{S}} V_{DD}$$

- Eliminate one variable (V_{Th}) and find $P_{min}(V_{DD})$

Nose, ASP-DAC'00

Minimum energy: $E_{Sw} = 2E_{Lk}$

 


- Large $(E_{Lk}/E_{Sw})^{opt}$
- Flat E_{Op} minimum
- Topology dependent


$$(E_{Lk}/E_{Sw})_{opt} = \frac{2}{\ln\left(\frac{L_d}{\alpha_{avg}}\right) - K}$$

Optimal designs have high leakage ($E_{Lk}/E_{Sw} \approx 0.5$)

Subthreshold Optimum

 

$f = 30\text{kHz}$

 

Minimum is independent of V_T

Calhoun, JSSC 9/05




6. Clocks and Supplies

Clock Subsystem

- Clock Generation
- Clock Distribution
- Synchronization

Clock Subsystem

 - Intel Xeon – Bowhill, ISSCC'15
 - Independent clocks for 4-18 cores
- Self-biased (SB) and LC PLLs




6.B Clock Generation




Clock Generation


Delay-Locked Loop (Delay Line Based)

 

Phase-Locked Loop (VCO/DCO-Based)

 

PLL Signals

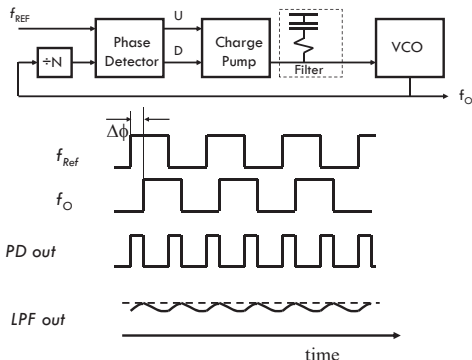


Loop Performance

• Ideal clock

> Clock w/ jitter



 
> Phase offset, peak-to-peak jitter, RMS jitter



> Bandwidth, locking time, frequency range


Phase Detector

• Detects the phase difference


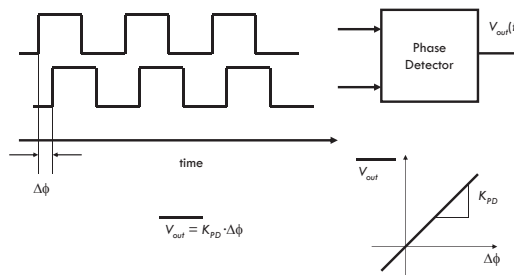


Delay-Locked Loop

 
- First order loop: inherently stable
- No filtering of input jitter
- Constant frequency (no synthesis)
- No phase error accumulation



DLL Locking

  

Delay-Locked Loop

 


> Open loop transfer function

$$\frac{D_O(s)}{D_I(s) - D_O(s)} = K_{PD} \frac{1}{sC} I_{CP} K_{DL} F_{REF} = \frac{1}{s} K_{PD} K_F K_{DL}$$

> Closed loop transfer function

$$H(s) = \frac{D_O(s)}{D_I(s)} = \frac{K_{PD} K_F K_{DL}}{s + K_{PD} K_F K_{DL}}$$


Delay-Locked Loop

 

- $\omega_N >$ an order of magnitude below F_{REF}
- Use of DLLs requires low-jitter input
- VCDL must span adequate delay range + reset to min delay
- Noise sources:
 - Delay line (Supply sensitivity)
 - Clock buffers that follow
 - Device noise (small)

Voltage-Controlled Delay Line

 - Delay controlled by voltage with proportionality K_{DL}



DLL Use

18CS2418 L24 CLOCK


18CS2418 L24 CLOCK

 6.C Clock Generation: PLLs



Phase-Locked Loop

- PLL is locked when the phase difference is zero
- Second/third order loop
- $\pm N$ for frequency synthesis (and $\times M$)
- Filters input jitter
- Accumulates phase error




Voltage-Controlled Oscillator

- Oscillation frequency controlled by voltage



$$\omega_{out} = \omega_{FR} + K_{VCO} V_{ctrl}$$
 
$$y_{out}(t) = A \cos(\omega_{FR} t + K_{VCO} \int_{-\infty}^t V_{ctrl} dt)$$



ω_{FR} - free-running frequency

18CS2418 L24 CLOCK

18CS2418 L24 CLOCK

PLL vs. DLL Dynamics


- The key difference is in the VCDL vs. VCO transfer characteristics
- VCO integrates (accumulates) phase

$$H_{VCO}(s) = K_{VCO}/s$$


18CS2418 L24 CLOCK

Example VCO

- Ring-oscillator-based VCO: RC loaded

 
 
> Ring-oscillator-based VCO: Current-starved




18CS2418 L24 CLOCK

18CS2418 L24 CLOCK

Charge Pump


- Push/pull current source operation

 

18CS2418 L24 CLOCK

18CS2418 L24 CLOCK

Charge-Pump PLL

 


Phase transfer function


$$H(s) = \frac{\frac{K_{PFD} \cdot K_{VCO}}{s}}{1 + \frac{K_{PFD} \cdot K_{VCO}}{s}} = \frac{K_{PFD} K_{VCO}}{s^2 + K_{PFD} K_{VCO}}$$

Charge Pump PLL with a Zero

 - Charge pump PLL has a stability problem
- Compensation by adding a zero



Charge Pump PLL with a Zero

 


$$\omega_n = \sqrt{\frac{I}{2\pi C_P} K_{VCO}}$$

$$\zeta = \frac{R}{2} \sqrt{\frac{I C_P}{2\pi} K_{VCO}}$$

$$H(s) = \frac{\frac{K_{VCO} \cdot I}{2\pi C_P} \cdot (RC_P s + 1)}{s^2 + \frac{I}{2\pi} K_{VCO} R s + \frac{I}{2\pi C_P} K_{VCO}}$$


Higher Order Loops

 - Another pole naturally exists
 - Filters the control voltage V_{CTRL}
 - Lowers phase margin
 - Reduces the lock range




Phase Noise at the PLL Input

- Low-pass characteristic

 

 
$$H(s) = \frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$




VCO Phase Noise

- High-pass characteristic

 
 
$$\frac{\Phi_{out}(s)}{\Phi_{VCO}(s)} = \frac{s(s + \omega_{LPF})}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$



Next Lecture

- Finish clocks and supplies
- Finale