

EE241B : Advanced Digital Circuits

Lecture 25 – Power Supply

Borivoje Nikolić



Time for course surveys!

Course Evaluations: Best Practices for Faculty

Reserve time in-class.

Give students time during class to complete the online course survey. Anecdotally, this is more effective when the time set aside is at the **start** of class.



Inform students about the purpose of evaluations.

Give students examples of useful feedback you have received in the past and **how** the course has changed or benefited.



Offer students incentives (e.g. extra credit).

To encourage broad, representative responses, instructors may choose to offer incentives to complete evaluations. An effective strategy has been to offer all students extra credit if a **minimum percentage** of students (e.g. 85%) respond.

85% ✓




Announcements

- Quiz today!
- Final on Thursday, April 30, 9:30-11 am
- Project presentations on Monday, May 4
- Course surveys:
 - <https://drive.google.com/file/d/1saRVPwUtLIRBApUzZ0Y9XAAG9vAhFkdV/view>



Outline

- **Module 6**
 - Supply distribution

 




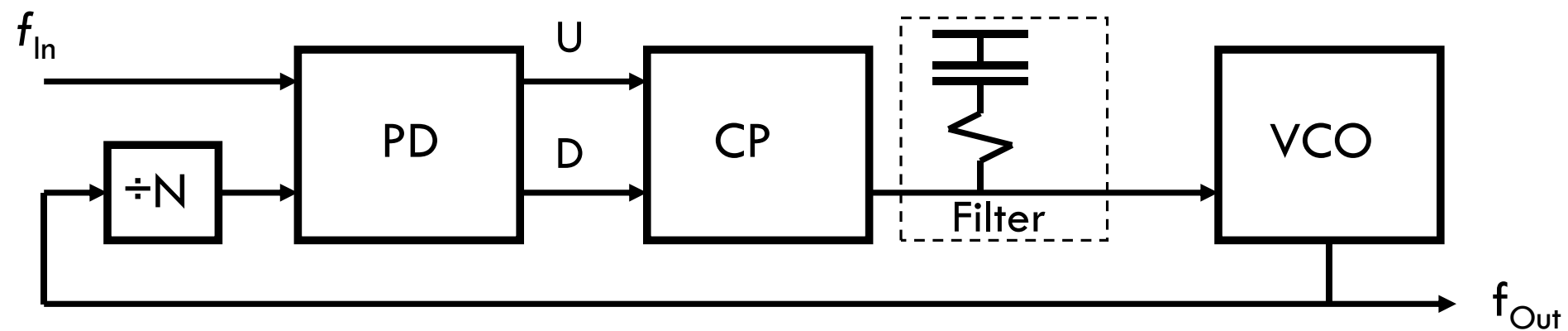6.C Clock Generation: PLLs


Phase-Locked Loop

- PLL is locked when the phase difference is zero
- Second/third order loop
- $\div N$ for frequency synthesis (and $\times M$)
- Filters input jitter
- Accumulates phase error




Voltage-Controlled Oscillator

 - Oscillation frequency controlled by voltage



$$\omega_{out} = \omega_{FR} + K_{VCO}V_{ctrl}$$

 
$$y_{out}(t) = A \cos\left(\omega_{FR}t + K_{VCO} \int_{-\infty}^t V_{ctrl} dt\right)$$




ω_{FR} – free-running frequency

Example VCO

- Ring-oscillator-based VCO: RC loaded

 

 - Ring-oscillator-based VCO: Current-starved




PLL vs. DLL Dynamics

- The key difference is in the VCDL vs. VCO transfer characteristics
- VCO integrates (accumulates) phase


$$H_{VCO}(s) = K_{VCO}/s$$

Charge Pump

- Push/pull current source operation

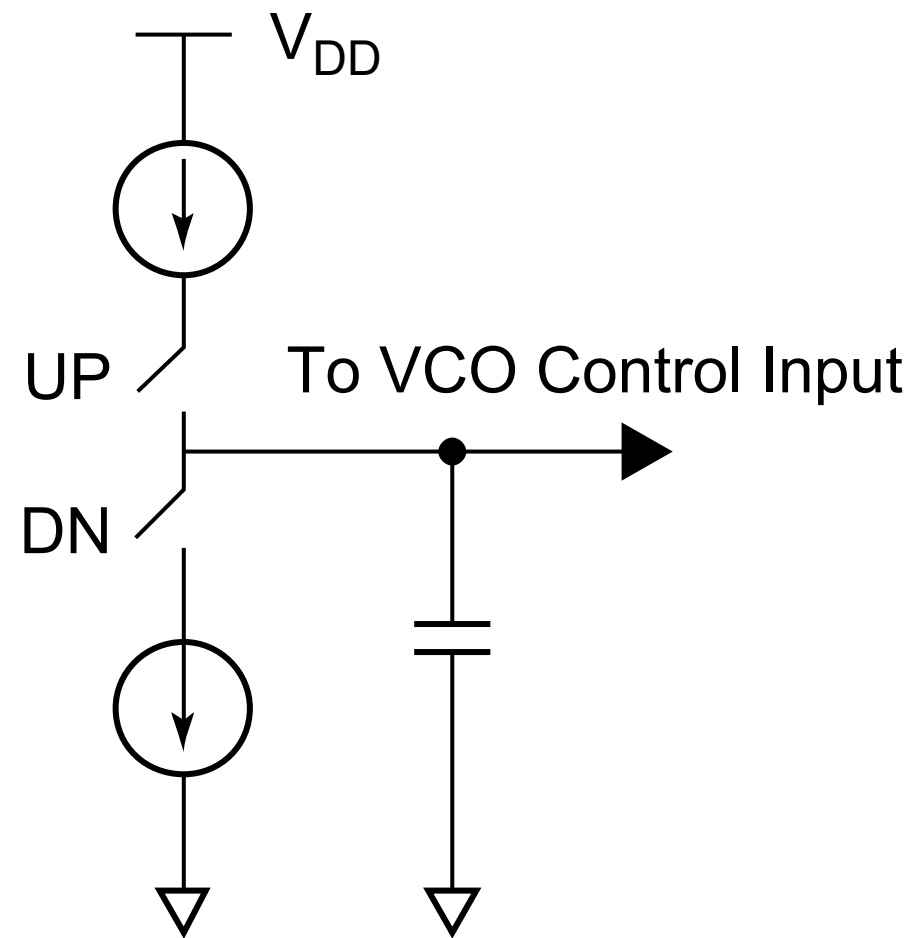

Charge-Pump PLL

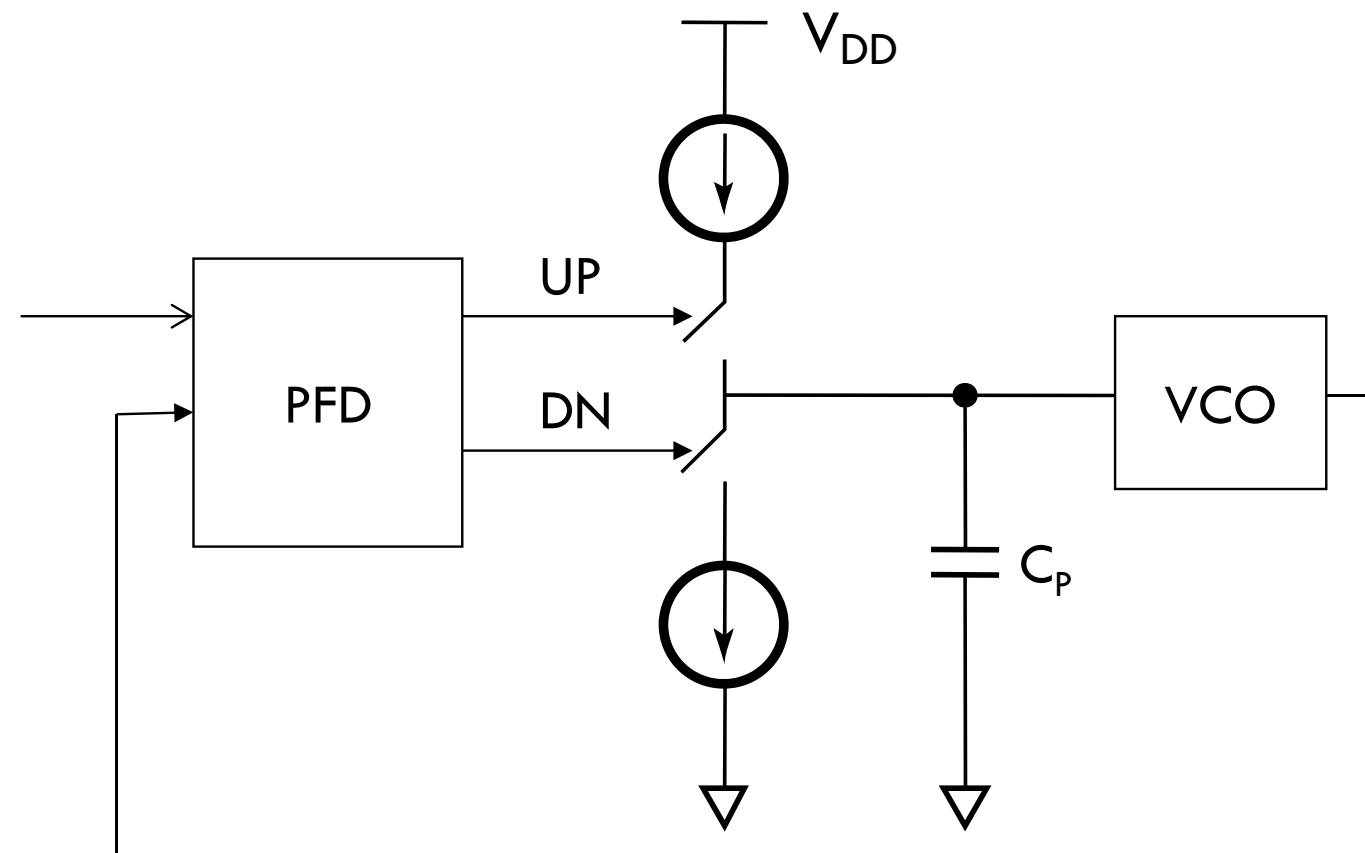


- Phase transfer function


$$H(s) = \frac{\frac{K_{PFD}}{s} \cdot \frac{K_{VCO}}{s}}{1 + \frac{K_{PFD}}{s} \cdot \frac{K_{VCO}}{s}} = \frac{K_{PFD}K_{VCO}}{s^2 + K_{PFD}K_{VCO}}$$

Charge Pump PLL with a Zero

 - Charge pump PLL has a stability problem
- Compensation by adding a zero



Charge Pump PLL with a Zero

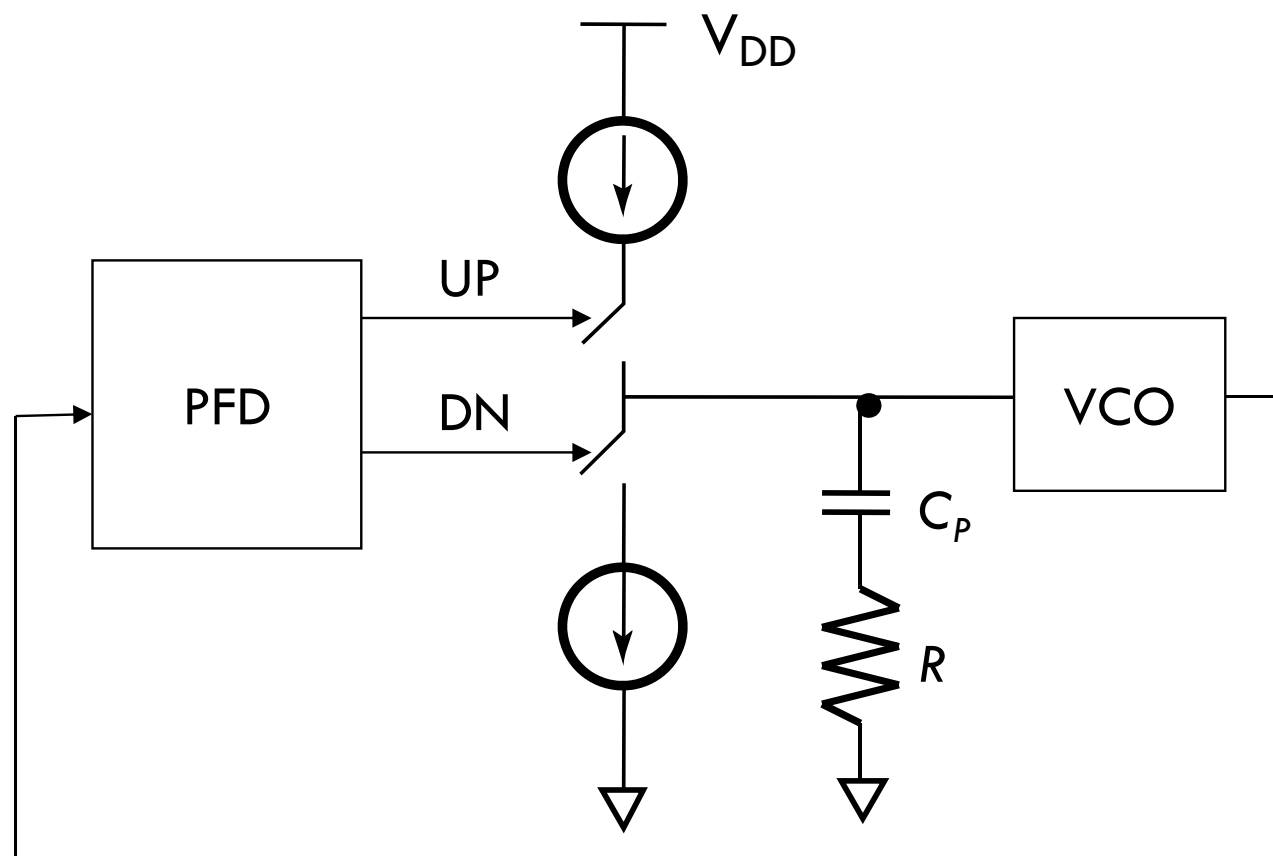


$$\omega_n = \sqrt{\frac{I}{2\pi C_P} K_{VCO}}$$

$$\zeta = \frac{R}{2} \sqrt{\frac{I C_P}{2\pi} K_{VCO}}$$

$$H(s) = \frac{\frac{K_{VCO} \cdot I}{2\pi C_P} \cdot (RC_P s + 1)}{s^2 + \frac{I}{2\pi} K_{VCO} R s + \frac{I}{2\pi C_P} K_{VCO}}$$


Higher Order Loops

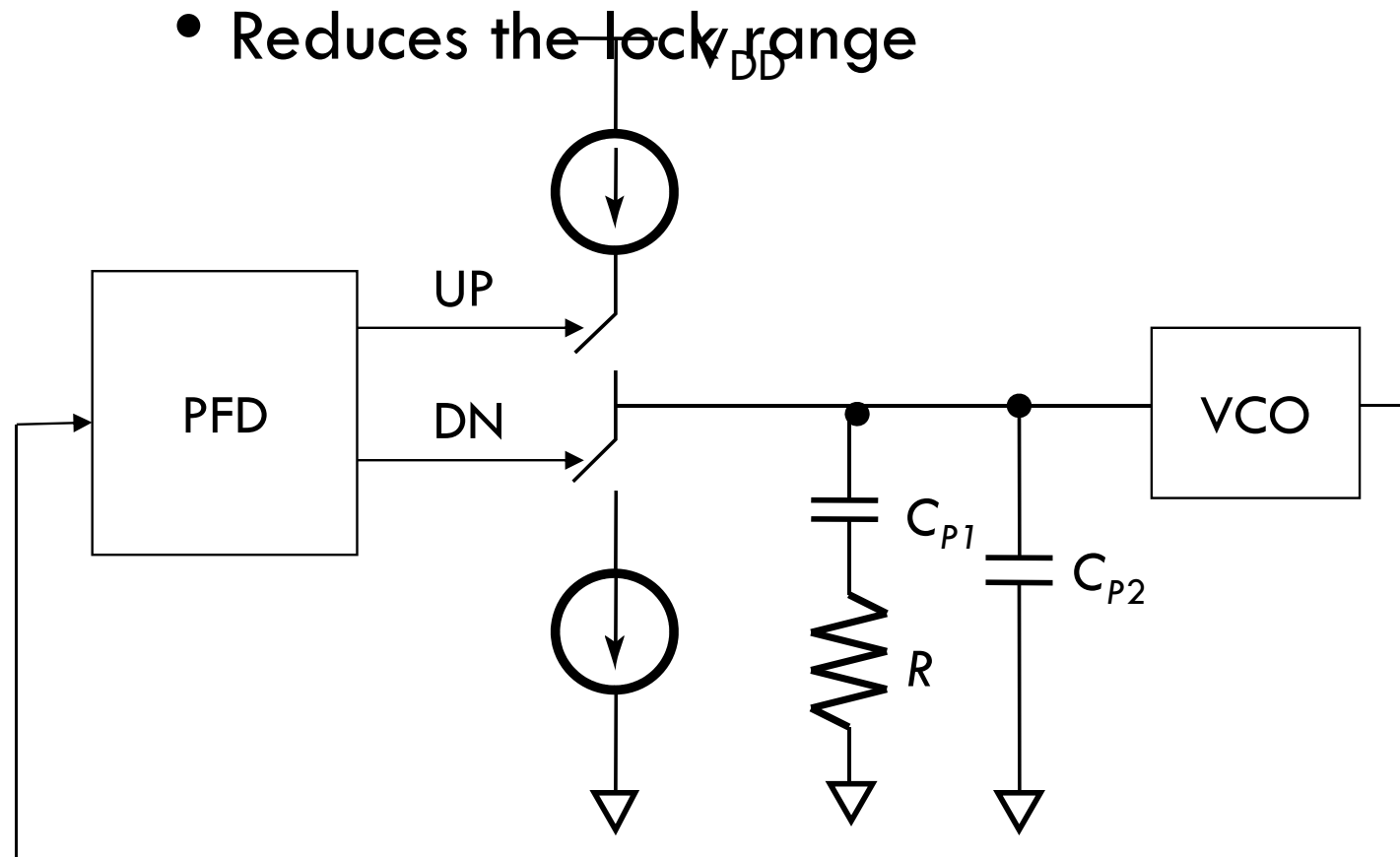- Another pole naturally exists
 - Filters the control voltage V_{CTRL}
 - Lowers phase margin
 - Reduces the lock range




Phase Noise at the PLL Input

- Low-pass characteristic

 


$$H(s) = \frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

$|\log \Phi_{out}/\Phi_{in}|$

 


VCO Phase Noise

- High-pass characteristic

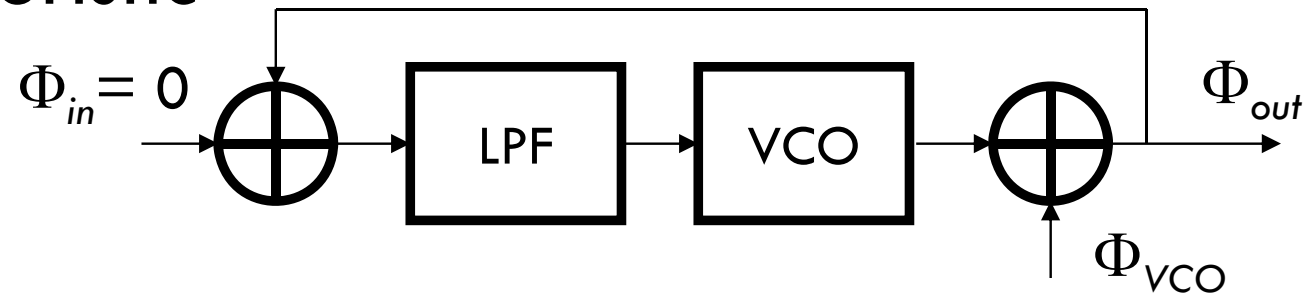
 
$$\frac{\Phi_{out}(s)}{\Phi_{VCO}(s)} = \frac{s(s + \omega_{LPF})}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$







6.D Interaction with Supply


Power Delivery

- Decoupling in Core i7

Andreas Hopf/Flickr

  



Skylake-SP, ISSCC'18

 


- Decoupling in Skylake-SP

Integrated VR Technology

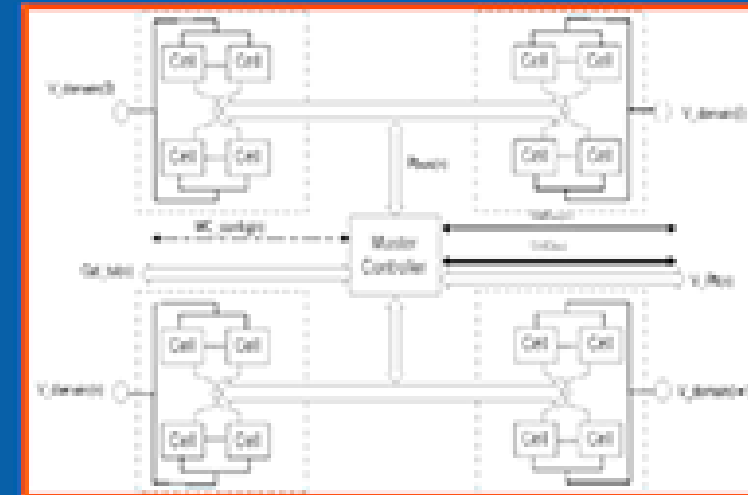 - 'Common Cell' Architecture – 20 cells
- Architecture supports flat efficiency curve
- Fine grain power management
 - Allows for multiple voltage rails
- Telemetry and Margining features
- Active Voltage Positioning for current sharing and balance
- Control features, including: JTAG, FPGA, Test/BIST




General Arch

 



12.977mm



8.144mm

 


Power cell
- 2.8 mm²

  

Review: Power Cell Architecture

 - **Each Power cell = Mini VR**
 - Up to 25A rating* - tested
 - Programmable switching frequency 30MHz to 140MHz
 - Ring coupled inductor topology
- **16 phases per power cell, 320 phases per chip**
 - High phase count reduces noise, ripple
 - High granularity
 - Cell shedding
 - Bridge shedding
- **BIST**
 - Self-load and characterization system.



* Thermally constrained



Intel Broadwell



- Inductors moved to a small PCB



HSW U/Y
40x24x1.5mm





BDW-Y
30x16.5x1.04mm

  

Power Delivery

- Typical model

 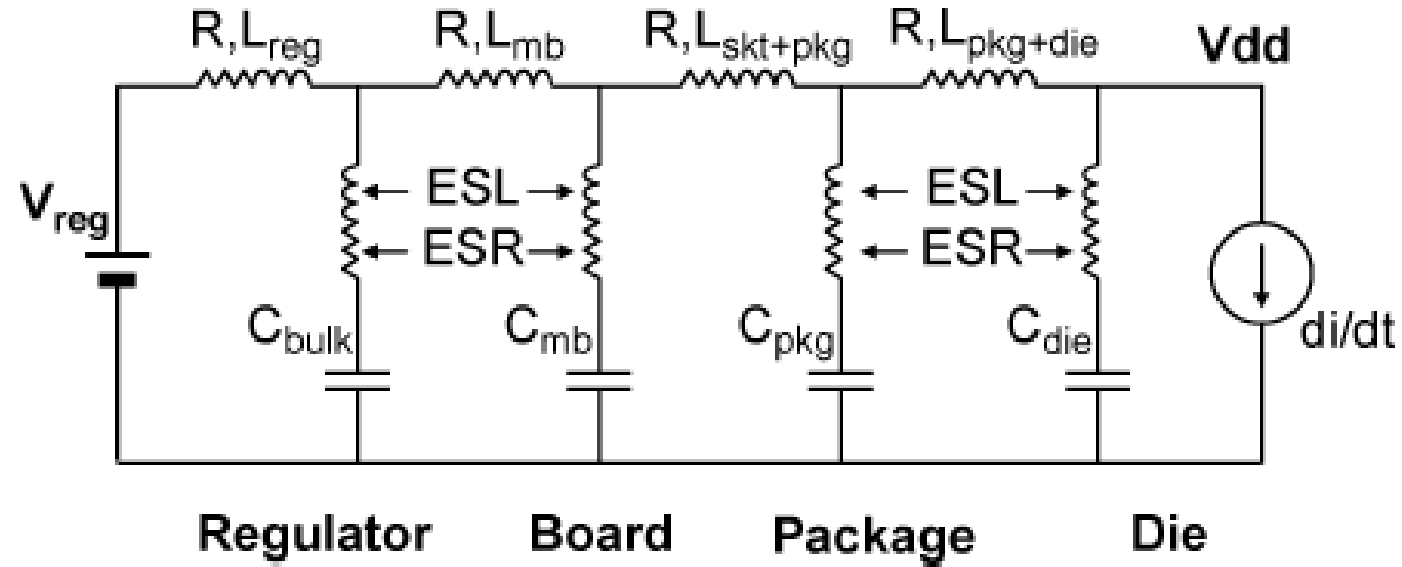


Wong, JSSC'06

Supply Resonances

- **First droop**
 - Package L + on-die C
- **Second droop**
 - Motherboard + package decoupling
- **Third droop**
 - Board capacitors


What happens with supply?

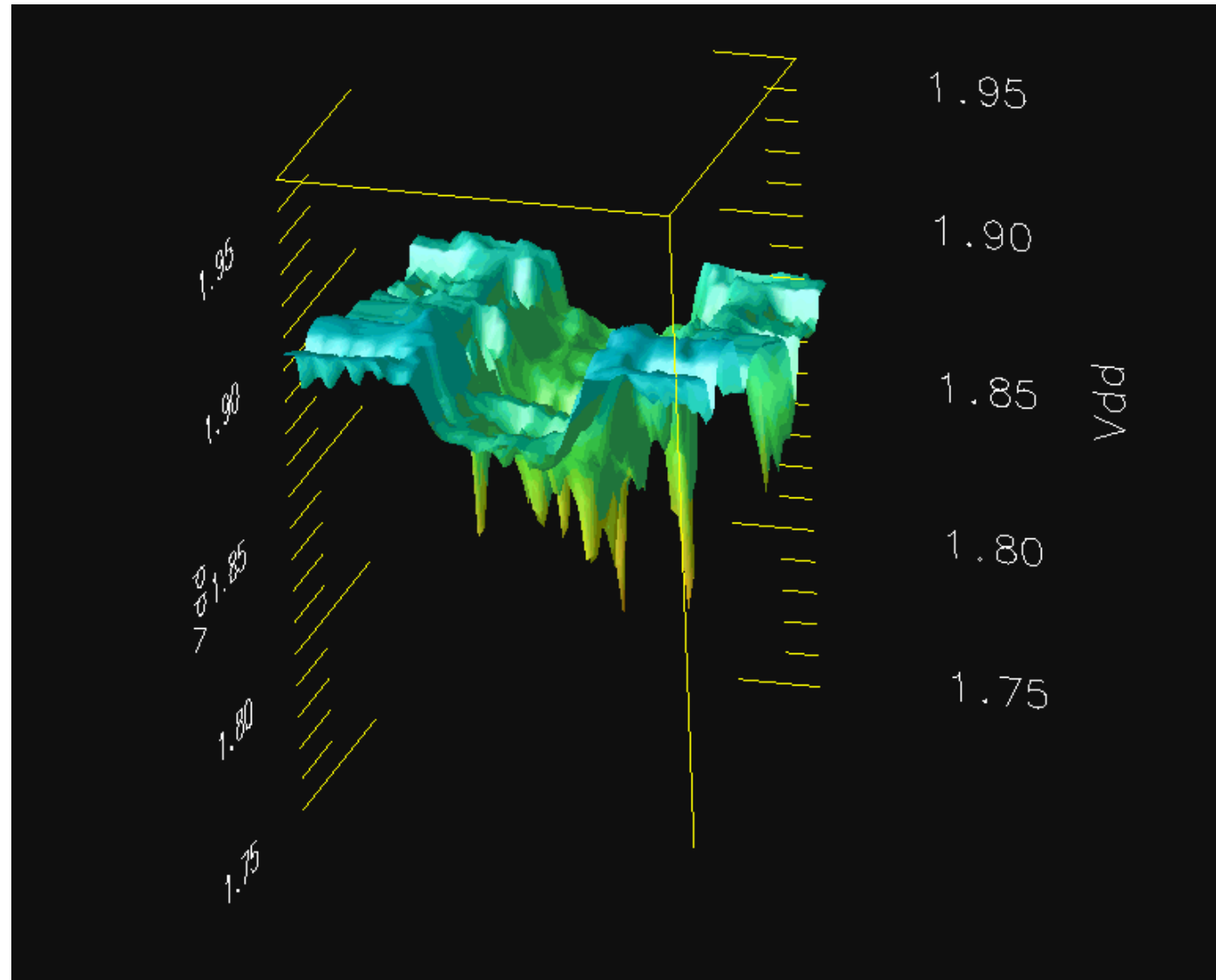http://www.research.ibm.com/people/r/restle/Animations/DAC01_top.html



How to model

- Abstracted delay line




 


Wong, JSSC'06

Period modulation from successive modulated delays

Droop Detection

- Hashimoto, JSSC 4/18

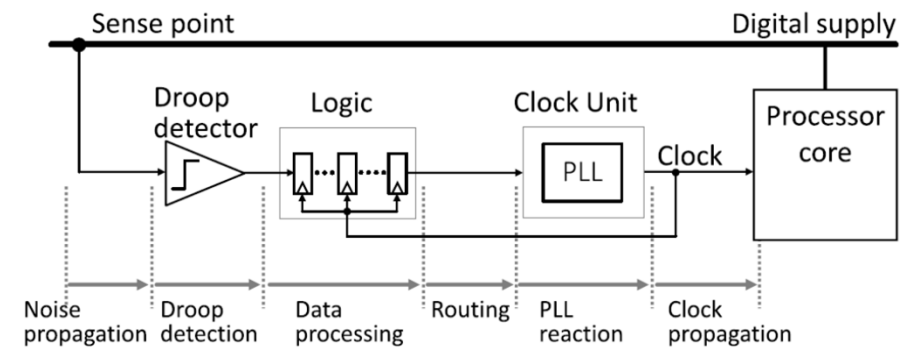 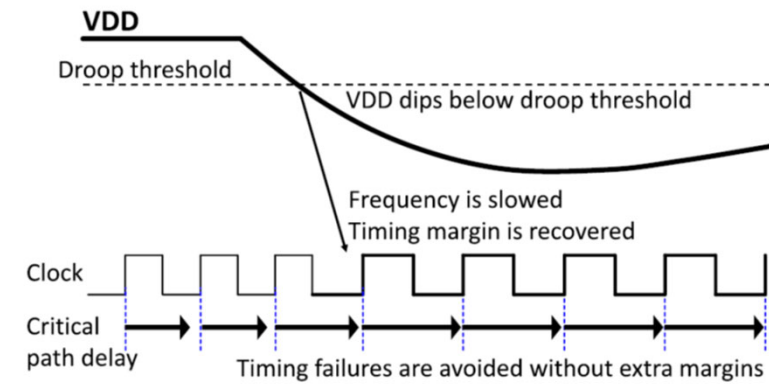 

This Class

- Put design choices in technology perspective
- The design constraints have changed and will be changing
 - Cost, energy, (power, leakage, ...), performance
- Focused on variability, power-performance tradeoffs, power management
- Did not cover arithmetic, domino, I/O, supply generation, packaging, ...


This Field

- Moore's law will end sometime during your (my?) career
 - 5nm in 2020 scales to 0.1nm by 2050 with 2-yr cycles (or to 1nm with 4-yr cycles)
- Physics will stop CMOS somewhere $\sim 3\text{nm}$ (?)
 - Will we see a different CMOS device in the meantime
- Economics will likely stop it somewhere while still in single digits
 - And the nodes will be stretched out
- We will see multi-chip/packaging solutions
- Don't worry: Creativity is unlimited!
 - What can you build with 10B/100B/1 trillion transistors?
 - Even filling 10B-transistor chips with SRAM is not trivial!



This Field

 - Focus on principles
- Watch out for opportunities
- Stay current!



Technology Strategy / Roadmap

2000

2005

2010


2015

2020


2025

2030


Plan A: Extending Si CMOS

 

Plan B: Subsystem Integration

 

Plan C: Post Si CMOS Options

 

Plan Q: Quantum Computing

