 


EE241B : Advanced Digital Circuits

Lecture 5 – Leakage, Delay Models

Borivoje Nikolić



The passing of Barrie Gilbert (1937-2020). He was well known for his invention of numerous analog circuit concepts, holding over 100 patents worldwide, and for the discovery of the Translinear Principle. His name is attributed to a class of related topologies loosely referred to as the Gilbert cell, one of which is a mixer - a key frequency translation device - used in every modern wireless communication device.



Announcements

- Homework 1 posted today, due in 2 weeks

Outline


- Module 2
 - MOS transistor leakage
 - C-V models
 - Delay revisited

Recap last lecture

- Scaled transistors are different than the ones in textbooks
- But the same principles still apply
- Sizing:
 - P/N ratio is set by mobilities
 - Mobility enhancements are more effective on PMOS devices
 - ~1:1 in sub 16nm
 - Stack sizing set by velocity saturation
 - Stack of 2 reduces NMOS current by ~2/3
 - PMOS depends on the degree of saturation, also ~2/3 in sub 16nm

Recap last lecture: Logical Effort

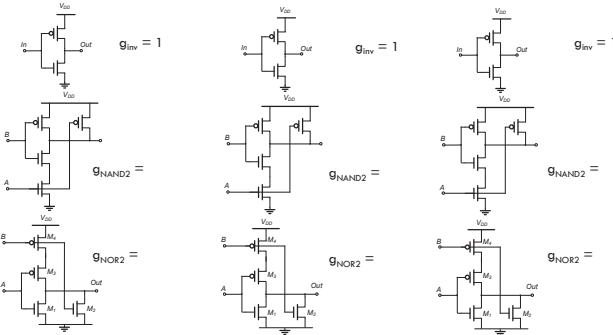- Older CMOS (>1µm)
- Planar CMOS (~28nm, bulk, FDSOI)
- FinFET (16nm-7nm)



2.E Other Velocity Saturation Models




Other Models: Alpha Power Law Model

- Simple model, sometimes useful for hand analysis

$$I_{DS} = \frac{W}{2L} \mu C_{ox} (V_{GS} - V_{Th})^\alpha$$

Parameter α is between 1 and 2.

 


Sakurai, Newton, JSSC 4/90

Alpha Power Law Model

- This is not a physical model
- Simply empirical:
 - Can fit (in minimum mean squares sense) to variety of α 's, V_{Th}
 - Need to find one with minimum square error – fitted V_{Th} can be different from physical
 - Can also fit to $\alpha = 1$
 - What is V_{Th} ?

$K(V_{GS} - V_{THZ})$ Model ($\alpha = 1$)

Drain current vs. gate-source voltage

 

Saturation Currents


Model	Usage
$I_{DS} = K \frac{W}{L} (V_{GS} - V_{THZ})$	Delay estimates with $V_{DD} \gg V_{TH}$
$I_{DS} = \frac{W}{L} \frac{\mu C_{ox}}{2} (V_{GS} - V_{TH})^2$	Long channel devices (rare in digital)
$I_{DS} = \frac{W}{L} \frac{\mu C_{ox}}{2} (V_{GS} - V_{TH})^\alpha$	Delay estimates in a wider range of V_{DD} 's
$I_{DS} = \frac{W}{L} \mu C_{ox} \left((V_{GS} - V_{TH}) V_{DSat} - \frac{V_{DSat}^2}{2} \right)$	Easy to remember, does not handle stacks correctly
$I_{DS} = \frac{W}{L} \frac{\mu C_{ox}}{2} \frac{E_C L (V_{GS} - V_{TH})^2}{(V_{GS} - V_{TH}) + E_C L}$	Handles stacks correctly, sizing

2.F Transistor Leakage




Transistor Leakage

Transistor Leakage

 


Leakage current is exponential with V_{GS}

Transistor Leakage (130nm)

 

- Two effects:
- diffusion current (like a bipolar transistor)
 - exponential increase with V_{DS} (DIBL)

Transistor Leakage (32nm LP PTM)

 

Another view of DIBL
>10x increase in leakage

Subthreshold Current

- Subthreshold behavior can be modeled physically

$$I_{ds,subth} = \mu_{eff} C_{ox} \frac{W}{L} (m-1) \left(\frac{kT}{q} \right)^2 e^{\frac{V_{GS} - V_{th}}{m k T / q}} \left(1 - e^{-\frac{V_{DS}}{k T / q}} \right)$$

$$m = 1 + \frac{C_{dm}}{C_{ox}} \quad (m \sim 1.1-1.4)$$


Or (approx):

$$I_{ds,subth} = I_0 \frac{W}{W_0} 10^{\frac{(V_{GS} - V_{th}) - \gamma V_{DS}}{S}}$$

Taur, Ning, Modern VLSI Devices

$$S = 2.3m \frac{kT}{q}$$


Leakage Components

 

Courtesy of IEEE Press, New York. © 2000

Leakage Components (250nm)

 1. pn junction reverse bias current
2. Weak inversion
3. Drain-induced barrier lowering (DIBL)
4. Gate-induced drain leakage (GIDL)
5. Punchthrough
6. Narrow width effect
7. Gate oxide tunneling
8. Hot carrier injection



Leakage Components


- Drain-induced barrier lowering (DIBL)
 - Voltage at the drain lowers the source potential barrier
 - Lowers V_{th} no change on S
- Gate-induced drain leakage (GIDL)
 - High field between gate and drain increases injection of carriers into substrate -> leakage (band-to-band leakage)



2.H Transistor C-V

MOS Transistor as a Switch

Discharging a capacitor

 

• Can solve:

$$i_{DS} = i_{DS}(V_{DS})$$

$$i_{DS} = C(V_{DS}) \frac{dv_{DS}}{dt}$$

- Prefer using equivalent resistances
- Find t_{pHL}
- Find equivalent C, R

$$t_{pHL} = \int \frac{C(V_{DS}) dv_{DS}}{i_{DS}(V_{GS}, V_{DS})}$$

MOS Capacitances

- Gate capacitance
 - Non-linear channel capacitance
 - Linear overlap, fringing capacitances
 - Miller effect on overlap, fringing capacitance
- Non-linear drain diffusion capacitance
 - PN junction
- Wiring capacitances
 - Linear

Gate and Drain Capacitances


Gate capacitance

Gate Capacitances

Drain capacitance


Gate Capacitances

- Gate capacitance is non-linear
 - First order approximation with $C_{ox}WL$ ($C_{ox}L = 2fF/\mu m$)
- Need to find the actual equivalent capacitance by simulating it
- Since this is a linear approximation of non-linear function, it is valid only over the certain range
 - Different capacitances for HL, LH transitions and power computation
- Drain capacitance non-linearity compensates
 - But this changes with fanout

 

2.1 Delay Revisited

MOS Transistor as a Switch (EECS251A)

 

MOS Transistor as a Switch (EE241A)

Solving the integral:

$$R_{eq} = \frac{1}{-V_{DD}/2} \int_{V_{DD}/2}^{V_{DD}} \frac{V}{I_{DSAT}(1 + \lambda V)} dV \approx \frac{3}{4} \frac{V_{DD}}{I_{DSAT}} \left(1 - \frac{2}{9} \lambda V_{DD}\right)$$


with appropriately calculated I_{dsat}

Averaging resistances:


$$R_{eq} = \frac{1}{2} \left(\frac{V_{DD}}{I_{DSAT}(1 + \lambda V_{DD})} + \frac{V_{DD}/2}{I_{DSAT}(1 + \lambda V_{DD}/2)} \right) \approx \frac{3}{4} \frac{V_{DD}}{I_{DSAT}} \left(1 - \frac{5}{6} \lambda V_{DD}\right)$$

CMOS Performance

 Propagation delay: $t_{pHL} = (\ln 2) R_{eqn} C_L$ $t_{pLH} = (\ln 2) R_{eqp} C_L$




Switching Trajectory

 

Effective Current

 
- $I_{on}(V_{DD})$ is never reached
- Define $I_{eff} = (I_H + I_L)/2$
- $I_L = I_{DS}(V_{GS}=V_{DD}/2, V_{DS}=V_{DD})$; $I_H = I_{DS}(V_{GS}=V_{DD}, V_{DS}=V_{DD}/2)$,



DIBL Matters


• A. Loke, VLSI'16

• FinFET, FDSOI – less DIBL

 



Less DIBL \rightarrow higher I_{eff} & r_{out} for same I_{Dsat}

Transistor Stacks

 


Effective Current in Stacks

➤ Add linear current, I_3

  

Model: $I_{stack1} = C_{I1} I_1 + C_{I2} I_2 + C_{I3} I_3 \Rightarrow$
 Inverter: $I_{stack1} = 0.45 I_1 + 0.48 I_2 + 0.07 I_3$
 NAND2/NOR2: $I_{stack2} = 0.18 I_1 + 0.38 I_2 + 0.44 I_3$
 NAND3/NOR3: $I_{stack3} = 0.08 I_1 + 0.36 I_2 + 0.56 I_3$

Von Arnim, IEDM'2007

 

Next Lecture

- Standard Cells

