

# EE241B : Advanced Digital Circuits

## Lecture 7 – Static Timing

**Borivoje Nikolić**



**February 7, 2020, (Inc.) Elon Musk Says He's About to Deliver the Future of High-Speed Internet.**

**Get your investment dollars ready.**

Elon Musk has been saying for years that he believes the future of the internet resides in space. And now he's planning to make a major change that could facilitate that transition sooner rather than later.

In a move that could send shock waves through the internet space, SpaceX is planning to spin out its Starlink satellite-based internet service into its own entity. It'll also make Starlink public, allowing investors to get a piece of what Musk believes is the future of internet connectivity.



# Announcements

- Homework 1 due on February 17
- No class on February 18 (ISSCC)
- Project abstracts due on February 20
  - Teams of 2
  - Title
  - One paragraph
  - 5 relevant references

# Outline


- **Module 2**
  - Standard cells
  - Static timing




## 2.L Delay Revisited
 
# How to Account for Input Slope?

$$t_p = \ln 2 RC = 0.7 R_{eq} C_L$$
$$T_{r,10-90} = 2.2 R_{eq} C_L$$
$$T_{r,20-80} = 1.4 R_{eq} C_L$$




- $t_{pHL} = 0.7 R_{eq} C_L$

 

- $t_{pHL} = 0.7 R_{eq} C_L$

different  $R_{eq}$ !

# Input Slope Dependence

 


$$I_{out} = C_L \frac{dV_{out}}{dt} = I_{NMOS} - I_{PMOS}$$

- One way to analyze slope effect
  - Plug non-linear I-V into diff. equation and solve...
- Simpler, approximate solution:
  - Use  $V_{ThZ}$  model

# Slope Analysis

- For falling edge at output:
  - For reasonable inputs, can ignore  $I_{PMOS}$
  - Either  $V_{DS}$  is very small, or  $V_{GS}$  is very small
- So, output current ramp starts when  $V_{in} = V_{ThZ}$ 
  - Could evaluate the integral
  - Learn more by using an intuitive, graphical approach

# Slope Dependence

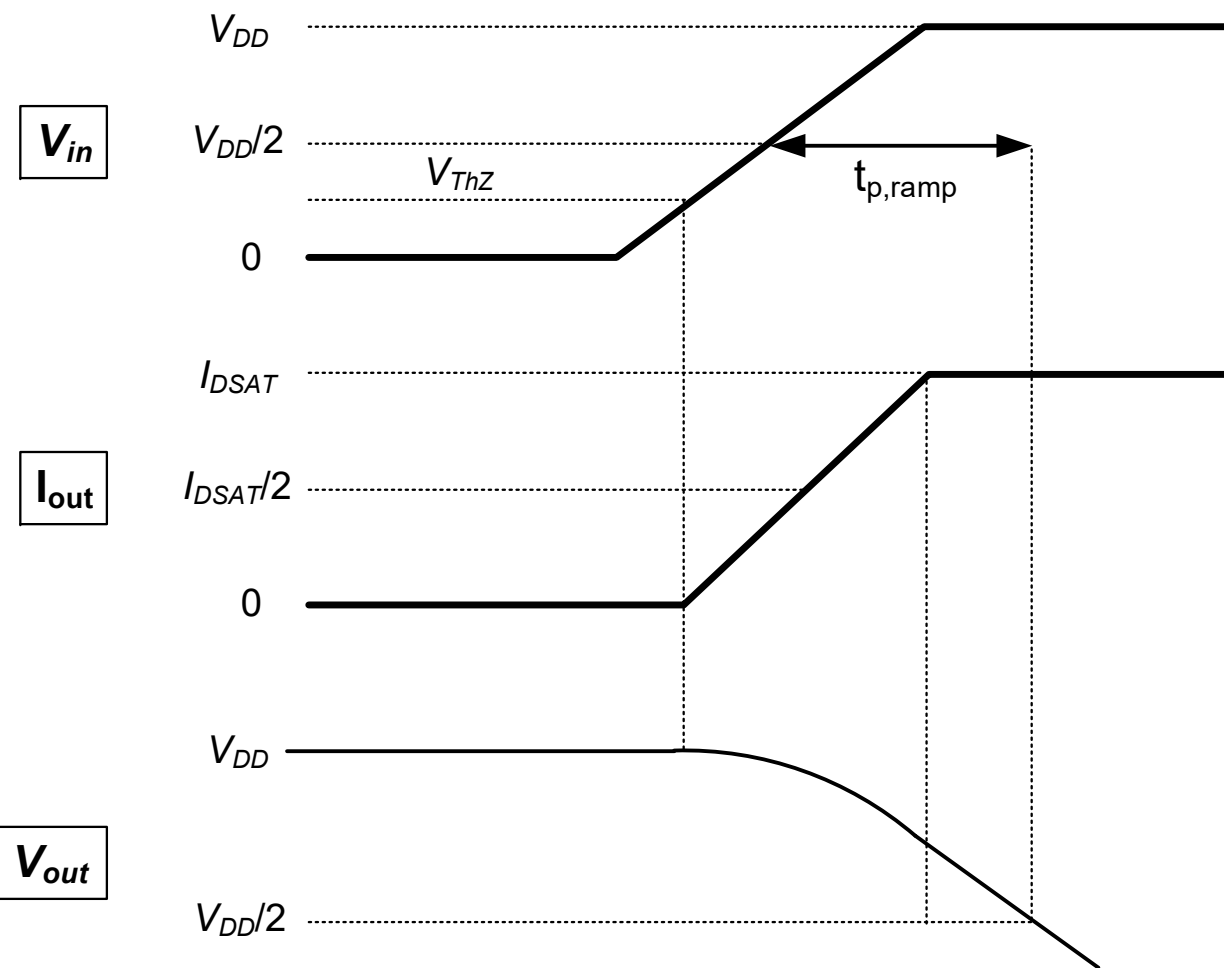

- $I_{out}$  ramps linearly for

$$V_{ThZ} < V_{in} < V_{DD}$$

- Constant once  $V_{in} = V_{DD}$

- $C_L$  integrates  $I_{out}$


- $V_{ThZ} < V_{in} < V_{DD}$ :  $V_{out}$  quadratic

- $V_{in} = V_{DD}$ :  $V_{out}$  linear



# Slope Dependence

# Slope Dependence

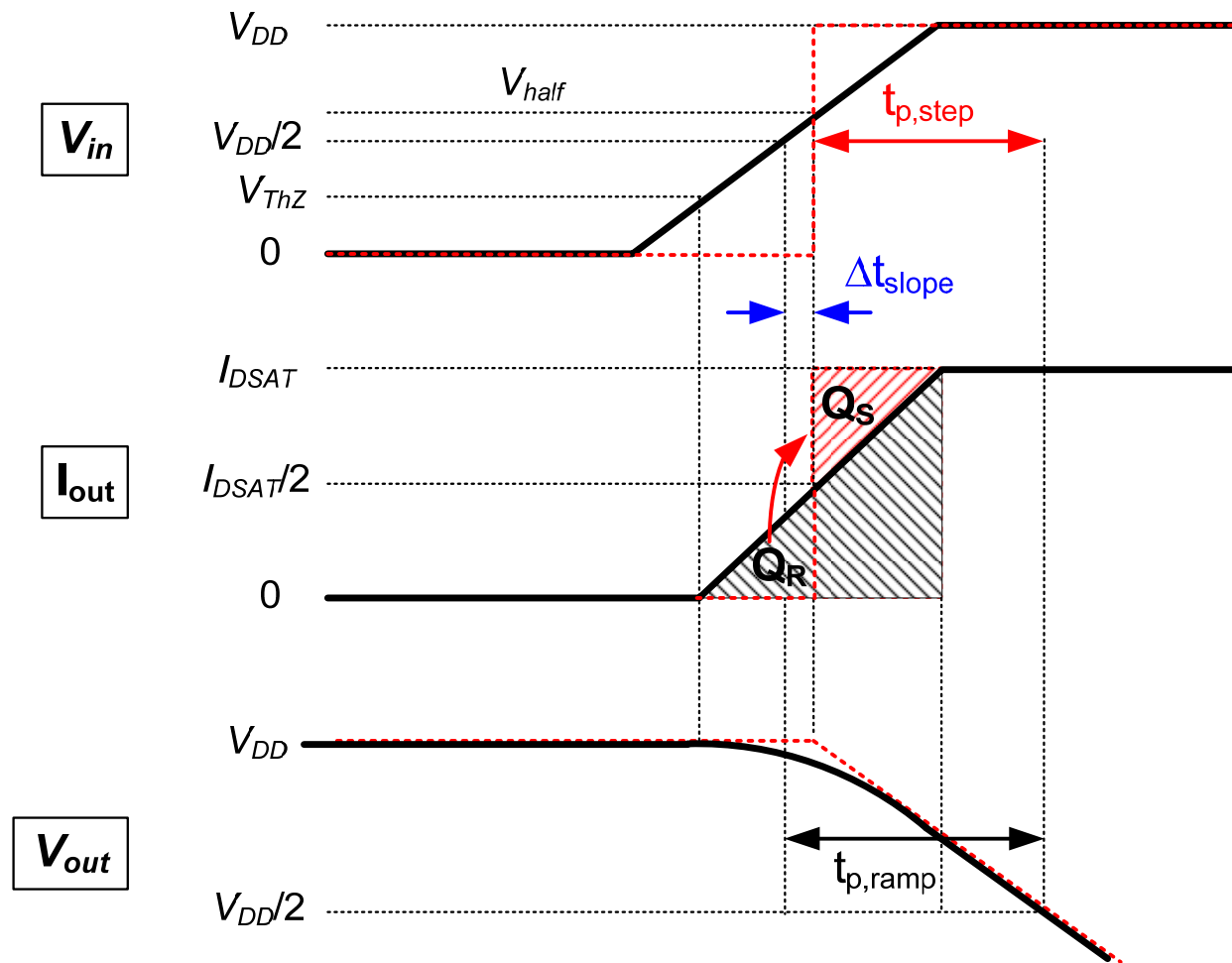

- Consider step input whose output crosses  $V_{DD}/2$  at same time

- $V_{out}$  set by charge removed from  $C_L$

- Need to make


$$Q_R = Q_S$$

- Step has to shift to when

$$I_{out} = I_{DSAT}/2$$

From E. Alon

# Slope Dependence

 

- To find  $\Delta t_{slope}$ :
  - Find  $V_{in}$  when  $I_{out} = I_{DSAT}/2$  ( $V_{half}$ )
  - And use input  $t_r$
- $I_{DSAT} \propto (V_{DD} - V_{ThZ})$ :
 
$$V_{half} - V_{ThZ} = V_{DD}/2 - V_{ThZ}/2$$

$$V_{half} = (V_{DD} + V_{ThZ})/2$$
- So  $\Delta t_{slope} = (V_{ThZ}/2)/k_r$ 
  - $k_r = V_{DD}/(t_{r,20-80}) = V_{DD}/(2*t_{p,in})$

$$t_{p,ramp} = t_{p,step} + \frac{V_{ThZ}/2}{k_r} = t_{p,step} + \frac{V_{ThZ}}{V_{DD}} t_{p,in}$$

# Result Summary


- For reasonable input slopes:

$$t_{p,ramp} = t_{p,step} + \frac{V_{Thz}/2}{k_r} = t_{p,step} + \frac{V_{Thz}}{V_{DD}} t_{p,in}$$

- For  $t_{p,avg}$ ,  $V_{Thz}$  is  $(V_{ThzN} + V_{ThzP})/2$ 
  - $V_{Thz}/V_{DD}$  typically  $\sim 1/3-1/2$  at nominal supplies
- Propagation delay is a function of
  - Drive strength ( $R_{eq}$ )
  - Load ( $C_L$ )
  - Input rise/fall time (which is proportional to the propagation delay of the previous gate)

 
# Model vs. Spice Data

- For reasonable input slope
  - Model matches Spice very well
- Model breaks with very large  $t_r$ 
  - Input looks “DC” – traces out VTC
  - Have other problems here anyways
    - Short-circuit current




# Signal Arrival Times

- NAND gate:

 


# Signal Arrival Times

- NAND gate:

 


# Simultaneous Arrival Times

- NAND gate:

 



# Impact of Arrival Times

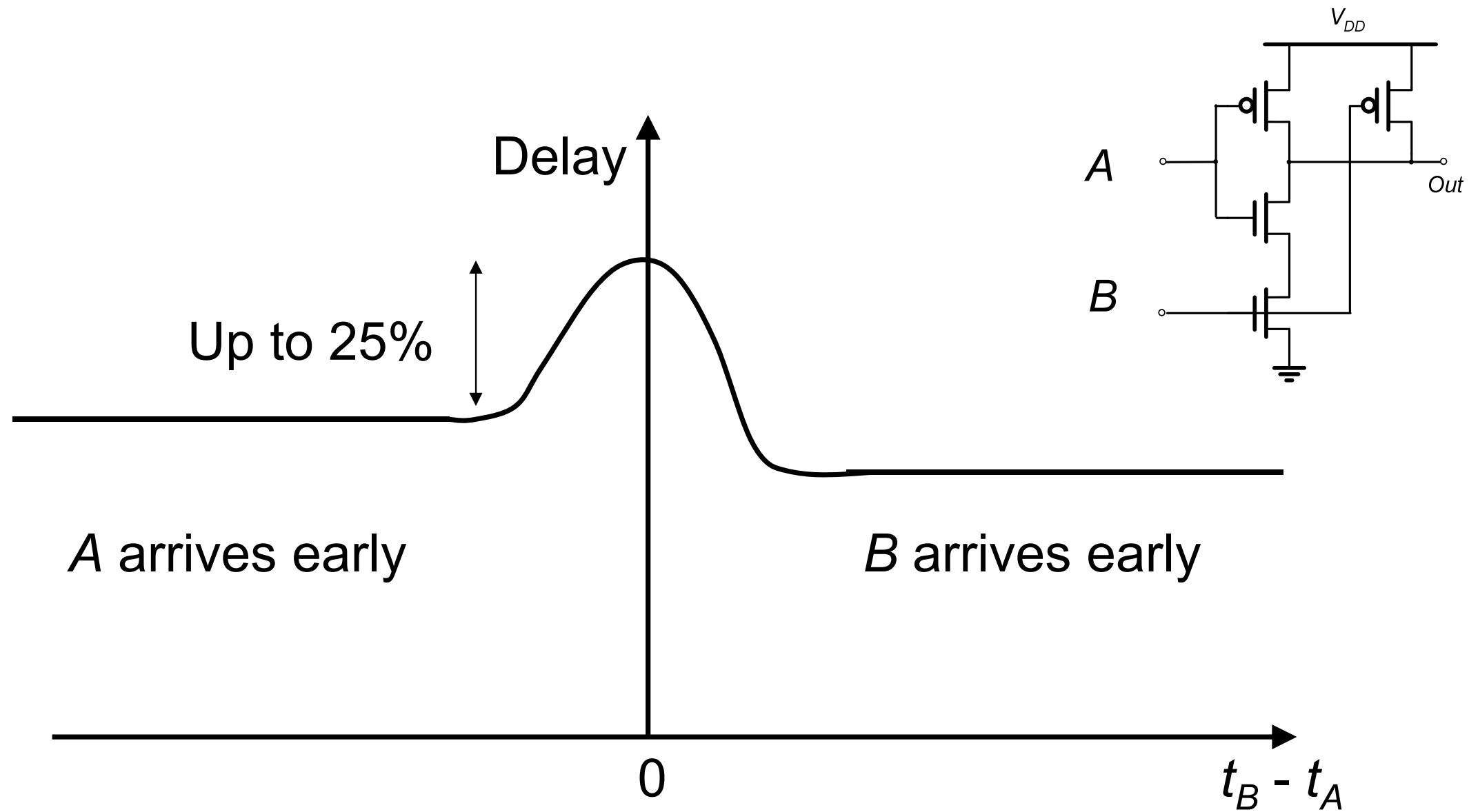

The edge can also advance in the opposite transition  
Not in models; add derating during design

## Key Point

- Timing of a cell is set by its load and input rise/fall time
  - Enables static delay computation
- Circuits described as graphs
  - Timing as a graph solving problem



## 2.M Standard Cell Library

# Standard Cell Library


- Contains for each cell:
  - Functional information:  $\text{cell} = a * b * c$
  - Timing information: function of
    - input slew
    - intrinsic delay
    - output capacitancenon-linear models used in tabular approach
  - Physical footprint (area)
  - Power characteristics
  - Noise sensitivity
- Wire-load models - function of
  - Block size
  - Fan-out



K. Keutzer, EE244

# Synopsys Delay Models

- Linear (CMOS2) delay model

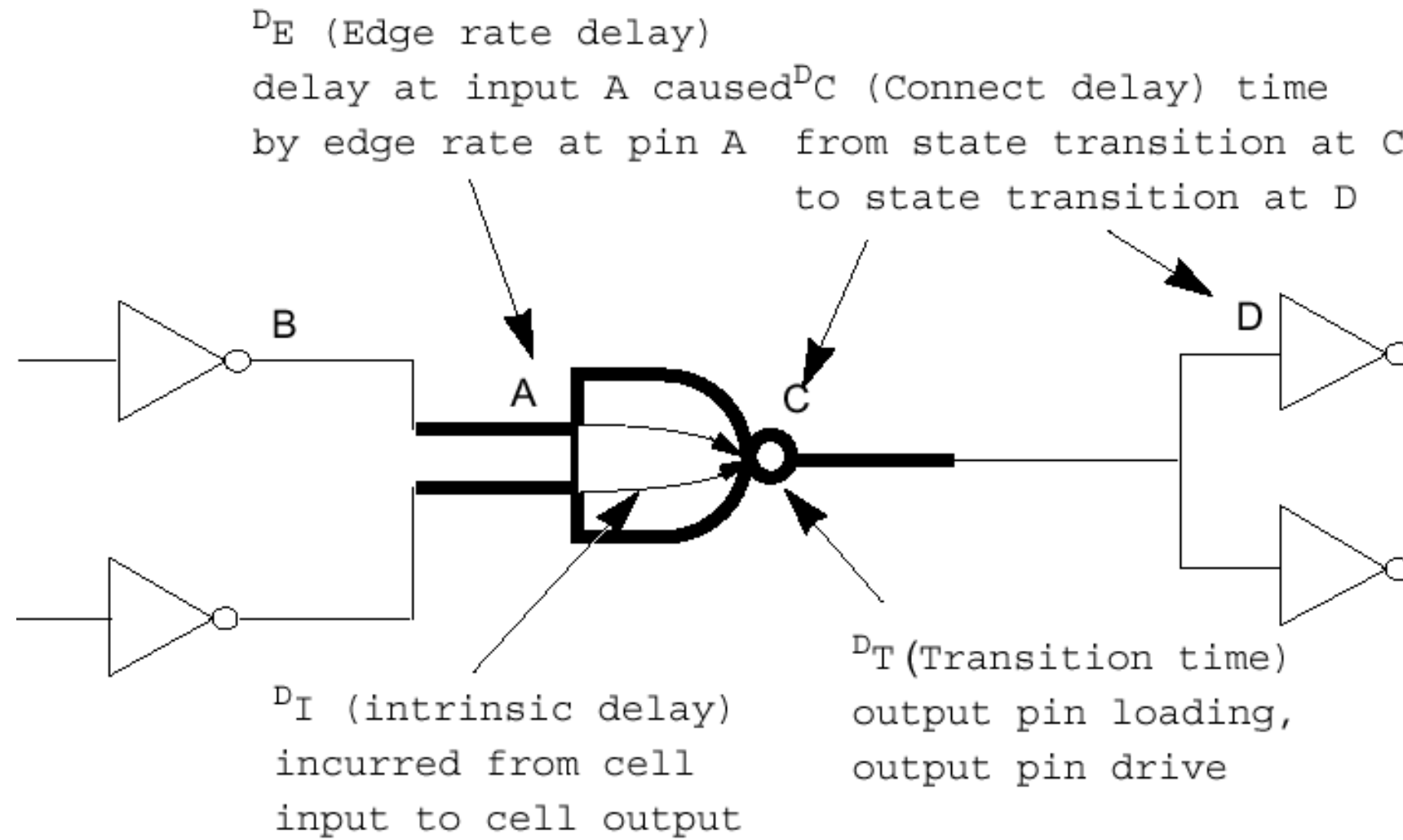

# Example Cell Timing

- From Synopsys training materials

From pin: U28/A  
To pin: U28/Z

```
arc type :                cell
arc sense :               unate
Input net transition times: Dt_rise = 0.1458, Dt_fall = 0.0653
```


Rise Delay computation:

```
rise_intrinsic           0.48 +
rise_slope * Dt_rise     0 * 0.1458 +
rise_resistance * (pin_cap + wire_cap) / driver_count
0.1443 * (2 + 0) / 1
rise_transition_delay :   0.2886
-----
Total                    0.7686
```

# Cell Characterization (Linear Model)

```
cell(NAND2) {
  area : 1;
  pin(X) {
    function : "(A B)";
    direction : output;
    edge_rate_rise : 0.24;
    edge_rate_fall : 0.14;
    edge_rate_load_rise : 5.4;
    edge_rate_load_fall : 3.4;
    timing() {
      intrinsic_rise : 0.34;
      intrinsic_fall : 0.24;
      rise_resistance : 3.4;
      fall_resistance : 1.4;
      edge_rate_sensitivity_r0 : 0.24;
      edge_rate_sensitivity_f0 : 0.14;
      edge_rate_sensitivity_r1 : 0.14;
      edge_rate_sensitivity_f1 : 0.04;
      related_pin : "A";
    }
  }
  timing() {
    intrinsic_rise : 0.34;
    intrinsic_fall : 0.24;
    rise_resistance : 3.4;
    fall_resistance : 1.4;
    edge_rate_sensitivity_r0 : 0.24;
    edge_rate_sensitivity_f0 : 0.14;
    edge_rate_sensitivity_r1 : 0.14;
    edge_rate_sensitivity_f1 : 0.04;
    related_pin : "B";
  }
  pin(A) {
    direction : input;
    capacitance : 0.10;
  }
  pin(B) {
    direction : input;
    capacitance : 0.10;
  }
}
```

# Synopsys Nonlinear Delay Model (NLDM)

 


Delay is a function of:

- Rise propagation
- Cell rise
- Fall propagation
- Cell fall
- Rise transition
- Fall transition



 
# Synopsys Nonlinear Delay Model

- Interpolates between characterization points



 
# Composite Current Source (CCS) Model

- **Driver model**
  - Composite current source (time and voltage dependent)
- **Receiver model**
  - A set of capacitance models
  - Wire model
- **Interpolate**



Matches both delay and rise/fall times

 

Synopsys