

# EE241B : Advanced Digital Circuits

## Lecture 9 – Timing

### Borivoje Nikolić



February 14, 2020, EETimes: Five Chip Companies Hold 53% of Global Wafer Capacity

An increasing percentage of the world's capacity is getting concentrated in the hands of the largest producers.

Worldwide Wafer Capacity Leaders  
(Monthly Installed Capacity in Dec 2019, 200mm-equivalents)

2019 Rank	2018 Rank	Company	Headquarters Region	Dec-2018 Capacity (K w/m)	Dec-2019 Capacity (K w/m)	Yr/Yr Change	Share of Worldwide Total	Inclusion or Exclusion of Capacity Shares from JV Fabs
1	1	Samsung	South Korea	2,934	2,935	0%	15.0%	
2	2	TSMC	Taiwan	2,439	2,505	3%	12.8%	shares of SSMC & VIS
3	3	Micron	North America	1,685	1,841	9%	9.4%	share of IM Flash in '18
4	4	SK Hynix	South Korea	1,630	1,743	7%	8.9%	
5	5	Kioxia/WD	Japan	1,361	1,406	3%	7.2%	

Source: Companies, IC Insights' Global Wafer Capacity 2020-2024 Report



# Announcements

- Project abstracts due today, by e-mail
  - Teams of 2
  - Title
  - One paragraph
  - 5 relevant references
- Can also combine with CS252 or EE290 projects
- Quiz 1 on Tuesday, Feb 25, in class
- Office hour moved to 11 am on Monday

# Outline

- ISSCC recap
- Module 2
  - Technology variability
- Module 3
  - Flip-flop timing




## 2.P Design Variability Some Random Effects


# Negative Bias Temperature Instability

- PFET  $V_{Th}$ 's shift in time, at high negative bias and elevated temperatures
- The mechanism is thought to be the breaking of hydrogen-silicon bonds at the Si/SiO<sub>2</sub> interface, creating surface traps and injecting positive hydrogen-related species into the oxide.
- Also other charge trapping and hot-carrier defect generation
- Systematic + random shifts

Tsujikawa, IRPS'2003

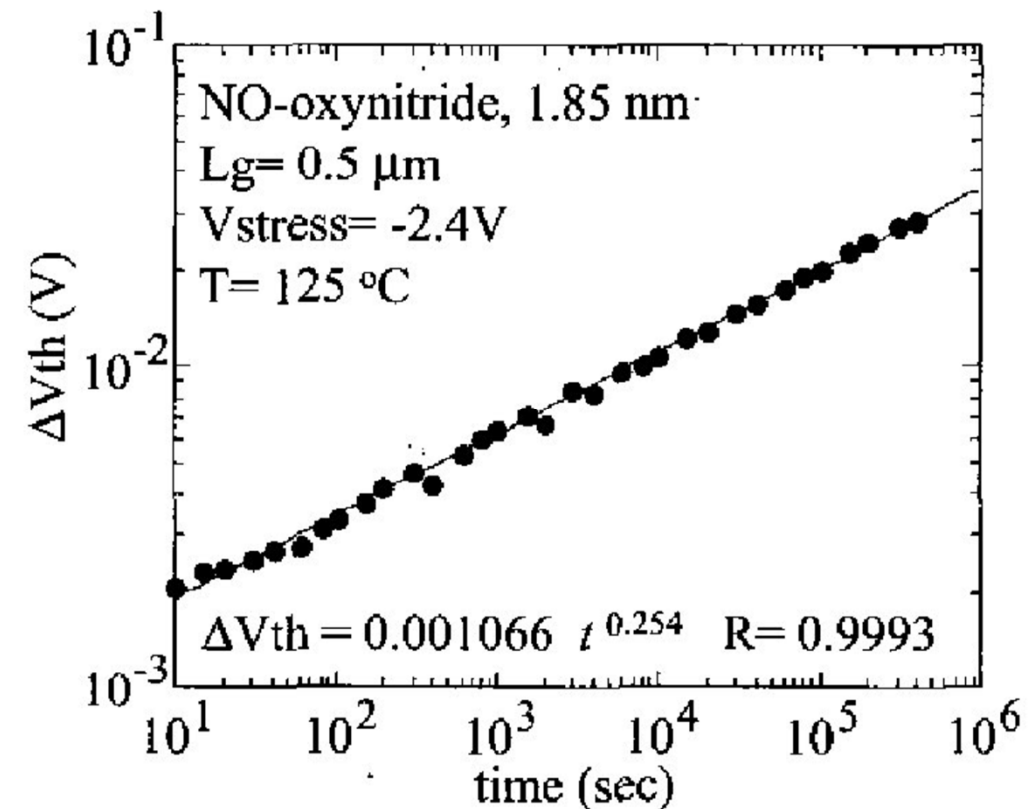

# Random Telegraph Signal (RTS)

 


- Trapping of a carrier in oxide traps modulates  $V_{th}$  or  $I_{ds}$
- $\tau_e$  and  $\tau_c$  are random and follow exponential distributions

# RTS and Technology Scaling

- RTS exceeds RDF at 3 sigma with 20nm gates

$$\Delta V_{th, RTS} \sim \frac{1}{WL}$$
 
$$\Delta V_{th, RDF} \sim \frac{1}{\sqrt{WL}}$$



Tega *et. al*, VLSI Tech. 09




## 3. Design for Performance

### 3.A Flip-Flop Timing




# Flip-Flop Parameters

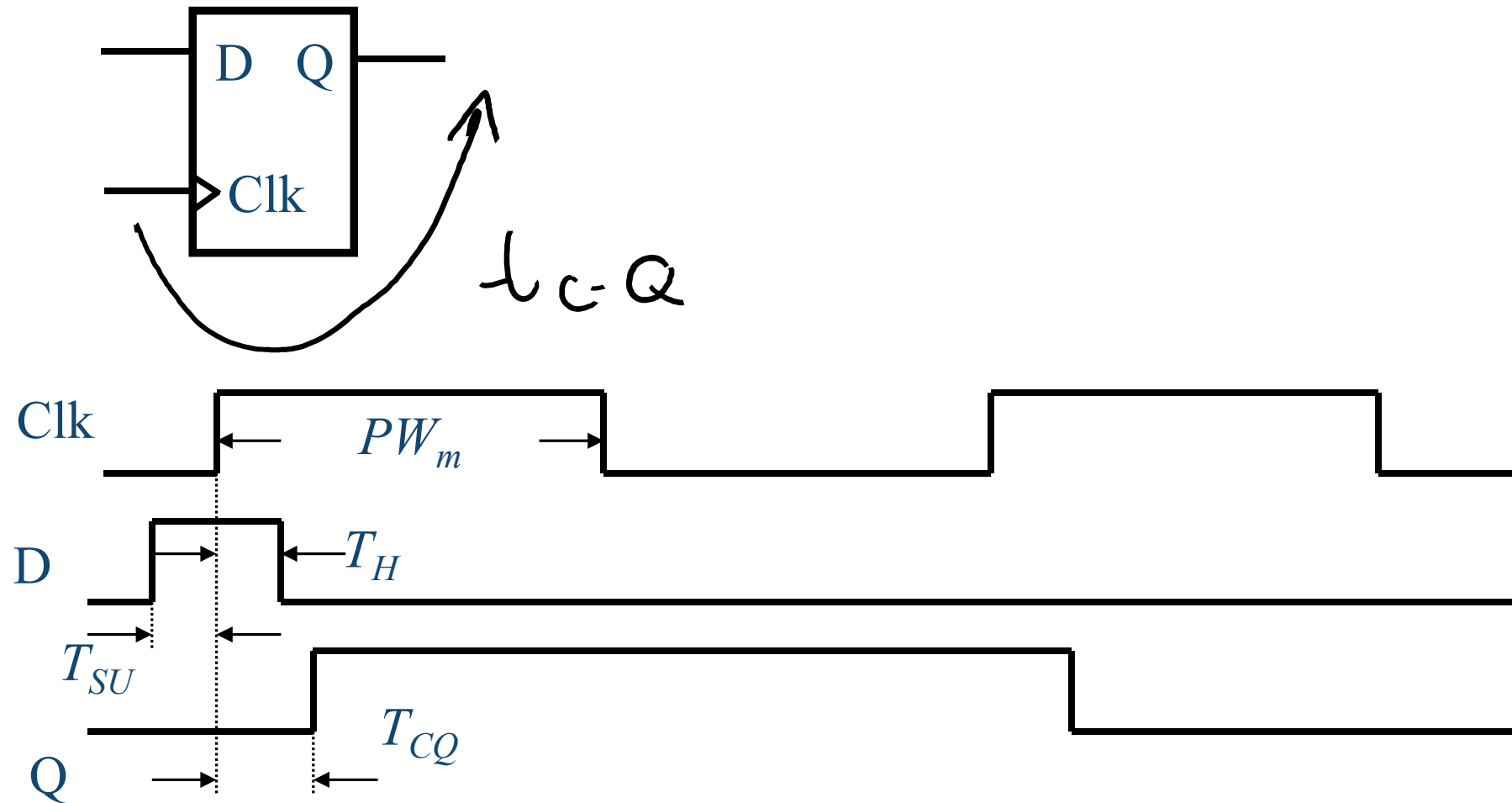


*Delays can be different for rising and falling data transitions*

# Latch Parameters

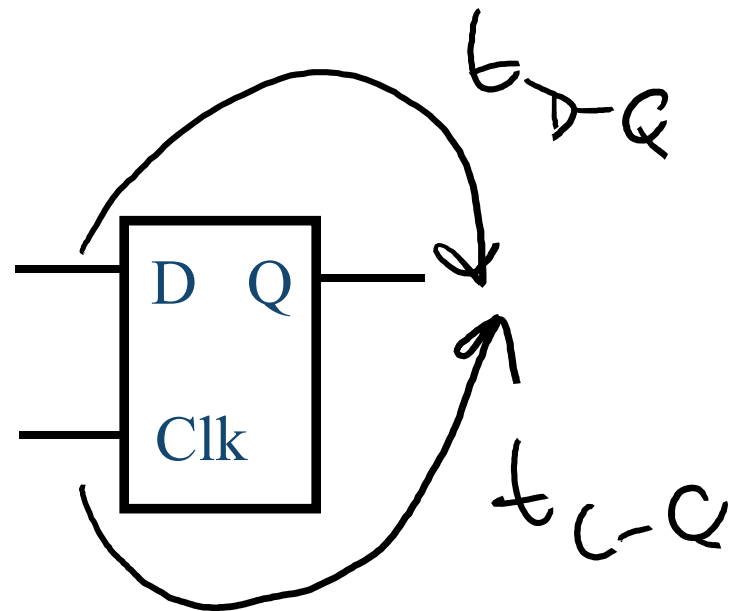

Unger and Tan  
Trans. on Comp.  
10/86

 

*Delays can be different for rising and falling data transitions*

4.5 MHz

40 MHz

32 kHz




2-4 GHz

CORR  
UNCORR


CATING  
(2-3 levels)

$\frac{N}{M} f_{SYSCLK}$

Global clock

 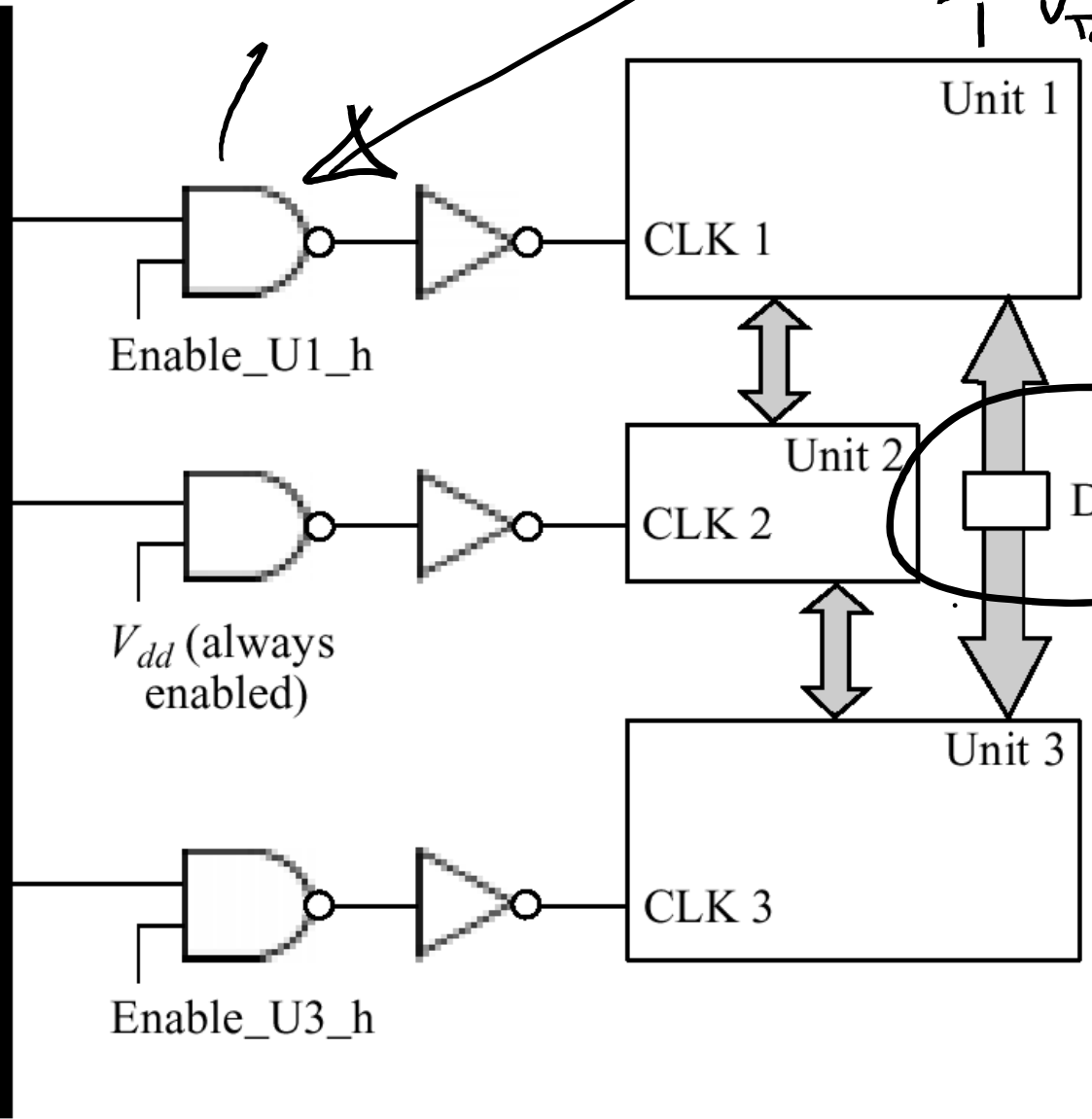 


RESYNC

 

# Clock Nonidealities


- Clock skew
  - Spatial variation in temporally equivalent clock edges; deterministic + random,  $t_{SK}$
- Clock jitter
  - Temporal variations in consecutive edges of the clock signal; modulation + random noise
  - Cycle-to-cycle (short-term) -  $t_{JS}$
  - Long-term -  $t_{JL}$
- Variation of the pulse width
  - for level-sensitive clocking

# Clock Skew and Jitter

 


- Both skew and jitter affect the effective cycle time
- Only skew affects the race margin, if jitter is from the source
  - Distribution-induced jitter affects both

# Clock Uncertainties

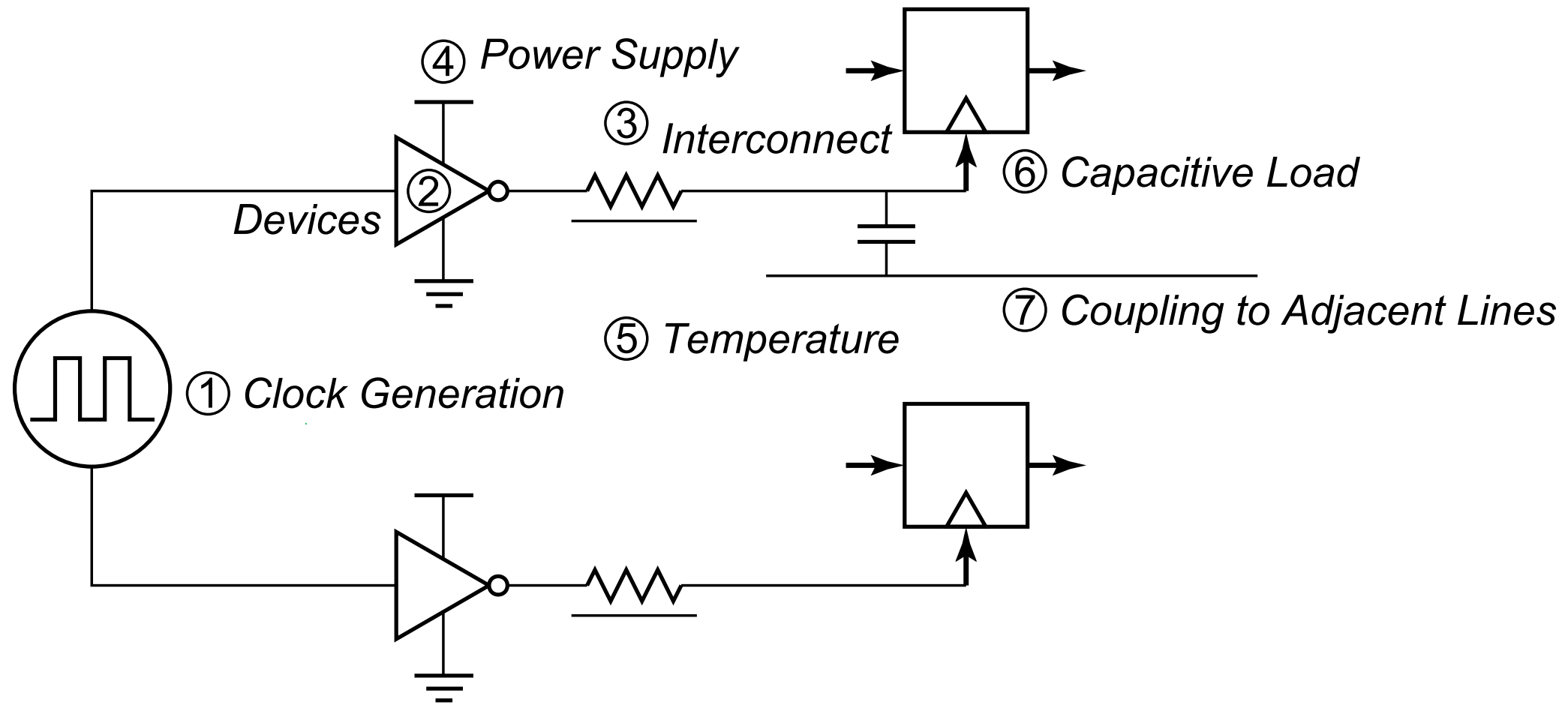

*Sources of clock uncertainty*
 
# Clock Constraints in Edge-Triggered Systems



$$t_{CL} \leq (t_{CY} - t_{SK} - t_{JS}) - (t_{SU} + t_{CQ})$$

$$t_{CL} \geq t_{SK} + (t_H - t_{CQ})$$

